



AN1489 Application note

VIPower: non isolated power supply using VIPer20 with secondary regulation

Introduction

Output voltage regulation with adjustable feedback compensation loop is very simple when a VIPer device is used in low cost non-isolated applications. In this paper such a simple regulation circuit is introduced and analyzed in Buck and Buck-boost converter based on VIPer20, a monolithic smart power with an integrated PWM controller. The device is suitable for off-line applications and features integrated protection circuits such as over-temperature and over-current protection.

Obsolete Product(s) - Obsolete Product(s)

Contents

1	Non isolated power supply	3
1.1	Buck converter	3
1.2	Buck-boost converter	3
2	VIPer20 in non isolated secondary regulation	4
2.1	Comp pin control	4
2.2	Inductor and frequency selection	5
3	Application examples	6
3.1	Buck converter	6
3.2	Experimental results	8
3.3	EMI behavior	9
3.4	3Buck-boost converter	10
4	Conclusion	13
5	Revision history	13


1 Non isolated power supply

1.1 Buck converter

In the basic circuit, shown in [Figure 1.](#), when the switch is closed current flows through the inductor L producing an output voltage. When the switch opens the magnetic field in L changes polarity and the freewheeling diode provides a return path for the current to circulate through the load.

Varying the diode voltage waveform duty-cycle can control the output voltage.


Figure 1. Buck converter

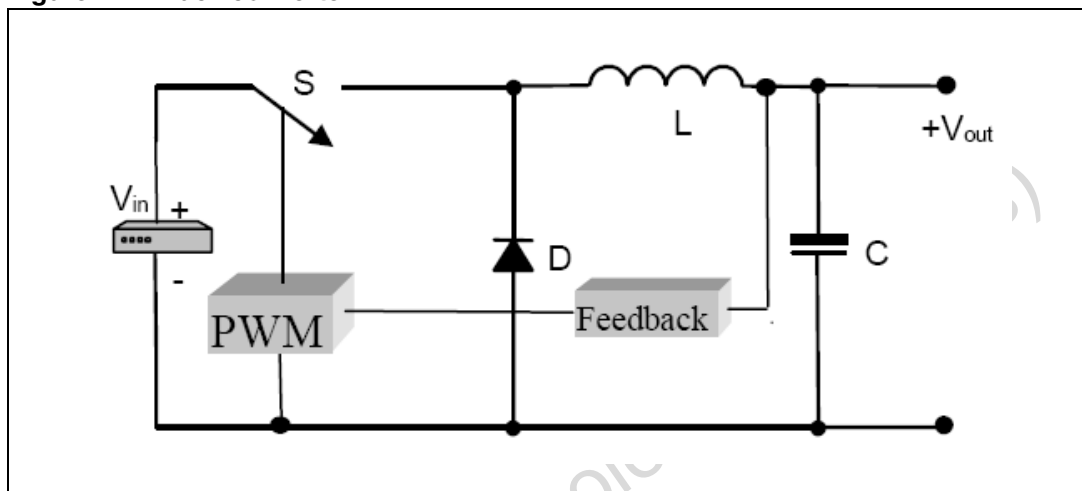

1.2 Buck-boost converter

In this configuration the energy is stored in the inductor L during the on time of the switch, when the switch is off the voltage across L reverses as the inductor transfers the stored energy to the smoothing capacitor and to the load. The output voltage is the opposite polarity to the input.

Figure 2. Buck-boost converter

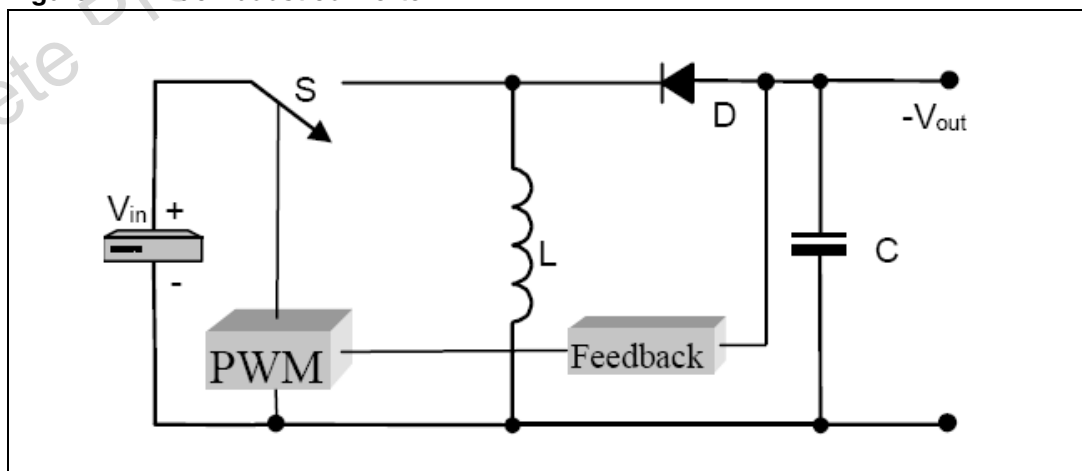

2 VIPer20 in non isolated secondary regulation

VIPer20 is an integrated device with: 620V breakdown voltage Power MOSFET (700V VIPer20A), PWM controller, start up circuit and protections.

The start up of the power supply is provided through the DRAIN pin by means of an integrated high voltage current source, which is switched off during normal operation. The VDD pin provides two functions. The first one is to supply the control section of the power IC; in fact if VDD goes below 8V, the start-up current source is turned on and the Power MOSFET is switched off until the VDD voltage reaches 11V. During the start up the internal current consumption is reduced, the VDD pin provides a current of about 2mA and the COMP pin is shorted to ground. After that (VDD=11V), the current source is switched off, and the device starts switching. The second function is related to the control of the device since this pin is also connected to the error amplifier, in order to allow primary as well as secondary regulation configurations. In case of primary regulation, an internal 13V trimmed reference voltage is used to maintain VDD at 13V. For secondary regulation, a voltage between 8.5V and 12.5V will be put on VDD pin, in order to stick the error amplifier output transconductance to the high state. The COMP pin behaves as a constant current source, and can easily be connected to the output of an optocoupler. Note that any over-voltage due to regulation loop failure is still detected by the error amplifier through the VDD voltage, which cannot overpass 13V. The output voltage will be somewhat higher than the nominal one, but still under control.

The COMP pin provides two functions: it is the output of the error amplifier, and allows the connection of a compensation network to provide the desired transfer function of the regulation loop (R3, C2). Its bandwidth can be easily adjusted using usual component values. As stated above, secondary regulation configurations are also implemented through the COMP pin. When the COMP voltage goes below 0.5V, the shutdown of the circuit occurs, with a zero duty cycle for the Power MOSFET. This feature can be used to switch off the converter, and is automatically activated by the regulation loop (whatever is the configuration) to provide a burst mode operation in case of negligible output power or open load condition.

The switching frequency is set by an RC network connected to the OSC pin, regardless VDD value in the range from 8V to 15V. This pin also provides a synchronization capability, when connected to an external frequency source.

2.1 Comp pin control


In order to perform secondary regulation a suitable control circuit is applied to COMP pin, as shown in [Figure 3](#). Since the output voltage supplies directly the VIPer20 by means of a high voltage diode, it has to be in the range $8V \div 12.5V$, in order to guarantee the minimum supply voltage and to avoid the primary regulation.

The control circuit consists in an npn transistor Q1, a Zener diode Dz, a high voltage decoupling diode D2 and a bias network (C1, R1 and R2). The feedback circuit (D2,Dz) works during the off state of the power switch, charging the capacitor C1.

During the on state, the voltage across C1 drives Q1 base, through R1 and R2, drawing current from the COMP pin and performing the regulation. The capacitor value is selected considering both the feedback precision and stability, thus it depends on the desired output precision and the switching frequency. In steady state condition the voltage across C1 is

constant. As an output voltage change is detected by the feedback network (D2, Dz), the voltage across C1 changes driving the base current of the transistor Q1 and consequently the comp pin voltage. Thus the regulation loop sets the output voltage to the proper value.

Figure 3. COMP pin control scheme

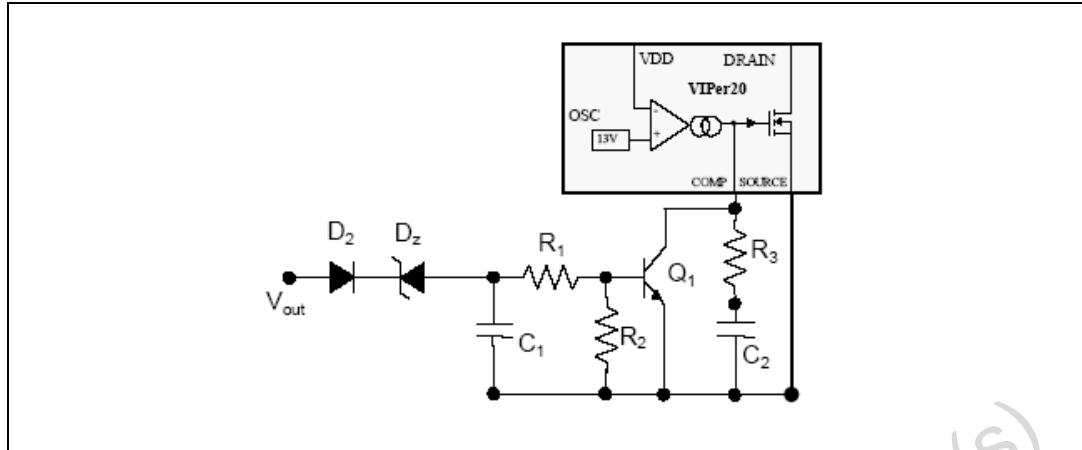

2.2 Inductor and frequency selection

The Inductor and frequency value are based to maximum output current and mode of operation, besides the peak drain current has not to overcome 0.5A. It suitably works in discontinuous mode in which the inductor current never goes to zero, in fact it is better to avoid the continuous mode because of several reasons:

- higher switching losses in the switch and in the free wheeling diode
- the inductor size and price would increase
- regulators operating in the discontinuous are very stable and have a very good closed loop response
- higher EMI

The interaction between inductor and switching frequency in order to have the maximum output current with limited drain current peak lower (for VIPer20 is 0.5A), can be calculate by means of following formula:

Equation 1

$$L = \frac{2 \cdot V_{out} \cdot I_{out}}{I_{dmax}^2 \cdot f_{sw}}$$

We can do two considerations

- fixed inductor, the maximum output current increased with the switching frequency
- fixed switching frequency, the maximum output current increased with the inductor value

The following relation shows interaction between inductor value and switching frequency in order to work in discontinuous mode:

Equation 2

$$f < \frac{V_{out}}{I_{out} \cdot 2 \cdot L}$$

3.1 Buck converter

The maximum output current is related to the drain current limitation of the VIPer. The typical value for VIPer20 is 0.67A with a minimum guaranteed value of 0.5A. As the output current increases over the current limitation the output voltage drops down to the minimum supply voltage (8V) shutting down the device.

Parameter	Value
AC input voltage V_{inac}	85 - 265Vac
Output current I_{out}	300mA
Output voltage V_{out}	+12V
Switching frequency	20kHz
Output voltage ripple	5%

[illegible]

Reference	Value	Part number
R _f	10Ω / 1/2W 5%	
R _L	10KΩ / 1/2W 5%	
R ₁	10KΩ / 1/4W 5%	
R ₂	47KΩ / 1/4W 5%	
R ₃	8.2KΩ / 1/4W 5%	

Table 2. Components list (continued)

Reference	Value	Part number
R ₄	10KΩ / 1/4W 5%	
C _{in}	10μF / 400V Electrolytic	
C _{in1}	3.3μF / 400V Electrolytic	
C _{out}	100μF / 25V Electrolytic	
C ₁	470nF / 25V Ceramic	
C ₂	100nF / 25V Ceramic	
C ₃	10μF / 25V Electrolytic	
C ₄	10nF / 25V Ceramic	
D _r		Diode 1N4007
D ₁		Diode STTA106
D ₂		Diode 1N4005
D ₃		Diode 1N4005
D _Z	9.1V Zener	
D _{Z0}	13V Zener	
L	2.1mH Inductor	
L _f	470μH Inductor	
Q ₁		Transistor BC547B
I _{C1}		STMicroelectronics VIPer20DIP

Figure 5. PCB layout using VIPer20 in secondary regulation (not in scale)

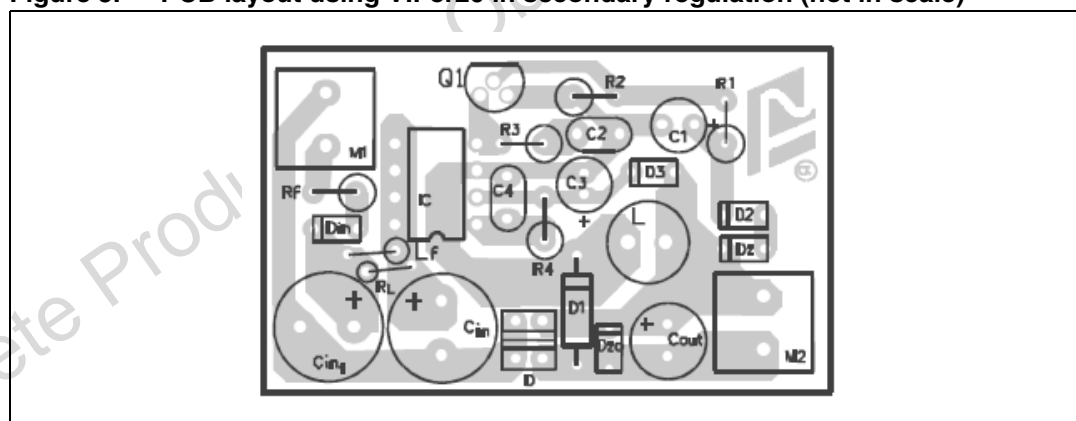
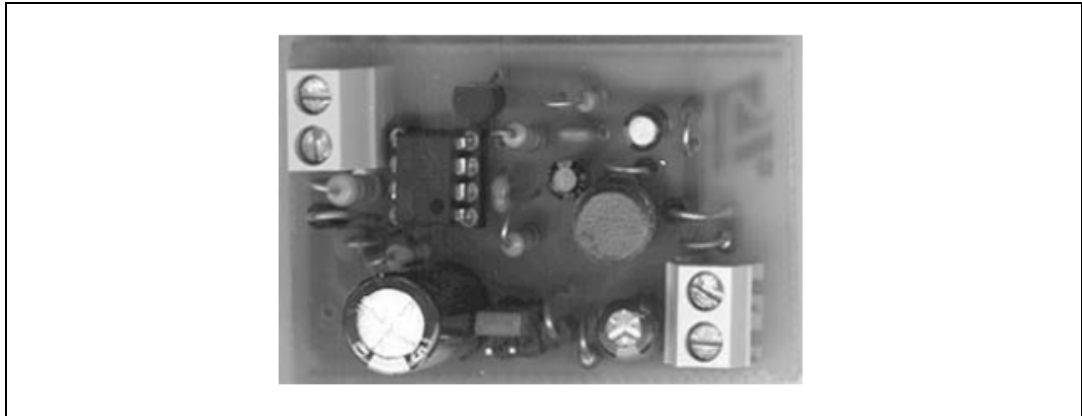


Figure 6. VIPer20 board in secondary regulation

3.2 Experimental results

In this section some experimental waveforms are shown and a performance evaluation is carried out in terms of line and load regulation as well as efficiency.

The output voltage is almost independent of input voltage, featuring a horizontal line as the input voltage changes from 80V to 265V, confirming the superior regulation behavior.

Load regulation is performed as well, ranging from 10.8V to 12V as the load increases from no load to 300mA.

The efficiency has been evaluated and it is shown in the figure as function of output current. The circuit works with a good efficiency that is always over 55% with peak over 75%.

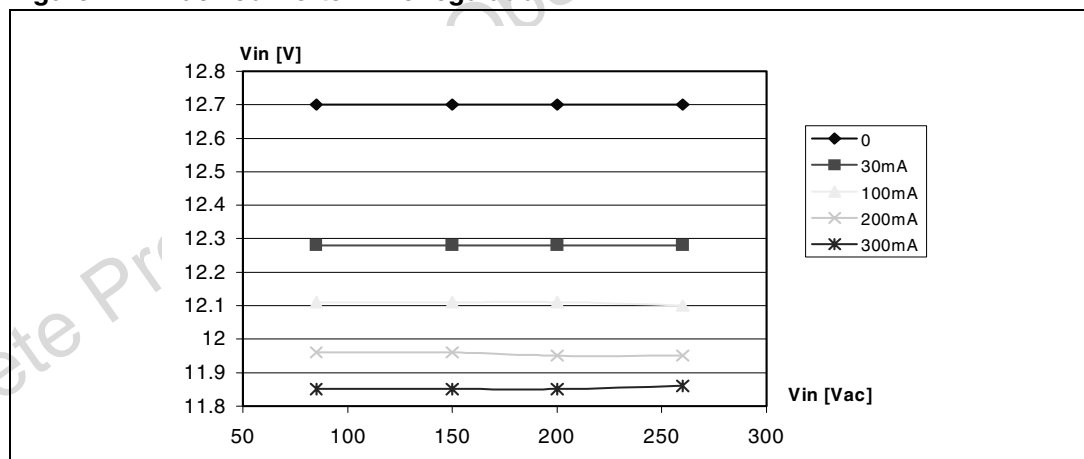
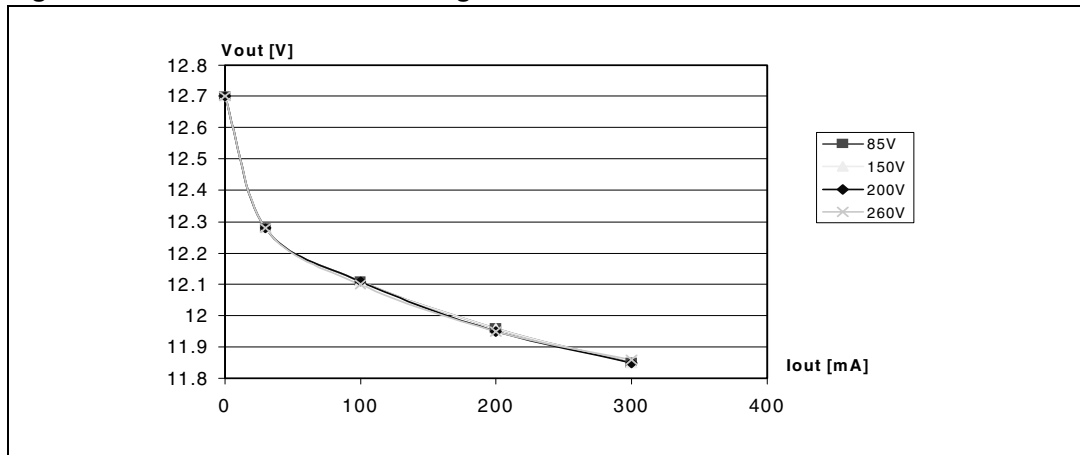
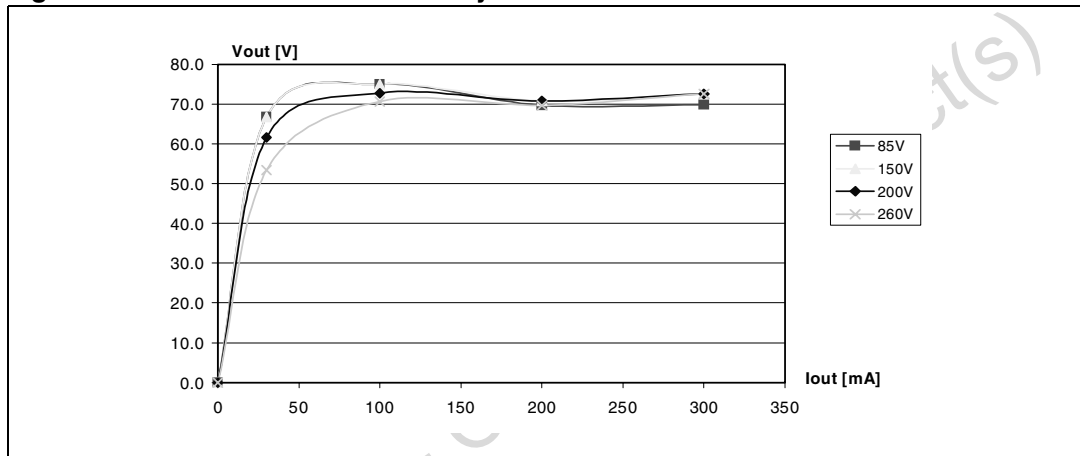
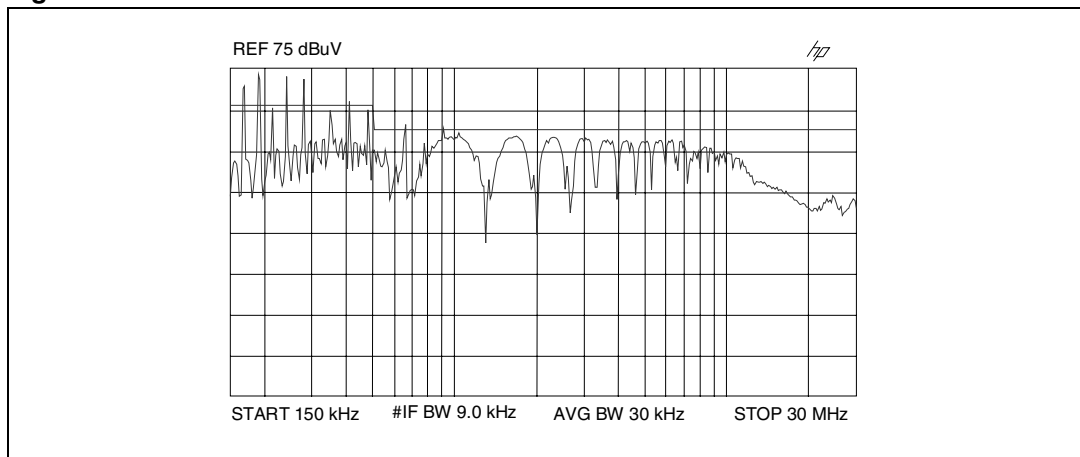
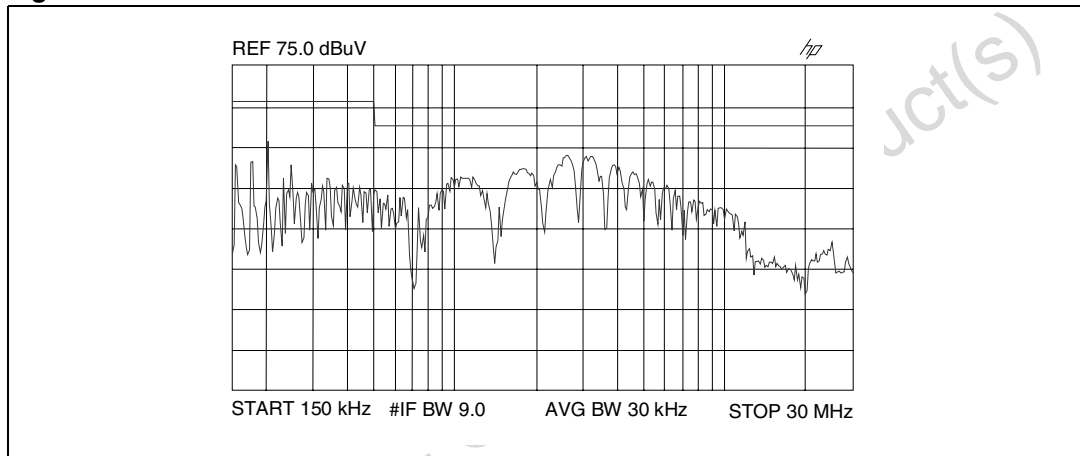
Figure 7. Buck converter: line regulation

Figure 8. Buck converter: load regulation**Figure 9. Buck converter: efficiency**

3.3 EMI behavior

In this session the circuit EMI behavior has been analyzed, both with an LC filter and without, in the following conditions:

- $V_{in} = 185V_{ac}$
- $V_{out} = 9.34V_{dc}$
- $P_{in} = 1.5W$
- $R_{out} = 100\Omega$
- $I_{out} = 100mA$

Figure 10. EMI behavior without filter**Figure 11. EMI behavior with filter LC**

The [Figure 11](#) shows a good EMI behavior for the circuit with a LC filter.

3.4 3Buck-boost converter

The schematic of the circuit is shown in [Figure 12](#). The specifications of the power supplies are listed in [Table 3](#). The output voltage supplies directly the VIPer20, then it has to range from 8V to 12.5V, in order to keep on the VIPer and hold the error amplifier in saturation allowing voltage regulation through the COMP pin. The control circuit consists in a BC547B transistor and a 10V Zener diode.

Table 3. Buck-boost converter specifications

Parameter	Value
AC input voltage V_{inac}	85 - 265Vac
Output current I_{out}	300mA
Output voltage V_{out}	-11V

Table 3. Buck-boost converter specifications (continued)

Parameter	Value
Switching frequency	20kHz
Output voltage ripple	5%

Figure 12. Buck-boost converter using VIPer20 in secondary regulation

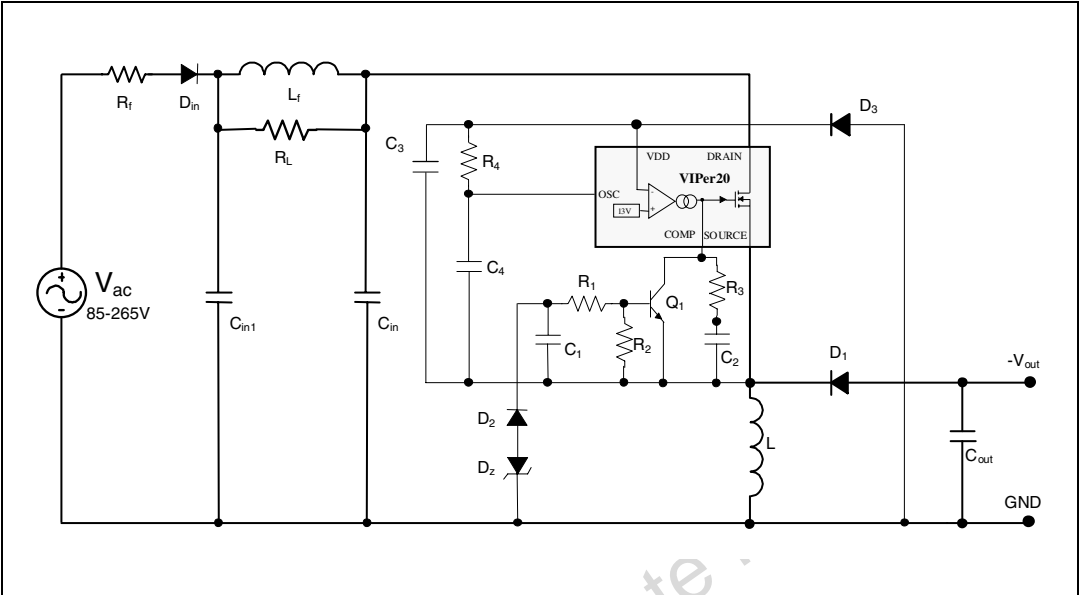
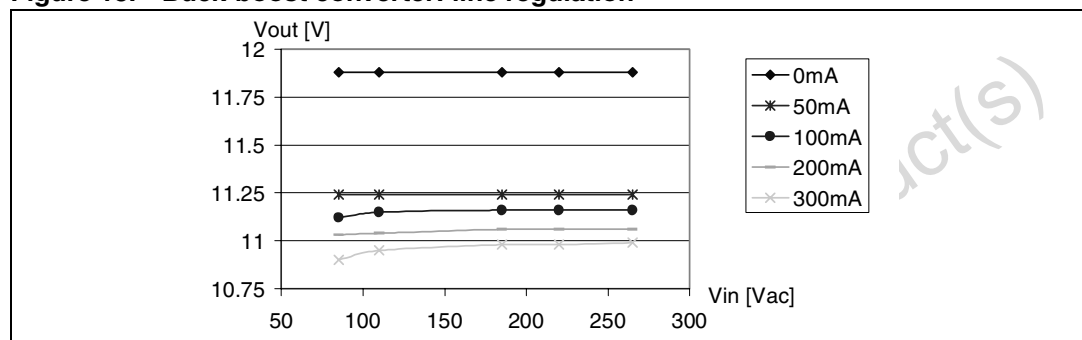
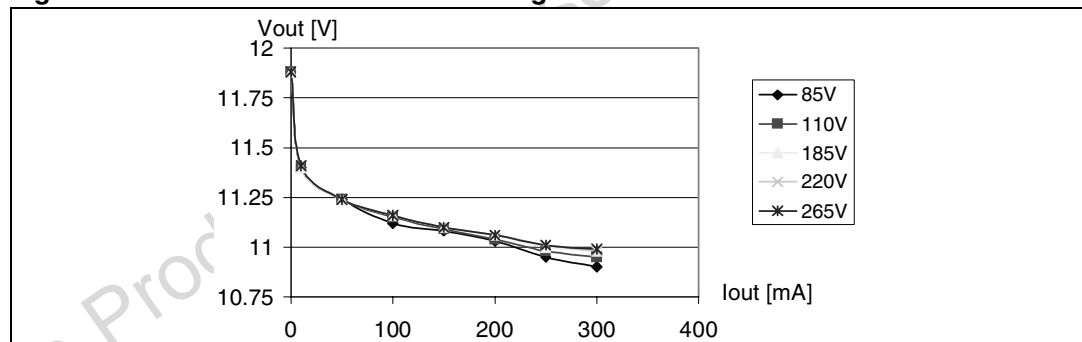
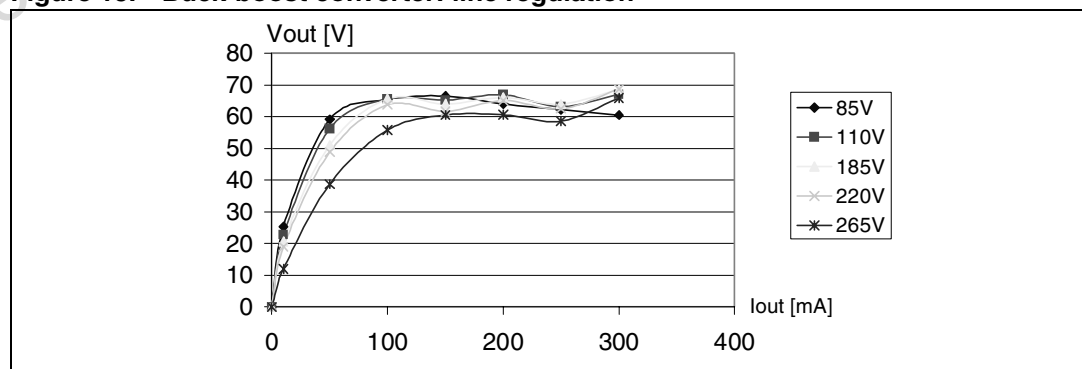


Table 4. Buck-boost converter component list

Reference	Value	Part number
R _f	10Ω / 1/2W 5%	
R _L	10KΩ / 1/2W 5%	
R ₁	10KΩ / 1/4W 5%	
R ₂	47KΩ / 1/4W 5%	
R ₃	8.2KΩ / 1/4W 5%	
R ₄	10kΩ 1/4W, 5%	
C _{in}	3.3μF, 400V Electrolytic	
C _{in1}	3.3μF, 400V Electrolytic	
C _{out}	100μF, 25V Electrolytic	
C ₁	470nF, 25V Ceramic	
C ₂	100nF, 25V Ceramic	
C ₃	10μF, 25V Electrolytic	
C ₄	10nF, 25V Ceramic	
D _r		Diode 1N4007
D ₁		Diode STTA106

Table 4. Buck-boost converter component list (continued)

Reference	Value	Part number
D ₂		Diode 1N4005
D ₃		Diode 1N4005
D _Z	10V Zener	
D _{Z1}	13V Zener	
L	2.1mH Inductor	
L _f	470μH Inductor	
Q ₁		Transistor BC547B
I _{C1}		STMicroelectronics VIPer20DIP

Figure 13. Buck-boost converter: line regulation**Figure 14. Buck-boost converter: line regulation****Figure 15. Buck-boost converter: line regulation**

4 Conclusion

A simple way to obtain secondary regulation in an off-line power supplies based on VIPer20 family has been introduced. The circuit features high efficiency and good overall performance in terms of load and line regulation. In such a way there is no need of any linear post regulator improving efficiency and reducing the size and cost of the supply. The considered topology can be realized with other devices of the VIPer family for higher power level.

For further information about SMPS PWM controller ICs please consult the VIPower web pages at: <http://www.st.com/vipower>.

5 Revision history

Table 5. Revision history

Date	Revision	Changes
04-Jan-2005	1	First issue
18-Dec-2006	2	The document has been reformatted Updated text on Chapter 2

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2006 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com