

## **Introduction**

The STSPIN32F0 device is a system-in-package providing an integrated solution suitable for driving three-phase BLDC motors using different driving modes. One of the integrated features of this device is overcurrent protection, which protects the application against damaging when high currents are reached.

The protection is implemented using an integrated comparator with an adjustable threshold. The overcurrent event can be managed both by the gate driving logic and by the microcontroller, according to user selection.

This document gives an overview of the OC protection feature and explains how to connect the STSPIN32F0 pins in order to implement the desired current threshold.

---


# Contents

<b>1</b>	<b>Overcurrent internal block diagram</b> .....	<b>3</b>
<b>2</b>	<b>Overcurrent detection in a single shunt topology</b> .....	<b>4</b>
	Bias resistor on OC_COMP pin (single shunt) .....	6
<b>3</b>	<b>Overcurrent detection in a dual shunt topology</b> .....	<b>8</b>
	Bias resistor on OC_COMP pin (dual shunt) .....	9
<b>4</b>	<b>Overcurrent detection in a triple shunt topology</b> .....	<b>12</b>
4.1	Sizing components values .....	15
4.2	Bias resistor on OC_COMP pin (triple shunt) .....	16
<b>5</b>	<b>Conclusions</b> .....	<b>18</b>
	Application example .....	18
<b>6</b>	<b>Revision history</b> .....	<b>20</b>

# 1 Overcurrent internal block diagram

An internal block diagram of overcurrent protection is depicted in *Figure 1*. The voltage on the OC\_COMP pin is compared with a threshold, selectable by the MCU lines PF6 and PF7 (see *Table 1*). When the threshold is exceeded, the OC comparator forces the output and then the PB12 line of the MCU high. Depending on the status of the OC\_SEL signal (see *Figure 1*), the comparator output propagates to the control logic of gate drivers triggering the embedded protection. The OC protection implemented in the gate driving logic turns off the external high side power switches until all the high side driving inputs are low (refer to the STSPIN32F0 device datasheet for more details).

**Figure 1. Overcurrent protection block diagram**

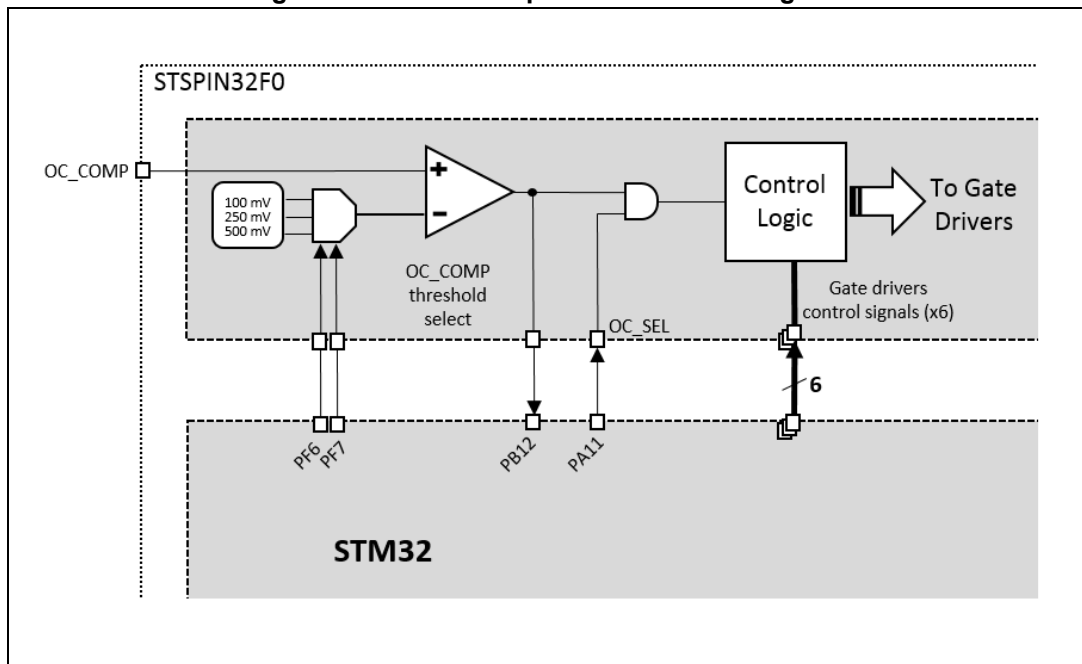

**Table 1. OC threshold values**

OC_TH_STBY2 (PF6)	OC_TH_STBY1 (PF7)	OC threshold [mV]	Note
0	0	N.A.	Standby mode
0	1	100	-
1	0	250	-
1	1	500	-

## 2 Overcurrent detection in a single shunt topology

The single shunt topology is shown in [Figure 2](#). As a convention, the phases are indicated by letters U, V and W. Each phase of the motor is connected to its output OUTU, OUTV and OUTW driven by a half-bridge. The currents are noted as  $I_U$ ,  $I_V$ , and  $I_W$  (positive values imply the current is flowing into the motor phase). The sum of the currents is always equal to zero:

**Equation 1**

$$I_U + I_V + I_W = 0$$

Currents are measured on a shunt resistor  $R_S$ , so the OC\_COMP pin is connected directly to it. Therefore, the current flowing in a phase can be measured only when the respective low side MOSFET is turned on. The overall current measured is a combination of  $I_U$ ,  $I_V$ , and  $I_W$  as listed in [Table 2](#). The value of the current in a phase can be determined using the information coming from the other two phases according to [Equation 1](#).

**Figure 2. Power stage and OC protection schematic - single shunt**

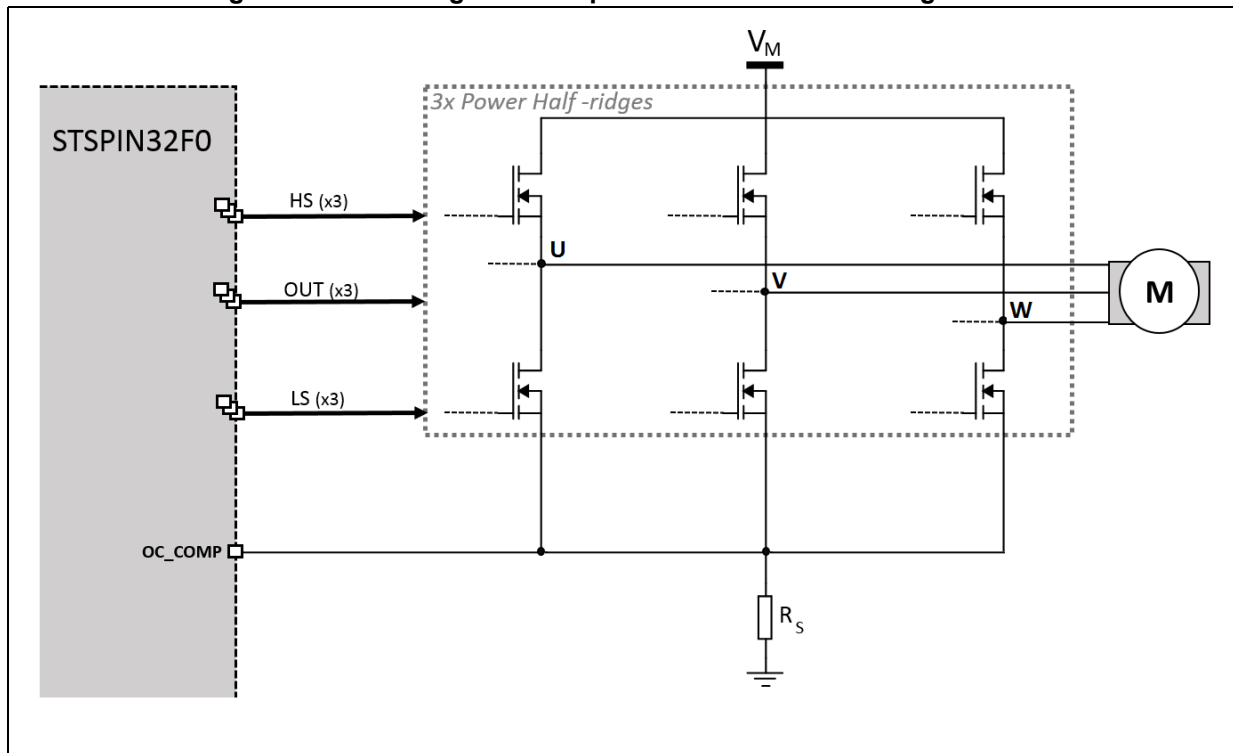


Table 2. Measured current according to power MOSFETs state - single shunt

Power MOSFET turned ON			Measured current on OC_COMP input
Phase U	Phase V	Phase W	
Low side	Low side	Low side	0
Low side	Low side	High side	$(I_U + I_V) \cdot R_S = -I_W \cdot R_S$
Low side	High side	Low side	$(I_U + I_W) R_S = -I_V \cdot R_S$
Low side	High side	High side	$I_U \cdot R_S$
High side	Low side	Low side	$(I_V + I_W) \cdot R_S = -I_U \cdot R_S$
High side	Low side	High side	$I_V \cdot R_S$
High side	High side	Low side	$I_W \cdot R_S$
High side	High side	High side	0

Considering the schematic shown in [Figure 2](#), the threshold current  $I_{max}$  at which protection acts is:

#### Equation 2


$$I_{max} = \frac{OC\_COMP_{th}}{R_S}$$

Where  $R_S$  is the value of the shunt resistor and  $OC\_COMP_{th}$  is the internal reference chosen by the firmware according to [Table 1](#). Should be noticed that power MOSFETs introduce noise when switching, hence a low pass filter can be added in order to reduce noise on the OC\_COMP pin. Referring to [Figure 3](#), a resistor  $R_{LP} \gg R_S$  is used to decouple the capacitor  $C_{LP}$  and  $R_S$ . The cut-off frequency of the low pass filter is:

#### Equation 3

$$f_{LP} \cong \frac{1}{2\pi R_{LP} C_{LP}}$$

Figure 3. OC protection schematic - single shunt with low-pass filter

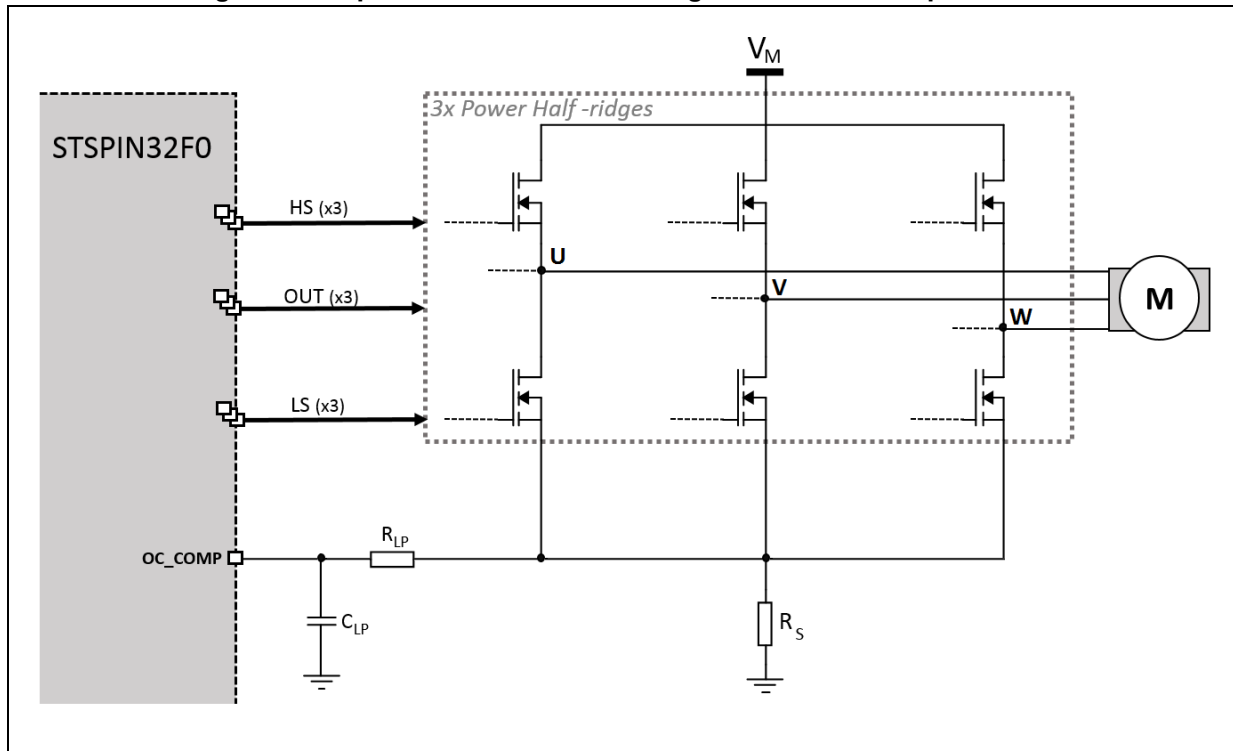

### Bias resistor on OC\_COMP pin (single shunt)

As [Equation 2](#) states, the current limit can be changed only changing the  $R_S$  or  $OC\_COMP_{th}$ . However in many applications is not possible to change the  $R_S$  and only three values are available for the  $OC\_COMP_{th}$  (see [Table 1](#)). To have a better resolution on the overcurrent threshold, it is possible to bias the OC\_COMP pin with a pull-up resistor connected to  $V_{DD}$ , supplied by the STSPIN32F0. Consequently, the equivalent threshold will be decreased by the same amount of the bias voltage.

Referring to [Figure 4](#), the OC\_COMP pin will be biased at:

#### Equation 4

$$V_{bias,OC\_COMP} = V_{DD} \cdot \frac{R_{LP}}{R_B + R_{LP}}$$

Due to the  $R_B$ , the signal coming from the shunt resistor  $R_S$  will be partitioned too; considering a current  $I_x$  flowing through the  $R_S$ , the voltage contribution on the OC\_COMP pin is:

#### Equation 5

$$V_{signal,OC\_COMP} = I_x R_S \cdot \frac{R_B}{R_B + R_{LP}}$$

Combining contributions described by [Equation 4](#) and [Equation 5](#) is possible to obtain the total voltage on the OC\_COMP pin. The value of the current  $I_x$ , for which voltage on the OC\_COMP becomes equal to the comparator internal reference  $OC\_COMP_{th}$ , is the value of the maximum current allowed ( $I_{max,b}$ ):

**Equation 6**

$$I_{max,b} \cdot R_S \cdot \frac{R_B}{R_B + R_{LP}} + V_{DD} \cdot \frac{R_{LP}}{R_B + R_{LP}} = OC\_COMP_{th}$$

In this way is possible to regulate the overcurrent threshold just changing the  $R_B$  resistor; its value can be found applying the following formula:

**Equation 7**


$$R_B \cong R_{LP} \cdot \left( \frac{V_{DD} - OC\_COMP_{th}}{OC\_COMP_{th} - I_{max,b} \cdot R_S} \right)$$

The presence of the  $R_B$  also modifies the low pass cut-off frequency stated in [Equation 3](#) as:

**Equation 8**

$$f_{LP} \cong \frac{1}{2\pi C_{LP} \frac{R_{LP} \cdot R_B}{R_{LP} + R_B}}$$

**Figure 4. OC protection schematic - single shunt with low-pass filter and bias**

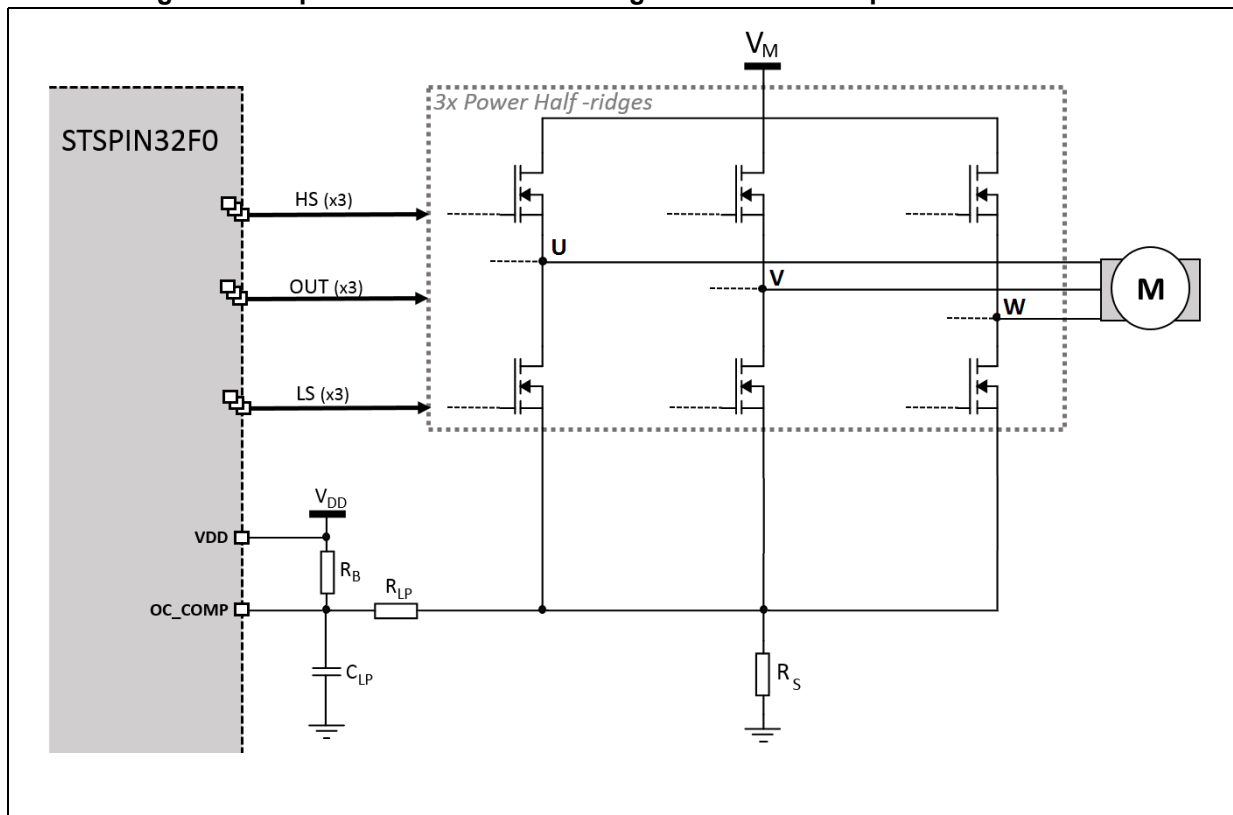

### 3 Overcurrent detection in a dual shunt topology

In this topology only two phases have a shunt resistor; the third one is connected directly to GND. *Figure 5* gives an example of the dual shunt configuration where no shunt is connected to the W phase.

The current flowing in a phase is measured only when the respective low side MOSFET is turned on. Otherwise, the current does not flow into the related shunt resistor. Therefore, the overall current measured can be a combination of  $I_U$ ,  $I_V$ , and  $I_W$  as listed in *Table 3*. According to *Equation 1* is possible to know the value of the current about a phase, using the value coming from the other two phases. This is the reason why the third shunt (e.g. on the phase W) is not connected.

However, potential issues can arise in overcurrent protection. Since the current on the phase W is not measured, high currents can flow in the phases but the signal coming from the other two shunt resistor is lower than expected. The worst case is when the U and V high side MOSFETs are on and the W low side MOSFET is on. In this situation, high currents can flow, but the voltage on the OC\_COMP pin is always zero, hence overcurrent protection cannot be triggered.

For this reason, the dual shunt configuration for overcurrent protection can be used but is not recommended. Taking into account this notice, the overcurrent protection in dual shunt configuration can be analyzed as done in *Section 2* for single shunt configuration.

**Figure 5. Power stage and OC protection schematic - dual shunt**

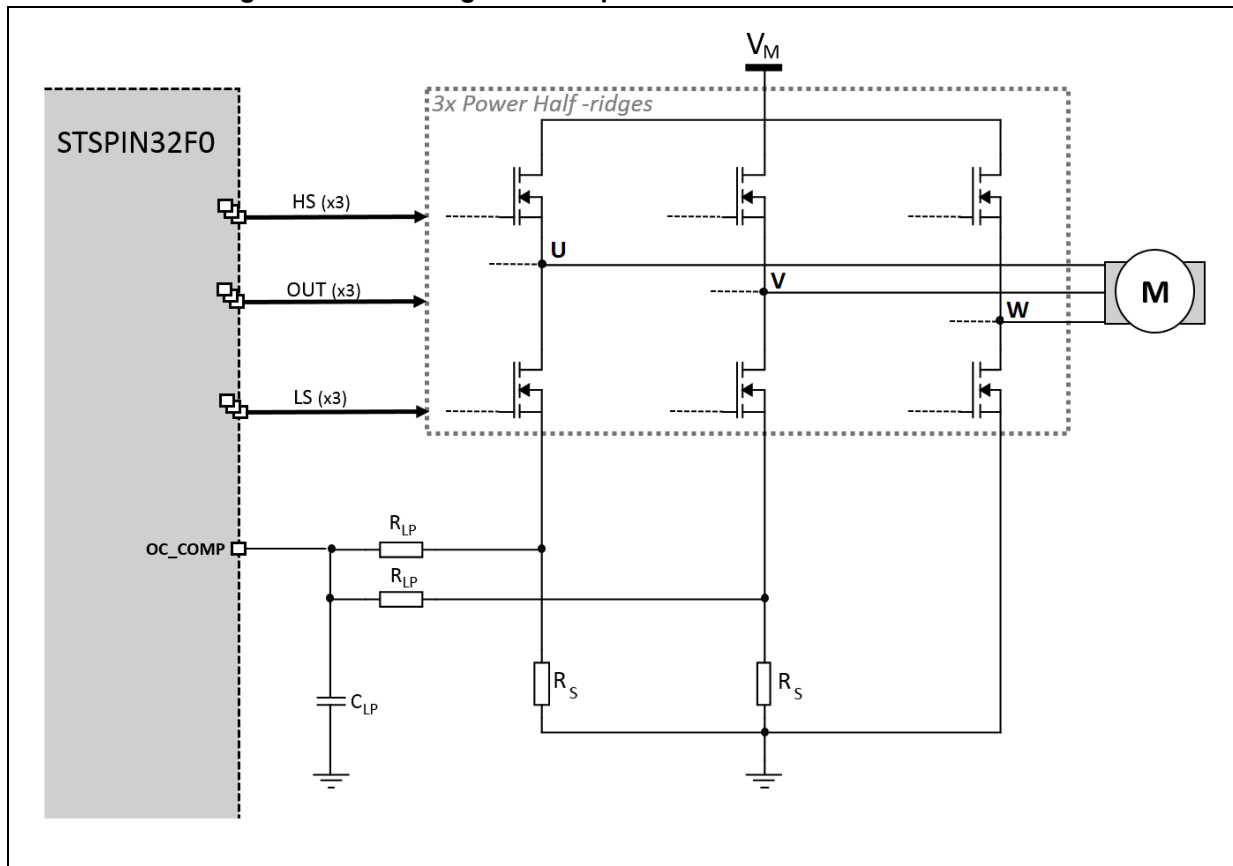




Table 3. Measured current according to power MOSFETs state - dual shunt

Power MOSFET turned ON			Measured current on OC_COMP input
Phase U	Phase V	Phase W	
Low side	Low side	Low side	$(I_U + I_V) \cdot R_S = -I_W R_S$
Low side	Low side	High side	$(I_U + I_V) \cdot R_S = -I_W R_S$
Low side	High side	Low side	$I_U \cdot R_S^{(1)}$
Low side	High side	High side	$I_U \cdot R_S$
High side	Low side	Low side	$I_V \cdot R_S^{(1)}$
High side	Low side	High side	$I_V R_S$
High side	High side	Low side	$0^{(1)}$
High side	High side	High side	0

1. Current is not measured on the phase W, potential issues can arise in overcurrent measurements.

According to the schematic shown in [Figure 5](#), the threshold current  $I_{max}$  at which protection acts is:

#### Equation 9

$$I_{max} = \frac{2 \cdot OC\_COMP_{th}}{R_S}$$

Where  $OC\_COMP_{th}$  is the comparator internal reference chosen by the firmware according to [Table 1 on page 3](#).

The low pass filter introduced by the  $C_{LP}$  reduces noise on the OC\_COMP pin. Referring to [Figure 5](#), the cut-off frequency of the filter is:

#### Equation 10

$$f_{LP} \cong \frac{1}{\pi R_{LP} C_{LP}}$$

## Bias resistor on OC\_COMP pin (dual shunt)

As [Equation 9](#) states, the current limit can be changed only by changing the  $R_S$  or  $OC\_COMP_{th}$ . However in many applications is not possible to change the  $R_S$  and only three values are available for  $OC\_COMP_{th}$  (see [Table 1](#)). To have a better resolution on the overcurrent threshold is possible to bias the OC\_COMP pin with a pull-up resistor connected to  $V_{DD}$ , supplied by the STSPIN32F0. Consequently, the equivalent threshold will be decreased by the same amount of the bias voltage.

Referring to [Figure 6](#), the OC\_COMP pin will be biased at:

#### Equation 11

$$V_{bias,OC\_COMP} = V_{DD} \cdot \frac{R_{LP}}{2R_B + R_{LP}}$$

Due to the  $R_B$ , the signal coming from the shunt resistors  $R_S$  will be partitioned too; considering the sum of the currents  $I_x$  flowing through the shunts  $R_S$  (in this specific case U and V), the voltage contribution on the OC\_COMP pin is:

**Equation 12**

$$V_{signal,OC\_COMP} = \sum_{x=U,V} I_x R_S \cdot \frac{R_B}{2R_B + R_{LP}}$$

Combining contributions described by [Equation 11](#) and [Equation 12](#) is possible to obtain the total voltage on the OC\_COMP. The total value of the current for which voltage on the OC\_COMP becomes equal to the comparator internal reference  $OC\_COMP_{th}$ , is the value of the maximum current allowed ( $I_{max,b}$ ):

**Equation 13**

$$I_{max,b} \cdot R_S \cdot \frac{R_B}{2R_B + R_{LP}} + V_{DD} \cdot \frac{R_{LP}}{2R_B + R_{LP}} = OC\_COMP_{th}$$

In this way is possible to regulate the overcurrent threshold just changing the  $R_B$  resistor; its value can be found applying the following formula:

**Equation 14**


$$R_B \cong R_{LP} \cdot \left( \frac{V_{DD} - OC\_COMP_{th}}{2 \cdot OC\_COMP_{th} - I_{max,b} \cdot R_S} \right)$$

The presence of the  $R_B$  also modifies the low pass cut-off frequency stated in [Equation 10](#).

**Equation 15**

$$f_{LP} \cong \frac{1}{2\pi C_{LP} \frac{R_{LP} \cdot R_B}{2R_B + R_{LP}}}$$

Figure 6. OC protection schematic with low-pass filter and bias - dual shunt

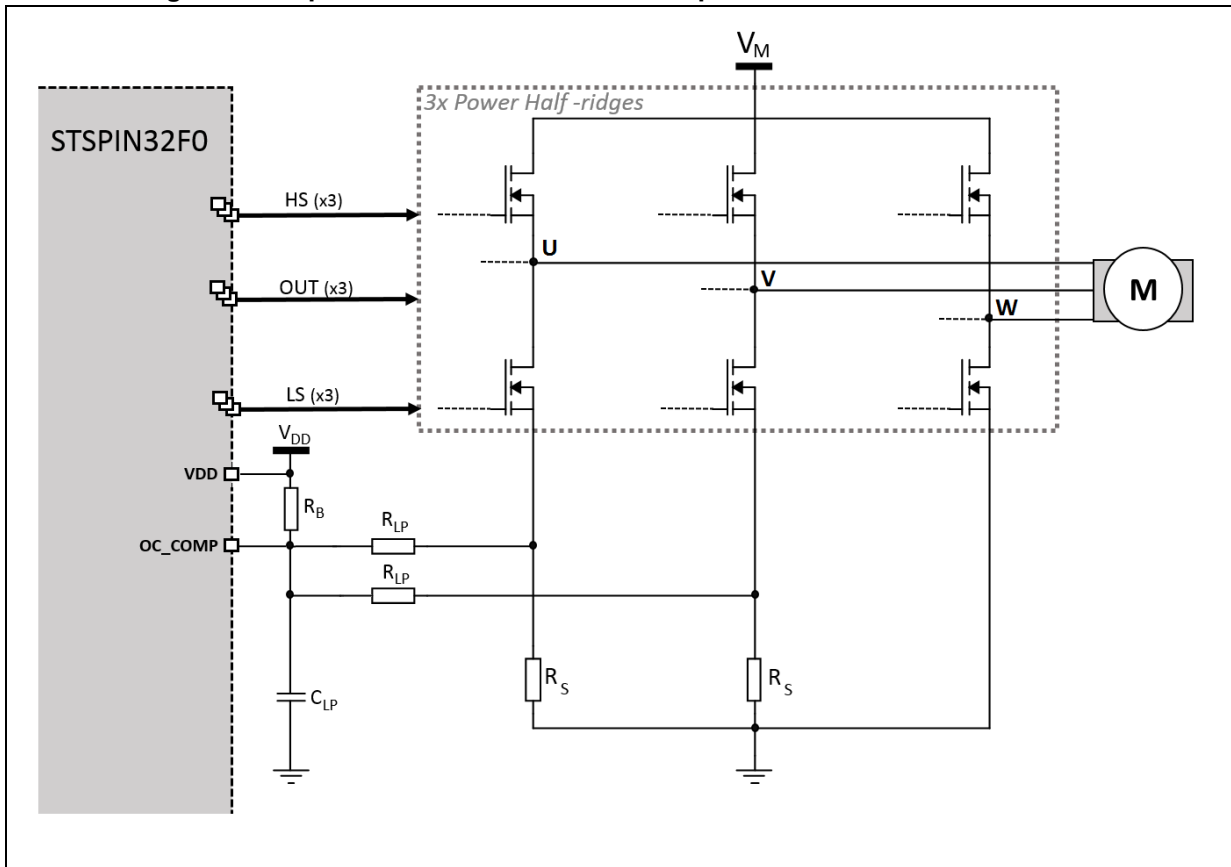

## 4 Overcurrent detection in a triple shunt topology

In this configuration the low side MOSFET of each half-bridge is connected to a shunt resistor used to measure the current in that phase. Referring to [Figure 7](#), three resistors ( $R_{LP}$ ) with the same value are used to sum the voltage of each shunt. Assume to choose  $R_{LP} \gg R_S$  so that all the current coming from a phase flows into the  $R_S$ . The voltage on the  $R_S$  is then reported on the OC\_COMP pin through the partition given by the  $R_{LP}$  resistors. For a given phase X the voltage on the shunt resistor  $V_{R,X}$  depends on the current flowing through the low side MOSFET on that phase:

### Equation 16

$$V_{R,X} \cong I_X \cdot R_S$$

The voltage  $V_{R,X}$  is then reported on the OC\_COMP pin through the partition made by the resistors  $R_{LP}$ . The resulting voltage on the OC\_COMP is:

### Equation 17

$$V_{OC\_COMP,X} \cong V_{R,X} \cdot \frac{1/2 (R_{LP} + R_S)}{R_{LP} + 1/2 (R_{LP} + R_S)}$$


Using [Equation 16](#) and considering  $R_{LP} \gg R_S$ , [Equation 17](#) becomes:

### Equation 18

$$V_{OC\_COMP,X} \cong 1/3 I_X \cdot R_S$$

Each phase gives its contribution according to [Equation 18](#), so that the overall signal on the OC\_COMP pin is the sum of the voltage on each shunt resistor. As [Equation 18](#) shows, the main disadvantage of this circuitry is that the signal generated on the shunt resistor is attenuated by 1/3; however just three more resistors are needed.

Figure 7. Power stage and OC protection schematic - triple shunt

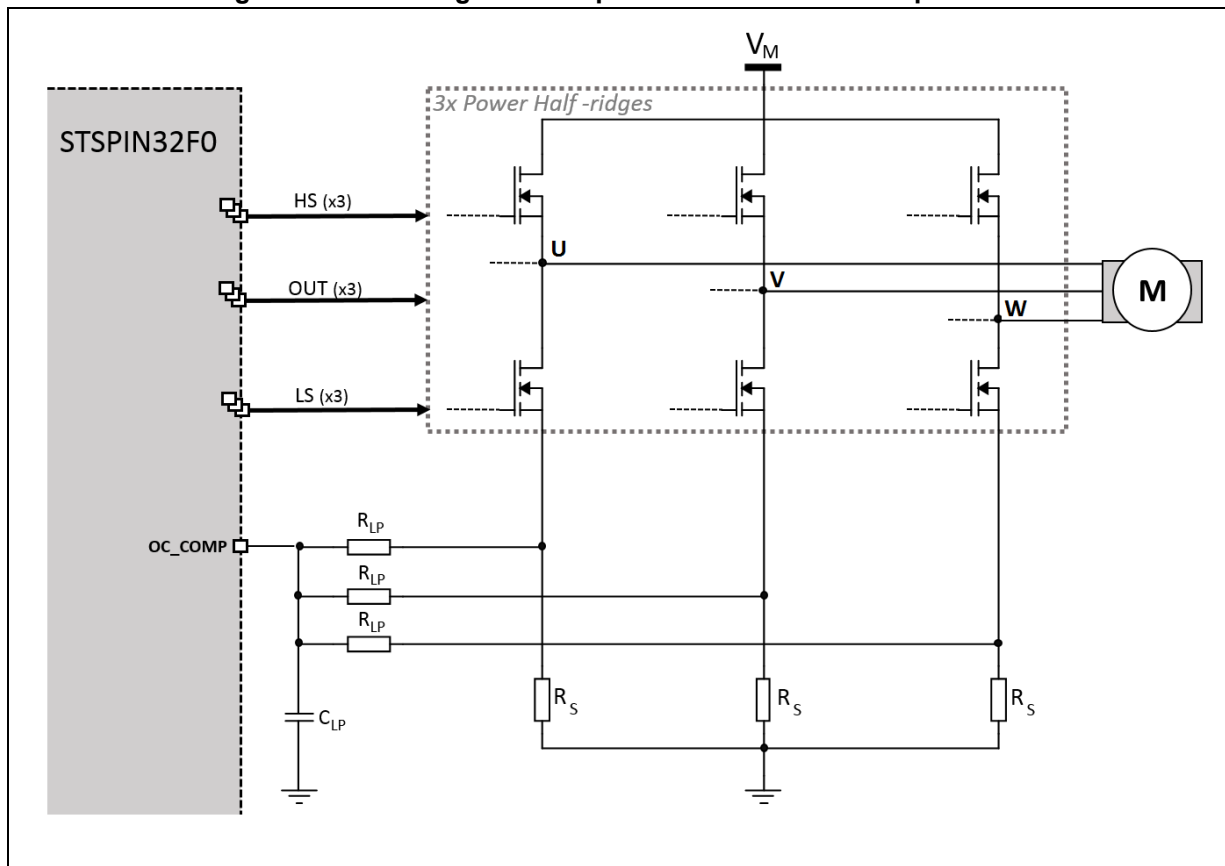


The current flowing in a phase is measured only when the respective low side MOSFET is turned on. Otherwise, the current does not flow into the related shunt resistor. Therefore, the overall current measured can be a combination of  $I_U$ ,  $I_V$ , and  $I_W$  as listed in [Table 4](#). The value of the current in a phase can be determined using the information coming from the other two phases according to [Equation 1 on page 4](#).

Table 4. Measured current according to power MOSFETs state

Power MOSFET turned ON			Measured current on OC_COMP input
Phase U	Phase V	Phase W	
Low side	Low side	Low side	0
Low side	Low side	High side	$1/3 \cdot (I_U + I_V) \cdot R_S = -1/3 \cdot I_W \cdot R_S$
Low side	High side	Low side	$1/3 \cdot (I_U + I_W) \cdot R_S = -1/3 \cdot I_V \cdot R_S$
Low side	High side	High side	$1/3 \cdot I_U \cdot R_S$
High side	Low side	Low side	$1/3 \cdot (I_V + I_W) \cdot R_S = -1/3 \cdot I_U \cdot R_S$
High side	Low side	High side	$1/3 \cdot I_V \cdot R_S$
High side	High side	Low side	$1/3 \cdot I_W \cdot R_S$
High side	High side	High side	0


It should be noticed that phases are inductive loads and their current is controlled using the PWM method. This means that voltages and currents are not instantly correlated; e.g. on a given phase X, the high side MOSFET can be turned on but the current  $I_x$  flows into  $OUT_x$ . Conversely, the low side MOSFET can be on but the current flows out from  $OUT_x$ . This happens when the current in the inductive load is discharging. However, the current limiting based on overcurrent protection acts when the loads are charging. In this case, the maximum current flowing through one phase can be measured as the sum of the other two currents, as shown in [Table 4](#) and considering [Equation 1 on page 4](#).

**Figure 8. Example showing the output currents**

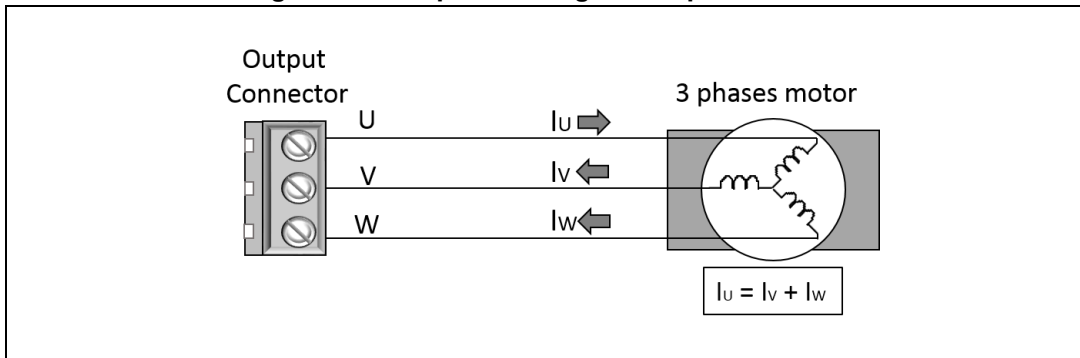

As an example let's now consider the specific situation depicted in [Figure 8](#), where the current is flowing into the phase U and comes back from the phase V and W. The PWM voltage signals are applied on the output nodes in order to control the currents ([Figure 9](#)). The higher current in this example is  $I_U$ : the maximum value that the OC\_COMP pin will reach is  $1/3 \cdot I_U \cdot R_S$ , just when the OUTU high side is on and the OUTV, W low sides are on. The amount of time for which OC\_COMP voltage stays at this value depends on PWM frequency and duty cycles of the outputs. Should be noticed that the  $C_{LP}$  must be sized taking into account this timing, together with the response time of the overcurrent protection.

Figure 9. Example showing PWM voltage signals and related OC\_COMP voltage

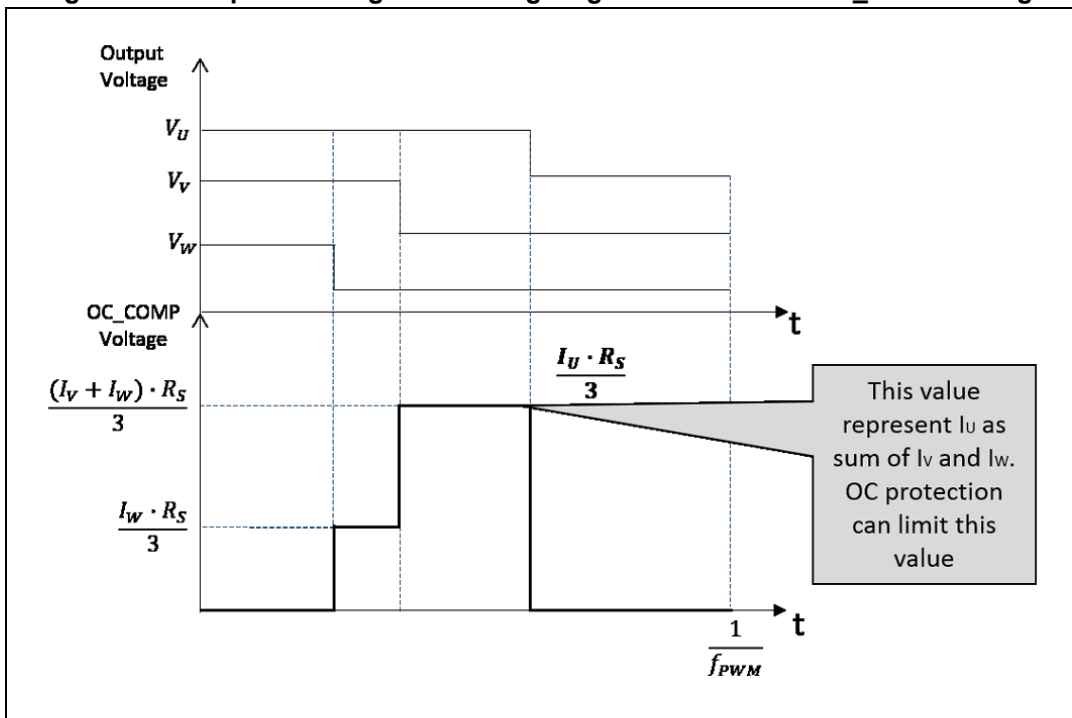

### 4.1 Sizing components values

Referring to the general schematic shown in [Figure 7](#), some consideration (already done in [Section 2 on page 4](#) and [Section 3 on page 8](#)) can be done for components sizing. The  $R_{LP}$  resistors are chosen to be much greater than the  $R_S$  in order to decouple the current signals on each phase: the error due to coupling effects is:

Equation 19

$$\epsilon = \frac{2R_S}{3(R_{LP} + R_S)} \cong \frac{2R_S}{3R_{LP}}$$

In the most of applications  $R_S < 1 \Omega$  and  $R_{LP} > 1 \text{ k}\Omega$ , so coupling error is negligible.

The capacitor  $C_{LP}$  on the OC\_COMP pin reduces noise and spikes generated by power MOSFET switching. The cut-off frequency of the low pass filter is:

Equation 20

$$f_{LP} \cong \frac{3}{2\pi R_{LP} C_{LP}}$$

The cut-off frequency can be chosen in order to have a response time of OC protection suitable for the application. A good trade-off between noise reduction and response time is to set the low pass frequency about 5 times the PWM frequency ( $f_{PWM}$ ).

The threshold current  $I_{max}$  at which the overcurrent protection acts is:

**Equation 21**

$$I_{max} \cong \frac{3 \cdot OC\_COMP_{th}}{R_S}$$

Where  $OC\_COMP_{th}$  is the comparator internal reference chosen by the firmware according to [Table 1 on page 3](#).

**Example 1**

Assume PWM control with a  $f_{PWM} = 40$  kHz that generates three sinusoidal currents in the motor phases. The nominal peak current is 1.5 A and the desired overcurrent threshold should be set at 3 A.

Using  $R_S = 0.1\Omega$ ,  $R_{LP} = 2.2$  k $\Omega$ ,  $C_{LP} = 1$  nF and choosing the  $OC\_COMP$  threshold at 100 mV is possible to disable the outputs when the current in one of the three phases reaches 3 A. The low pass filtering performed by the  $R_{LP}$  and  $C_{LP}$  has a frequency  $f_{LP} \sim 217$  kHz, which is about 5 times the PWM frequency.

## 4.2 Bias resistor on $OC\_COMP$ pin (triple shunt)

As [Equation 21](#) states, the current limit can be changed only changing the  $R_S$  or  $OC\_COMP_{th}$ . However in many applications is not possible to change  $R_S$  and only three values are available for  $OC\_COMP_{th}$  (see [Table 1 on page 3](#)). To have a better resolution on the overcurrent threshold, is possible to bias the  $OC\_COMP$  pin with a pull-up resistor connected to  $V_{DD}$ , supplied by the STSPIN32F0. Consequently, the equivalent threshold will be decreased by the same amount of the bias voltage.

Referring to [Figure 10](#), the  $OC\_COMP$  pin will be biased at:

**Equation 22**

$$V_{bias,OC\_COMP} \cong V_{DD} \cdot \frac{R_{LP}}{3R_B + R_{LP}}$$

Due to the  $R_B$ , the signal coming from the shunt resistors  $R_S$  will be partitioned too; considering the sum of the currents  $I_x$  flowing through the  $R_S$  for each phase, the voltage contribution on the  $OC\_COMP$  pin is:

**Equation 23**

$$V_{signal,OC\_COMP} = \sum_{x=U,V,W} I_x R_S \cdot \frac{R_B}{3R_B + R_{LP}}$$



Combining contributions described by [Equation 22](#) and [Equation 23](#) is possible to obtain the total voltage on the OC\_COMP. The total value of the current for which voltage on the OC\_COMP becomes equal to the comparator internal reference  $OC\_COMP_{th}$ , is the value of the maximum current allowed ( $I_{max,b}$ ):

#### Equation 24

$$I_{max,b} \cdot R_S \cdot \frac{R_B}{3R_B + R_{LP}} + V_{DD} \cdot \frac{R_{LP}}{3R_B + R_{LP}} = OC\_COMP_{th}$$

In this way is possible to regulate the threshold just changing the  $R_B$  resistor; its value can be found applying the following formula:

#### Equation 25

$$R_B = R_{LP} \cdot \left( \frac{V_{DD} - OC\_COMP_{th}}{3 \cdot OC\_COMP_{th} - I_{max,b} \cdot R_S} \right)$$

The presence of the  $R_B$  also modifies the low pass cut-off frequency stated in [Equation 20](#).


#### Equation 26

$$f_{LP} \cong \frac{1}{2\pi C_{LP} \frac{R_{LP} \cdot R_B}{3R_B + R_{LP}}}$$

#### Example 2

Referring to [Example 1](#), consider to change the overcurrent threshold to 2 A using the same values of the  $OC\_COMP_{th}$  and  $R_S$ . According to [Equation 25](#) using a  $R_B \cong 70 \text{ k}\Omega$  is possible to reduce the overcurrent threshold from 3 A to 2 A thus matching the new requirement on the overcurrent threshold. The filter frequency becomes slightly increased at 219 kHz, so no changes are needed on the  $C_{LP}$ .

Figure 10. OC COMP read-out with schematic (biased)

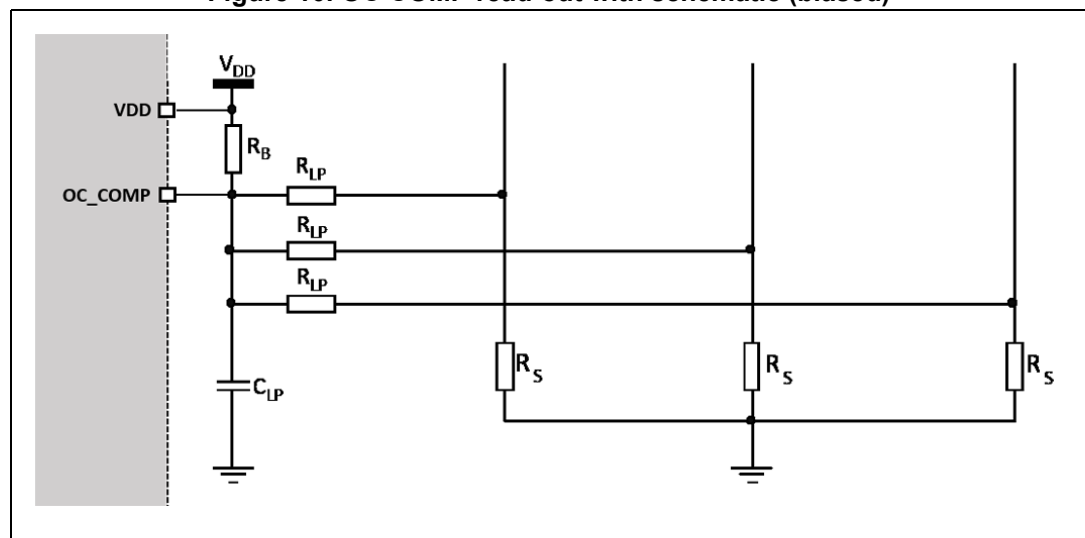

## 5 Conclusions

Despite of different shunt configurations described in [Section 2 on page 4](#), [Section 3 on page 8](#), and [Section 4 on page 12](#), the results obtained are similar. Hereafter all the parameters used in the formulas are listed:

- $I_{max,th}$ : current threshold at which the OC protection is triggered
- $OC\_COMP_{th}$ : internal reference for the comparator (can be 100, 250 or 500 mV - see [Table 1 on page 3](#))
- $R_S$ : shunt resistor(s)
- $R_{LP}$ : resistor used to bring the signal from the shunt resistor(s) to the OC\_COMP pin
- $C_{LP}$ : filter capacitor on the OC\_COMP pin
- $R_B$ : optional resistor for the OC\_COMP pin biasing
- $V_{DD}$ : digital voltage supplied by the STSPIN32F0 (3.3 V typ.)
- $F_{PWM}$ : frequency of the PWM driving signals

Moreover consider the parameter  $N_S$ , which represents the number of the shunt resistors used (e.g. for single shunt configuration  $N_S = 1$ ). [Table 5](#) summarizes the formulas, with or without the OC\_COMP biasing the resistor  $R_B$ .

**Table 5. Formulas summary**

Bias condition	Resistor to be chosen	Low pass cut off frequency
No bias on OC_COMP	$R_S = \left( \frac{N_S \cdot OC\_COMP_{th}}{I_{max,th}} \right)$	$f_{LP} = \frac{N_S}{2\pi R_{LP} C_{LP}}$
OC_COMP biased	$R_B = R_{LP} \cdot \left( \frac{V_{DD} - OC\_COMP_{th}}{N_S \cdot OC\_COMP_{th} - I_{max,th} \cdot R_S} \right)$	$f_{LP,b} = \frac{N_S R_B + R_{LP}}{2\pi R_{LP} C_{LP} R_B}$

### Application example

This paragraph analyzes the setup described in [Example 1](#), and shows how to act the OC protection feature. The power MOSFETs are connected to the STSPIN32F0 in a three shunt configuration and the OC\_COMP pin is connected as shown in [Figure 7 on page 13](#).

The firmware loaded into the internal MCU generates the 6 PWM signal resulting in 3 sinusoidal currents in the motor phases. Sinewaves are delayed of 120° each other, in order to implement open-loop voltage driving: PWM duty cycles are modulated in order to have a sinusoidal profile with specified amplitude.

As stated in [Example 1](#), the following conditions are used:


- $f_{PWM} = 40$  kHz
- $R_S = 0.1 \Omega$
- $R_{LP} = 2.2$  kΩ
- $C_{LP} = 1$  nF
- $OC\_COMP_{th} = 100$  mV

Since the triple shunt configuration is used,  $N_S = 3$ . The current threshold which triggers the OC protection is  $I_{max,th} = 3\text{ A}$  - see [Equation 21 on page 16](#). The analysis here described wants to highlight the effects of the OC protection: therefore, a peak current higher than the threshold is imposed. In this example, PWM duty cycles are chosen in order to have a current in each phase equal to the 7 A peak.

The resulting current acquisition for a single phase is reported in [Figure 11](#). When the OC protection is disabled ( $OC\_SEL = 0$ ) the power MOSFETs work without limitations and the value of the peak current reaches the expected value of 7 A. Otherwise enabling the OC protection ( $OC\_SEL = 1$ ), the power MOSFETs are disabled whenever the current reaches the limit of 3 A, so the current is clamped and cannot reach the peak value of 7 A.

Although [Figure 11](#) shows just one phase, the clamping due to the OC protection is present in the same way on all the three phases.

**Figure 11. OC protection effect on a phase current**

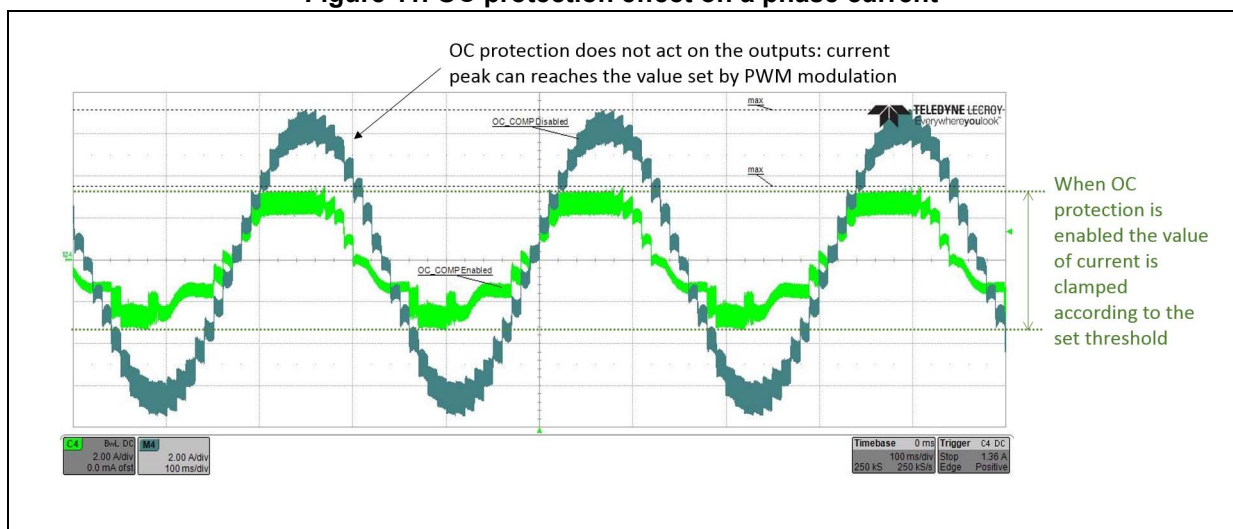

## 6 Revision history

Table 6. Document revision history

Date	Revision	Changes
31-Jan-2017	1	Initial release.

**IMPORTANT NOTICE – PLEASE READ CAREFULLY**

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2017 STMicroelectronics – All rights reserved