



## ST1S03 alternative topology: Using a buck in a negative buck-boost configuration

*Designs from our labs describe tested circuit designs from ST labs which provide optimized solutions for specific applications. For more information or support, visit [www.st.com](http://www.st.com)*

By Nicola Siciliano

Main components	
ST1S03	1.5 A, 1.5 MHz adjustable, step-down switching regulator

### Specification

- ST1S03 (Buck regulator) in buck-boost configuration
- $V_{in}=3.3V$ ,
- $V_{out}=-5V$ ,
- $I_{out}$  up to  $-500mA$

### Circuit description: From a buck to a buck-boost

#### 1) Buck topology: Basic Working Principle in Continuous Conduction Mode

The schematic in Figure 1 shows the ST1S03 configured as a step-down converter. The  $V_{out}$  is adjustable through the external resistor divider  $R_1$  and  $R_2$  according to the following equation:

$$V_{OUT} = V_{FB} \left[ 1 + \frac{R_1}{R_2} \right] \text{ with a duty cycle of } D = \frac{V_{out}}{V_{in}} .$$

During  $T_{ON}$ , the internal switch (between  $V_{in-SW}$  and  $SW$ ) is ON and the inductor  $L_1$  is connected between  $V_{IN}$  and  $V_{OUT}$ . The inductor current ( $I_L$ ) rate of change is given by:

$$\frac{di}{dt} = \frac{V_{in} - V_{out}}{L} .$$

During  $T_{OFF}$ , the inductor starts to release the energy (stored during  $T_{ON}$ ) so the voltage across it changes polarity to keep the current flowing in the same direction. Assuming for simplicity the voltage drop across diode  $D1$  is negligible, the inductor current ramps down at a rate of:


$$\frac{di}{dt} = \frac{V_{out}}{L}$$

The steady-state load current is always carried by the inductor during both ON and OFF times. The average inductor current is equal to the load current, and the peak-to-peak inductor ripple current is

$$I_{L(PP)} = \frac{(V_{in} - V_{out})D}{f_{sw}L}$$

where  $f_{sw}$  is the switching frequency, which is 1.5MHz for the ST1S03.

**Figure 1. ST1S03 in Step-Down (Buck) configuration**

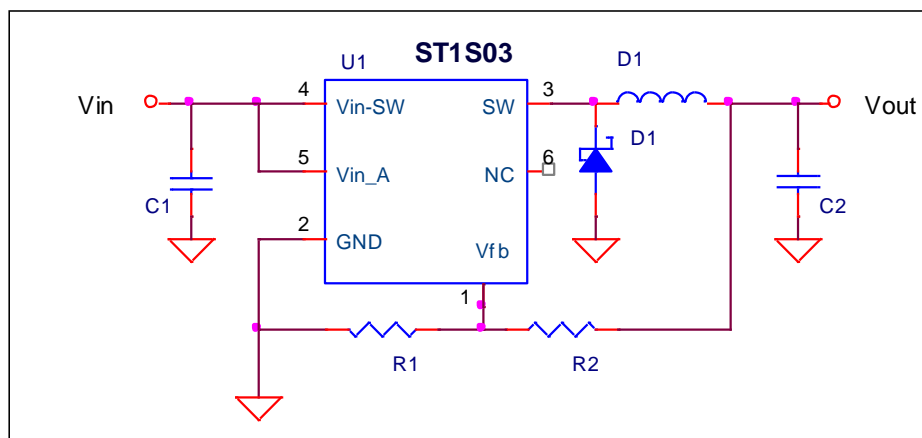


## 2) **Alternative Buck-boost topology: Basic Working Principle in Continuous Conduction Mode**

Starting from the application schematic in Figure 1, it is possible, with only a few adjustments, to switch from a buck configuration to an inverting buck-boost configuration.

The new schematic is shown in Figure 2. Compared to the buck configuration, the main differences are:

- 1) Device GND (pin2) is connected to the Output, which is the point at the lowest potential in the application.
- 2) The Schottky diode D1 is reversed, with the cathode toward the device and the anode toward Vout.
- 3) The inductor L1 is tied to the GND of the system.
- 4) Capacitor C3 is added between Vin and Vout as a bypass capacitor across the device voltage input (pin2 and pin 4).

Figure 2. ST1S03 in Buck-Boost configuration @ Vin=3.3V, Vout=-5V, Iout up to -500mA

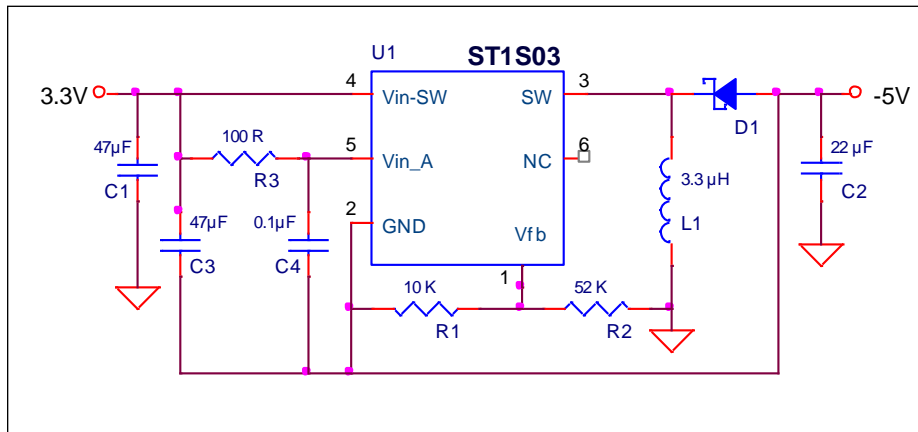

At power-up ( $t_0$  of the Vcc ramp-up), the device GND (pin2) is at the same potential as the GND system ( $V_{out}=0V$ ). Once the input voltage rises above 2.5V, the circuit starts switching, energizing the inductor.  $V_{out}$  then starts to increase “negatively”, until the drop across R1 reaches 0.8V above  $V_{out}$ .

The output voltage is still determined by the resistors divider R1 and R2, according to the equation:

$$|V_{out}| = V_{FB} \left[ 1 + \frac{R_1}{R_2} \right]$$

But in this case,  $V_{out}$  is negative. With a duty cycle of:

$$D = \frac{|V_{out}|}{V_{in} + |V_{out}|}$$

During  $T_{ON}$ , the internal switch (between  $V_{in-SW}$  and SW) is ON, so the inductor L1 is connected between  $V_{IN}$  and GND, and the inductor current ( $I_L$ ) rate of change is given by:

$$\frac{di}{dt} = \frac{V_{in}}{L}$$

During this phase, only the output capacitor C2 provides the output current.

At  $T_{OFF}$  (internal switch is off), the inductor starts to release the energy stored during  $T_{ON}$  so the voltage across it changes polarity to keep the current flowing in the same direction. The voltage across the inductor becomes approximately  $V_{OUT}$ , and the inductor current decreases at a rate of:

---

$$\frac{di}{dt} = -\frac{V_{out}}{L}$$

During  $T_{OFF}$  the inductor supplies current to the load and also replenishes the energy lost by the capacitor during  $T_{ON}$ . For the buck-boost circuit, the average inductor current is:

$$I_{L(avg)} = \frac{I_{out}}{1-D}$$

and the peak-to-peak inductor current is:

$$I_{L(PP)} = \frac{V_{in}D}{f_{SW}L}$$

The average inductor current cannot exceed the average rated current of the switching regulator ( $I_{SW}$ ); therefore the buck-boost output current is reduced by a factor of  $1 - D$ . In this configuration, the maximum available DC output current is:

$$I_{OUT} = I_{SW}(1-D).$$

and, the ST1S03 rated current ( $I_{SW}$ ) is 1.5A.

These basic differences between the two circuits' functionality must be taken in to consideration when a buck converter IC is used as a buck-boost converter.

### 3) Input Voltage and output current

In the buck-boost topology of Figure 2, the ST1S03 ground pin is connected to  $V_{OUT}$ . Therefore the voltage across the device is  $V_{IN} + |V_{OUT}|$ , rather than just  $V_{IN}$  as in the buck topology. The differential between the two voltages cannot exceed the ST1S03 maximum rating of 16V.

$$V_{in} + |V_{out}| < 16V$$

In addition, a minimum  $V_{IN} = 3V$  it is needed to guarantee the application start-up.


The current capability depends on the application's input and output voltages, which dictate the duty cycle and therefore the maximum output current.

## Measurement results

The suggested buck- boost topology (based on ST1S03) was tested using the schematic in Figure 2. The waveforms in Figure 3 show a typical behavior under the following conditions:

- $V_{in} = 3.3V$
- $V_{out} = -5V$
- $I_{out} = -500mA$

**Figure 3. Buck-Boost waveforms @  $V_{in}= 3.3V$ ,  $V_{out}= -5V$ ,  $I_{out}= -500mA$**

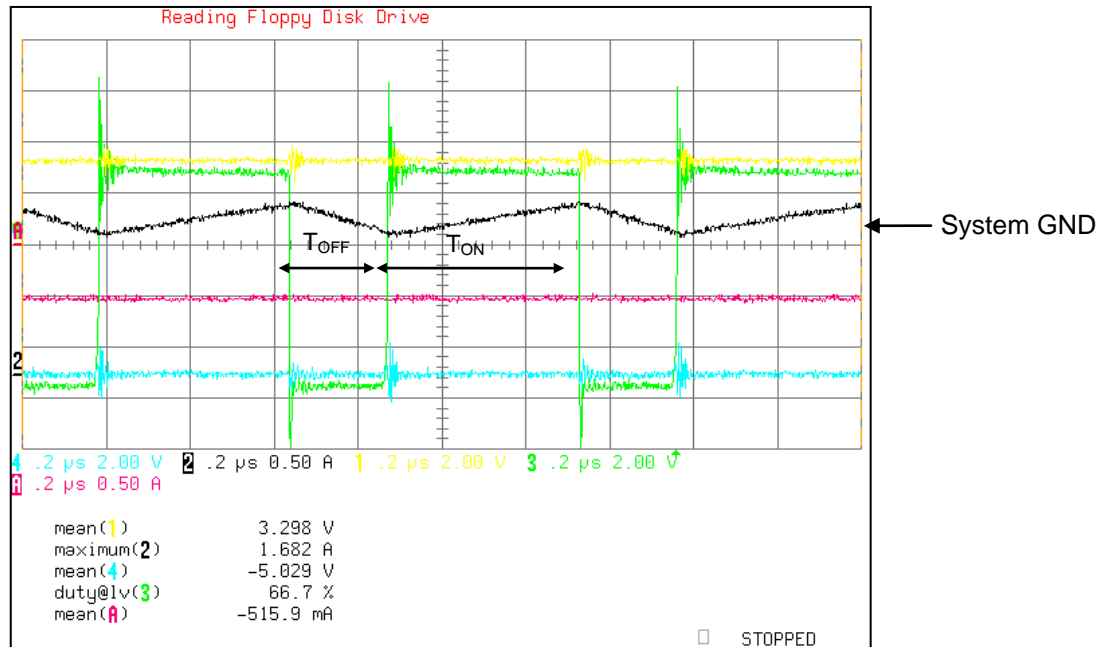

- Channel 1 (yellow) is  $V_{in} = 3.3V$
- Channel 2 (black) is the inductor current; 1.7A max
- Channel 3 (green) is the switching node (pin 3 on the ST1S03), duty-cycle 66%
- Channel 4 (light blue) is  $V_{out} = -5.0V$
- A (purple) is  $I_{out} = -500mA$

The test results show the impact of the losses due to the ST1S03, diode and the additional components, which are not accounted for in the formulas here presented (Table 1).

### Consideration

When an asynchronous buck converter such as the ST1S03 is used in an inverting buck-boost configuration, certain considerations must be made. The basic design equations of the two topologies presented here are collected in Table 1. These equations address the continuous conduction mode in simplified form because they assume the losses on the semiconductors and other components are negligible.

**Table 1. Basic design equations in continuous conduction mode**

	<b>Buck</b>	<b>Buck-boost</b>
Duty cycle	$D = \frac{V_{out}}{V_{in}}$	$D = \frac{ V_{out} }{V_{in} +  V_{out} }$
Average inductor current	$I_{L(avg)} = I_{out}$	$I_{L(avg)} = \frac{I_{out}}{1-D}$
Peak-to-peak inductor ripple current	$I_{L(PP)} = \frac{(V_{in} - V_{out})D}{f_{sw}L}$	$I_{L(PP)} = \frac{V_{in}D}{f_{sw}L}$
Ramp-up inductor current	$\frac{di}{dt} = \frac{V_{in} - V_{out}}{L}$	$\frac{di}{dt} = \frac{V_{in}}{L}$
Ramp-down inductor current	$\frac{di}{dt} = \frac{V_{out}}{L}$	$\frac{di}{dt} = -\frac{V_{out}}{L}$

## Variations

The following are some of the ST asynchronous buck regulators that can be configured as negative buck-boost

- L497x family
- L597x family
- L5980,1, 3, 5, 6 & 7
- L798x family

## Support material

<p><b>Product Evaluation board:</b></p> <ul style="list-style-type: none"> <li>• STEVAL-ISA042V2: 1.5 A / 3.3 V step-down DC-DC converter demonstration board based on the ST1S03</li> <li>• STEVAL-ISA042V1: 1.5 A / 1.2 V step-down DC-DC converter demonstration board based on the ST1S03</li> </ul>
<p><b>Datasheet</b> – ST1S03: 1.5 A, 1.5 MHz adjustable, step-down switching regulator</p>
<p><b>Application note :</b></p> <ul style="list-style-type: none"> <li>• AN2093: ST1S03 buck converters for HDD power supplies</li> <li>• AN2837: Positive to negative buck-boost converter using ST1S03 asynchronous switching regulator</li> </ul>

## Revision history

Date	Version	Changes
30-Aug-2012	1	Initial release

---

### Please Read Carefully

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at anytime, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2012 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)