

---

## Improving voltage regulation of a buck converter using the VIPerPLUS

---

By Jianwen Shao

Main components	
Viper06L	Fixed frequency VIPer™ plus family
Viper16	Fixed frequency VIPer™ plus family
Viper26	Fixed frequency VIPer™ plus family
STTH1R06A	TURBO 2 Ultrafast High Voltage Rectifier

### Purpose and benefits

The Viperx6 buck converter, part of the VIPerPLUS family of high voltage offline SMPS converters that includes the Viper06, Viper16, and Viper26, has been designed to start at very low input voltages and can operate with up to 700V input.


During shutdown of the Viperx6 and at very low input voltages below 40 volts, however, it can lose regulation if the load is very light. In this Design Tip, different options are presented to address this issue.

### Description

The solution for improving the voltage regulation is to add a few simple components to limit the output voltage. Three options are presented that work well, taking into account the trade-offs between power and cost.

To illustrate the solution, a power converter design with a target range of 45V to 450V, with some margin, has been implemented by modifying ST's standard demo board, STEVAL-ISA130V1. Figure 1 shows the schematic for a 15V 100mA non-isolated power supply using the Viper06.

Figure 1. Circuit diagram of power converter with target range of 46V to 450V

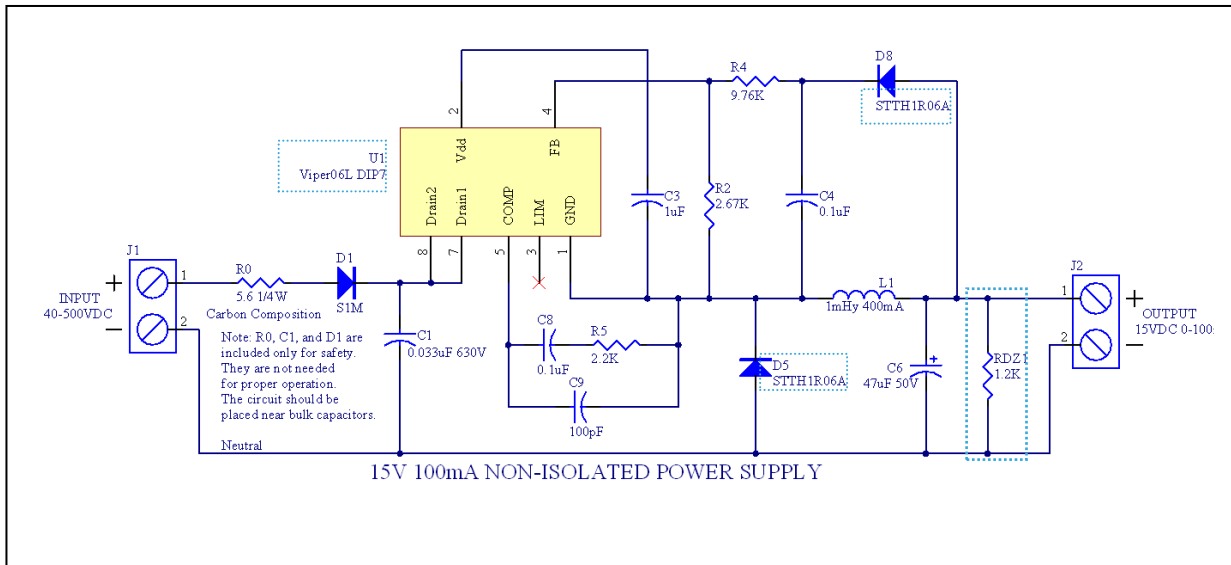

## Design Specifications

Input 46V to 450Vdc  
Output: 15Vdc +/-10%

## Performance Outside of Specified Input Range

The converter was tested to determine if there were any concerns regarding whether the input range was being exceeded on either end.

For high input voltages, there were no issues as the unit operated correctly to over 530Vdc input.

For low input voltages, it is assumed that the unit will run from large capacitors used to filter the power electronics and these will slowly discharge below the specified range. As the input voltage is reduced, the unit loses regulation with very light loads and the output voltage rises. Therefore, for a low input voltage, a light load or a voltage clamp is required.

This can easily be addressed in one of three ways. As it takes about 14mA of load current to hold the output voltage in the specified range, the solution is to add a simple component to limit the output voltage as shown in Figure 1 for RDZ1.

Three possible solutions for RDZ1 including cost-power dissipation trade-offs are described:

1. Add a single preload resistor of 1.2K $\Omega$  that dissipates about 0.23 Watts. This solution is the simplest and least expensive one but dissipates the most power.
2. Increase the preload resistor to 3.3K $\Omega$ , assuming the other side has a minimum load of 10mA, for 0.07 Watt dissipation. The benefit is

better power dissipation than the third option, but it relies on minimum load.

3. Install an 18V Zener diode which dissipates about 0.25 watts minus light load power worst case during shutdown. The benefit is very low power dissipation during normal operating mode with normal input voltage range.

After adding the component for RDZ1 as described in #1 above, typical results for the regulation test data are shown below.

**Figure 2. Regulation test data**

Input V	No Load	10mA	30mA	100mA
45	16.04	15.81	15.55	15.33
100	15.7	15.47	15.27	15.17
200	15.49	15.36	15.22	15.15
300	15.7	15.37	15.27	15.17
400	16.11	15.69	15.32	15.15
500	16.39	15.96	15.49	15.13

Final note: please use ultrafast diode STTH1R06 in this application. Using a slow diode will cause severe ringing and malfunction of VIPerX6 device.

## Support material

List any related support material such as evaluation boards, Gerber files etc. and any documents which might be useful to the customer, for example the datasheets, the evaluation board user manual etc.

Related design support material
Product Evaluation board – STEVAL-ISA130V1 12V, 140mA 30 kHz non-isolated buck topology regulator based on VIPer06XN <a href="http://www.st.com/web/en/catalog/tools/PF258332#">http://www.st.com/web/en/catalog/tools/PF258332#</a>
Gerber files – STEVAL-ISA130V1 <a href="http://www.st.com/st-web-ui/static/active/en/resource/technical/layouts_and_diagrams/board_manufacturing_specification/steval-isa130v1_gerber.zip">http://www.st.com/st-web-ui/static/active/en/resource/technical/layouts_and_diagrams/board_manufacturing_specification/steval-isa130v1_gerber.zip</a>
bill of materials – STEVAL-ISA130V1 <a href="http://www.st.com/st-web-ui/static/active/en/resource/technical/document/bill_of_materials/steval-isa130v1_bom.pdf">http://www.st.com/st-web-ui/static/active/en/resource/technical/document/bill_of_materials/steval-isa130v1_bom.pdf</a>
schematics files – STEVAL-ISA130V1 <a href="http://www.st.com/st-web-ui/static/active/en/resource/technical/layouts_and_diagrams/schematic_pack/steval-isa130v1_schematic.pdf">http://www.st.com/st-web-ui/static/active/en/resource/technical/layouts_and_diagrams/schematic_pack/steval-isa130v1_schematic.pdf</a>
Documentation
Datasheet VIPER06, VIPER16, and VIPER26, Fixed-frequency VIPer™ plus family

## Revision history

Date	Version	Changes
17-June-2014	1	Initial release

---

**Please Read Carefully**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at anytime, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**ST PRODUCTS ARE NOT DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2014 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)