

# Designing Low Power SMPS with VIPerPlus Family of Products

Ivan Yank Ivanov

Applications Engineer




Technology Tour 2019  
Schaumburg, IL | April 25


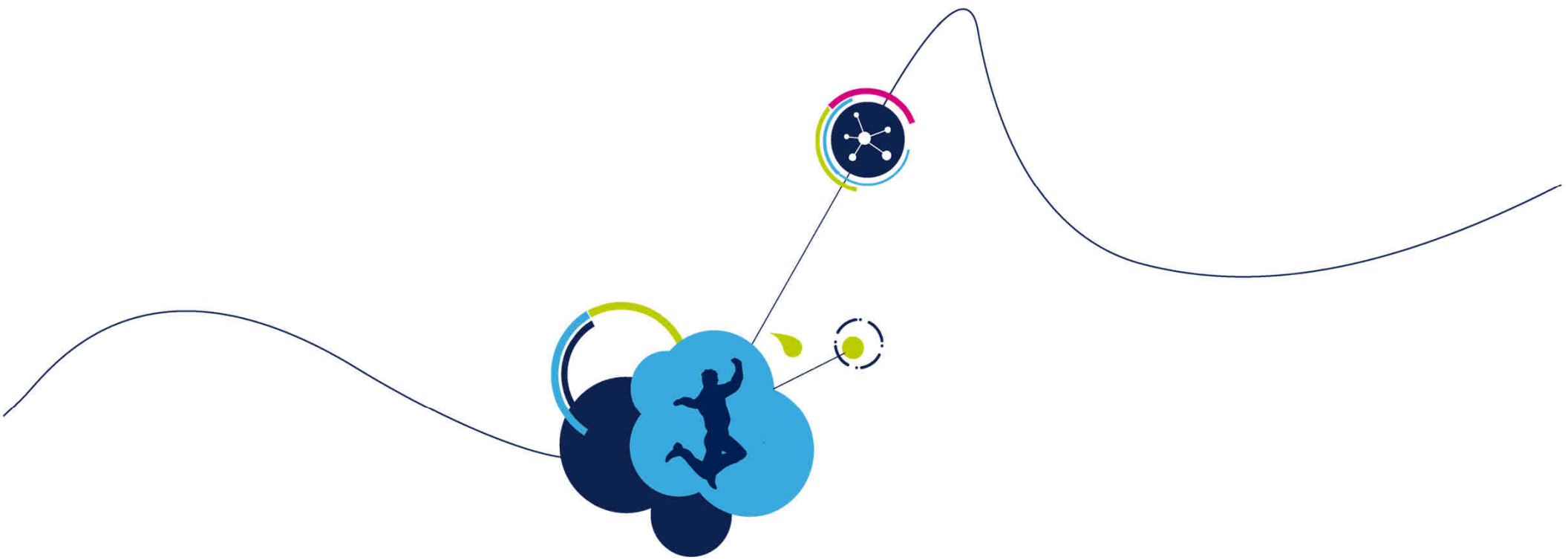
# Agenda 2

- Flyback Topology
- Buck Topology
- eDesignSuite Examples



# Introduction

## Auxiliary Power Supply

Major Appliances



Air conditioning



Industrials



Lighting



Electrical Vehicle



## Main Power Supply

Smart Meters



Smart Buildings



Small Industrials



Small Appliances




Adapters



# Products


5

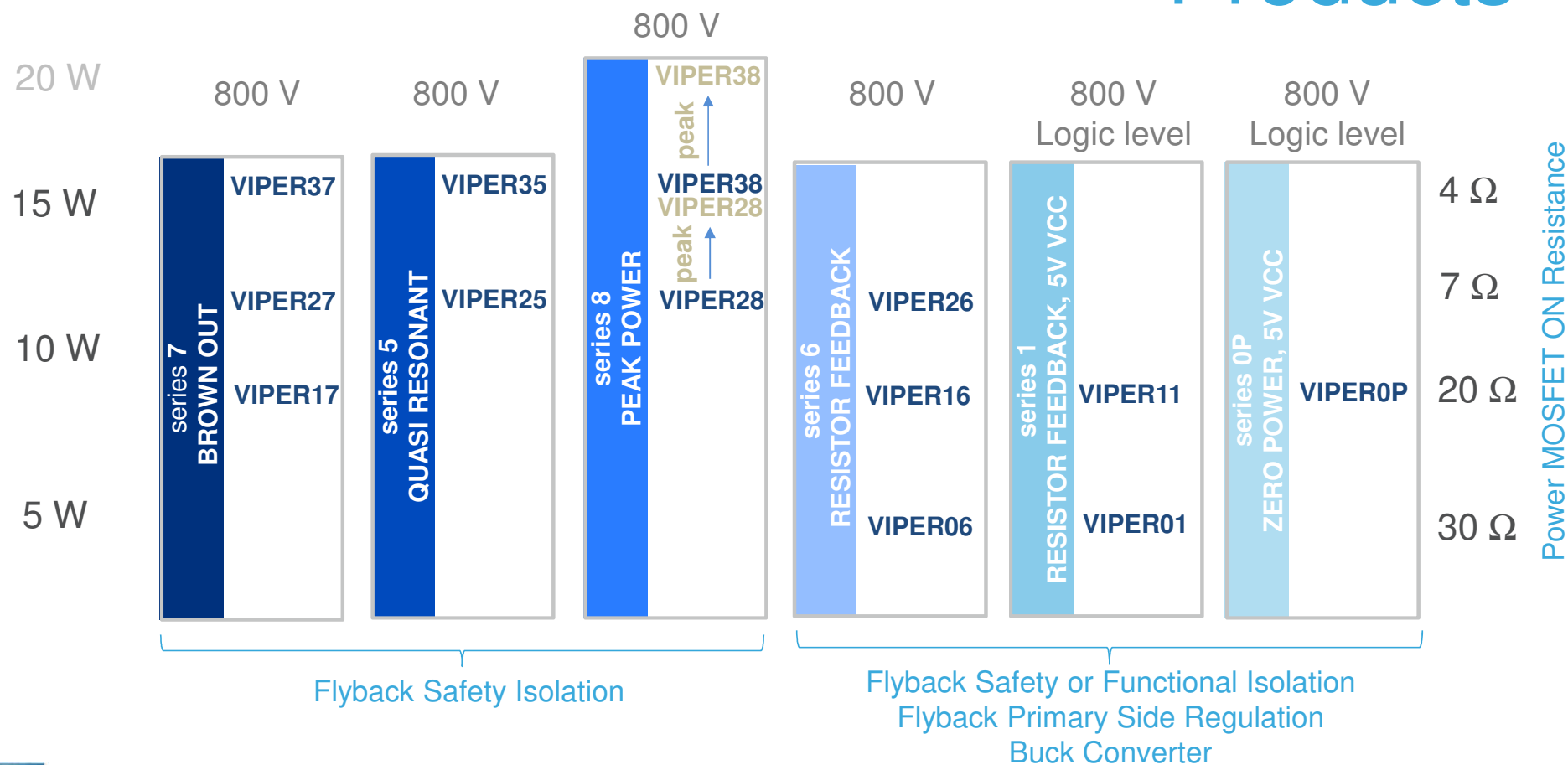

# Which Topology?

6
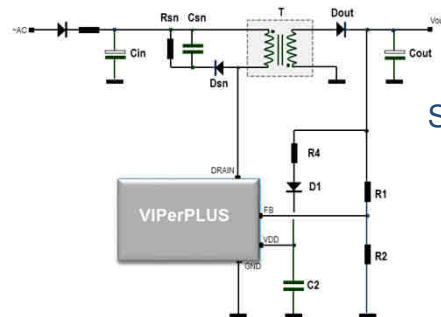
## Functional Isolation (Not Isolated Galvanically)



Secondary Regulation with Resistor Divider





Flyback Converter

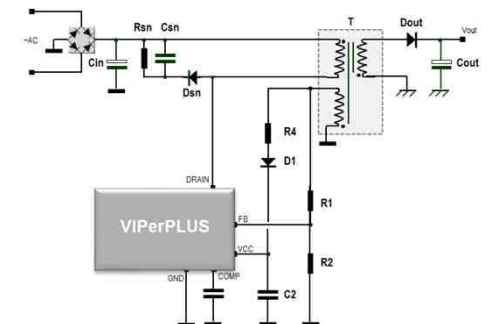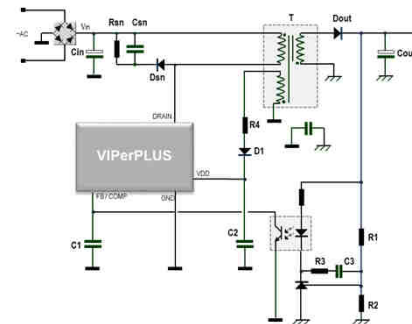
## Galvanic Isolation For Touchable Outputs

Secondary-Side Regulation With Opto-Coupler For Tight Regulation

Primary-Side Regulation Without Opto-Coupler



## Buck Non-Isolated

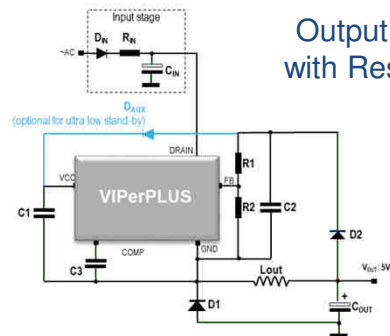

Output Regulation with Resistor Divider







Buck Converter  
Small Inductor  
Compact PCB



# Flyback Topology Optimization

# Flyback Operation

8

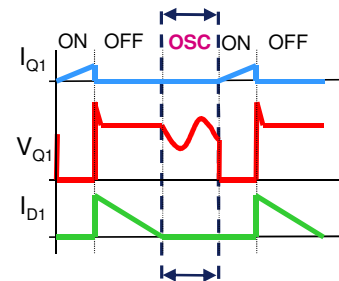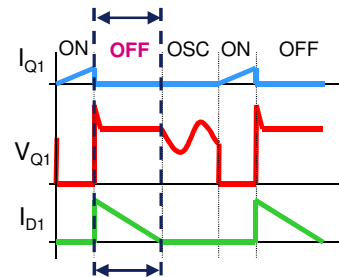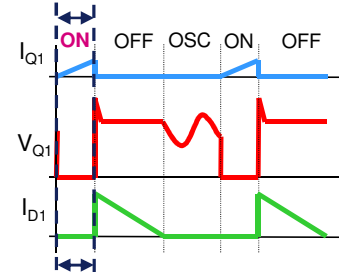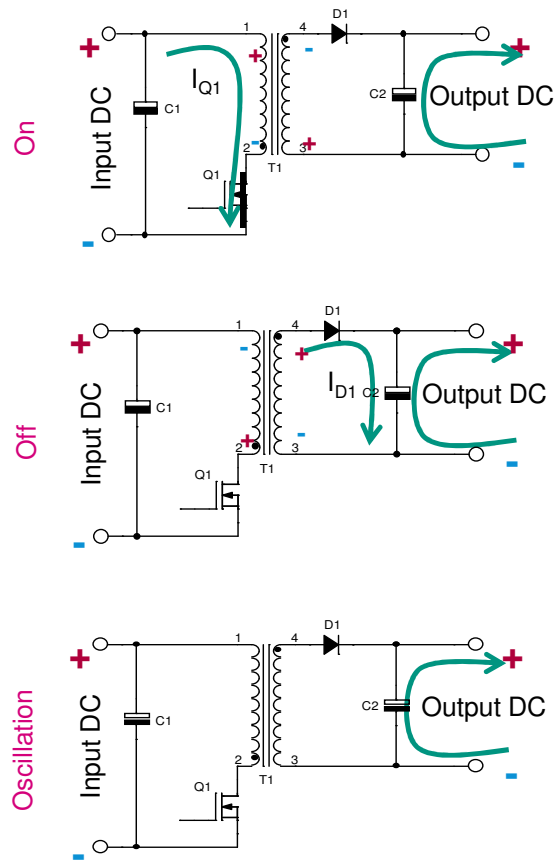

$$E_{T1} = \frac{1}{2} L_P I_{Q1PK}^2$$

$$P_{T1} = \frac{1}{2} L_P I_{Q1PK}^2 f_{SW}$$

$$I_{D1PK} = \frac{N_P}{N_S} I_{Q1PK} = n_{T1} I_{Q1PK}$$

$$E_{T1} = \frac{1}{2} L_S I_{D1PK}^2$$


$$L_S = \frac{L_P}{n_{T1}^2}$$



# Operation Modes


9

## Continuous Mode (CCM)

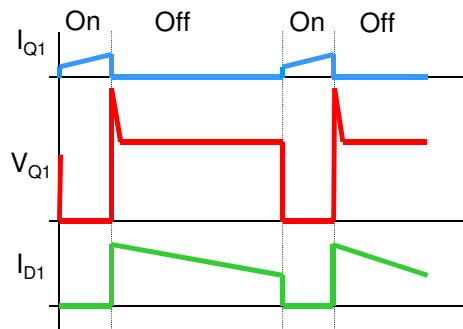


- **Benefit**
  - Higher power capability
  - Smaller transformer
  - Smaller output caps
- **Drawback**
  - Not ZCS – worse EMI and switching Losses
  - Control instability possible
- **Where to Use**
  - Higher peak power demands
  - Lower input voltages, e.g., 110V

## Discontinuous Mode (DCM)

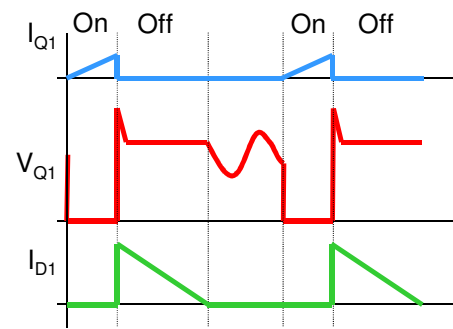

- **Benefits**
  - ZCS turn-on of MOSFET
  - ZCS turn-off of diode
  - Simple Feedback loop
  - Low noise
  - Lower switching cap loss
- **Drawbacks**
  - EMI due to self-oscillating
  - Unused Time slot
- **Where to Use**
  - Higher input voltage, e.g., 230V

## Transition Mode (TM)

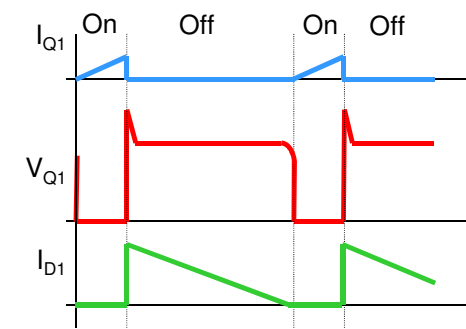

- **Benefits**
  - ZVS turn-on of MOSFET
  - ZCS turn-off of Diode
  - Simple feedback loop
  - Low noise
- **Drawback**
  - Variable frequency could be problematic for EMI
- **Where to Use**
  - When efficiency is a concern

# Select Switching Frequency

10

- Three fixed frequencies:  $30 \pm 3 \text{ kHz}$  ,  $60 \pm 4 \text{ kHz}$  and  $115 \pm 8 \text{ kHz}$
- Priority on transformer size?
  - Higher frequency allows to reduce  $L_p$  using less turns and smaller core size
- Priority on power efficiency?
  - Lower frequency allows to improve the efficiency

TYPICAL CORE SIZE VERSUS OPERATING FREQUENCY

Frequency	E10	E13	E16	E20	E25
30 kHz	1.5 W	2 W	4 W	7 W	
60 kHz	3 W	4 W	6 W	13 W	25 W
115/120 kHz	5 W	6 W	8 W	18 W	32 W

# Transformer Design


11

- Basic specification of transformer include
  - Size, isolation barrier, reflected voltage, peak (or saturation) current, frequency, input voltage range, output voltage and output current range
- Leakage inductance influence power loss, snubber and EMI
  - Typical leakage inductance is 1~3% of primary inductance depending on the transformer structure
  - $P_{Leakage} = \frac{1}{2} L_{Leakage} I_P^2 \times f_s$
- Reflected Voltage  $V_R$  is the voltage reflected from secondary output to the primary of transformer
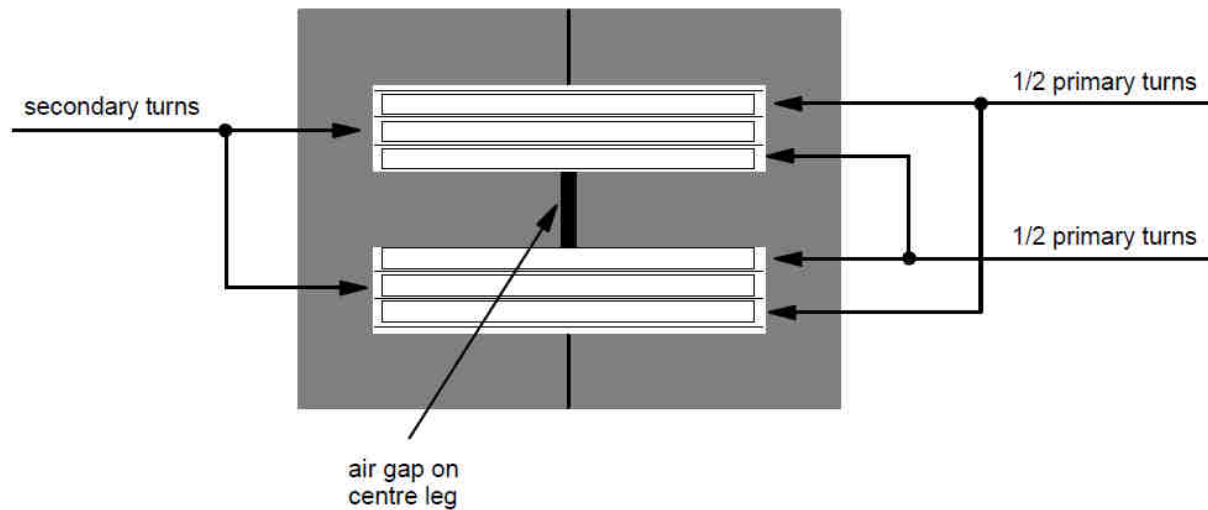
# Minimizing $L_{\text{leakage}}$ by Interleaving

12

- Leakage inductance can be reduced by splitting primary winding in 2 halves and sandwiching secondary winding in between



# Reflected Voltage Selection


13

- Optimize reflected voltage to set maximum duty cycle. As a rule of thumb, make it equal to minimum DC input voltage
- High reflected voltage means high  $V_{ds}$  stress and higher snubber losses
- Lower reflected voltage means higher off time, higher RMS losses and higher primary peak current
- A positive side effect of lower reflected voltage is that it leads to better magnetic coupling between windings, which, in turn, helps to reduce leakage inductance

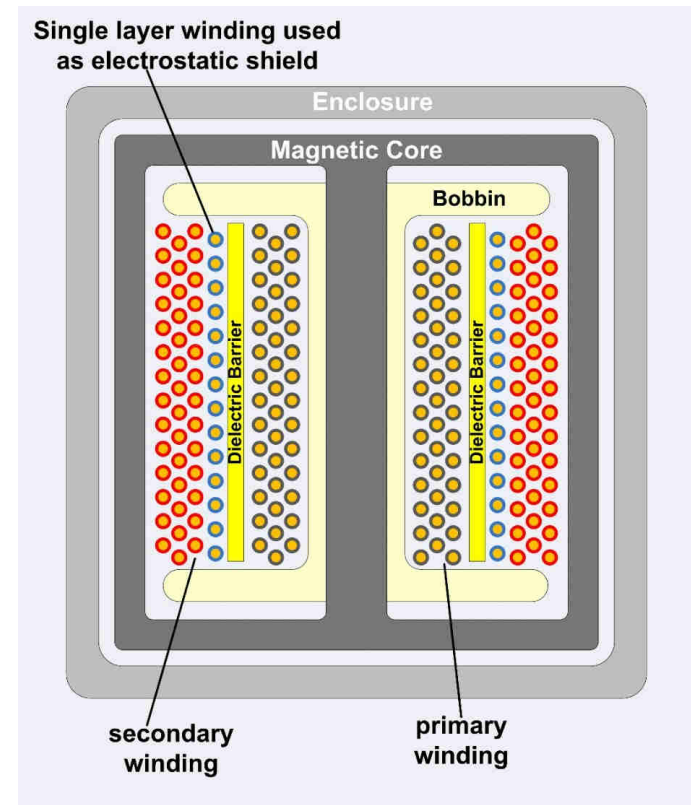
# Shielded or Non-Shielded

14




- Shielded transformer has better EMI but **larger leakage inductance**
- Non-shielded transformer has worse EMI but smaller leakage inductance



## Without Clamp Circuit

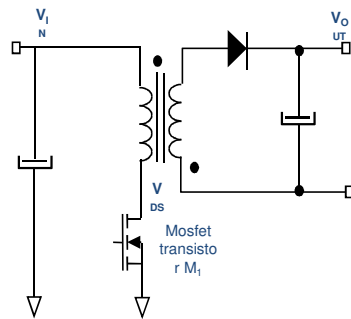


Spikes across PowerMOS turn-off

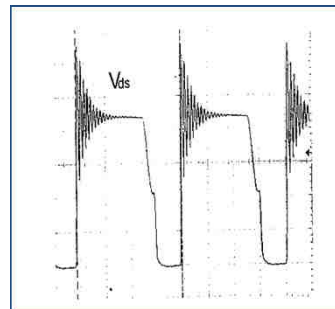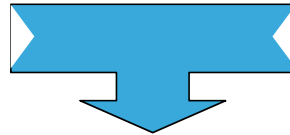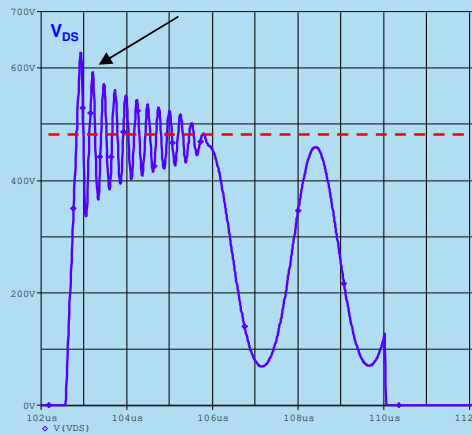


# Clamp Circuit

15

## With Clamp Circuit

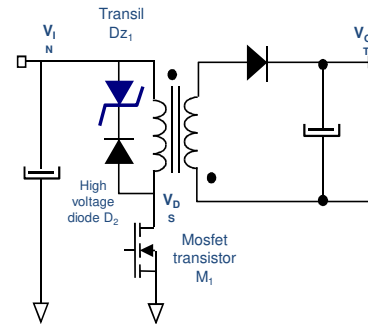


No spike

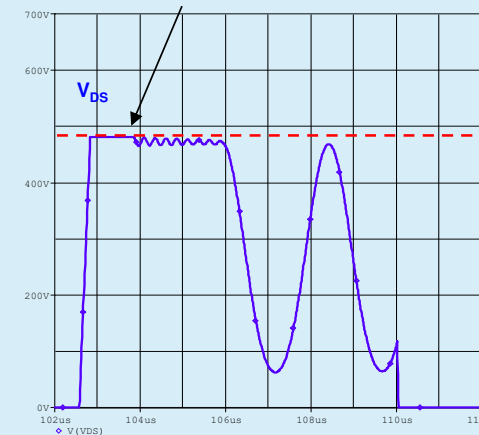


# Clamp Implementations


16

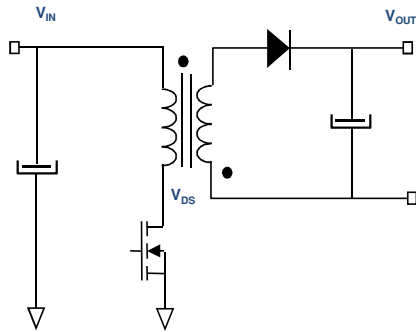

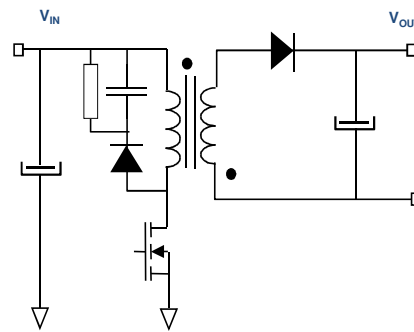- No protection
- Test to be performed to know max  $V_{DS}$
- MOS / IGBT to be oversized in voltage (more expensive, efficiency drop)



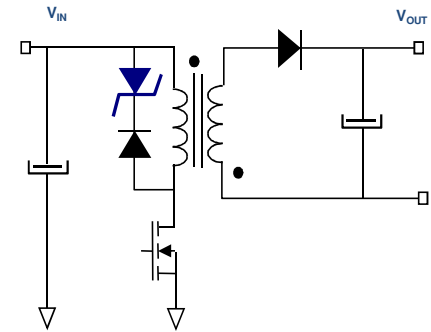- RC to limit  $dV/dt$ , then to limit overvoltage
- Slope may vary depending on components
- Margin on  $V_{DS}$  is depending on components
- Test to be done for validation




- Maximum clamping voltage only depends on STRVS
- Datasheet/product adapted to repetitive surges
- Margin on  $V_{DS}$  can be easily calculated
- Validate with minimal test




# New Clamping Technology: STRVS

17

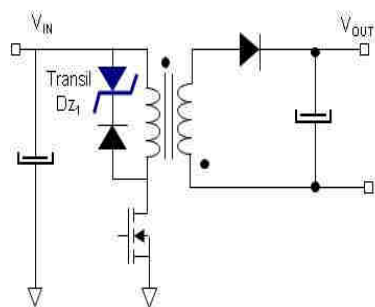

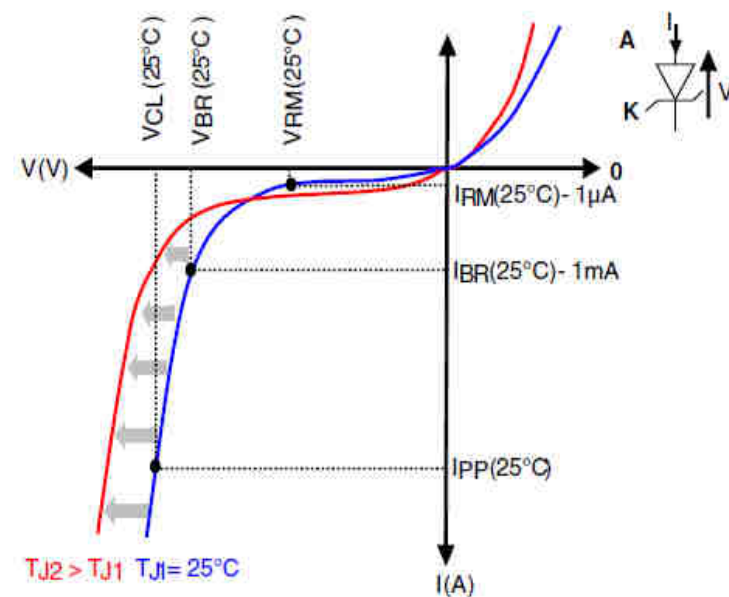
- VRM is stand-off voltage and must be selected to allow the FET to switch:  $VRM > VR$
- VCL is the clamping voltage and is critical to choose as close as possible to the application requirement
- Extensive data published on STRVS datasheet makes the selection for the right part easy and robust


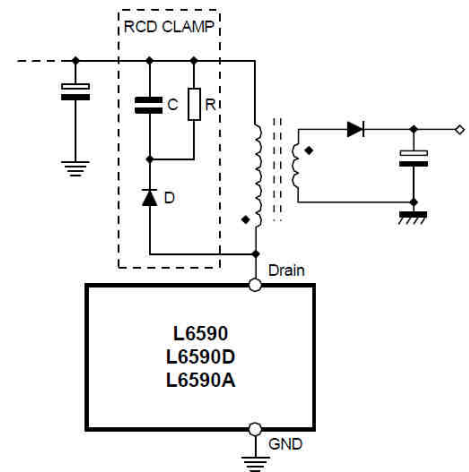
# RCD Snubber

18


- RCD sizes and values need to be carefully selected. There is a tradeoff between RC values, power dissipation, EMI and clamping effect
- RCD clamp dissipates power even under no-load conditions: there is always the reflected voltage across the clamp resistor R



R	C	$V_{CL}$	$V_{DS(PK)}$	EMI	$P_{DISS(R)}$	Cost
↓	↑	↓	↓	↓	↑	↑
↑	↓	↑	↑	↑	↓	↓

# Stand-By Consumption

19

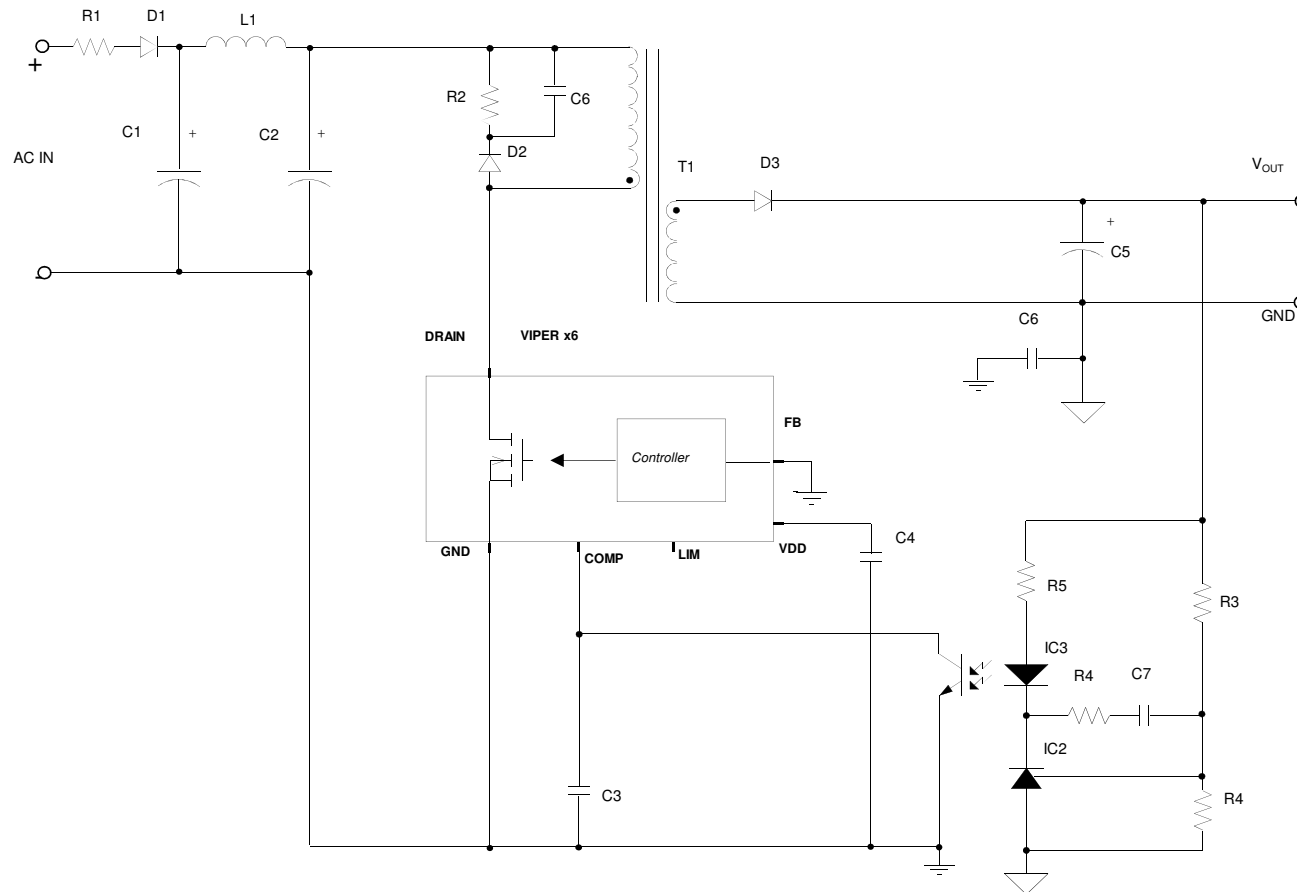


## 20



# Stand-By Consumption


21

Stand-by optimization , 30 mW  
D4, R6

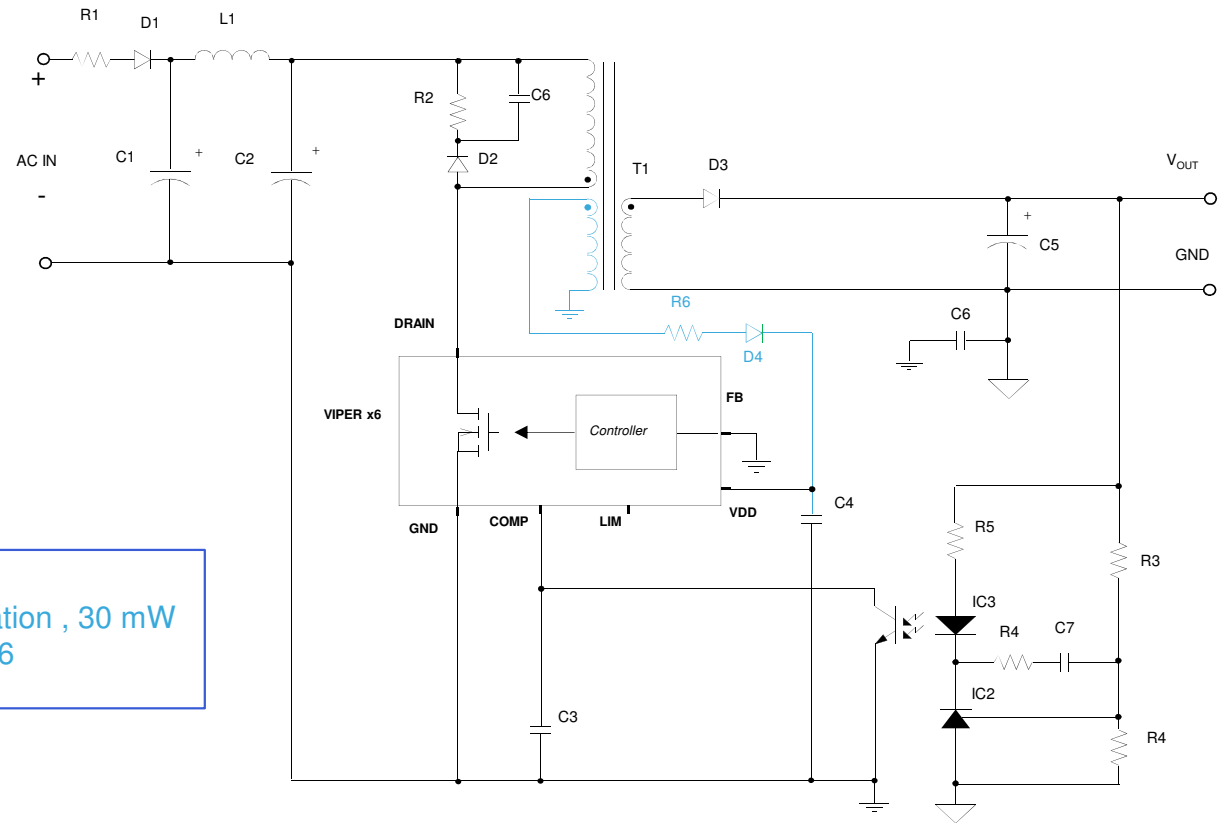

# Stand-By Consumption: HV Start-Up

22

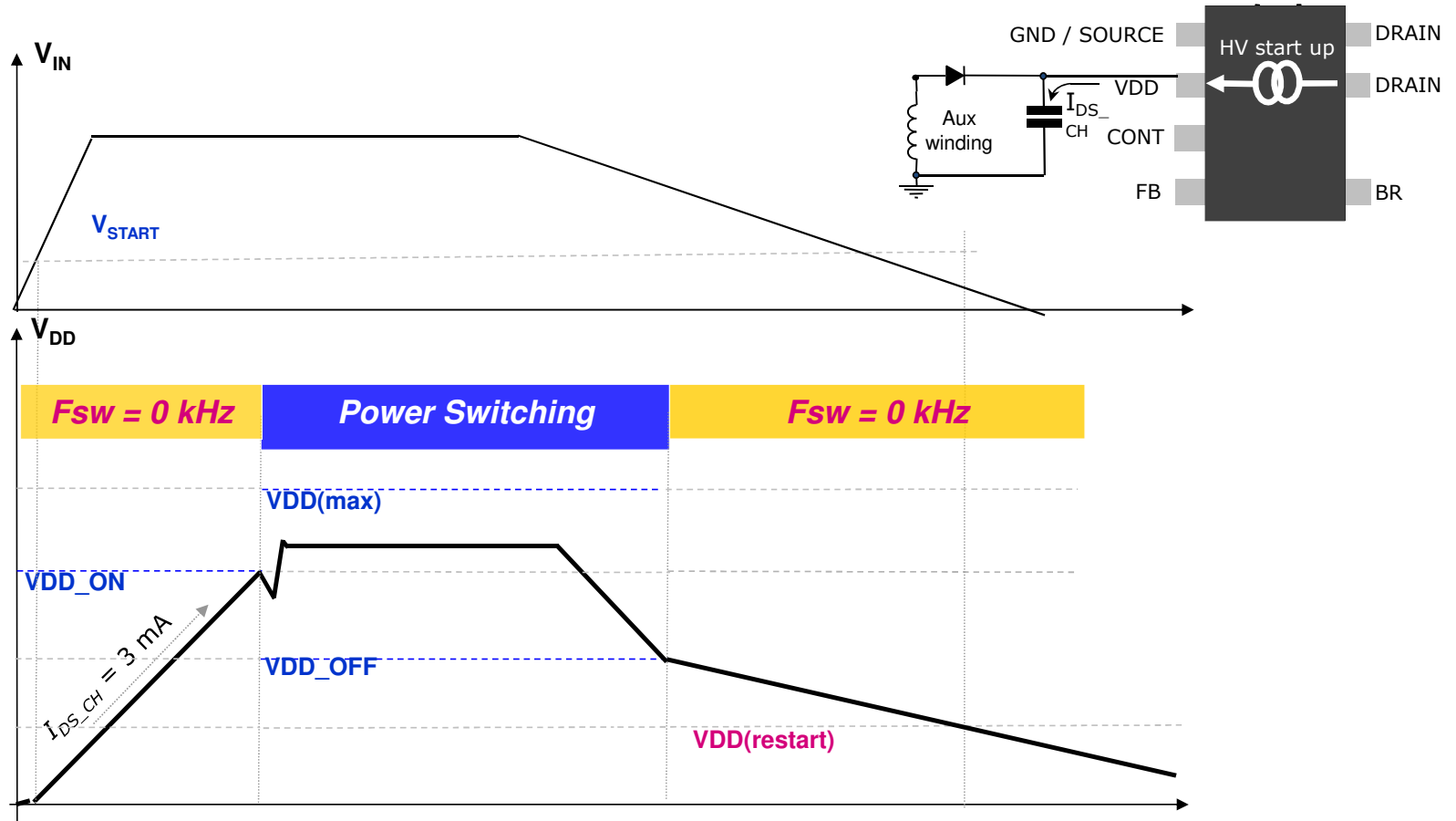


## 23



# Stand-By Consumption: Burst Mode

24

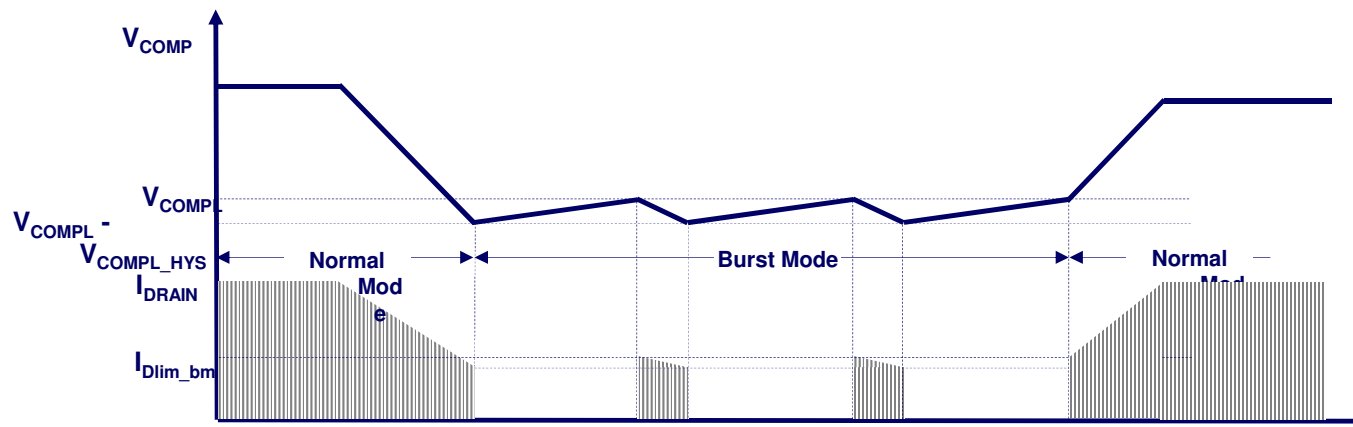


$V_{COMP} < V_{COMPL}$  starts burst mode



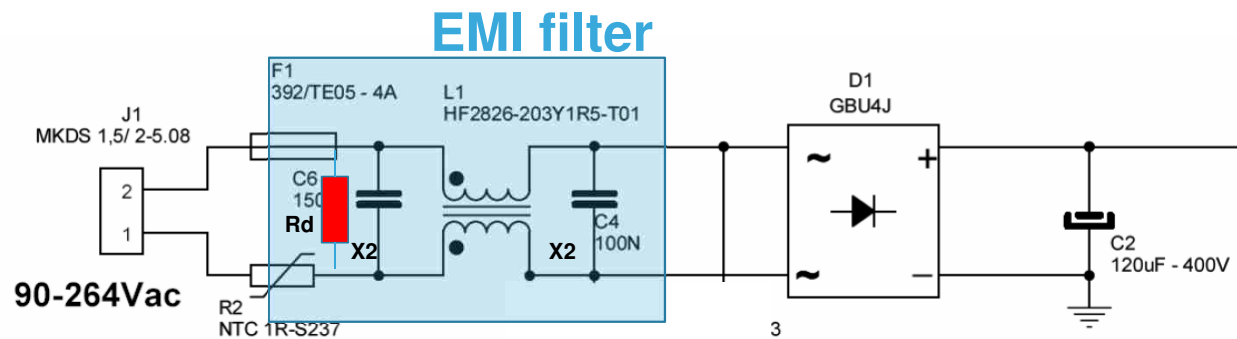
# X-Cap Discharge

25

- The EMI filter in the input of the power converter typically consists of capacitors across the AC mains and CM choke
- According to safety regulations, e.g. UL 1950 and IEC61010-1, capacitors on the mains must be discharged within a given time after the appliances is suddenly disconnected
- A discharge resistor is typically connected in parallel, resulting in additional power losses, as long as the appliance is plugged
- A new function has been recently introduced in order to actively discharge the X capacitor through the HV start-up circuit



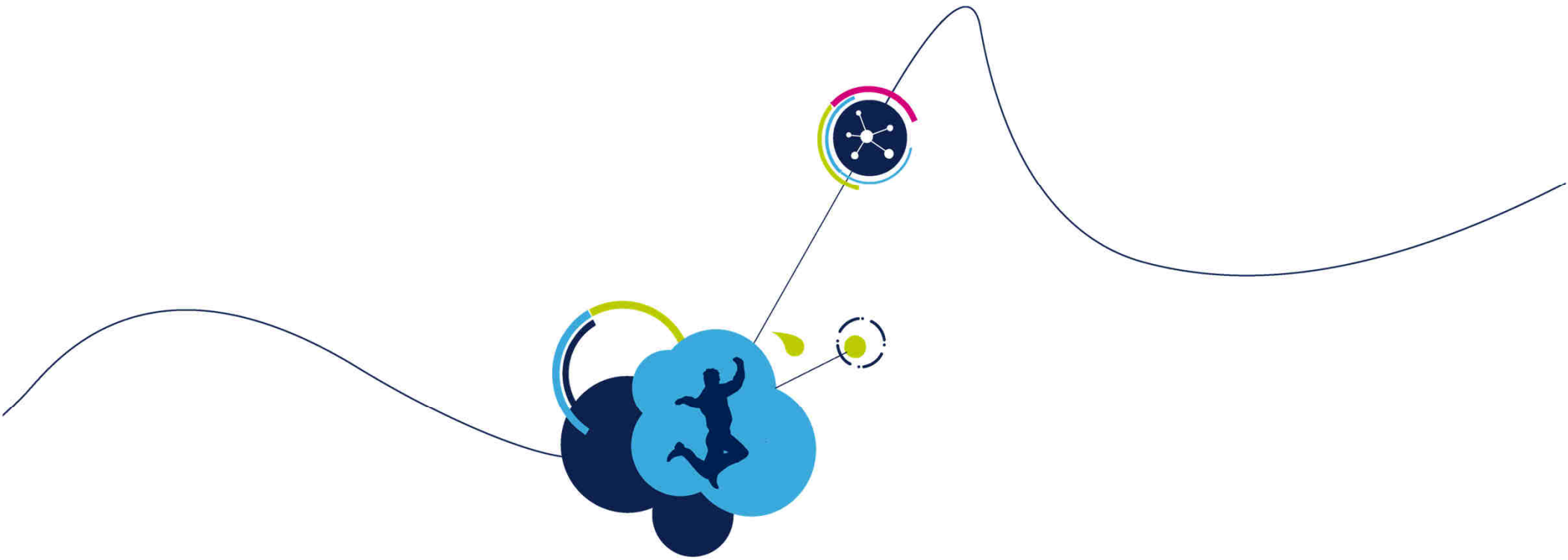

# Buck Topology Optimization




# “Flying Capacitor” Feedback Scheme

- C4 stores output voltage, transfers level into Viper feedback loop
- R4 – R2 discharge C4 slowly
- Load current is required to turn on D5 and D8 to charge C4
- A light load MUST be present to insure diode turn-on
- C4 must hold output voltage information when Viper is in burst mode
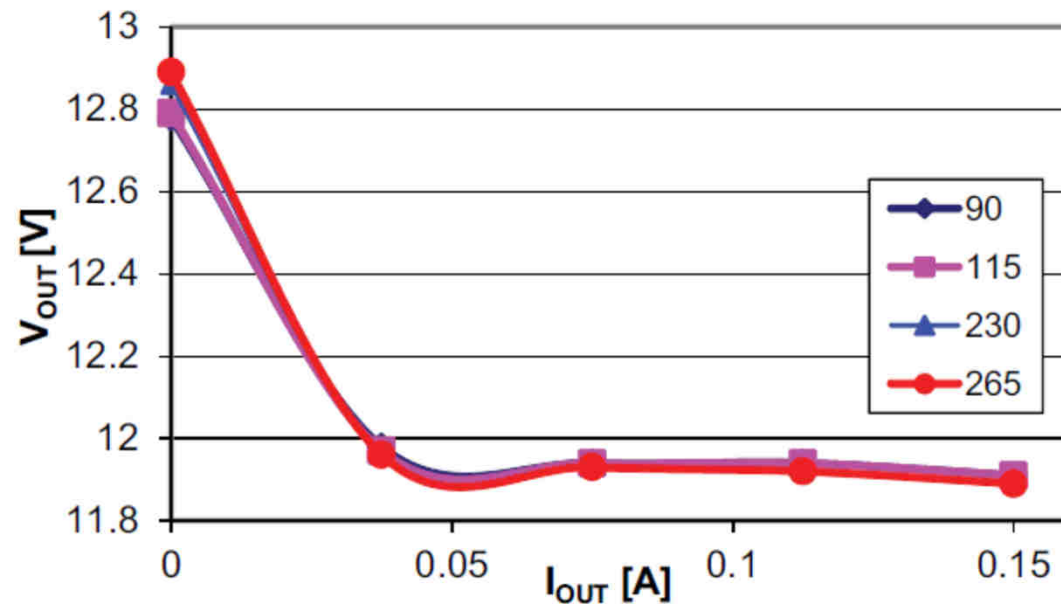
# “Flying Capacitor” Feedback Scheme (Cont.)

29

- Low cost solution
- Minimum load required



# Select Switching Frequency

30

## SELECT FREQUENCY FOR 5 V OUTPUT BUCK

Vin DC (V)	D (%) 5 V	t <sub>ON</sub> (μs) for 60 kHz 5 V	t <sub>ON</sub> (μs) for 30 kHz 5 V	VIPer01 Minimum ON time
100 (85 VAC)	5.0	0.83	1.67	0.35 μs
170V (120 VAC)	2.9	0.49	0.97	
325V (230 VAC)	1.5	0.26	0.50	
375V (265 VAC)	1.3	0.22	0.33	
622V (440 VAC)	0.8	0.13	0.26	





Lower frequency allows to handle the regulation even in the case of a very high ratio between input and output voltages

# Minimum ON Time 31

- Duty cycle of Viper Buck converter is limited by minimum on time
  - Viper06 450 ns
  - Viper01 350 ns
- If the required ON time is shorter then minimum ON time, Buck still works, but there is small instability and the maximum deliverable output current is reduced.
- The 30kHz version is strictly recommended for 5V output


# Diode Recovery Effect

32

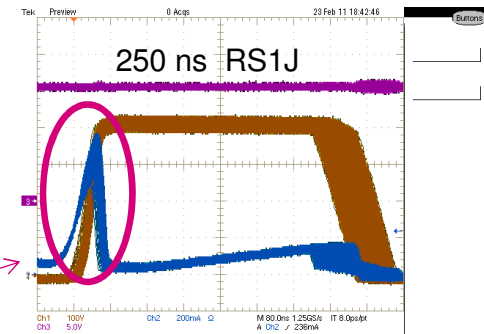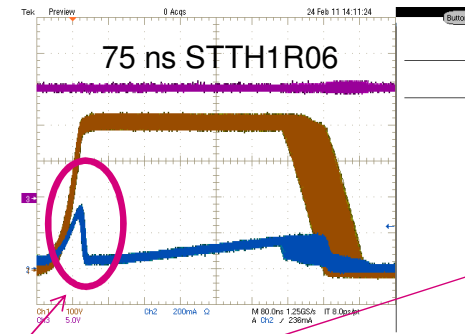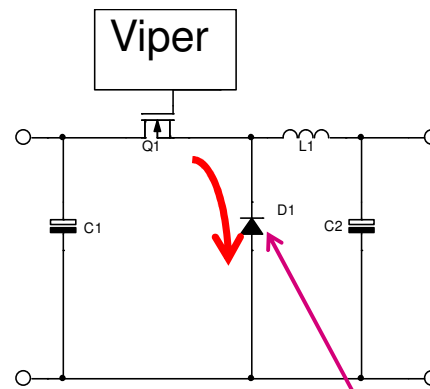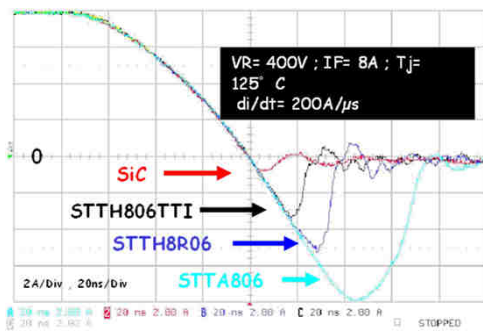

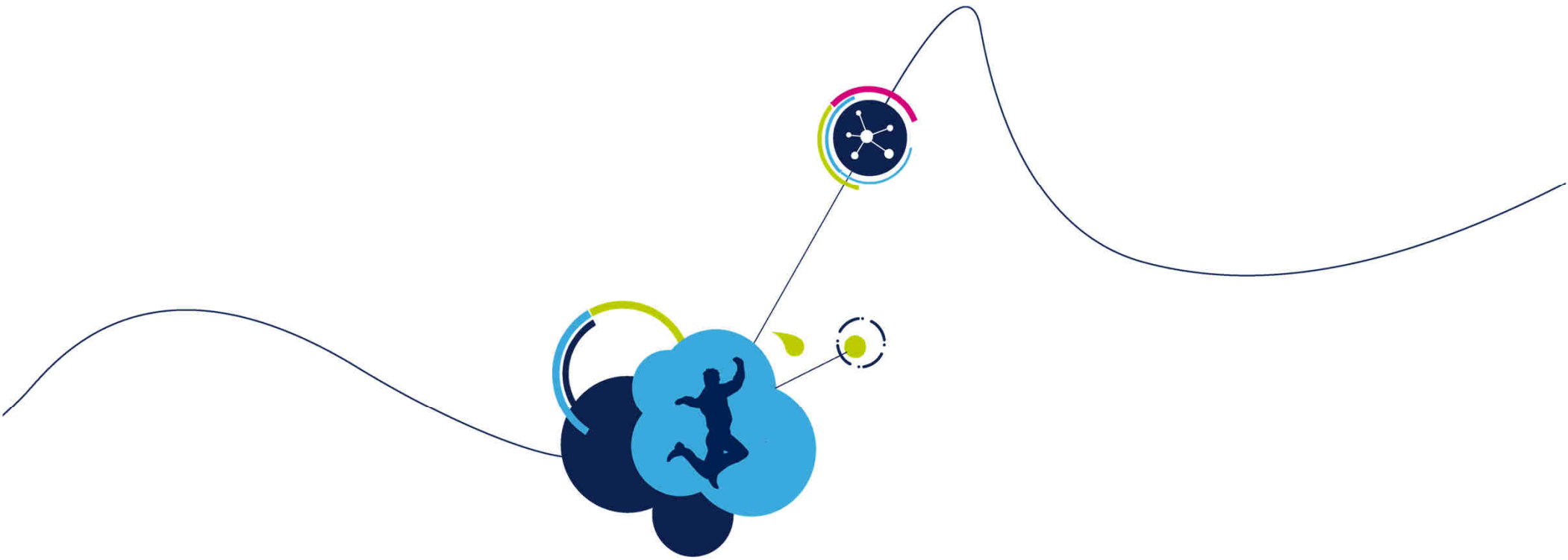Recovery effect causes short cross conduction every turn ON. Effect is much critical in case CCM => **DCM is recommended**. The lost energy is higher at higher power operating frequency => **The 30kHz version is recommended**.





# Layout and EMI Optimization

# Layout Optimization

34

- Minimize **interconnection lengths** of following components:
  - Input **filter caps**, input-side transformer (or inductor), **power MOSFET**, sensing resistors and active-clamp or **snubber circuits**
  - **Output-side transformer (or inductor)**, rectifier diodes and **output filter caps**
- Keep **power and signal circuitries separated** and be careful of connection between the signal and power grounds
- Assure component isolation and **spacing by safety standards**
- **Prioritize ground** over all routes
- **Large copper areas** for thermal and EMI
- Add **sufficient VIAs** for better thermal performance
- Keep the **feedback path** as far as possible from power components and noise traces
- External **compensation components** should be **close to IC**
- Copper **traces for power** should be **thick and short** and **sharp angles** should be avoided

# EMI Optimization


35

- EN 55022 is an European EMC standard applicable to information technology equipment with a rated supply voltage not exceeding 600 V
- Properly size EMI filter: **differential mode filter** for power < 5 W; X-, Y-caps, and **common mode choke** for power > 15 W
- Designers often use **snubbers and soft switching techniques** to minimize the EMI
- **Shielded transformer has better EMI** but also has larger leakage inductance
- Connect heatsinks to ground
- Focus on coupling paths from EMI sources to EMI sensitive components
- Strategic orientation and placement of components can reduce EMI generation significantly
- Eliminate **environmental interference on EMI test**
- Use an **accurate EMI analyzer** to carry **quasi-peak, and average** measurement to meet standards
- ST offers **PWM operation with frequency jittering** for low EMI

# Design Example

36

Electrical Schematic

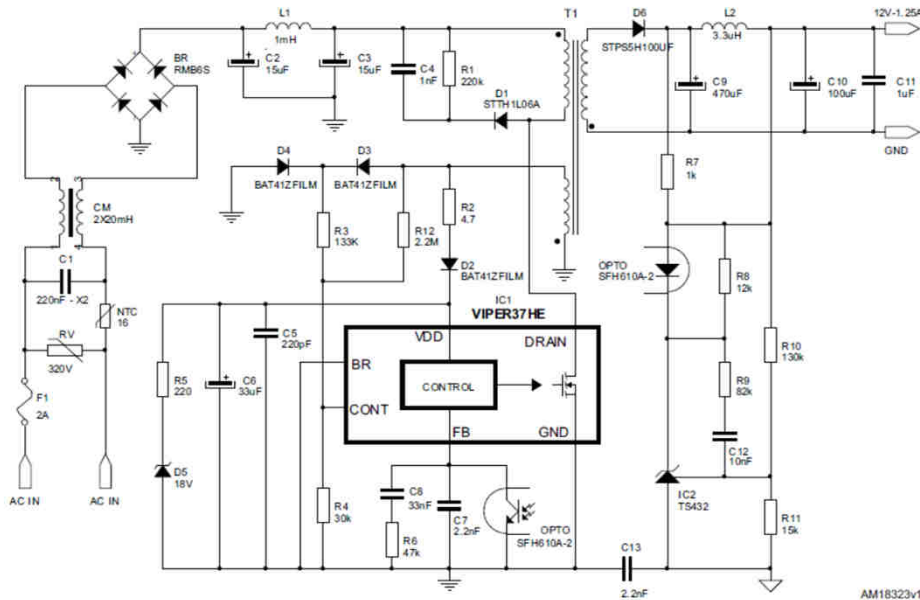


VIPER37HE 100~265 VAC IN, 12 VDC 15 W OUT

EMI Filter

Aux VDD for Viper

Optocoupler for Feedback

Output

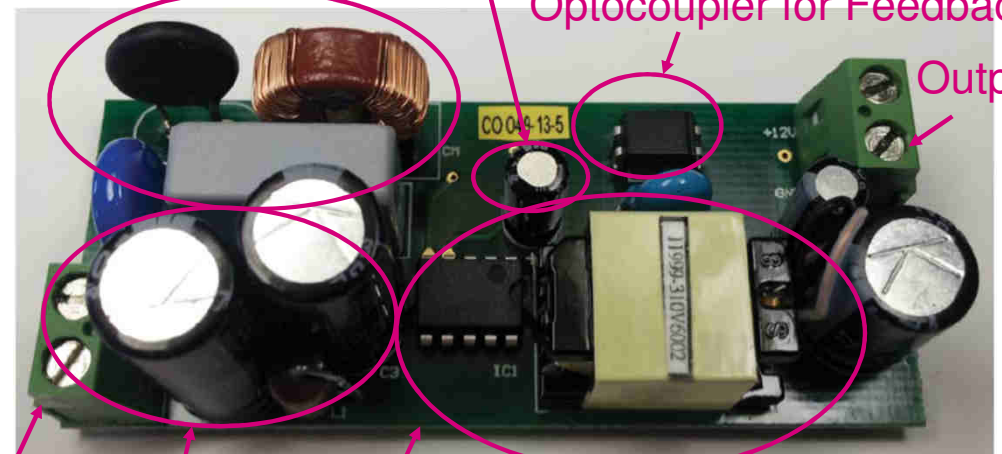


Input

Rectifier

Subber and Comp  
(Bottom Layer)


Compact Power Loop

Evaluation Board (30 x 72 mm) Max

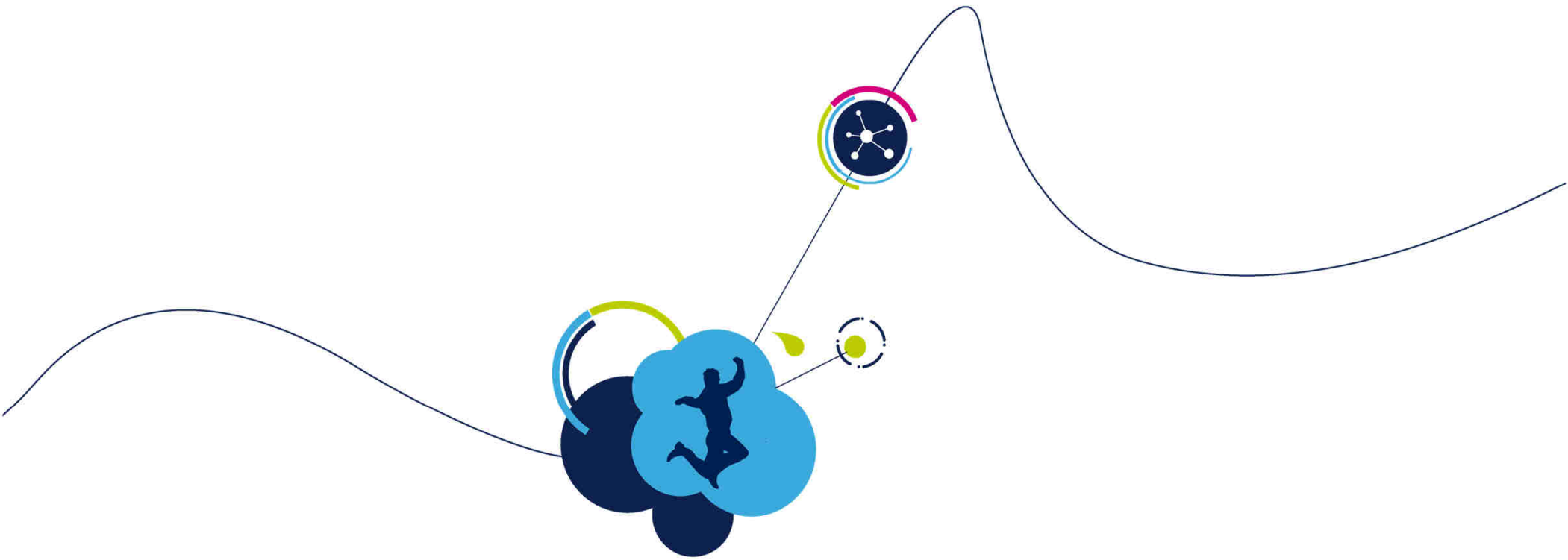
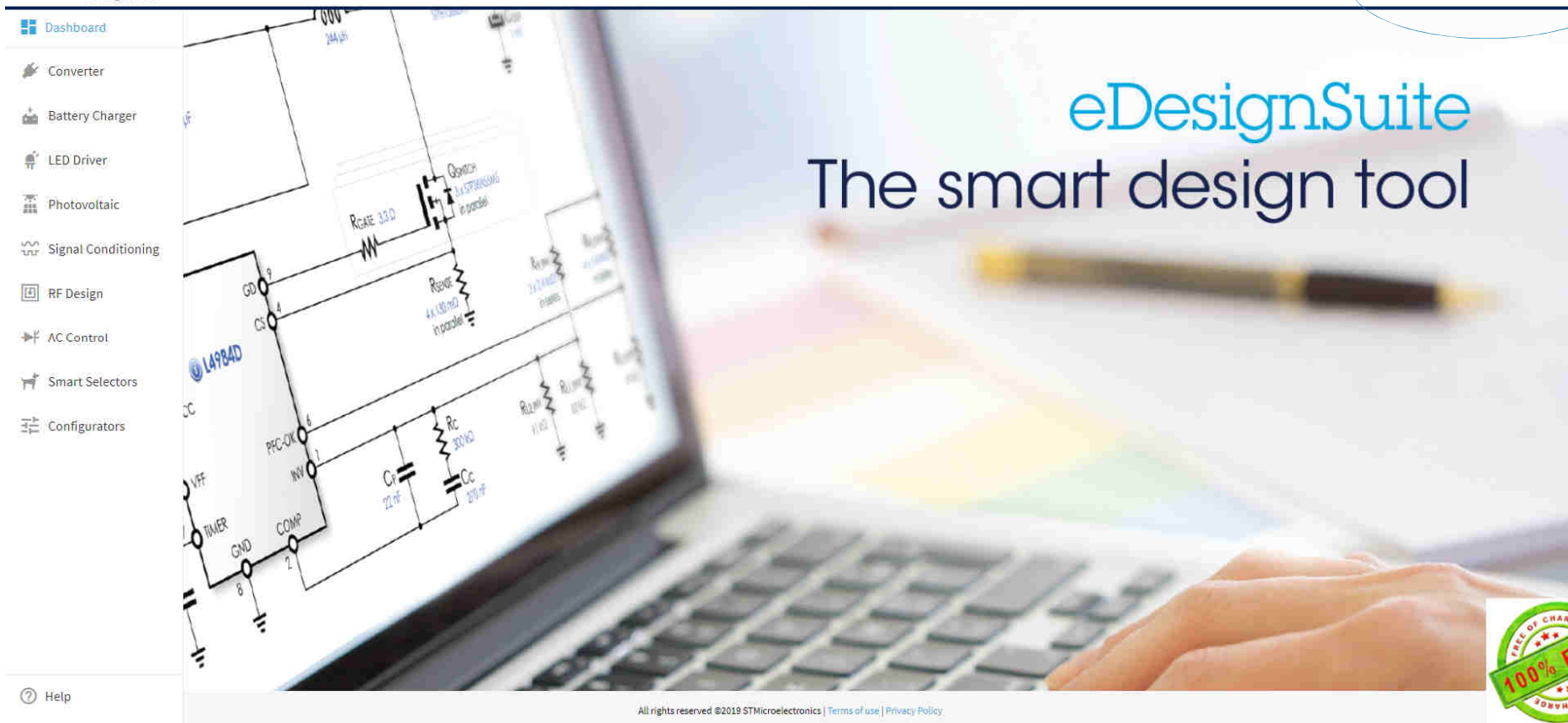
# eDesignSuite Examples

<https://my.st.com/analogsimulator/>  
Create an ST.com account and  
use it to sign in to eDesign Suite



**eDesignSuite**  
The smart design tool

Help

All rights reserved ©2019 STMicroelectronics | [Terms of use](#) | [Privacy Policy](#)



The image displays the ST eDesignSuite web application interface. The main view shows the 'Examples' tab with a sidebar menu containing items like Converter, Battery Charger, LED Driver, Photovoltaic, Signal Conditioning, RF Design, AC Control, Smart Selectors, and Configurators. Three smaller, semi-transparent screenshots are overlaid on the right, each showing a different view of the application. A blue arrow points from the 'Converter' menu item to the first overlay. A green arrow points from the 'Non isolated' menu item to the second overlay. A pink arrow points from the 'Isolated' menu item to the third overlay. The overlays show the 'AC/DC' section with various converter types like Buck, FF Flyback, and Isolated. The bottom of the main screenshot shows a 'Help' link and a copyright notice for 2019 STMicroelectronics.

ST eDesignSuite

Converter > AC/DC > Non isolated > Buck

Can search by part number

Search

Specifications

Input

Voltage: USA Range - 60 Hz Min V: 85 Max V: 140

50 Hz 60 Hz

Output

Voltage: 12 Current: 0.2

ADD OUTPUT

Output Power: 2.4 W

22 Results

Number of products available

Topology

For each feature you can click on it to select.

Included if you are looking for devices that have that feature

Excluded if you do not want devices having that feature

Package Type: SMD No filter

Programmable Current Limit: No filter

Package Type: Through-hole: No filter

Overshoot Protection: No filter

Burst Mode: Included

Fixed Frequency: Included

Overload Protection: Included

Soft Start: Included

Sw.Frequency: Not Selectable: Included

Thermal Shutdown: Included

Topology: Buck: Included

VIPER06HN Buck DIP 7

IDlim: 320 mA

VBVDSS: 800 V

RDSon: 30 Ω

fosc: 115 kHz

START DESIGN

VIPER06HS Buck DIP 7

IDlim: 320 mA

VBVDSS: 800 V

RDSon: 30 Ω

fosc: 115 kHz

START DESIGN

VIPER06LS Buck SS010

IDlim: 320 mA

VBVDSS: 800 V

RDSon: 30 Ω

fosc: 60 kHz

START DESIGN

VIPER06XN Buck DIP 7

VIPER06XS Buck SS010

VIPER013LS Buck SS010

Choose by features

ST life.augmented

All rights reserved ©2019 STMicroelectronics | Terms of use | Privacy Policy


Specification – input voltage range  
Output voltage/current





**VIPER115LS**  
Buck

SS010

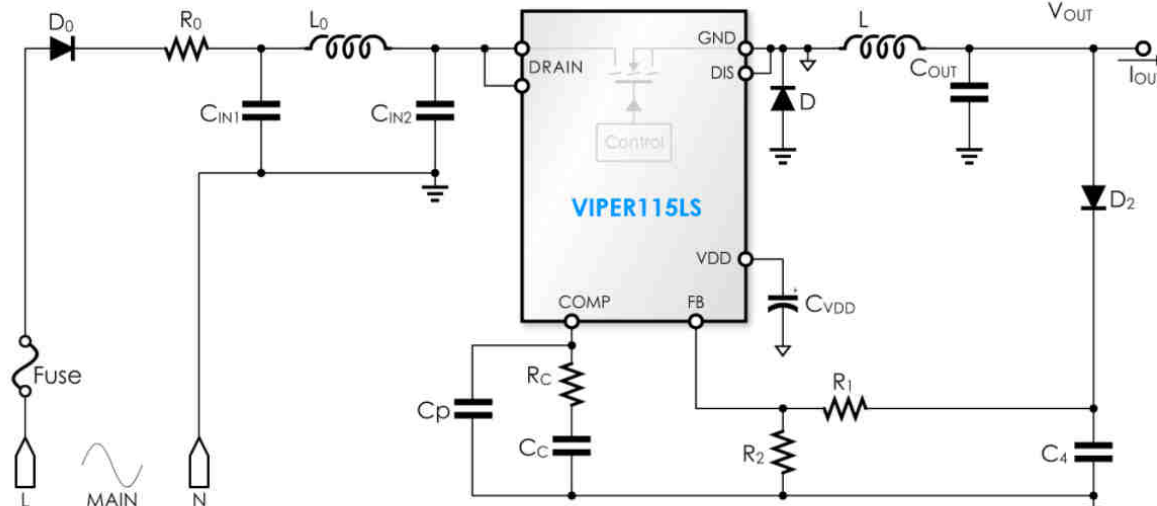

#### Specifications

Reset All

#### Input

Voltage: USA Range - 60 Hz  
Min V: 85  
Max V: 140

50 Hz 60 Hz

#### Output

Voltage: 12  
Current: 0.2

Output Power: 2.4 W

Selected device, design specification and generic schematic – once all that is ready proceed with **START DESIGN** button

**START DESIGN**

IDlim: 575 mA

VBVDSS: 800 V

RDSon: 17 Ω

fsw: 60 kHz

Datasheet


Product Folder

Energy saving off-line high voltage converter


Main features:

- 800 V avalanche-rugged power MOSFET allowing ultra wide range input VAC to be achieved.

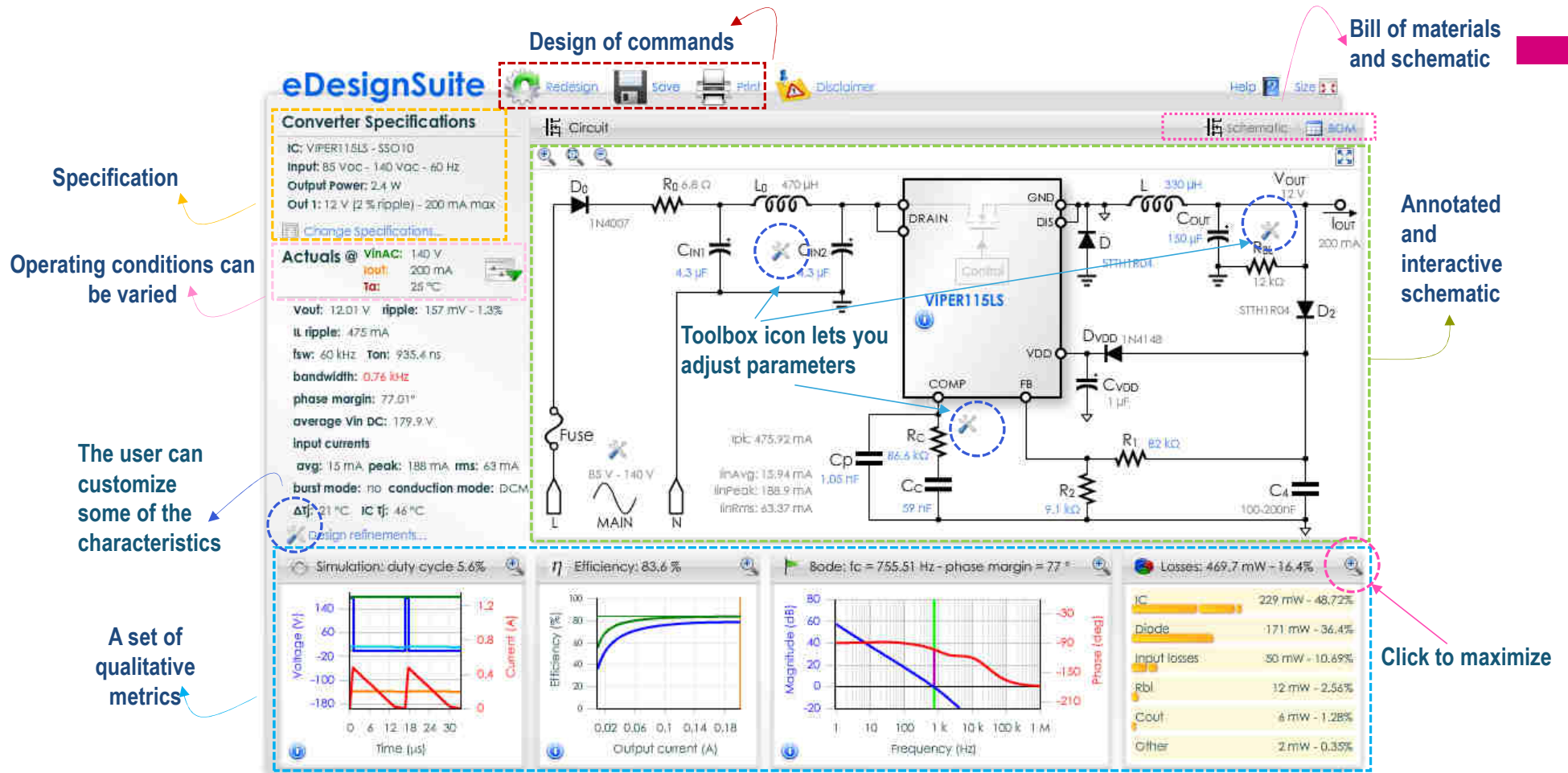More details on the selected device (e.g. Viper115LS) – datasheet link, main electrical parameters, features





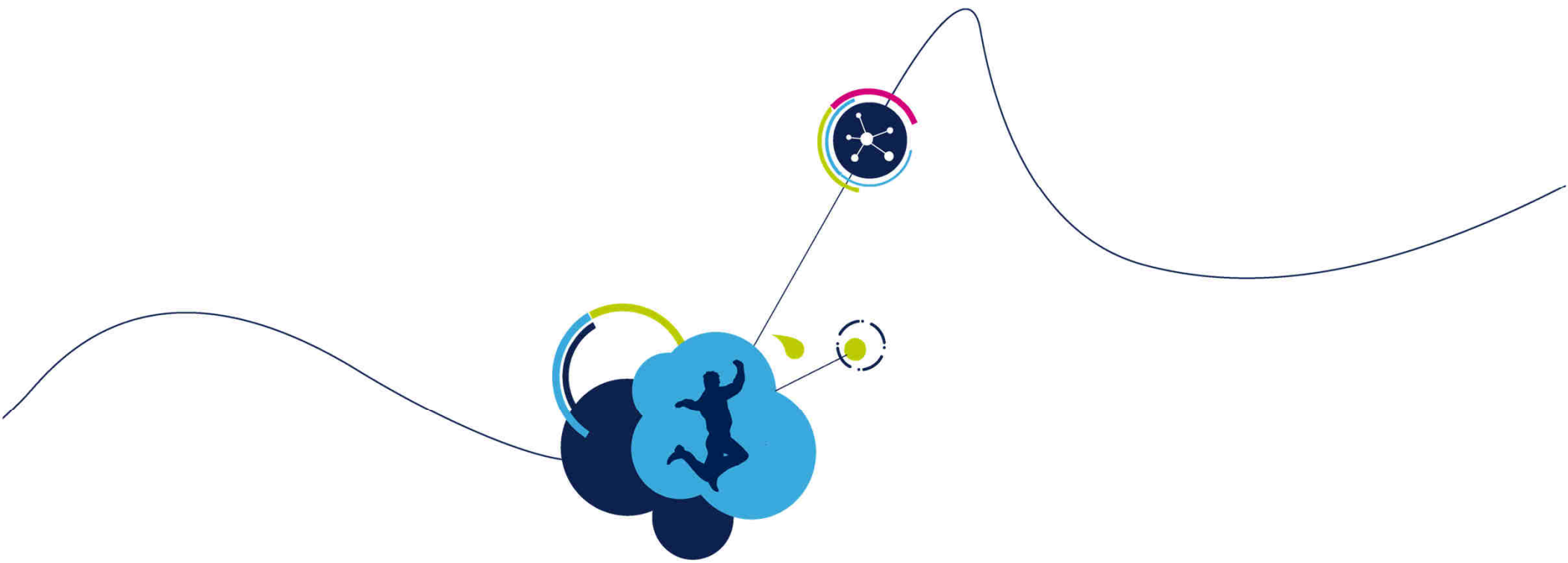

Thank you!