



Exploring current sense amplifiers

STMicroelectronics Tech days



Application-dependent error sources

Chapter 9

- Input bias current
- Shunt resistance



User guide

This presentation provides a written explanation of the topic covered in the nineteenth chapter of the video: “**Application-dependent error sources #9**”, which is available on our YouTube channel at the following link:



[Video on YouTube](#)

Recommendations

In this document you'll find key concepts explained through informative tables, graphs, sequences of graphs, followed by a detailed explanation.

- When you see this icon:  Explanation → the topic is explained in detail on the following page(s)
-  Each explanation page shows the page or page range where the topic is explained: (page # to #)
- If you see this icon:  the explanation continues on the next page(s)

Input bias current

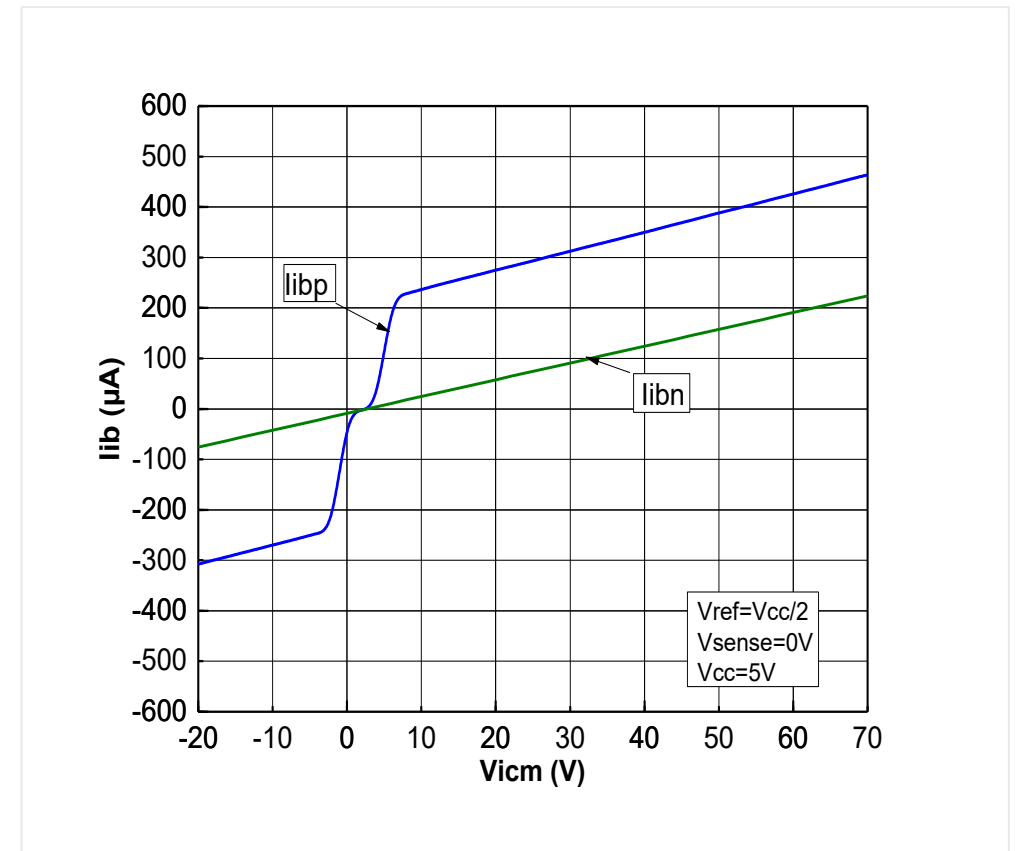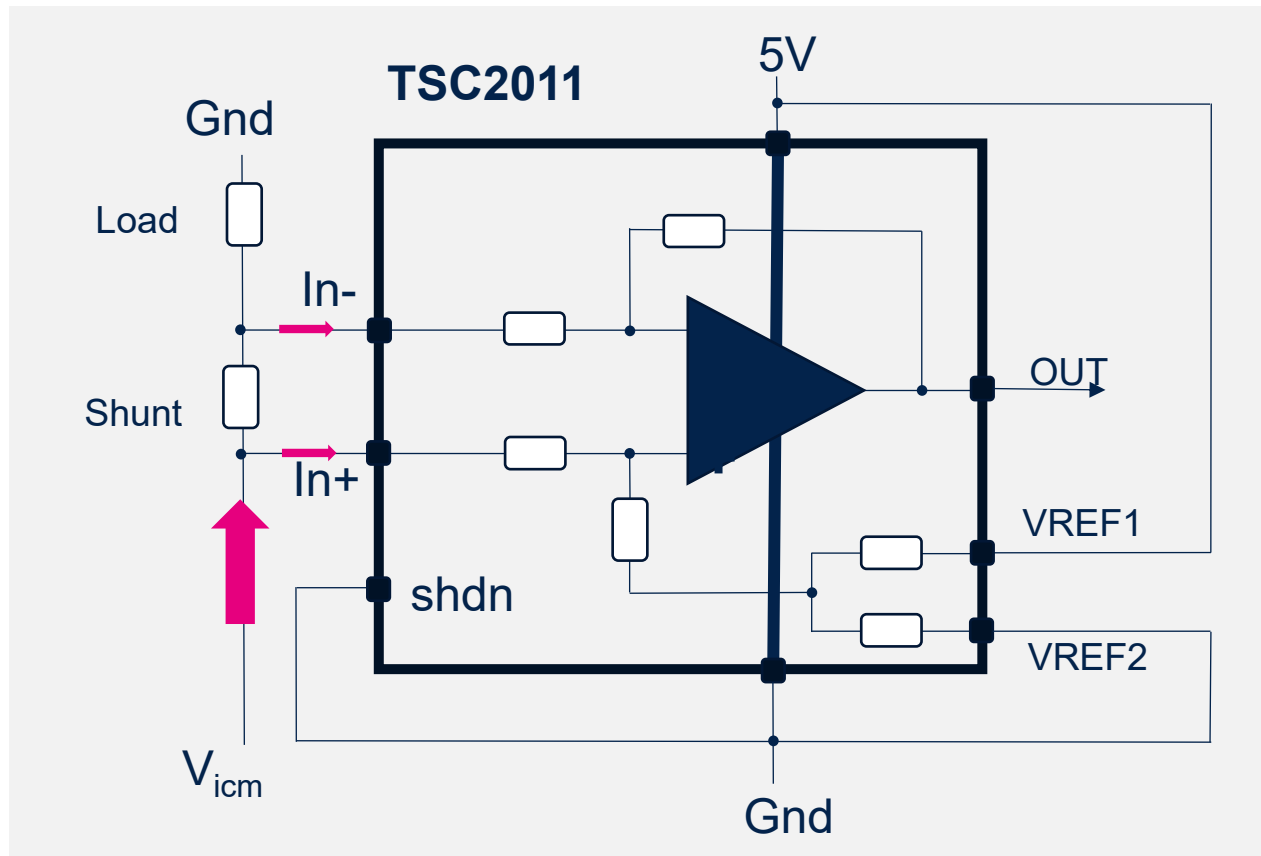

TSC2010 series

I_{b+}	Input bias current	$V_{icm} = 12\text{ V}$ $T_{min} < T < T_{max}$, $V_{icm} = -20\text{ to }70\text{ V}$	-400	350	600	μA
I_{b-}	Input bias current	$V_{icm} = 12\text{ V}$ $T_{min} < T < T_{max}$, $V_{icm} = -20\text{ to }70\text{ V}$	-150	100	350	

Explanation of page 4




The **input bias current** is the current flowing into the **positive and negative inputs** of the current sense amplifier. In current sense amplifiers, this current is usually higher than in standard operational amplifiers, typically ranging from a few μA to several hundred μA .

This is mainly due to the architecture of the current sense amplifier, which is designed to operate with an **input common-mode voltage** that can be far beyond the V_{CC} supply range.


For example, in a classic differential current-sense architecture such as the [TSC2010](#), when the common-mode voltage is higher than V_{CC} , current flows through the internal resistors. In addition, to withstand a common-mode voltage much higher than its own supply voltage, the input stage also requires current, which is drawn from the **common-mode supply bus**.

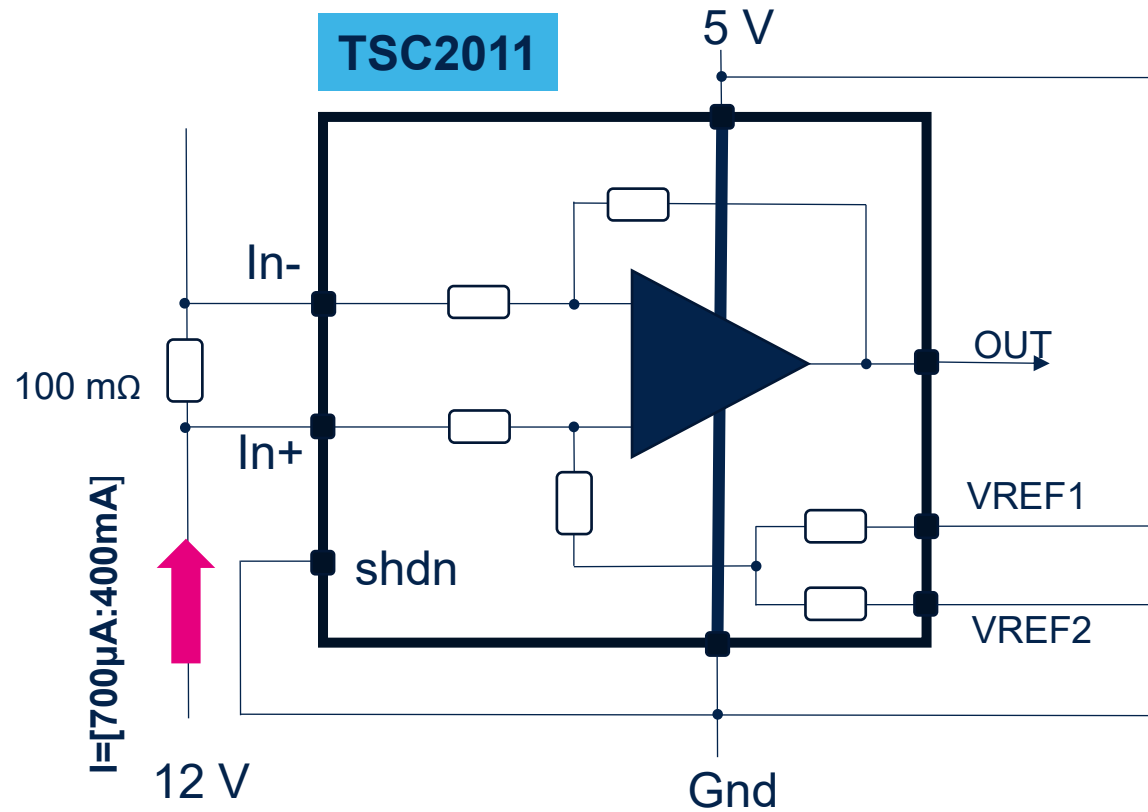Example

$$I_{ib} \text{ impact}(\%) = \frac{I_{ib}}{I_{sense}} * 100$$



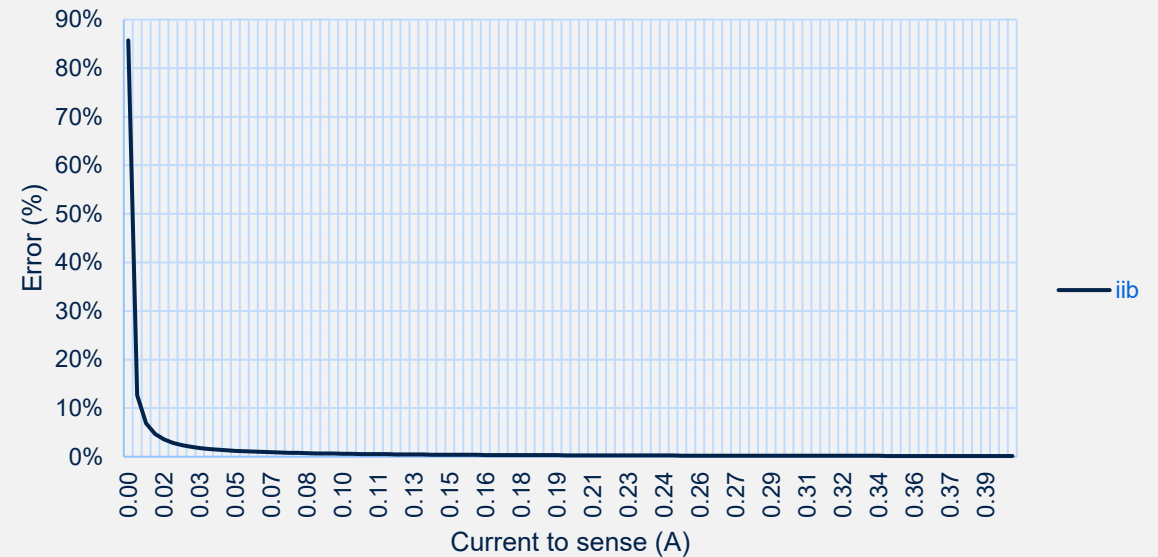Contribution of input bias current parameter in the overall error



Explanation of page 6



A first key point is that the current flowing through the shunt resistor should be **much higher than the input bias current**. Otherwise, the error caused by the input bias current must be included in the analysis.

This error can be expressed by the equation shown, which gives the ratio of the **input bias current** to the **measured current**.

$$I_{ib} \text{ impact}(\%) = \frac{I_{ib}}{I_{sense}} * 100$$

The graph illustrates the expected error over the current range when only the input bias current is considered. With the [TSC2011](#) at $V_{icm} = 12 \text{ V}$, a typical error below 5% can be expected only when the measured current is greater than 7 mA.

Shunt resistance error

Shunt tolerance (%)

Tempco (ppm/°C)

EMF (μV/°C)

STANDARD ELECTRICAL SPECIFICATIONS						
GLOBAL MODEL	SIZE	POWER RATING $P_{70\text{ }^{\circ}\text{C}}$ W	TOLERANCE $\pm \%$	RESISTANCE VALUE RANGE Ω	RESISTANCE VALUES CURRENTLY AVAILABLE ⁽¹⁾ Ω	WEIGHT (typical) g
WSBS5216	5216	12	5, 10	50μ to 250μ	100μ	19.2

TECHNICAL SPECIFICATIONS		
PARAMETER	UNIT	RESISTOR CHARACTERISTICS
Temperature coefficient	ppm/°C	± 150
Temperature coefficient (element material)	ppm/°C	± 20
Operating temperature range	°C	-65 to +170
Thermal EMF	μV/°C	< 1 for 100 μΩ
Inductance	nH	< 5
Maximum continuous current rating	A	$(P/R)^{1/2}$

Specification from Vishay shunt resistance

$$\text{Shunt error} = \varepsilon_{\text{shunt}} + \varepsilon_{\text{shunt}} t_{\text{tempco}} * \Delta T + EMF * \Delta T e_{2e}$$

($\Delta T e_{2e}$) temperature variations across the resistor

Shunt resistance error

Explanation of page 8



Although the shunt resistor isn't integrated into the current sense amplifier, it's an essential part of the current measurement and must be considered in the overall accuracy analysis.

Several shunt-related parameters contribute to measurement inaccuracy. The first is **shunt tolerance**. This error term depends on the application and isn't related to the current sense amplifier itself, but it's a major contributor to the total system error. Its effect is similar to the amplifier **gain error**, since it acts as a ratio on the measured current. As defined in the shunt datasheet, a 5% tolerance on the shunt resistance directly results in a 5% current measurement error.

The shunt resistance value also varies with temperature, so its **temperature coefficient** must be taken into account. In the example shown, a temperature increase of 100°C from ambient adds 1.5% error to the current measurement.

A last parameter to consider is the **thermal EMF**. This is a very small voltage, typically in the μV range, generated by an end-to-end temperature difference ΔT_{e2e} across the resistor. Its effect is closer to an **offset error**, such as dV_{io}/dt .

Example

Error estimation due to shunt resistance


$$\text{Shunt error} = 0.5\% + 100\text{ppm} \cdot 100^\circ\text{C} + 5\mu\text{V} \cdot 10^\circ\text{C}$$

Impact on current measurement 100mA

$$\begin{aligned}\text{Theoretical } V_{\text{sense}} &= 100\text{ mA} \cdot 10\text{ m}\Omega = 1\text{ mV} \\ V_{\text{sense}} \text{ due to shunt error} &= 1.065\text{ mV}\end{aligned}$$

Particularity

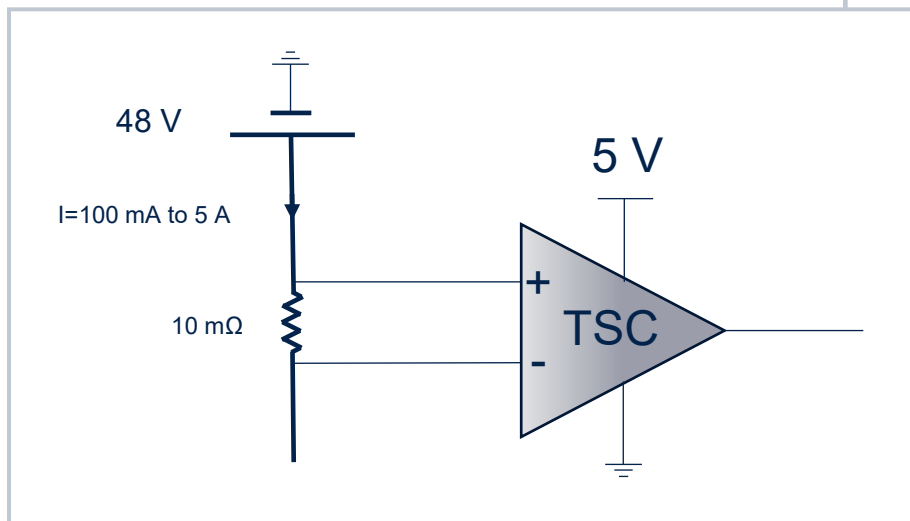- $I_{\text{load}} = 100\text{ mA to } 5\text{ A}$
- $R_{\text{shunt}} = 10\text{ m}\Omega$
- Tolerance = 0.5%
- $\text{Tempco} = 100\text{ ppm}/^\circ\text{C}$
- Temperature range = 125°C
- $\text{EMF} = 5\mu\text{V}/^\circ\text{C}$
- A temperature difference between both connections of the shunt is 10°C



The shunt adds 6.5% error @125 °C for a current of 100 mA to measure.

Explanation of page 10



This example shows how shunt resistor inaccuracies can significantly affect current measurement.

The application measures current from **100 mA to 5 A** using a **10 mΩ shunt** at **125°C**. Although a high-performance shunt is selected, the temperature gradient across its terminals is high.


The shunt has an initial tolerance error of **0.5%**. At **125°C**, the temperature coefficient must also be considered, increasing the shunt-related error to **1.5%**.

In addition, the temperature isn't uniform around the shunt, and a **10°C difference** appears between its two terminals. This creates a **thermal EMF** that adds a **50 μV offset** at **125°C**. For the minimum measured current, **100 mA**, this corresponds to an additional **5% error**.

Ideally, the sense voltage is **1 mV** for **100 mA** through a **10 mΩ shunt**. But when all shunt error sources and temperature effects are included, V_{sense} rises to **1.065 mV**, leading to a total shunt-related inaccuracy of **6.5%** for the **100 mA** measurement.

This example shows that choosing a current sensor with very low impact is important, but selecting the right shunt resistor with the same level of care is equally essential.

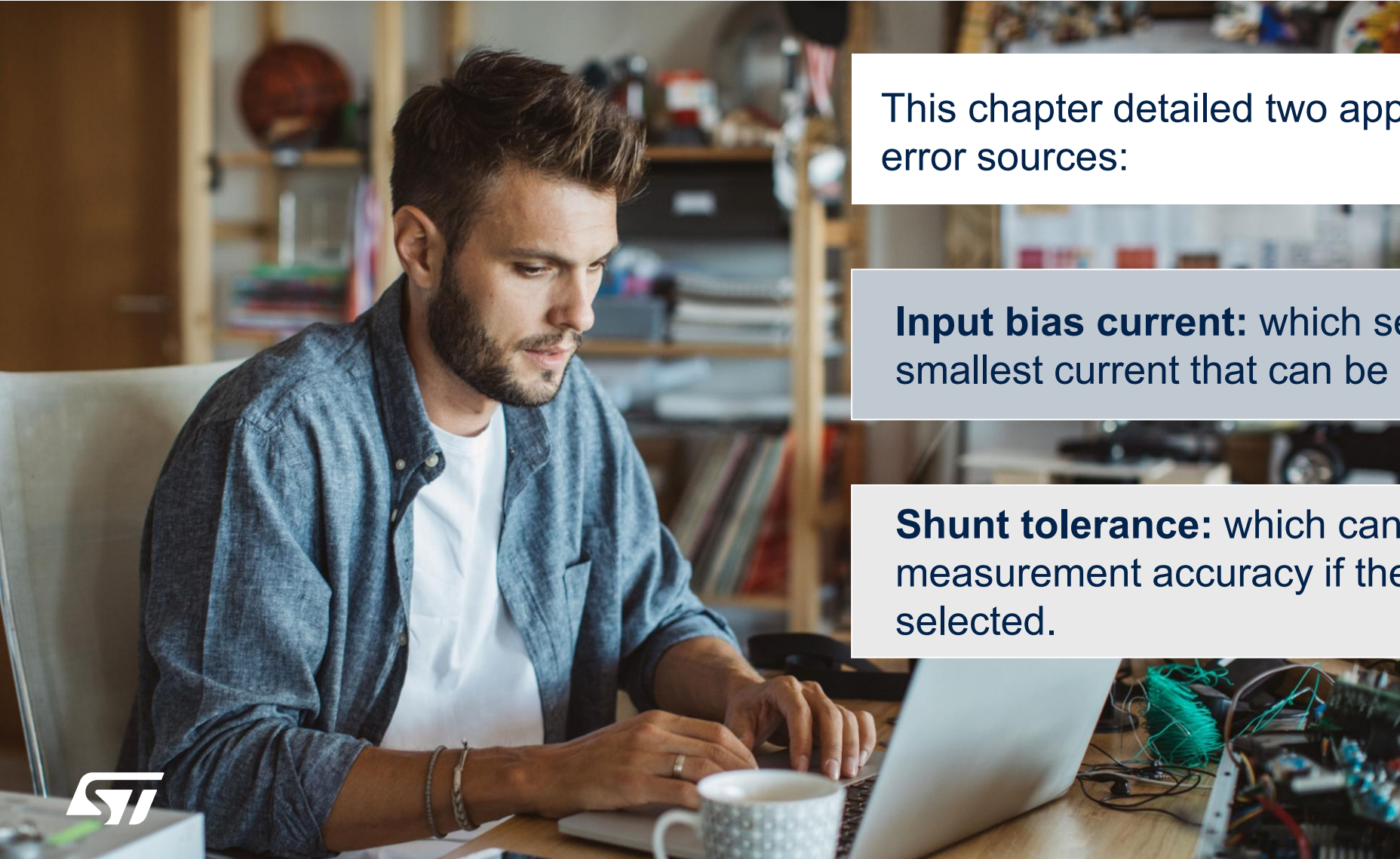Summary of percentage-based error sources



This chapter detailed two application-dependent error sources:

Input bias current: which sets a limit on the smallest current that can be measured accurately.

Shunt tolerance: which can significantly affect measurement accuracy if the shunt isn't carefully selected.

Summary of percentage-based error sources

Explanation of page 12



This chapter has presented **two error sources** that are more application-dependent

1. The input bias current, which sets a limit on the smallest current that can be accurately measured.
2. The shunt tolerance, which can significantly impact the measurement accuracy if the shunt isn't selected carefully.

Our technology starts with You



Find out more at www.st.com

© STMicroelectronics - All rights reserved.

ST logo is a trademark or a registered trademark of STMicroelectronics International NV or its affiliates in the EU and/or other countries.

For additional information about ST trademarks, please refer to www.st.com/trademarks.

All other product or service names are the property of their respective owners.

