



**STA333W demo board application note**

---

**Introduction**

The purpose in this document is:

- to describe how to connect the AN2481 demo board,
- how to evaluate the demo board performance with electrical curve data,
- how to avoid critical board and layout issues.

Application note can be configured for 2.0 channels of ternary. It is a total solution for the digital audio power amplifier in a TV and portable application.

*Note: All the test items and graph data in this document are measured by Audio Precision equipment.*

# Contents

<b>1</b>	<b>Test condition and connection of demo board</b>	<b>3</b>
1.1	Test condition	3
1.1.1	Power supply and interface connections	3
1.1.2	Output configuration	3
1.2	Equipment requirement	3
1.3	Connection method	4
1.3.1	Schematic	5
1.4	PCB Layout	6
1.4.1	Top view of PCB layout	6
1.4.2	Bottom view of PCB layout	6
1.4.3	Test connection	7
<b>2</b>	<b>Electrical characteristics</b>	<b>8</b>
<b>3</b>	<b>Test curve report</b>	<b>9</b>
3.1	BTL configuration	9
<b>4</b>	<b>Design guideline for PCB schematic and layout</b>	<b>23</b>
4.1	Schematic	23
4.1.1	Main driver for components selection	23
4.2	Decoupling capacitors	23
4.2.1	Output filter	23
4.3	Layout	26
<b>5</b>	<b>Revision history</b>	<b>34</b>

# 1 Test conditions and connection of demo board

## 1.1 Test conditions

### 1.1.1 Power supply and interface connections

1. Connect positive voltage of 12 V DC power supply to +Vcc pin and negative to GND.
2. Connect positive voltage of 3.3 V DC power supply to +3.3 V pin and negative to GND.
3. Connect GUI LPT interface board to the J1 connector of AN2481 demo board.
4. Connect the S/PDIF signal cable to the RCA jack on the interface board, the other side connecting to the signal source such as Audio precision or DVD player.
5. The voltage range of the DC power supply for Vcc is from 5 V to 18 V.

### 1.1.2 Output configuration

STA333ML demo board can be configured in the ternary state for 2.0 channels.


## 1.2 Equipment requirement

- Audio Precision (System 2700) by AP Co., USA
- DC power supply (5 V to 18 V)
- Digital oscilloscope (TDS3034B) by Tektronix
- PC (with AN2481 GUI control software installed)

## 1.3 Connection method

Top view of demo board.

**Figure 1. Block diagram**

 

### 1.3.1 Schematic

Figure 2. Schematic diagram


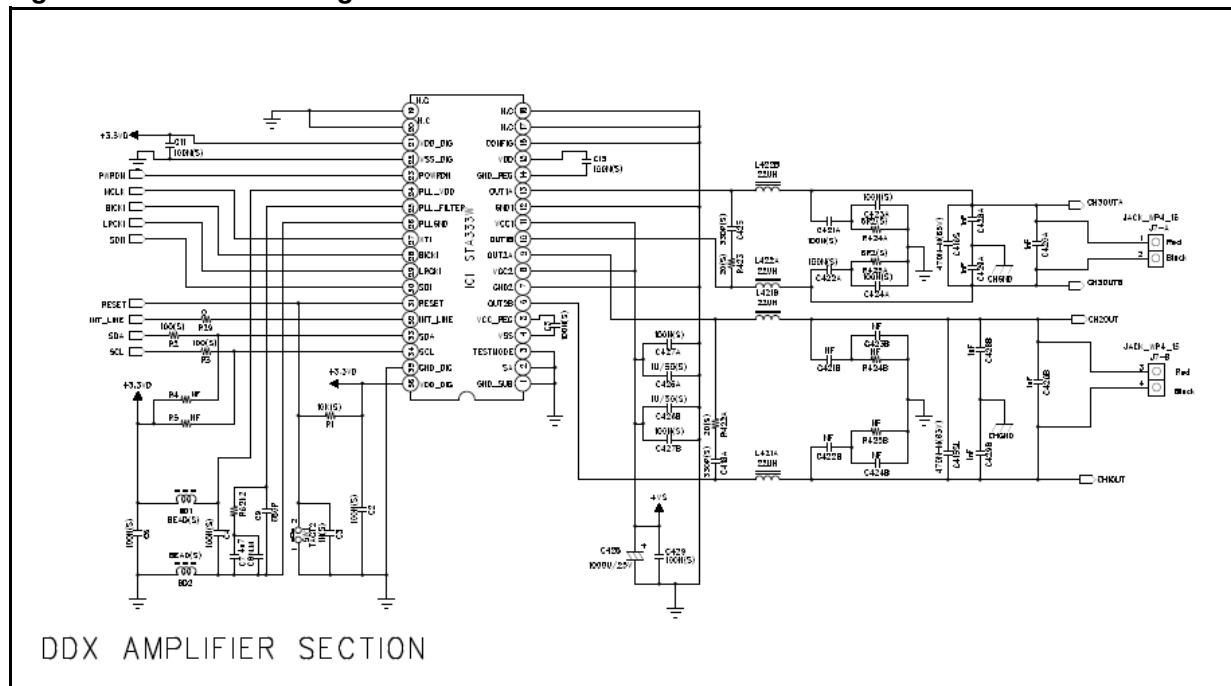



Figure 3. Headphone schematic diagram

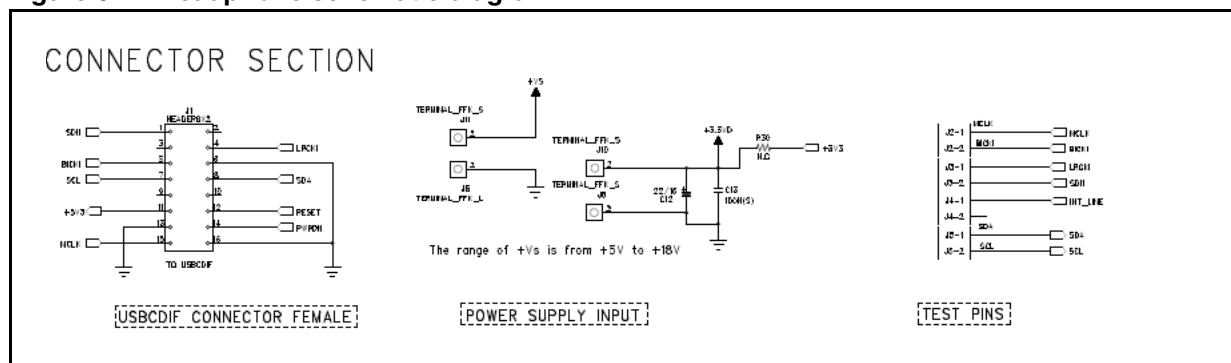

## 1.4 PCB Layout


### 1.4.1 Top view of PCB layout

Figure 4. Top layout

 


### 1.4.2 Bottom view of PCB layout

Figure 5. Bottom layout

 

### 1.4.3 Test connection

Figure 6. Block diagram of test equipment

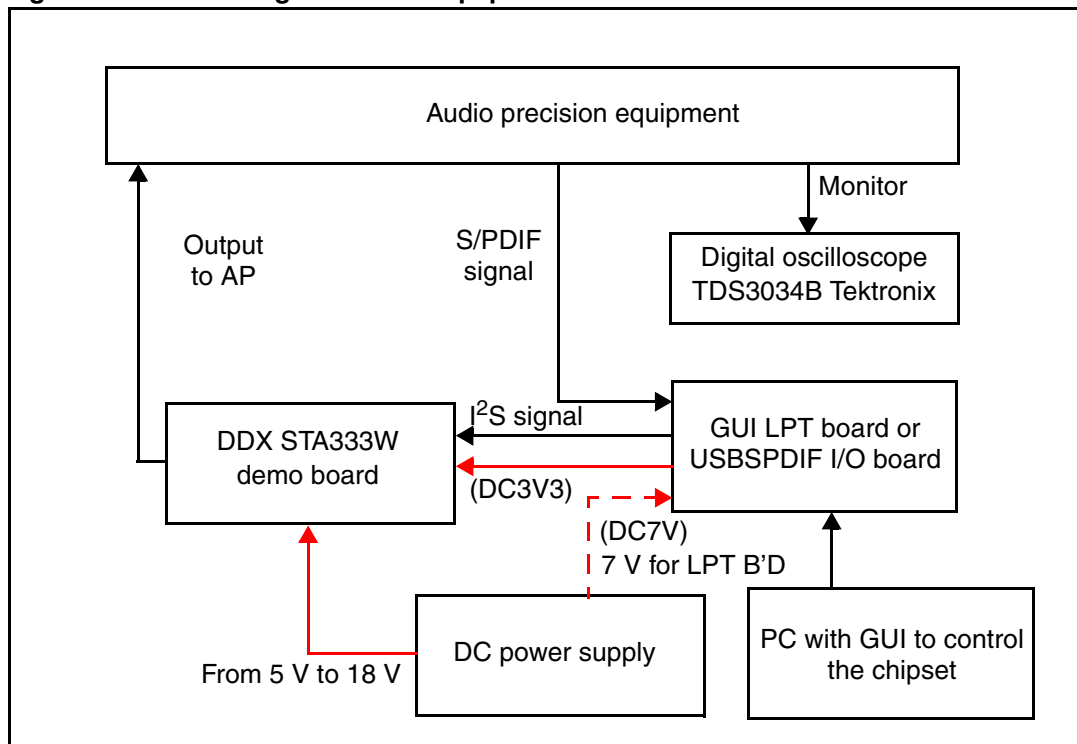

## 2 Electrical characteristics

**Table 1. Electrical characteristics<sup>(1)</sup>**

Parameter	Configuration	Test condition	Unit
PSRR (50 Hz - 120 Hz)	BTL configuration	Please refer to measurements section	65 dB
Min SNR	BTL configuration	1 W output, -20 dBFs input, 1 KHz	100 dB
Max modulation index	DDX modulation mode		98.5%
Vcc current (18 V)	BTL configuration	Operating Quiescent Standby/sleep	40 mA 30 mA 0 mA


1. Refer to the STA333W demo board circuit. Vs= +18 V, Tamb = 25.5 °C, f = 1 KHz, Ref = 1 W unless otherwise specified.

*Note: THD works better with high impedance loading (based on a fixed value of  $R_{dsON}$ ).*



### 3 Test curve report

Figure 7. Ternary mode efficiency (2.0 BTL configuration)

 

Condition:  $R_{LOAD} = 8\ \Omega$ ;  $V_{CC} = 18\ V$

#### 3.1 BTL configuration

Figure 8. Output power versus supply voltage

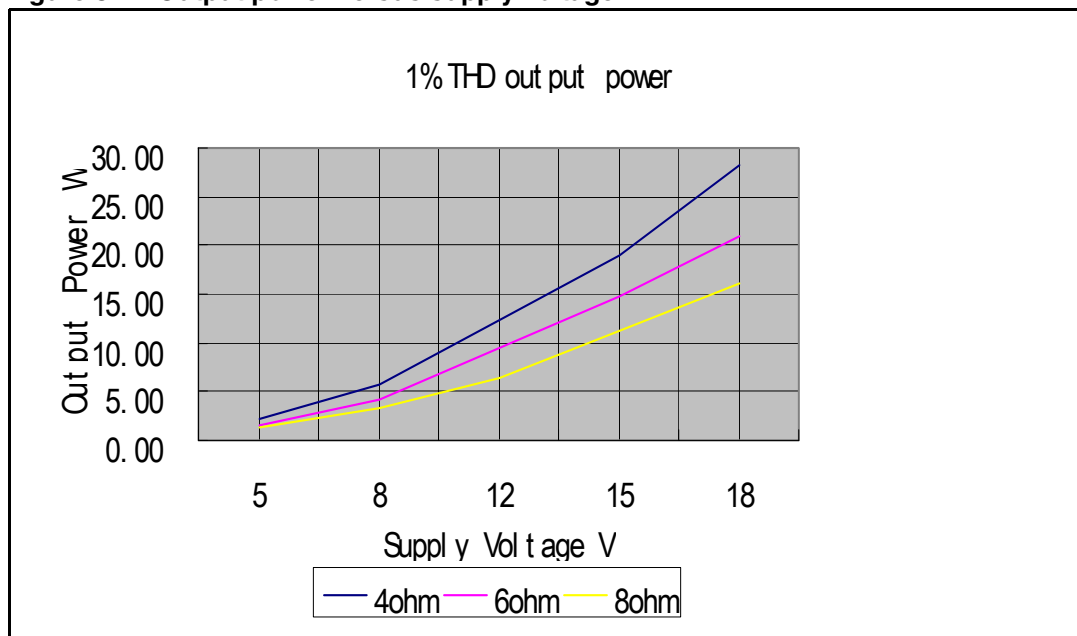


Figure 9. Channel separation 5 V 1 W 4 ohm

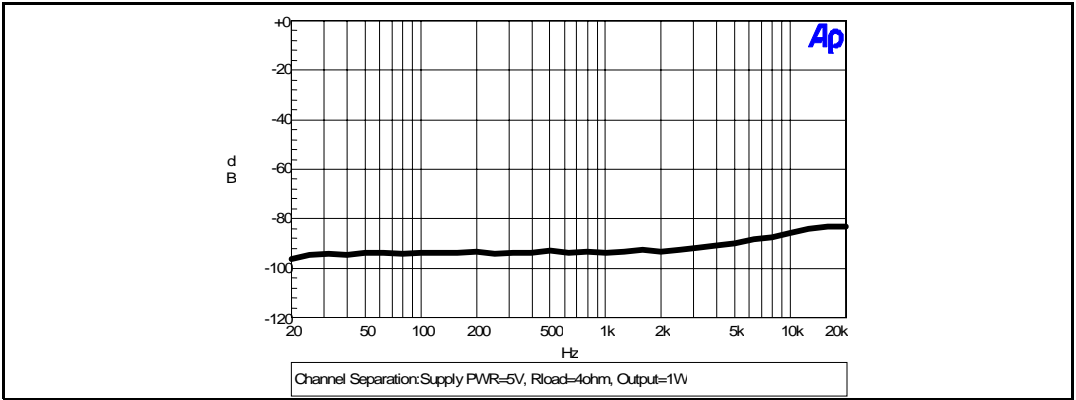


Figure 10. Channel separation 5 V 1 W 6 ohm

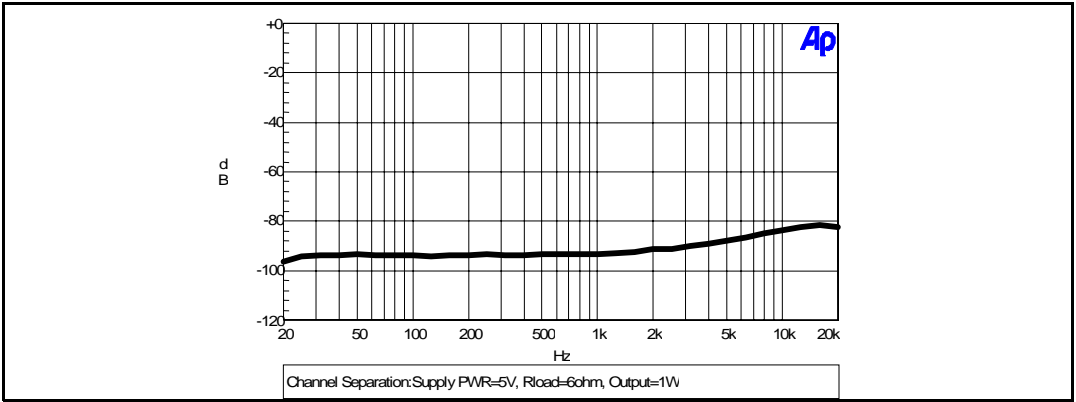


Figure 11. Channel separation 5 V 1 W 8 ohm

 


Figure 12. FFT 0 dBFs 1 KHz 5 V 4 ohm

 


Figure 13. FFT -60 dBFs 1 KHz 5 V 4 ohm

 


Figure 14. FFT 0 dBFs 1 KHz 5 V 6 ohm

 


Figure 15. FFT -60 dBfs 1 KHz 5 V 6 ohm

 


Figure 16. FFT 0 dBfs 1 KHz 5 V 8 ohm

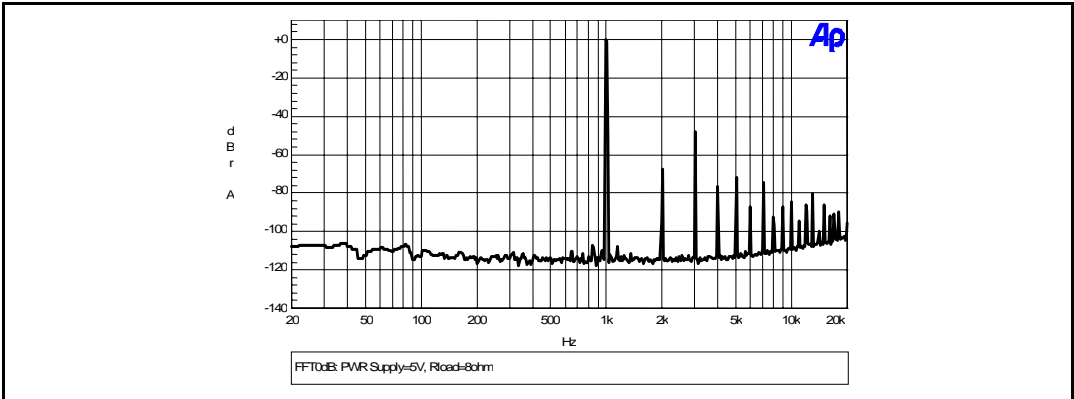


Figure 17. FFT -60 dBfs 1 KHz 5 V 8 ohm

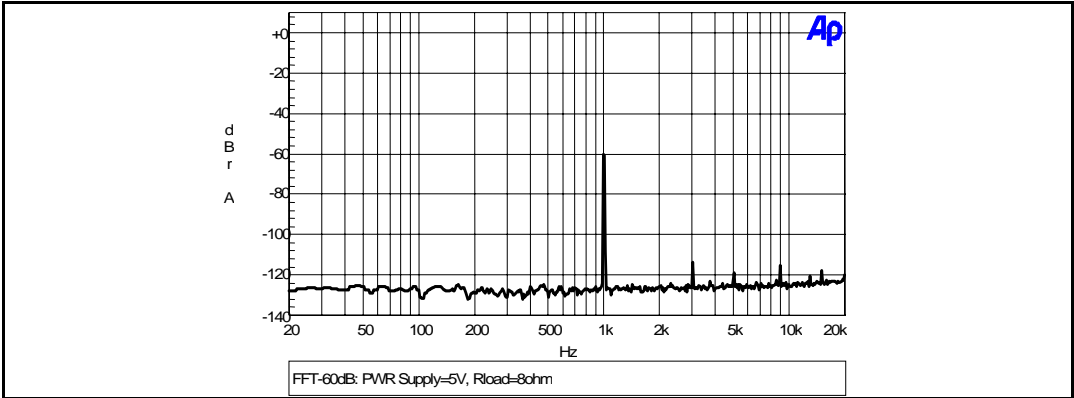


Figure 18. THD + N versus Freq. 5 V Vcc 4 ohm

 


Figure 19. THD + N versus Freq. 5 V Vcc 6 ohm

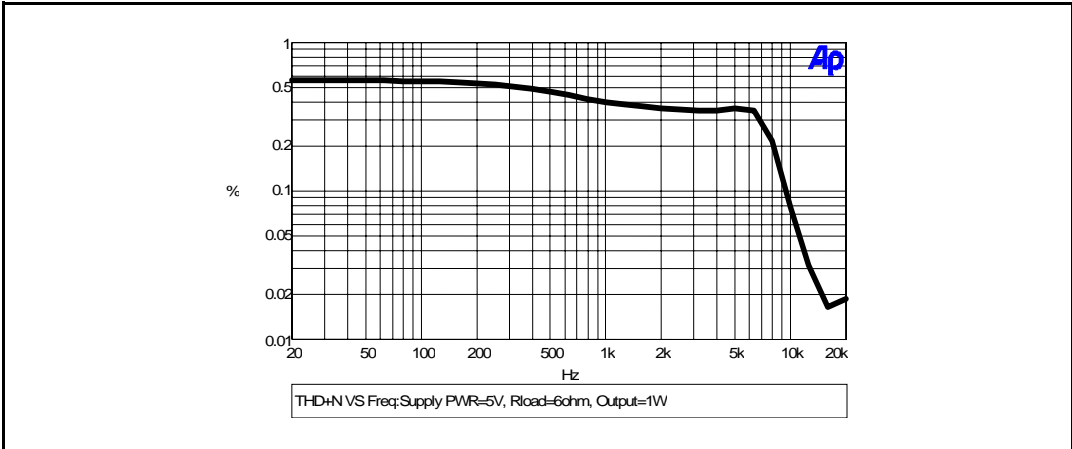


Figure 20. THD + N versus Freq. 5 V Vcc 8 ohm

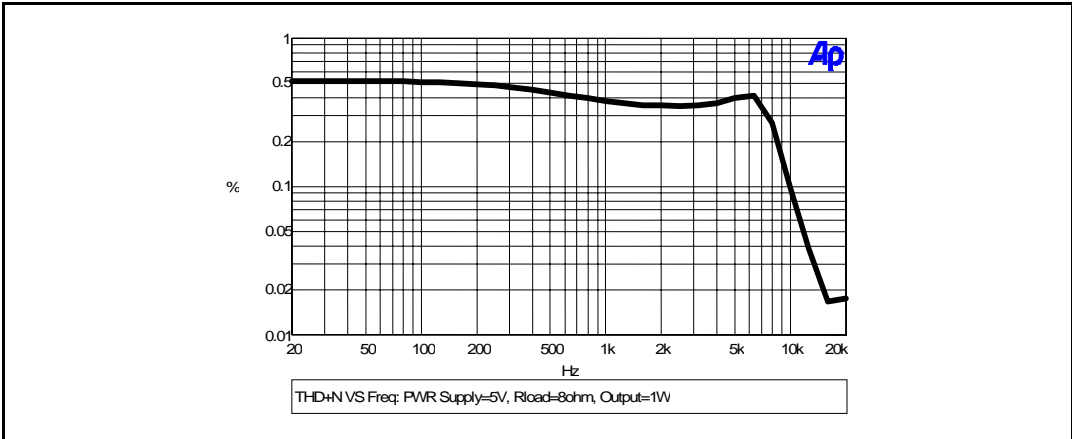


Figure 21. Channel separation 12 V 1 W 4 ohm)

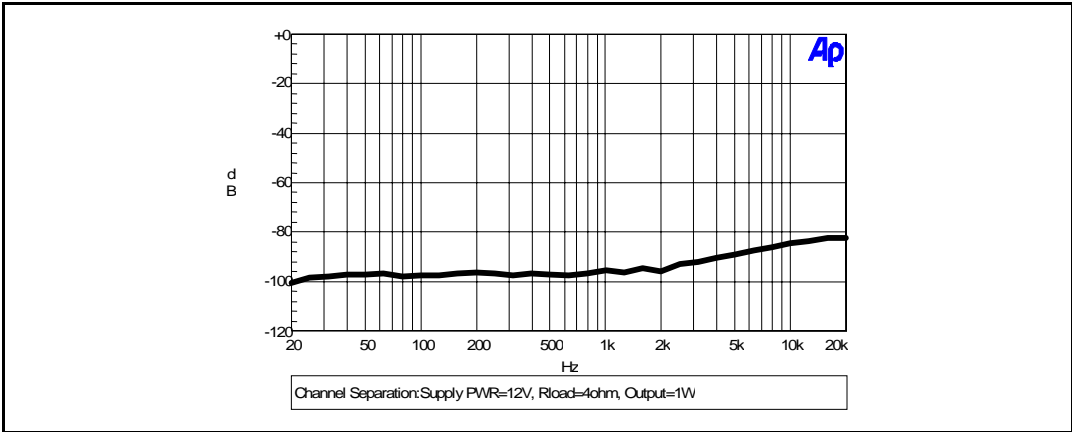


Figure 22. Channel separation 12 V 1 W 6 ohm)

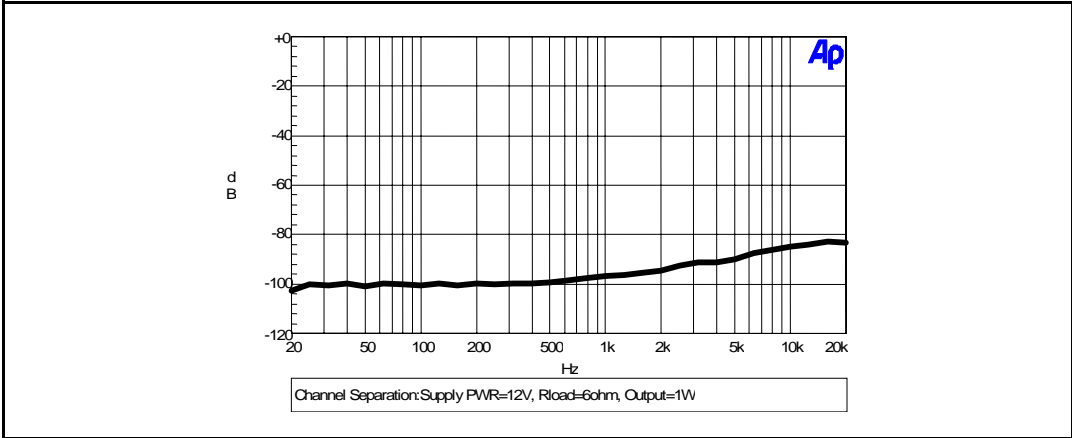


Figure 23. Channel separation 12 V 1 W 8 ohm)

 


Figure 24. FFT 0 dBFs 1 KHz 12 V 4 ohm

 


Figure 25. FFT -60 dBFs 1 KHz 12 V 4 ohm

 


Figure 26. FFT 0 dBFs 1 KHz 12 V 6 ohm

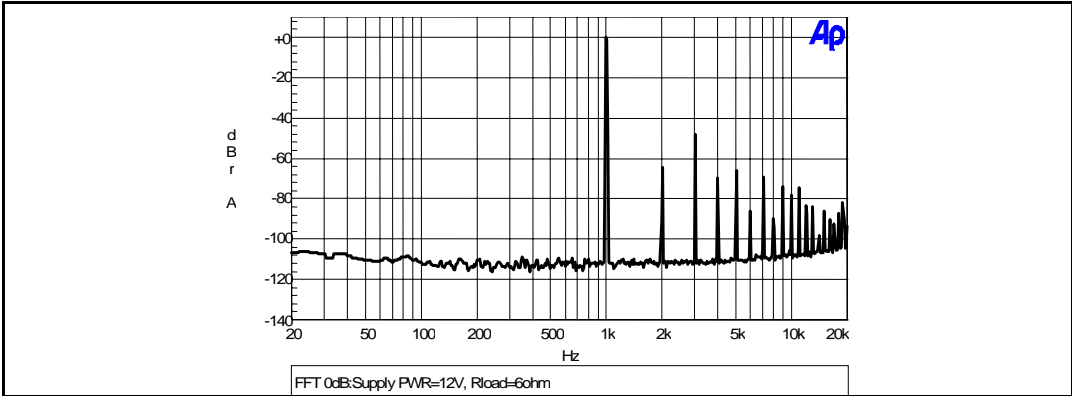


Figure 27. FFT -60 dBfs 1 KHz 12 V 6 ohm

 


Figure 28. FFT 0 dBfs 1 KHz 12 V 8 ohm

 


Figure 29. FFT -60 dBfs 1 KHz 12 V 8 ohm

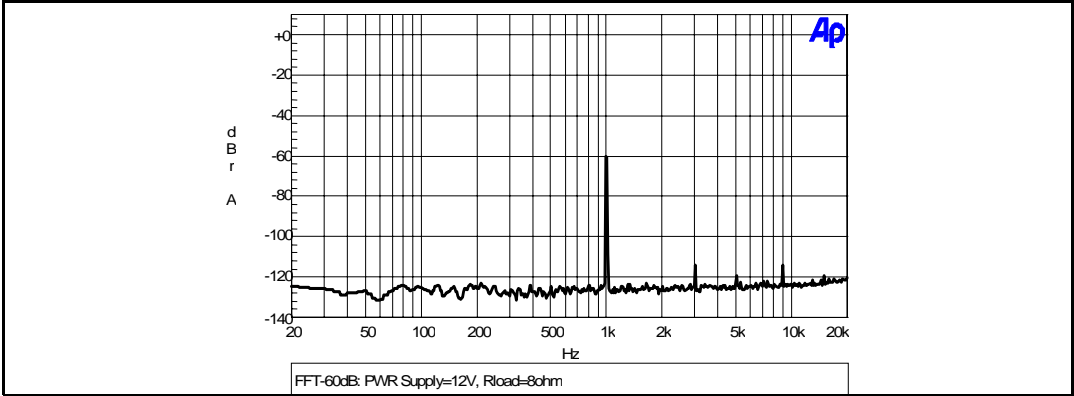




Figure 30. THD versus Freq 12 V Vcc 4 ohm

 


Figure 31. THD+N versus Freq 12 V 6 ohm

 


Figure 32. THD+N versus Freq 12 V 8 ohm

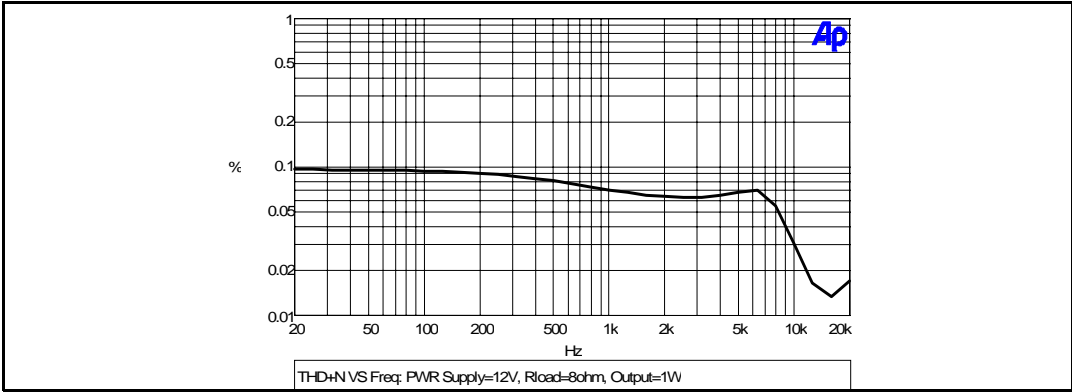


Figure 33. Channel separation 18 V 1 W 4 ohm

 


Figure 34. Channel separation 18 V 1 W 6 ohm

 


Figure 35. Channel separation 18 V 1 W 8 ohm

 


Figure 36. FFT 0 dBFs 1 KHz 18 V 4 ohm

 


Figure 37. FFT -60 dBFs 1 KHz 18 V 4 ohm

 


Figure 38. FFT 0 dBFs 1 KHz 18 V 6 ohm

 


Figure 39. FFT -60 dBfs 1 KHz 18 V 6 ohm

 


Figure 40. FFT 0 dBfs 1 KHz 18 V 8 ohm

 


Figure 41. FFT -60 dBfs 1 KHz 18 V 8 ohm

 


Figure 42. THD versus Freq. 18 V Vcc 4 ohm

 


Figure 43. THD versus Freq. 18 V Vcc 6 ohm

 


Figure 44. THD versus Freq. 18 V Vcc 8 ohm

 


Figure 45. THD versus PWR 4 ohm load

 


Figure 46. THD versus PWR 6 ohm load


 


Figure 47. THD versus PWR 8 ohm load

 

## 4 Design guideline for PCB schematic and layout

### 4.1 Schematic

#### 4.1.1 Main driver for components selection

- Absolute maximum rate: 20 V.
- Bypass capacitor 100 nF in parallel to 1  $\mu$ F for each power Vcc branch. Preferable dielectric is X7R.
- Vdd and ground for PLL filter separate of the power supply.
- Coil saturation current compatible with the peak current of the application.


### 4.2 Decoupling capacitors

There are two different ways to use the decoupling capacitors:

- shared among the channels: the best practise layout route must be used for the board,
- one decoupling system per channel: it is mandatory that the decoupling capacitor must be as close as possible to the IC pins.

#### 4.2.1 Output filter

Figure 48. Output filter

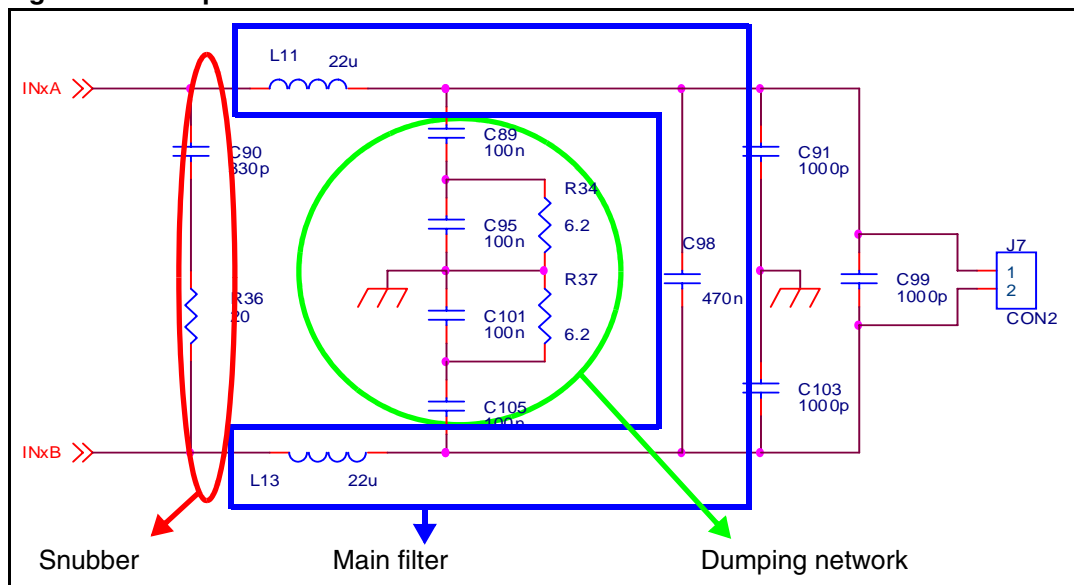

- The key function of a snubber network is to absorb energy from the reactance in the power circuit. The purpose of the snubber RC network is in order to avoid the high pulse energy (such as spikes) in the power circuit which can be dangerous to the system. When using the snubber network, the energy is transferred to and from the snubber network, ensuring the system can work safely.

- The purpose of the main filter is to remove frequency higher than audible range of 20 KHz. The main filter uses the Butterworth formula to define the cut off frequency, which must be higher than 20 KHz, otherwise the frequency response is affected.
- The purpose of the dumping network is to avoid high frequency oscillation on the output circuit. After using the dumping network the THD can be improved, and can also avoid the inductive copper on the PCB route when the system is working in high frequency with PWM or PCM.


### Snubber filter

The snubber circuit must be optimized for the application. Starting values are 330 pF in series to 22 ohm. The power can be defined by the following formula which considers the power supply, frequency and capacitor value:

$$P = C \cdot f \cdot (2 \cdot V)^2$$

This power is dissipated in series resistance.


**Figure 49. Snubber filter**

 

### Dumping network

The C-R-C is a dumping network. It is mainly intended for high inductive loads.

**Figure 50. Dumping filter**

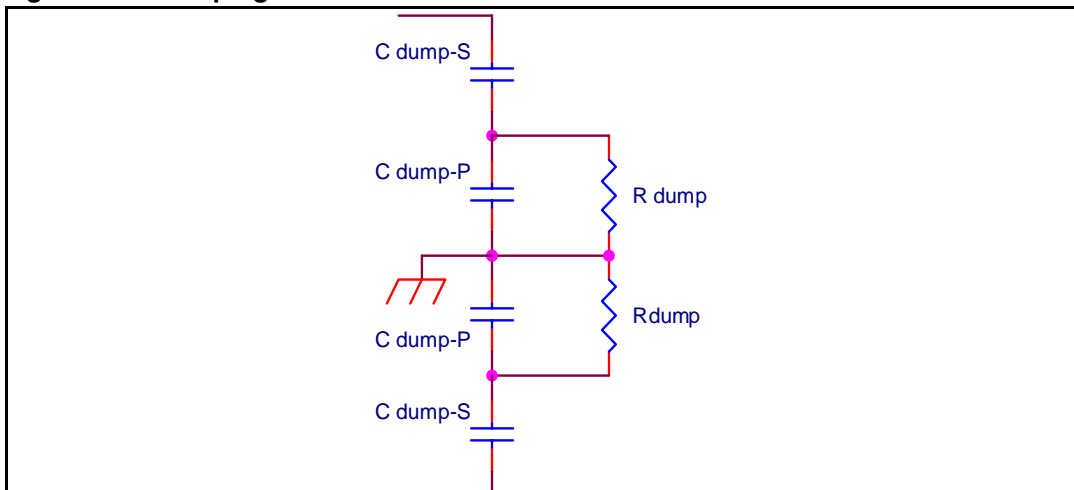


### Main filter

The main filter is an L and C based Butterworth filter. The cut-off frequency must be chosen between the upper limit of the audio band (20 KHz) and the carrier frequency (384 KHz).



Figure 51. Main filter

 


Recommended values

Rload	8 ohm	4 ohm
Lload	22 μH	10 μH
Cload	470 nF	1 μH
C dump-S	100 nF	220 nF
C dump-P	220 nF	220 nF
R dump	6.2	2.7

Recommended power up and power down sequence


Figure 52. Main filter

 

## 4.3 Layout


1. Solder snubber network as close as possible to the IC related pin.

**Figure 53. Snubber network**

 


2. Use electrolytic capacitor first to separate the Vcc branches.


**Figure 54. Separate the Vcc branches**

 


3. Minimize the path between Vcc pins and ground pin in order to avoid inductive paths.

 **Figure 55. Minimized paths between Vcc and GND**

4. To dissipate the thermal with a ground plane.

  
**Figure 56. Dissipate thermal**

5. Solder PLL filter as close as possible to the FILT pin.


**Figure 57. PLL filter**

6. For differential application create symmetrical paths for the output stage.

**Figure 58. Symmetrical paths for output stage**

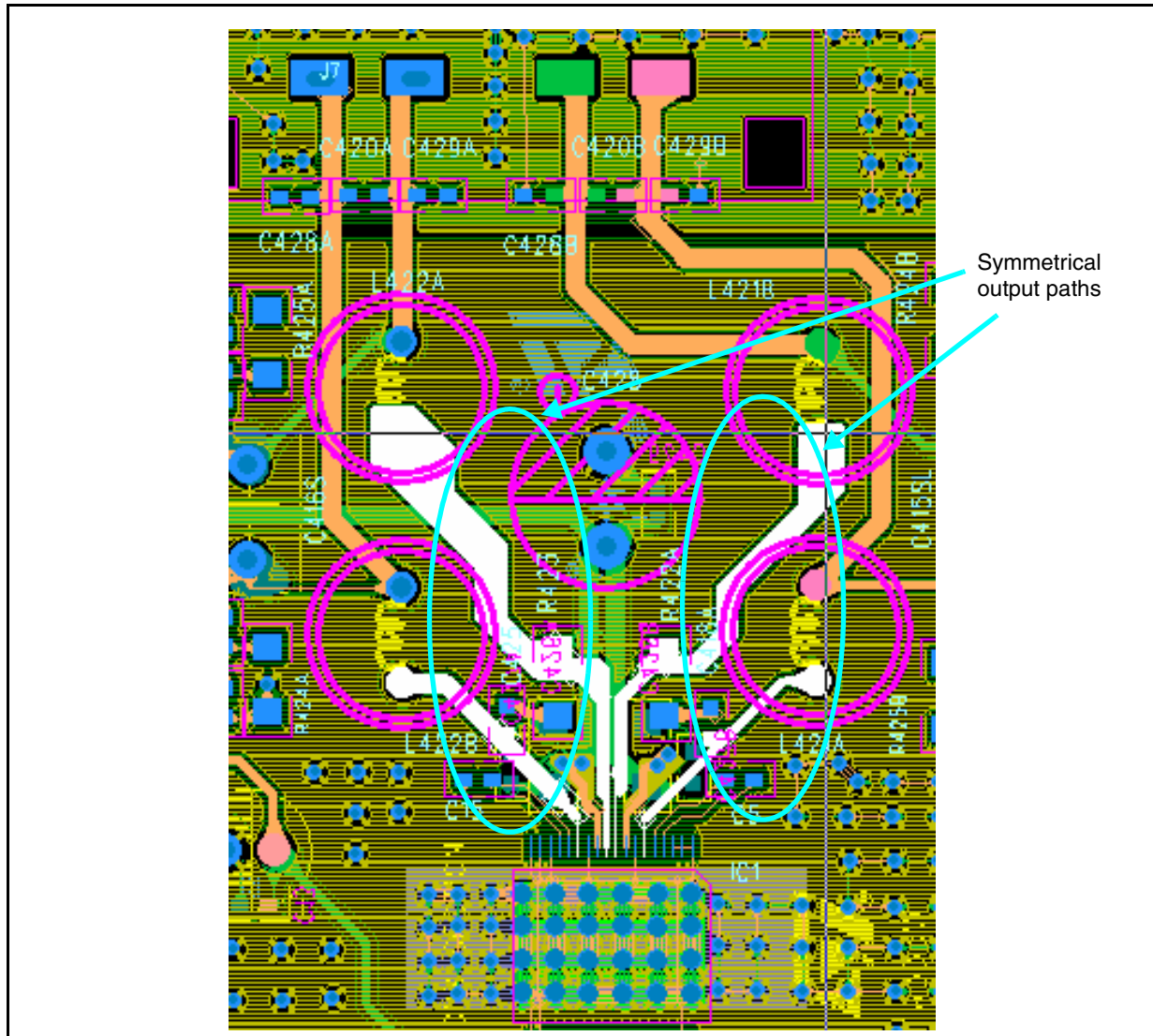


7. Separate the coil and the neighboring coil are vertical to avoid crosstalk.

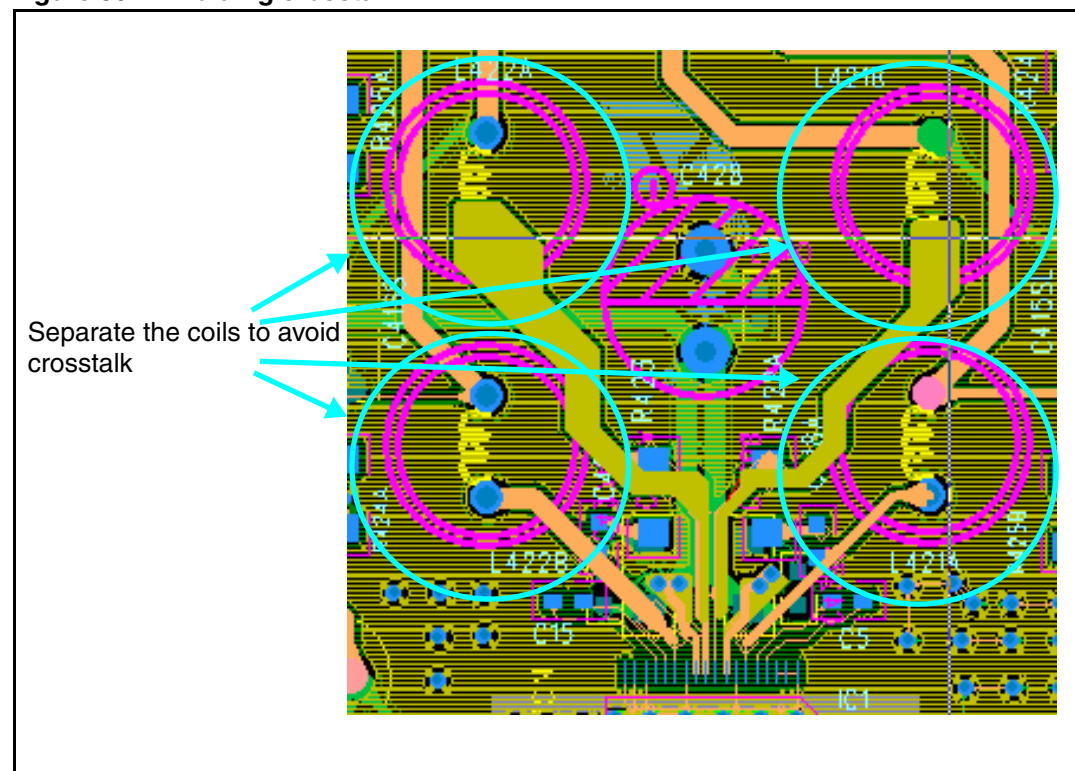**Figure 59. Avoiding crosstalk**


8. Consider ground layout. To avoid interference between ground power and small signal ground, it is necessary to divide the grounding as shown in [Figure 60](#).

**Figure 60. Ground layout**

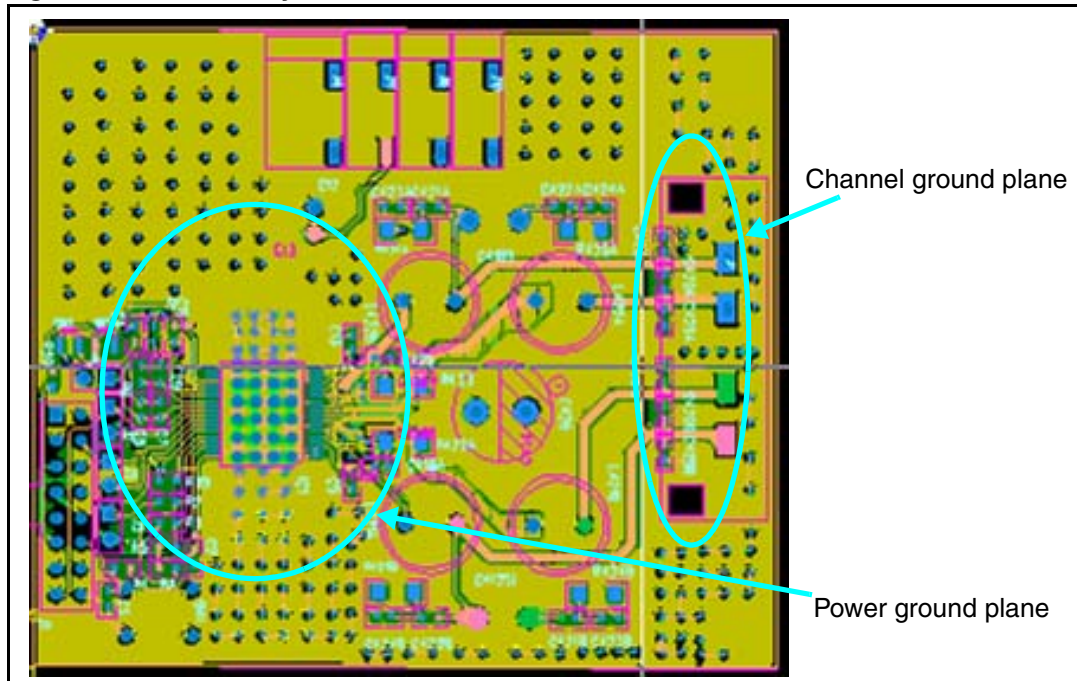


9. Thermal layout with big ground (for thermal and soldering holes). The thermal resistance junction at the bottom of the STA333W to the ambient obtainable with a ground copper area of 4 x 4 cm and with 24 via holes (see [Figure 61](#)).

**Figure 61. Thermal layout (2 of 2)**

 

10. VCC routing. The best route for the Vcc supply is one which avoids interference between different signals (for example, part A is idle whilst part B is working at full load).

Figure 62. Vcc routing

 

## 11. Vcc filter for high frequency.

The PWM system works with a fast switch (frequency of 340 KHz approximately) which means the copper wire works as a coil. In order to avoid this, a ceramic capacitor should be used to balance resistance. It is a mandatory requirement that ceramic capacitors are placed as close as possible to the related pins. The distance between the capacitor and their respective pins should be less than 5 mm in order to minimize inductive coil effect generated by the copper wire.



Figure 63. Vcc filter

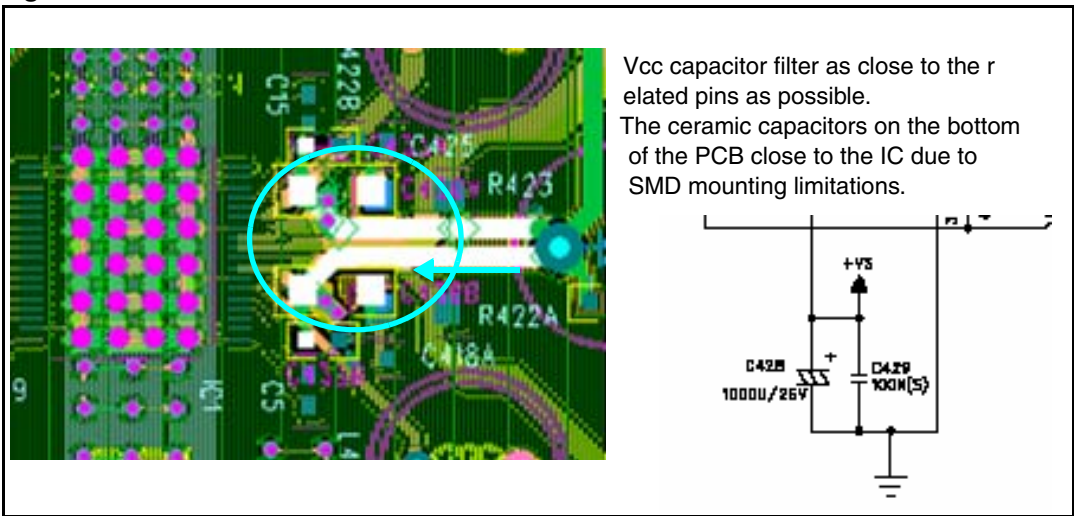


Figure 64.  
12. Snubber filters for high frequency spike protection on the PWM.

Figure 65. Snubber filter placement


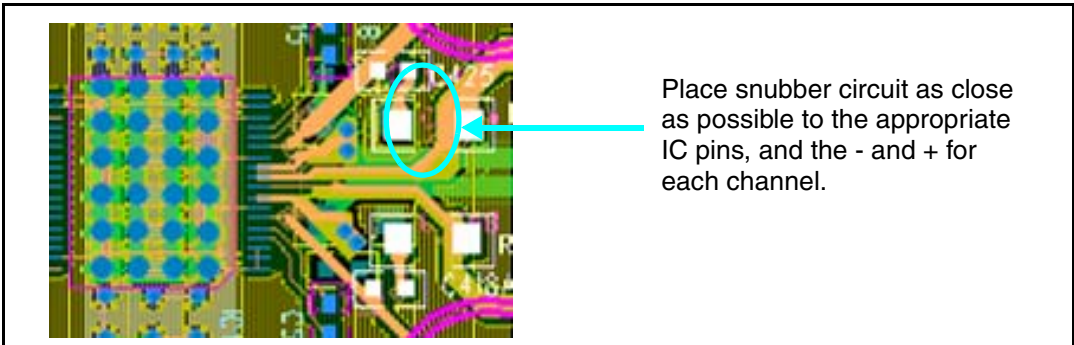


Figure 66. Examples of snubber filter placement

 




**Caution:** A spike can occur if there > 3 mm distance between the snubber network and the pins. This can cause damage to the IC. Therefore the distance must be kept below 3 mm.

### 13. Thermal layout

**Note:** The thermal pad must be connected to ground in order to properly set the IC references. It is necessary to allow the heat to flow freely to all sides of the board including top and bottom. For optimum heat dissipation it is recommended that the PCB has some solder via holes.

**Figure 67. Output routing**

 

## 5 Revision history

**Table 2. Document revision history**

Date	Revision	Changes
07-Dec-2006	1.0	Initial release.

**Please Read Carefully:**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2006 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)