


### Positive to negative buck-boost converter using ST1S03 asynchronous switching regulator

#### Abstract

The ST1S03 is a 1.5 A, 1.5 MHz adjustable step-down switching regulator housed in a DFN6 package with internal power switch.

The device is a complete 1.5 A switching regulator with internal compensation that eliminates the need for additional components. In this document the design of a polarity inverting converter is discussed.

**Figure 1. Polarity-inverting regulator using the ST1S03, 5 V<sub>IN</sub> to -5 V<sub>OUT</sub>, 500 mA**

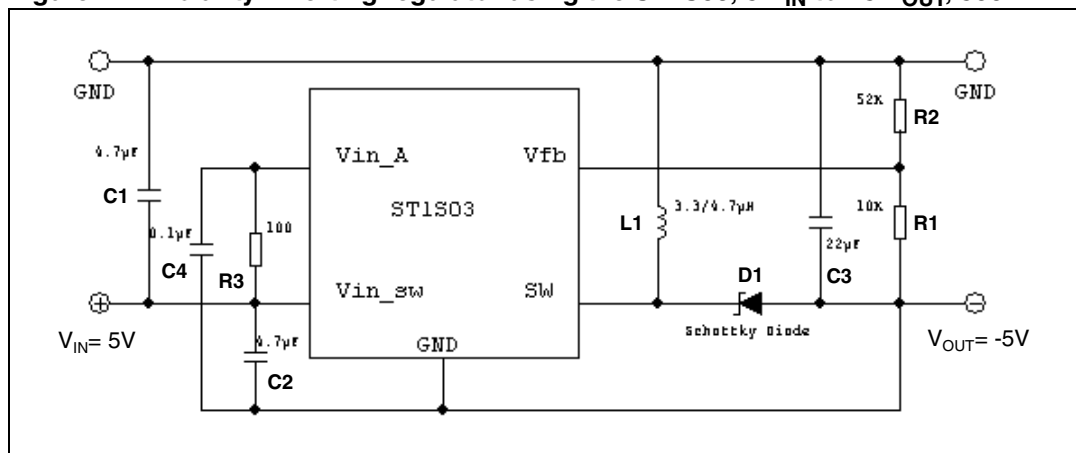

# 1 Principle of operation

The polarity-inverting converter uses the basic principle of energy storage in the inductor L during the ON time of the operating period (*Figure 2*), and then transfers the energy via the freewheeling diode D to the output during the OFF time (*Figure 3*).


When the switch turns ON, the diode is reverse-biased and current flows only in the inductor.

When the switch is turned OFF, it reverses its polarity, thus the freewheeling diode is forward-biased, and the energy stored in the inductance is transferred to the load as well as the capacitor.

The output voltage across the capacitor becomes negative because the inductor current is negative with respect to ground.


This circuit is also known as a buck-boost converter because this type of converter can step-up and step-down the magnitude of the input voltage.

Figure 2. Basic configuration of a polarity-inverting converter (buck-boost) <sup>(1)</sup>

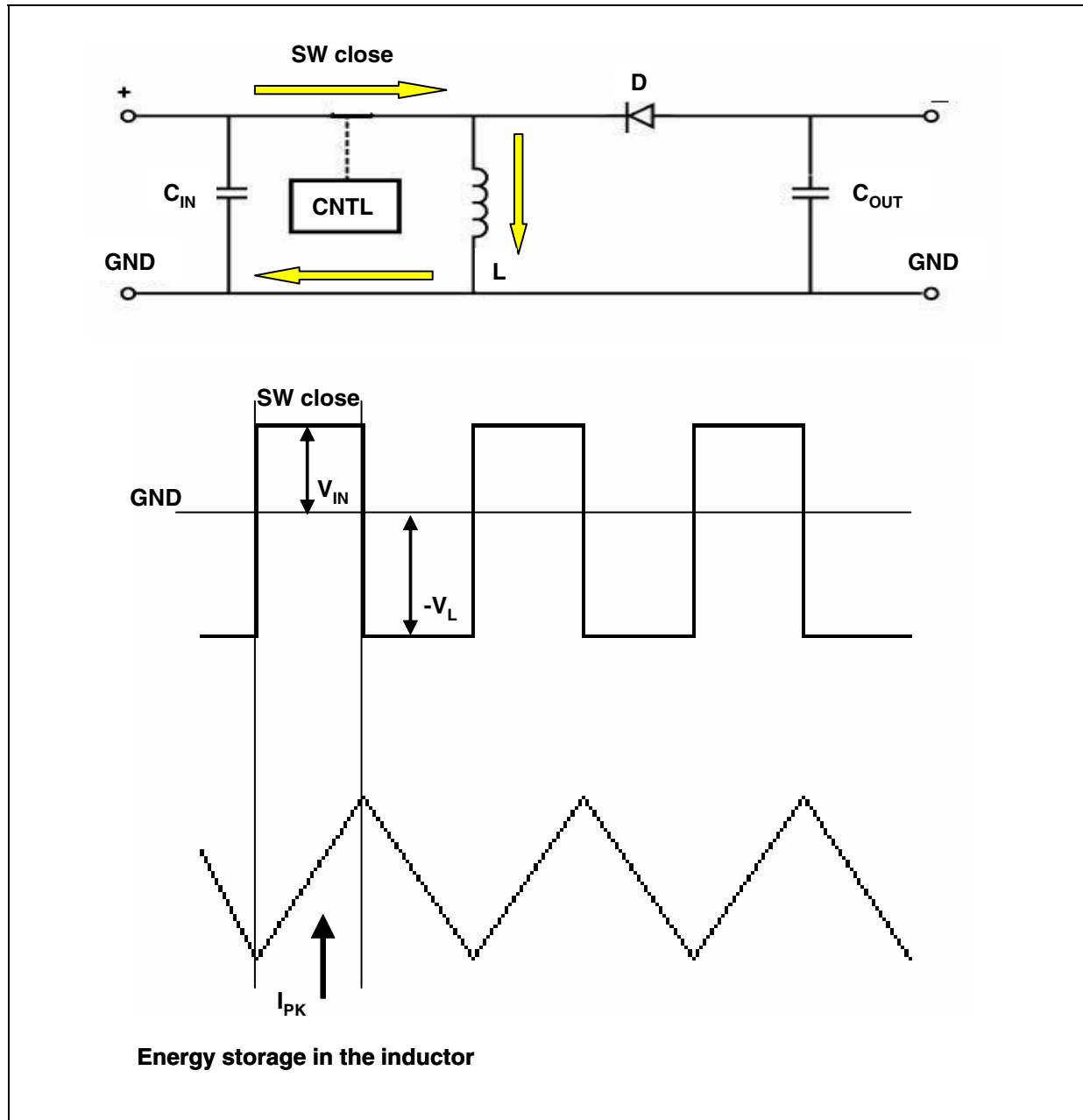

1. Energy is stored in inductor L during the ON time of the operating period.

Figure 3. Basic configuration of a polarity-inverting converter (buck-boost) <sup>(1)</sup>

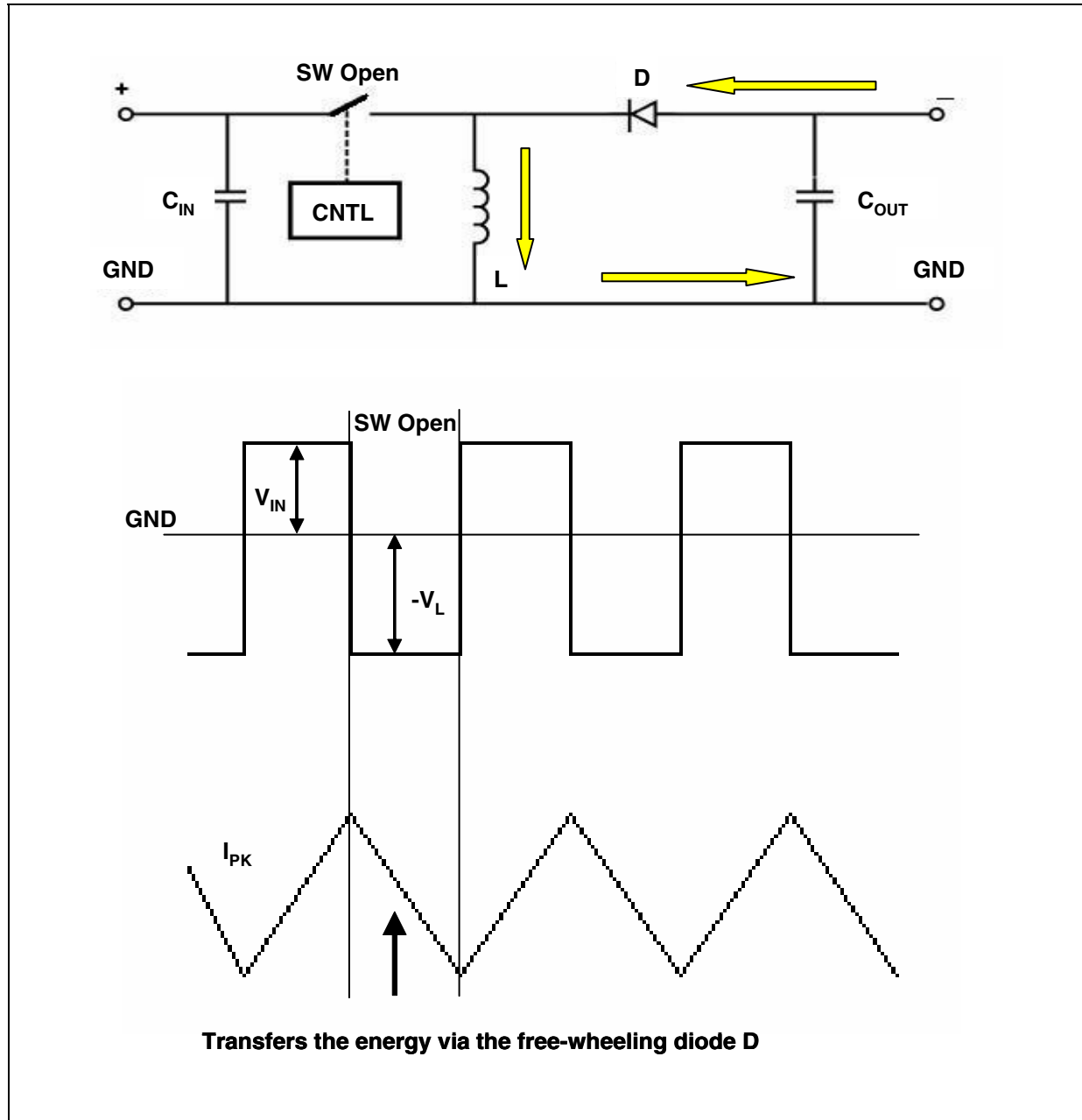


1. Energy is transferred via freewheeling diode D to the output during the OFF time of the operating period with polarity inverted referred to GND.

## 2 Design considerations

*Figure 1* shows the typical configuration of a polarity inverting regulator using the ST1S03. Note that the ground is connected to the negative output and the feedback is referred to GND, so the device is supplied by  $V_{IN}$  plus the magnitude of  $V_{OUT}$  (i.e. for 5 V<sub>IN</sub> and -5 V<sub>OUT</sub>, the total  $V_{IN}$  for device is 10 V). For this reason, the AMR of device cannot be exceeded. For example, 12 V<sub>IN</sub> and -12 V<sub>OUT</sub> for a 24 V total it not possible due to the 18 V AMR (see *Figure 4*).

**Figure 4. Total voltage of inductor**

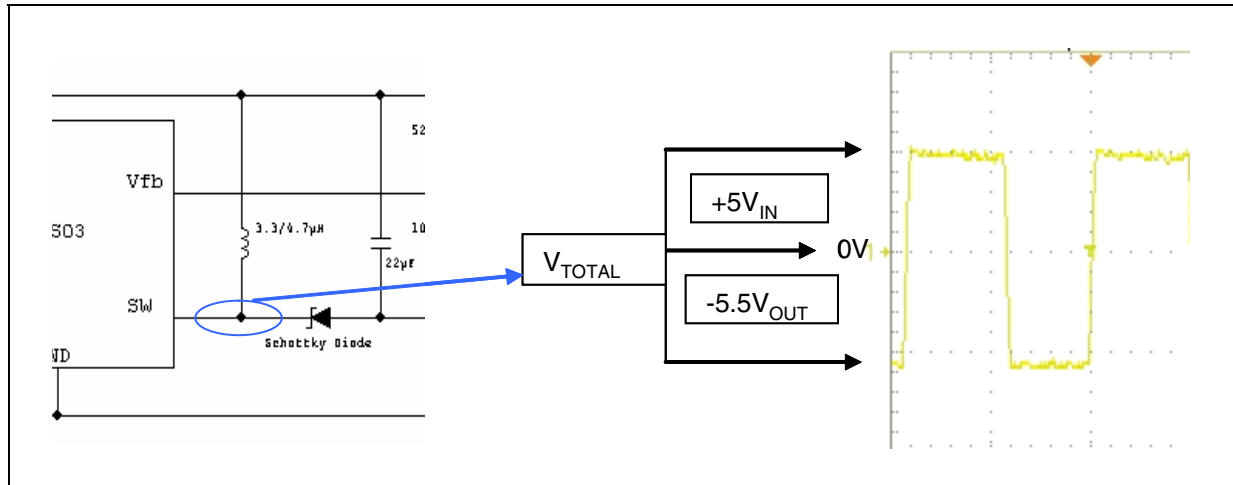

The output voltage is programmed by connecting feedback resistors from GND to  $-V_{OUT}$  (close the output capacitor to have best performance in terms of stability).

Small capacitor C2 is connected from the input to the negative output in order to provide more phase margin to stabilize the regulator loop. R3 and C4 form a simple R-C filter on the analog input, which helps to reduce noise on the supply voltage, as well as improve stability.

Figure 5. Typical waveform of the switching regulator, 5 V<sub>IN</sub>, - 5.5 V<sub>OUT</sub>, no load



Figure 6. Typical waveform of the switching regulator, 5 V<sub>IN</sub>, - 5.5 V<sub>OUT</sub>, 500 mA I<sub>OUT</sub>


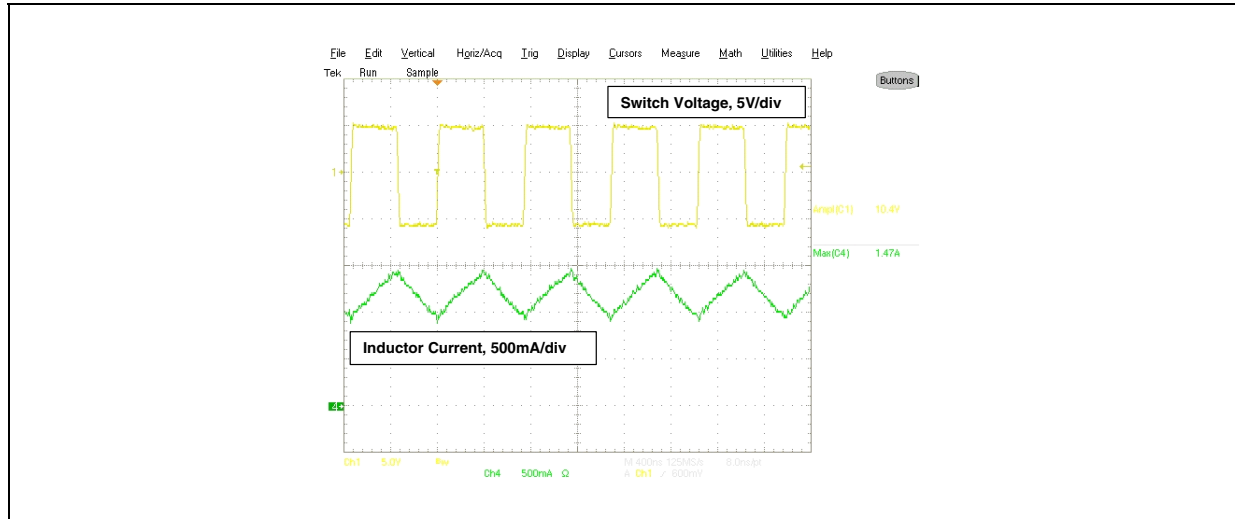



Figure 5 and Figure 6 show the typical waveforms of the switching regulator.

The following figures show how the application functions well in step-down mode  $12 V_{IN} \rightarrow -5 V_{OUT}$  (Figure 7) and in step-up mode  $3.3 V_{IN} \rightarrow -5 V_{OUT}$  (Figure 8).

**Figure 7. Step-down mode,  $12 V_{IN}$ ,  $-5.5 V_{OUT}$ ,  $500 mA I_{OUT}$**

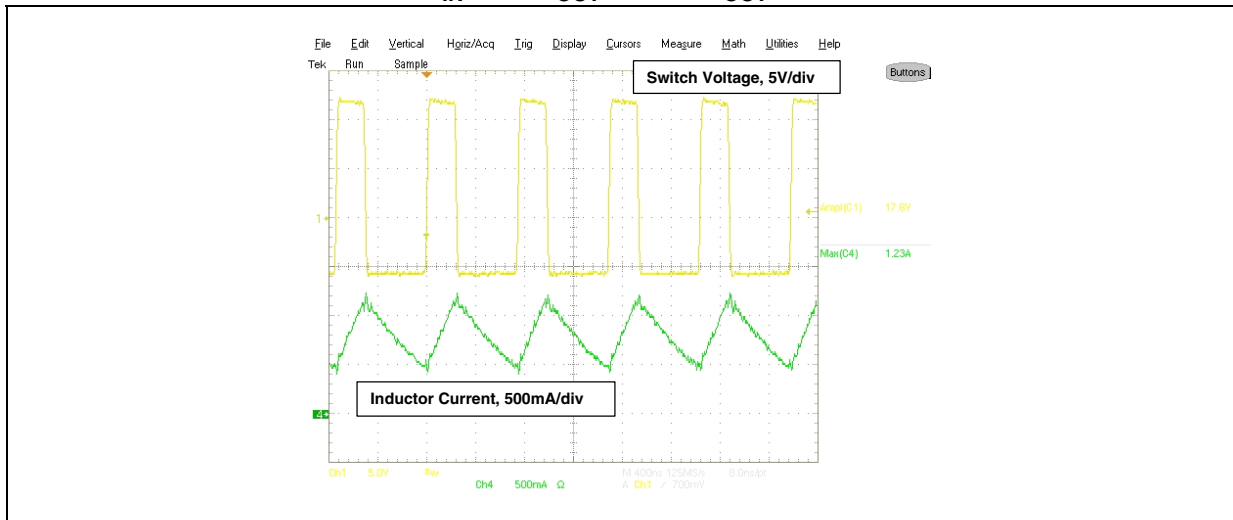

**Figure 8. Step-up mode,  $3.3 V_{IN}$ ,  $-5.5 V_{OUT}$ ,  $500 mA I_{OUT}$**

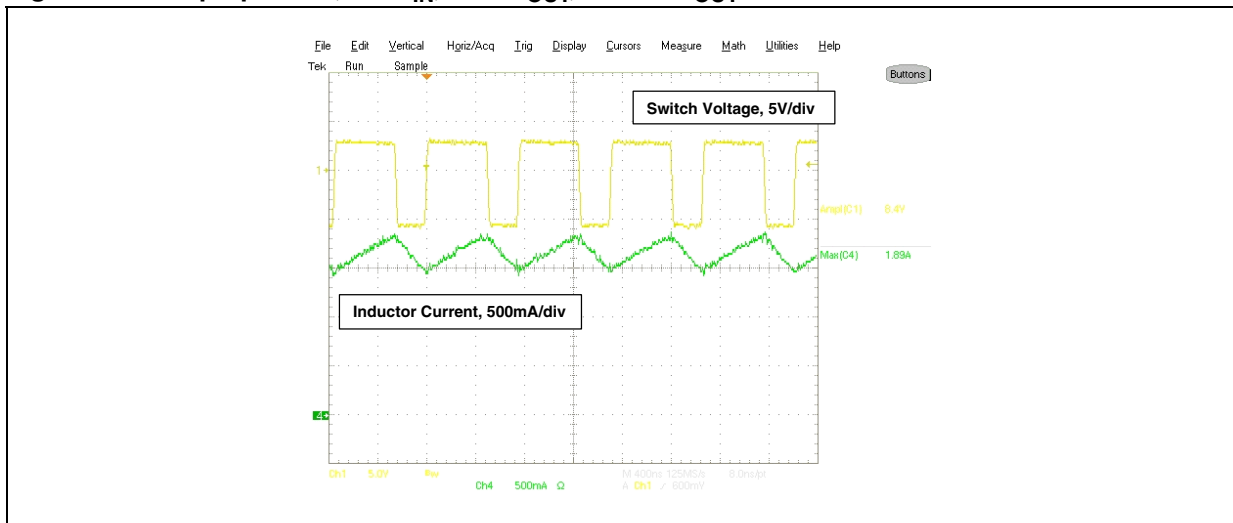

### 3 PCB layout guidelines

A recommended printed circuit board (PCB) layout for the ST1S03 inverting regulator is shown in *Figure 9*. It is very important to place the input capacitor as close as possible to the input pin of the regulator. In order to achieve the best performance, special care must be taken to ensure proper grounding. A good practice is to always use a separate ground plane, or at a minimum a single point ground structure.

High switching currents may cause voltage drops in the PCB metal trace, and long metal traces and component leads cause unwanted parasitic inductance as well, especially at switching frequencies of 1.5 MHz. This parasitic inductance is very often the main source of EMI problems and high voltage spikes at input and output lines. Therefore, place the inductor, freewheeling diode, and especially the input capacitor as close as possible to the device. Use big lines for the metal traces to these components. Wire the feedback circuit away from the inductor to avoid flux intersection. The use of a ground ring guard is recommended. Use shielded cores for better EMI performance. Capacitors with low ESR are recommended for inputs and outputs.

Figure 9. PCB layout - top side

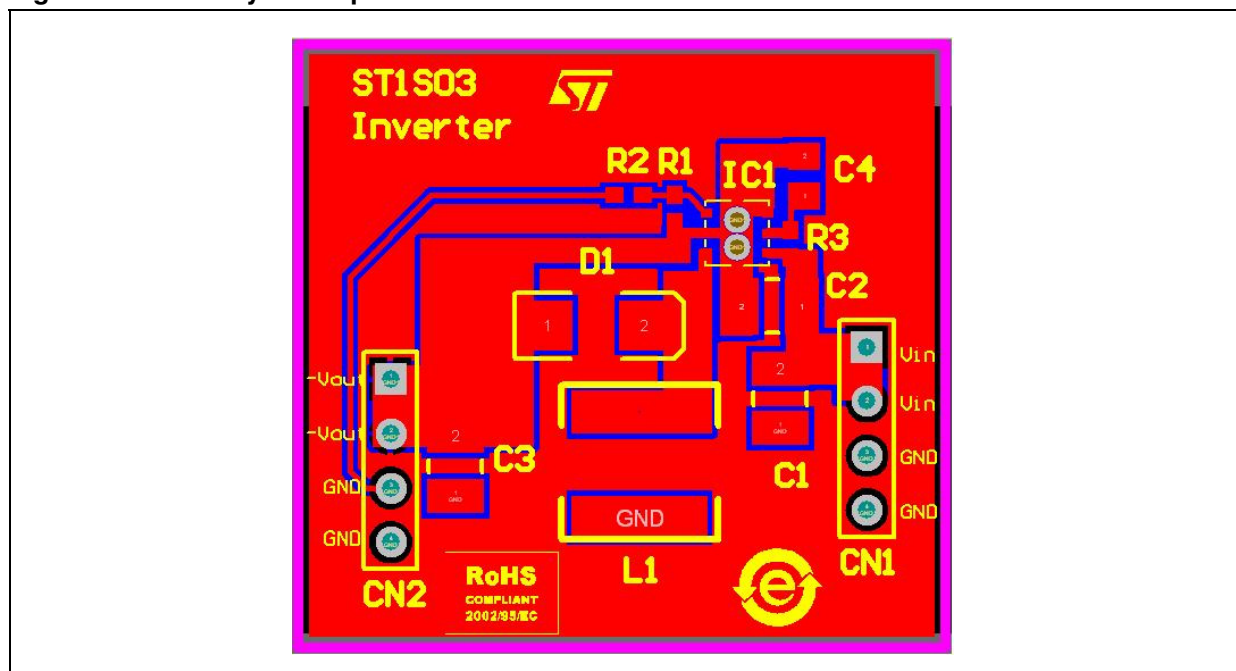




Figure 10. PCB layout - bottom side

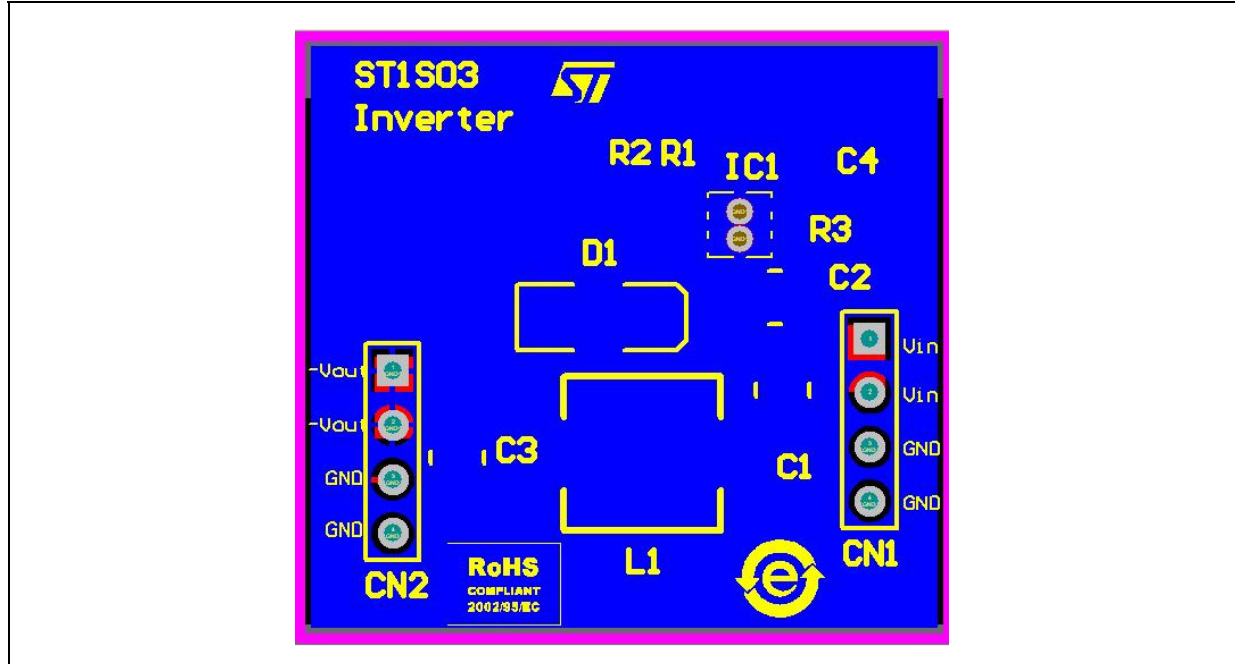



Table 1. Component list

Reference	Value	Description	Manufacturer
R1	10 k $\Omega$	Resistor	
R2	52 k $\Omega$	Resistor	
R3	100 $\Omega$	Resistor	
C1	4.7 $\mu$ F	Ceramic X5R or X7R	
C2	4.7 $\mu$ F	Ceramic X5R or X7R	
C3	22 $\mu$ F	Ceramic X5R or X7R	
C4	0.1 $\mu$ F	Ceramic X5R or X7R	
D1	2 A (0.3 V or less) Schottky diode	STPS2L25	STMicroelectronics
L1	4.7 $\mu$ H	DR734R7	Coiltronics
IC1	ST1S03	IC	STMicroelectronics
CN1	4 pins	Strip line male c.s.	
CN2	4 pins	Strip line male c.s.	


In polarity-inverting mode the ST1S03 is capable of supplying more output current, as shown in *Figure 11* and *Figure 12*.

With a 12 V input voltage (*Figure 12*), the ST1S03 should be able to provide up to 1.3 A of output current with good stability and performance. It is important not to exceed the maximum switching current limitation of 2.5 A that flows in the inductor. Choosing a good inductor, in terms of current capability and low series resistance, can help to improve efficiency.

**Figure 11. Polarity-inverting mode, 5 V<sub>IN</sub>, - 5.5 V<sub>OUT</sub>, 950 mA I<sub>OUT</sub>**

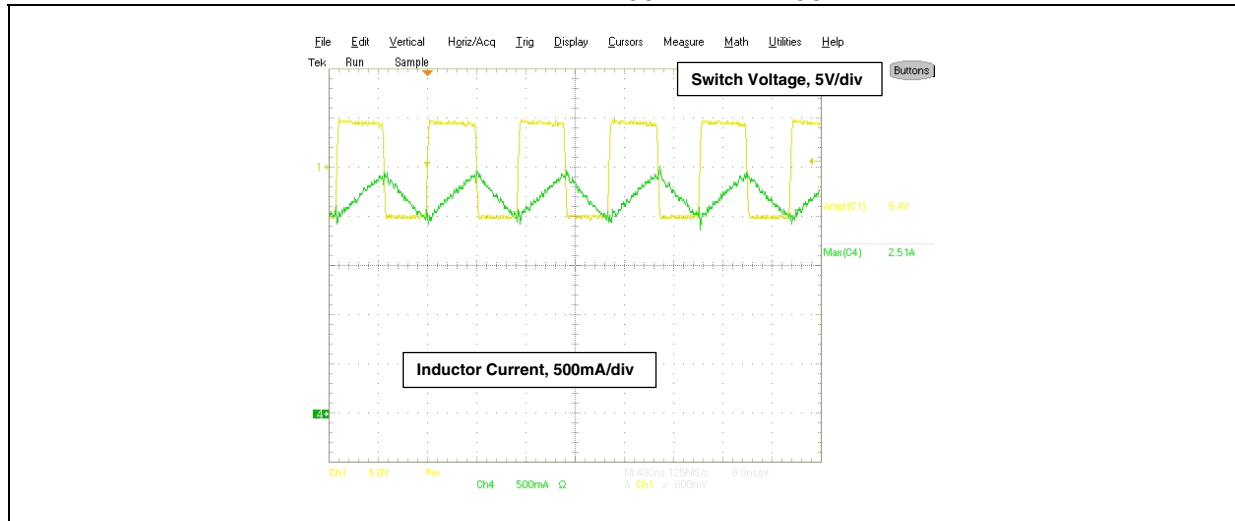

**Figure 12. Polarity-inverting mode, 12 V<sub>IN</sub>, - 5.5 V<sub>OUT</sub>, 1.3 A I<sub>OUT</sub>**

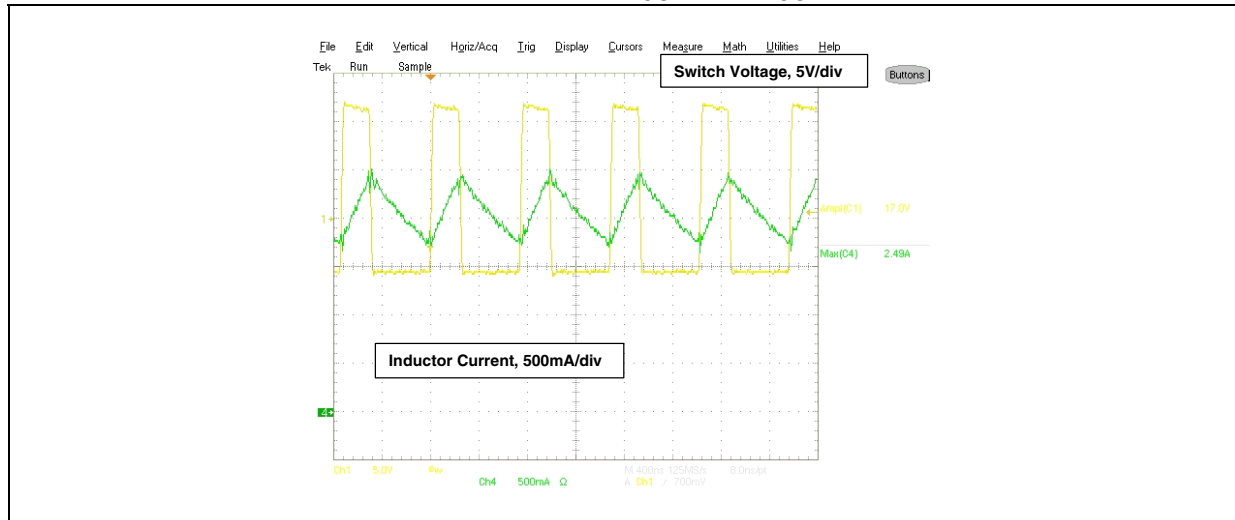

## 4 Revision history

**Table 2. Document revision history**

Date	Revision	Changes
26-Feb-2009	1	Initial release.

**Please Read Carefully:**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2009 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)