

How to design a 13.56 MHz customized antenna for ST25 NFC/RFID tags

Introduction

The ST25 NFC (near field communication) and RFID (radio frequency identification) tags extract their power from the reader field. The tag and reader antennas are inductances mutually coupled by the magnetic field, similarly to a voltage transformer (see [Figure 1](#)).

The efficient transfer of energy from the reader to the tag depends upon the loop antenna tuned to the carrier frequency (usually 13.56 MHz).

The purpose of this document is to give a step-by-step procedure to easily design and optimize a customized tag antenna for the products listed in [Table 1](#).

Table 1. Applicable products

Type	Applicable products
ST25 NFC/RFID tags	ST25TA, ST25TB, ST25TN, and ST25TV series NFC tags

Figure 1. RFID tag coupled to a reader magnetic field


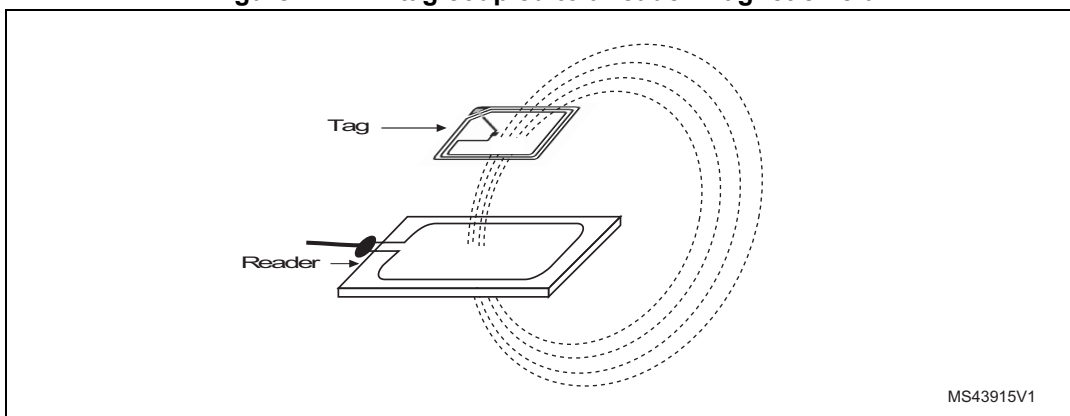


Figure 2. Tag antenna design example

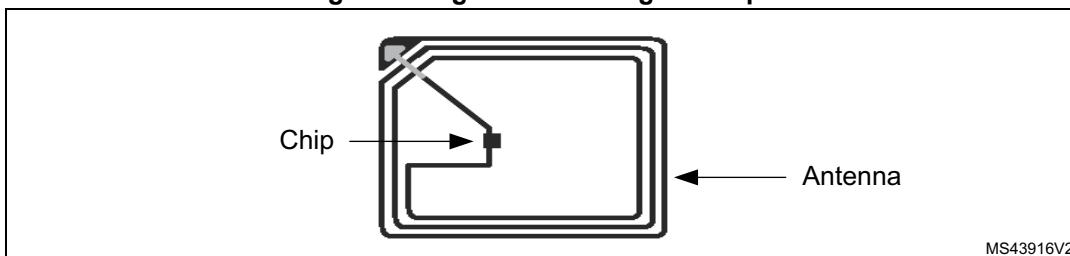

Contents

1	NFC/RFID tag and antenna equivalent circuit	5
2	Inlay equivalent circuit	6
3	Antenna design procedure	7
4	Designing the antenna coil	10
4.1	Inductance of a spiral antenna	10
4.2	Inductance of squared antennas	10
4.3	eDesignSuite antenna design tool	11
5	Antenna tuning contactless measurement method	13
5.1	Antenna measurement with a network analyzer	13
5.2	Antenna measurement with standard laboratory tools	14
6	Frequency versus application: recommendations	17
7	Revision history	18

List of tables

Table 1. Applicable products 1

Table 2. Antenna coil inductance for different C_{tun} values vs. tuning frequency 8

Table 3. K1 and K2 values according to layout 11

Table 4. Document revision history 18

List of figures


Figure 1.	RFID tag coupled to a reader magnetic field	1
Figure 2.	Tag antenna design example	1
Figure 3.	Equivalent circuit of a chip and its antenna	5
Figure 4.	Equivalent circuit of a chip, its antenna and connections	6
Figure 5.	Equivalent model of an NFC/RFID tag in presence of a magnetic field	7
Figure 6.	Antenna design procedure	9
Figure 7.	Spiral coil	10
Figure 8.	Square coils	11
Figure 9.	User interface screen of the planar rectangular coil inductance calculator.	11
Figure 10.	Measurement with a network analyzer	13
Figure 11.	Resonance traces of the prototype at different power levels	14
Figure 12.	ISO standard loop antenna.	14
Figure 13.	Measurement with standard laboratory equipment.	15
Figure 14.	Oscilloscope views	15
Figure 15.	Synthesis of resonance traces for different voltages	16

1 NFC/RFID tag and antenna equivalent circuit

Figure 3 shows the equivalent electrical circuit of an NFC/RFID tag chip and its antenna.

The NFC/RFID chip is symbolized by a resistor R_{chip} representing its current consumption, in parallel with a capacitor C_{tun} representing its internal tuning capacitance and internal parasitics.

Figure 3. Equivalent circuit of a chip and its antenna

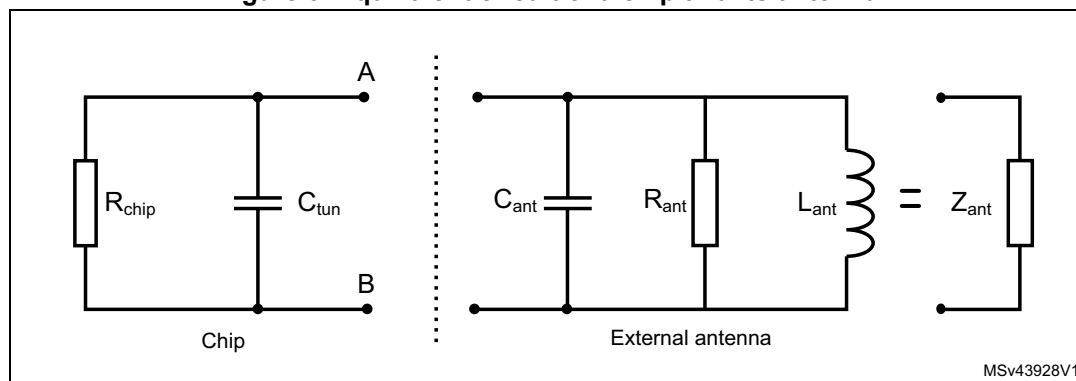

The equivalent model of the antenna involves three components in parallel:

- C_{ant} : overall stray capacitance of the loop antenna
- R_{ant} : resistive loss of the loop antenna
- L_{ant} : self-inductance of the loop antenna

The resulting antenna impedance is given by $Z_{\text{ant}} = C_{\text{ant}} // R_{\text{ant}} // L_{\text{ant}}$.

2 Inlay equivalent circuit


For products delivered in package, the schematic described in [Figure 3](#) is applicable.

For parts delivered in die and assembled on inlays, the equivalent schematic is the one shown in [Figure 4](#), which considers parasitics generated by the connections between chip and antenna:

- R_{1con} and R_{2con} : equivalent parasitic resistances
- C_{con} : equivalent parasitic capacitance

The parasitics due to assembly depend upon the process and the antenna material (copper, aluminum, conductive ink).

Figure 4. Equivalent circuit of a chip, its antenna and connections

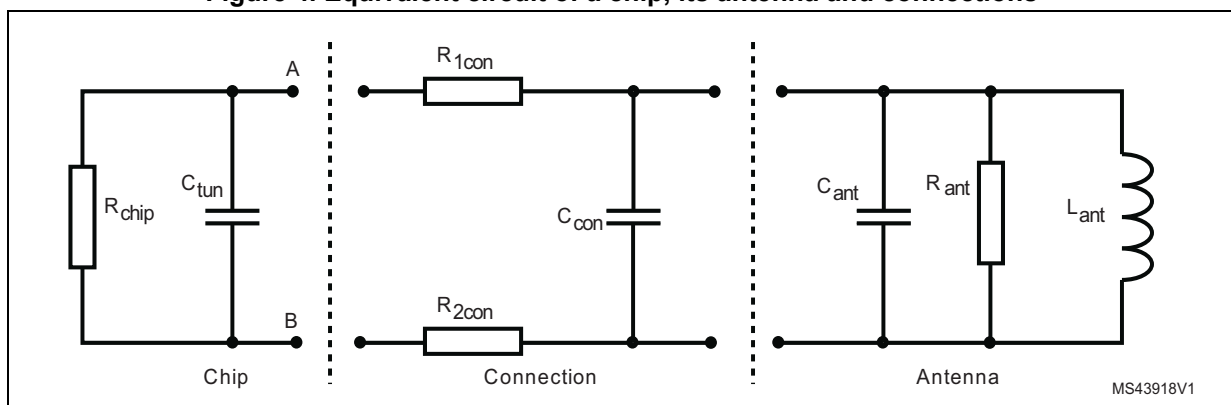

3 Antenna design procedure

The design starts with the simplified model shown in [Figure 3](#).

For a given antenna, R_{ant} , C_{ant} , and L_{ant} are constants but the resulting impedance Z_{ant} ($R_{ant} // C_{ant} // L_{ant}$) is frequency dependent, the imaginary part of the antenna impedance is positive and the antenna behavior is inductive.


[Figure 5](#) shows the equivalent model of an NFC/RFID tag in presence of a magnetic field. The loop antenna model includes:

- V_{oc} : open circuit voltage delivered by the antenna, depends upon the magnetic field strength, the antenna size, and the number of turns
- L_A : equivalent inductance defined by $L_A = X_A / \omega$, where X_A is the antenna reactance.

The NFC/RFID chip model includes:

- R_S : representing the equivalent power consumption
- C_S : serial equivalent tuning capacitance.

Figure 5. Equivalent model of an NFC/RFID tag in presence of a magnetic field

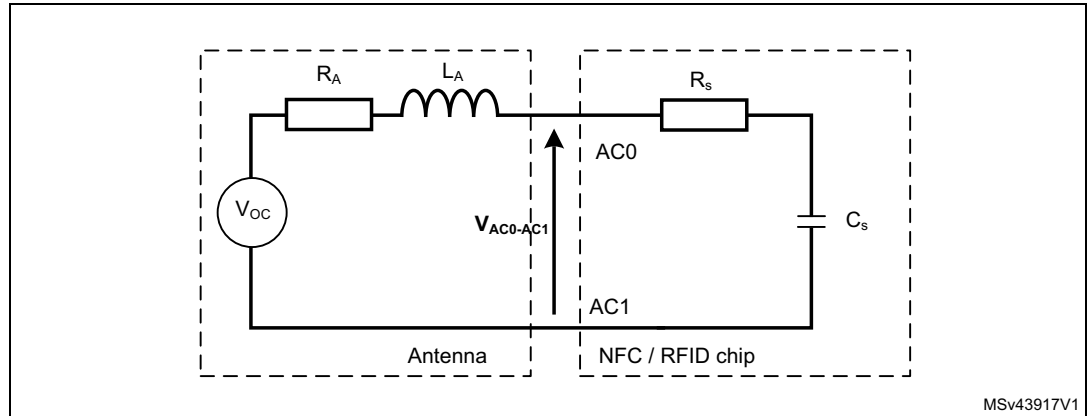

Basic equations

At low frequencies ($f < f_{self_res} / 10$), the stray capacitance C_{ant} is negligible, $L_A = L_{ant}$ and the antenna reactance is given by $X_A = j L_{ant} \omega$.

At 13.56 MHz, C_{ant} value gets in the range of some pF and $L_A > L_{ant}$.

The antenna impedance is $Z_{ant} = R_A + j L_A \omega$.

The NFC/RFID chip impedance is $Z_S = R_S + j / C_S \omega$.

For the equivalent RLC circuit, the total impedance is $Z_{tot} = Z_{ant} + Z_S$ and the resonant frequency is given by the condition $L_A C_S \omega^2 = 1$.

Optimum antenna tuning

At resonant frequency the total impedance reaches its minimum value $Z_{tot} = R_A + R_S$. The current in the antenna and the voltage delivered to the NFC/RFID chip are maximized, as the energy transferred to the device.

If the resonant frequency is close to the reader carrier frequency (13.56 MHz), the power transfer between reader and tag as well as the communication distance are maximized.

[Table 2](#) gives examples of some NFC/RFID devices and antenna inductance calculation.


Table 2. Antenna coil inductance for different C_{tun} values vs. tuning frequency

Product	C_{tun} (pF)	Tuning frequency (MHz)	Antenna coil inductance (μH)
ST25TA series	50.0	14.00	2.58
	27.5		4.70
ST25TB series	68.0	13.56	2.00
		14.40	1.80
ST25TN series	50.0	14.00	2.58
ST25TV series	23.0	13.56	5.95
	99.7		1.38

[Figure 6](#) describes an easy and reliable method to design and fine-tune an antenna in few steps, which can be summarized as:

- manufacture three antennas centered on the theoretical equivalent inductance L_A
- characterize and validate the performance of these antennas
- launch a second run with fine-tuned L_A values to get the optimized antenna.

Figure 6. Antenna design procedure

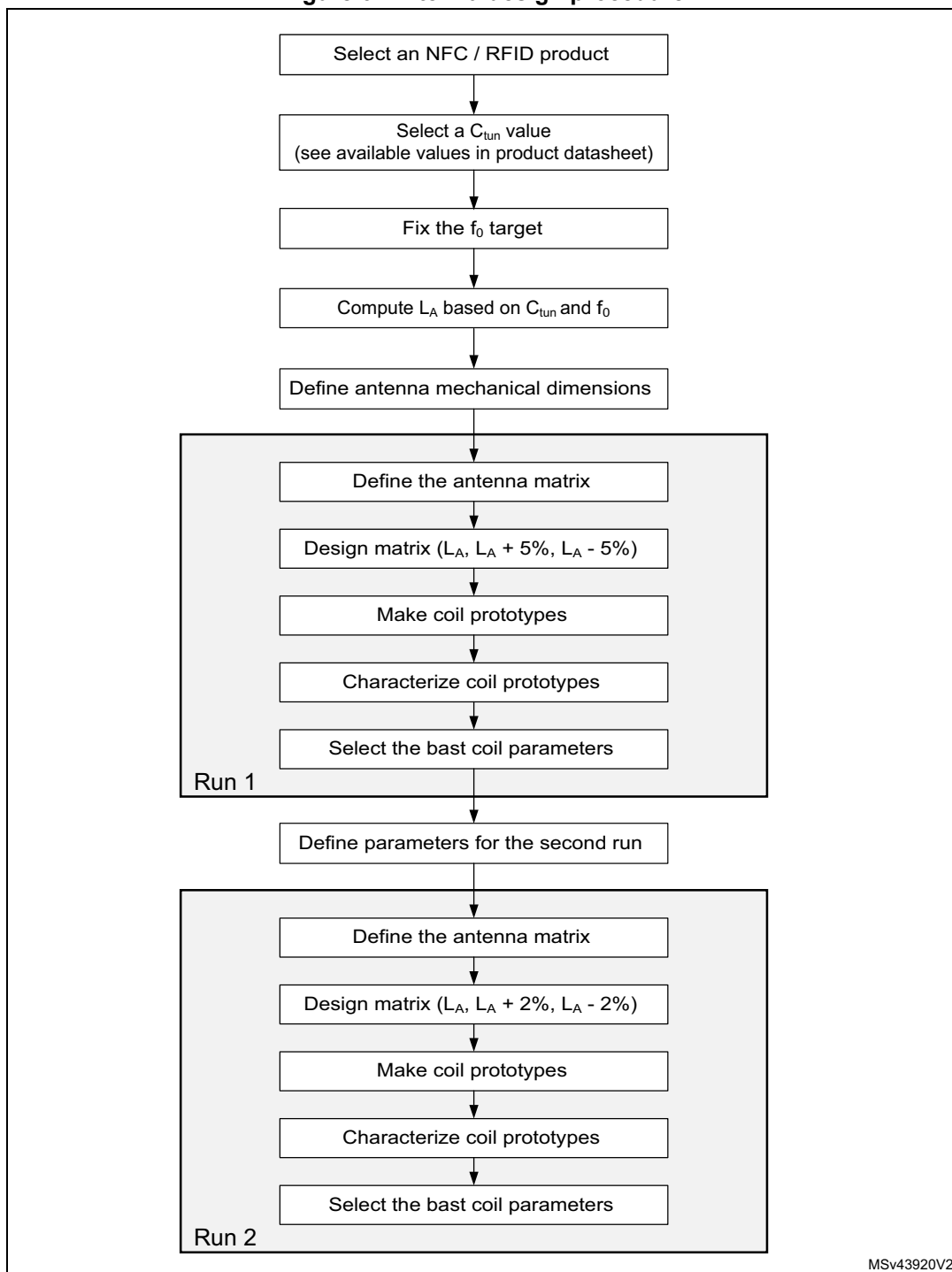

4 Designing the antenna coil

A 13.56 MHz antenna can be designed with different shapes, depending on the application requirements. As explained previously, the main parameter is the equivalent inductance L_A of the antenna around 13.56 MHz. The stray capacitance is generally in the range of a few pF for typical NFC/RFID products.

For the most common antenna shapes [Section 4.1](#) and [Section 4.2](#) give useful formulas to calculate the self-inductance L_{ant} .


[Section 4.3](#) presents a calculation tool called antenna design to calculate the equivalent inductance of rectangular antennas, taking into account an approximation of the stray capacitance.

4.1 Inductance of a spiral antenna

$$L_{ant} = 31.33 \times \mu_0 \times N^2 \times \frac{a^2}{8a + 11c}, \text{ where (see Figure 7):}$$

- $a = (r_{in} + r_{out}) / 2$ (the average radius, in meters)
- $c = r_{out} - r_{in}$, in meters
- $\mu_0 = 4 \pi \cdot 10^{-7}$ H/m
- L is measured in Henry

Figure 7. Spiral coil

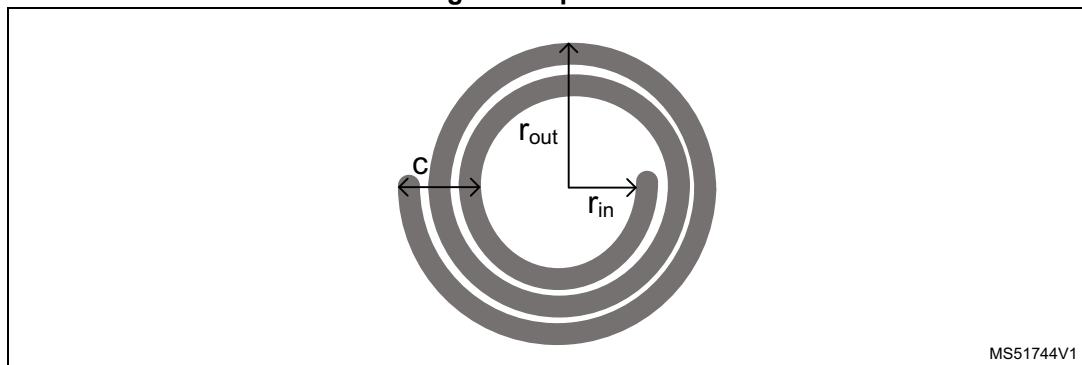

MS51744V1

4.2 Inductance of squared antennas

$$L_{ant} = K1 \times \mu_0 \times N^2 \times \frac{d}{1 + K2 \cdot p}, \text{ where (see Figure 8):}$$

- $d = (d_{out} + d_{in}) / 2$ (the average diameter, in meters)
- $p = (d_{out} - d_{in}) / (d_{out} + d_{in})$ in meters
- $K1$ and $K2$ depend upon the layout (refer to [Table 3](#) for values)

Figure 8. Square coils

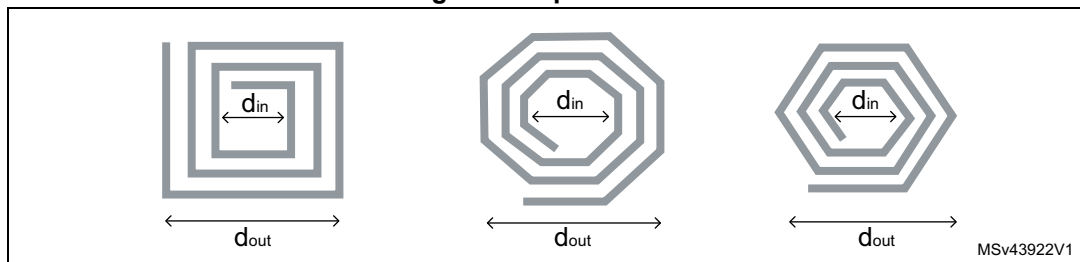


Table 3. K1 and K2 values according to layout


Layout	K1	K2
Square (left side of Figure 8)	2.34	2.75
Octagonal (center of Figure 8)	2.25	3.55
Hexagonal (right side of Figure 8)	2.33	3.82

4.3 eDesignSuite antenna design tool

Refer to the antenna design tool, part of the eDesignSuite tool available from www.st.com to compute the main parameters of rectangular antennas at 13.56 MHz.

This tool uses parameters related to the PCB material, the antenna dimensions, and estimates its equivalent inductance. [Figure 9](#) shows an example of antenna computation.

Figure 9. User interface screen of the planar rectangular coil inductance calculator

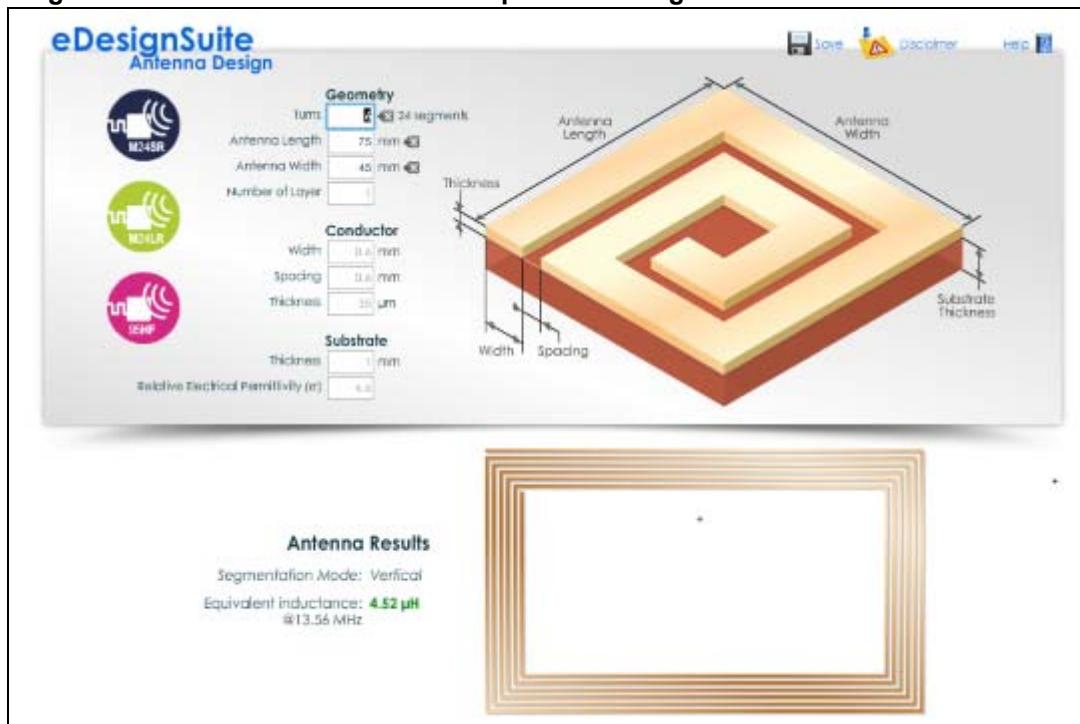

The user provides the following parameters:

Antenna geometry parameters

- Turns: number of complete turns (four segments per turn)
- Antenna length in mm
- Antenna width in mm
- Number of layers (1 by default)

Conductor parameters (copper is used by default)

- Width of tracks in mm
- Spacing between turns in mm
- Thickness of the conductor in μm

Substrate parameters

- Thickness in mm
- Dielectric permittivity

Once the antenna equivalent inductance is calculated, a prototype is produced. The antenna design is validated by measuring the antenna impedance (using an impedance analyzer, a network analyzer, or an LCR meter) or by measuring the tuning frequency of the tag by a contactless method (see [Section 5](#)).

5 Antenna tuning contactless measurement method

The following parameters impact the tuning frequency of the NFC/RFID tag:

- the precision of the antenna equivalent inductance computation
- the length of the connection between the chip and its antenna in the application
- the antenna environment (metal surface, ferromagnetic material).

It is important to check the actual resonant frequency in the final application, using one of the methods described in [Section 5.1](#) and [Section 5.2](#).

5.1 Antenna measurement with a network analyzer

The tuning frequency of the prototypes can be measured with a network analyzer with a loop probe, which generates the RF electromagnetic field to the output of the network analyzer, which is set in reflection mode (S11 measurement).

The loop probe either comes from the market or is a self-made single turn loop (using a coaxial connector and a copper wire twisted at the end). Building the loop probe like this makes it possible to adjust the size of the loop to the size of the tag antenna for a better coupling during the measurement.

Figure 10. Measurement with a network analyzer




This equipment setup directly displays the resonant frequency of the system.

Instructions

Here is an example of instrument setup:

- start frequency: 10 MHz
- stop frequency: 20 MHz
- S11 or reflection mode
- display format: log magnitude
- output power: -10 dBm

The frequency sweep can be adjusted as needed.

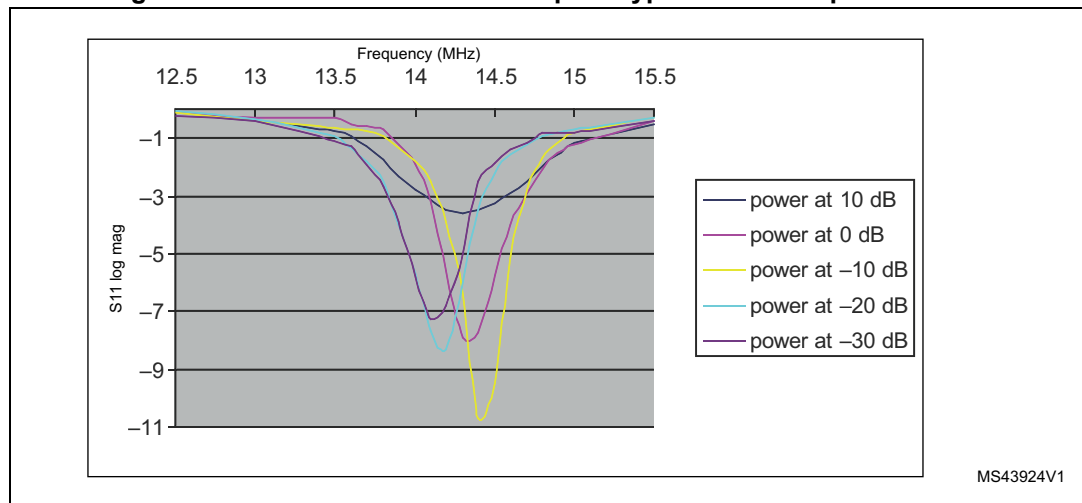Figure 11. Resonance traces of the prototype at different power levels

5.2 Antenna measurement with standard laboratory tools

Another method of measuring the tuning frequency is to use standard laboratory equipment:

- a signal generator
- an oscilloscope
- two loop antennas

Experimental setup

- Connect an ISO 10373-7 standard loop antenna (see [Figure 12](#)) to the signal generator
- Connect the second ISO 10373-7 standard loop antenna to the oscilloscope (see [Figure 13](#)) using a standard oscilloscope probe (1 M Ω or 10 M Ω input impedance) or by means of a 50 Ω BNC cable (oscilloscope input set to 50 Ω in this case).

Note: The ISO 10373-7 standard antennas can be replaced by self-made antennas.

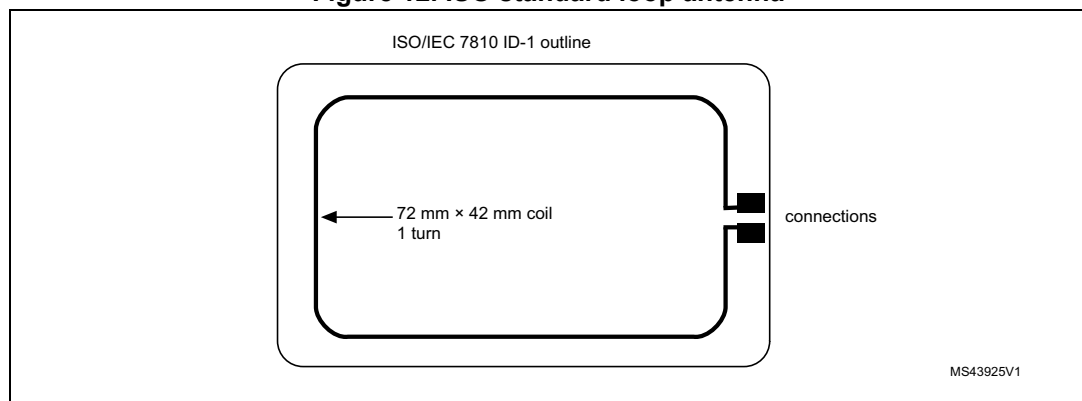
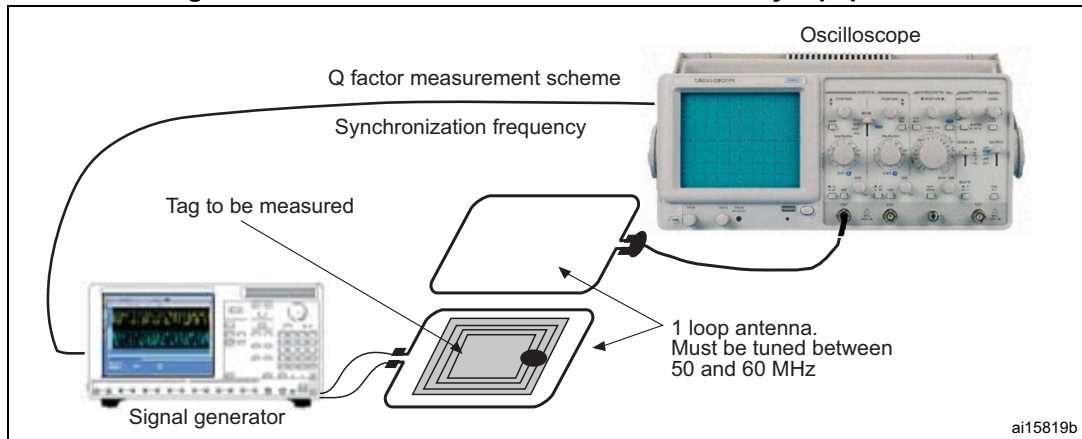
Figure 12. ISO standard loop antenna

Figure 13. Measurement with standard laboratory equipment

Experiments

1. Place the tag in front of the loop antenna connected to the signal generator. In the presence of a magnetic field, a current flows into the tag antenna. This current generates a magnetic field, captured by the second loop antenna connected to the oscilloscope. At the tag resonant frequency, the current flowing into the tag antenna is maximum, as the magnetic field generated by the tag antenna and the voltage amplitude displayed by the oscilloscope.
2. Place the prototype coil in the transmission loop probe (with the reception loop probe at about 0.5 cm from the prototype coil).
3. Generate a signal (13.56 MHz sine wave) at a voltage of 0.25 V.
4. Vary the transmission frequency to obtain the highest possible signal level on the reception side.
5. Use the oscilloscope to determine the signal level and the resonant frequency.

Figure 14 shows two signal waveforms at different transmission frequencies.

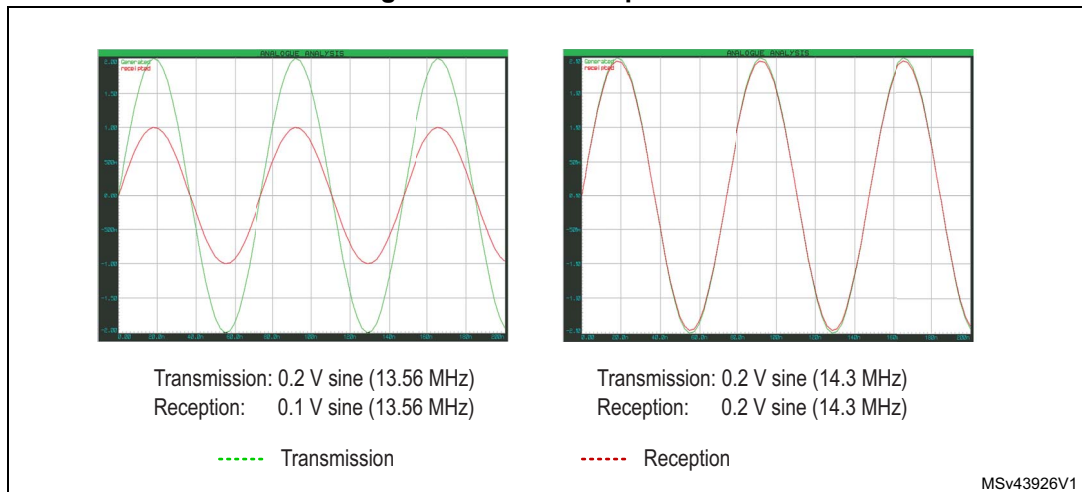
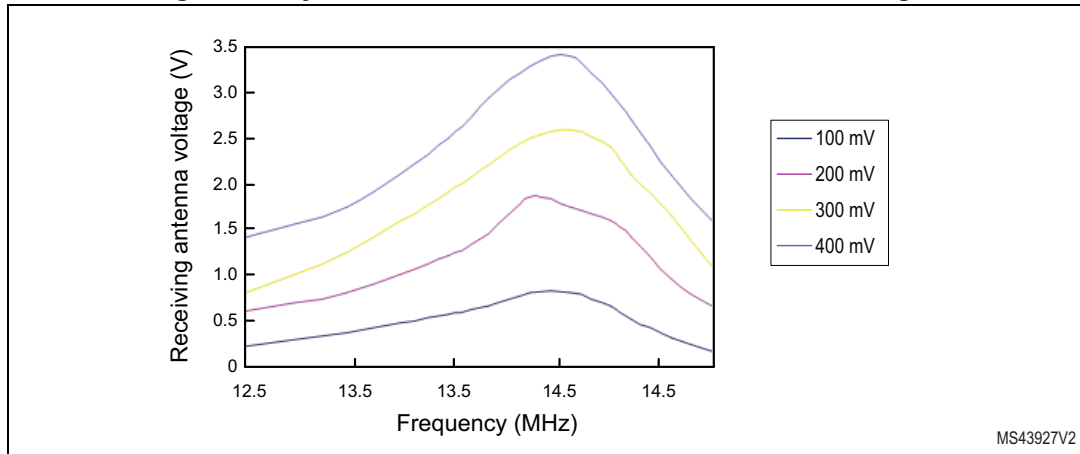
Figure 14. Oscilloscope views

Figure 15 summarizes the measurements obtained by plotting characteristic points for different frequencies. Each resonance trace represents a synthesis for a defined voltage transmission.

Figure 15. Synthesis of resonance traces for different voltages



Note: Without any tag, the scope trace must be as flat as possible. This is the reason why the antenna connected to the generator cannot be tuned at 13.56 MHz.

6 Frequency versus application: recommendations

When designing a tag antenna, it is important to know the frequency of the application:

- Long-range products (ST25TV series) are tuned between 13.6 and 13.7 MHz (for distance optimization).
- Standard short-range products (ST25TA and ST25TN series) are tuned between 13.6 and 14.0 MHz (for distance optimization).
- Short-range products (ST25TB series), used as transport tickets, are tuned between 14.0 and 15.0 MHz (for stack optimization).

The frequency shift due to the final label material and environment must be considered.

In the example (a sticker tag with a paper label), the paper and adhesive decrease the inlay antenna frequency by about 300 kHz. It is therefore necessary to tune the initial inlay at about 13.9 MHz, instead of the specified 13.6 MHz.

7 Revision history

Table 4. Document revision history

Date	Revision	Changes
15-Jan-2008	1	Initial release.
15-Dec-2016	2	Updated: <ul style="list-style-type: none"> – Introduction – Section 1: NFC/RFID tag and antenna equivalent circuit – Section 2: Inlay equivalent circuit – Section 3: Antenna design procedure – Section 4: Designing the antenna coil – Section 5: Antenna tuning contactless measurement method – Section 6: Frequency versus application: recommendations – Figure 3: Equivalent circuit of a chip and its antenna – Figure 4: Equivalent circuit of a chip, its antenna and connections – Figure 5: Equivalent model of an NFC/RFID tag in presence of a magnetic field – Figure 6: Antenna design procedure – Figure 9: User interface screen of the planar rectangular coil inductance calculator – Figure 13: Measurement with standard laboratory equipment – Table 1: Applicable products – Table 2: Antenna coil inductance for different C_{tun} values vs. tuning frequency
04-Feb-2019	3	Updated Section 4.1: Inductance of a spiral antenna and Section 4.2: Inductance of squared antennas . Updated Figure 6: Antenna design procedure and Figure 7: Spiral coil . Updated Table 2: Antenna coil inductance for different C_{tun} values vs. tuning frequency . Minor text edits across the whole document.
03-Dec-2020	4	Document scope narrowed to ST25TA, ST25TB and ST25TV series. Updated Table 1: Applicable products and Table 2: Antenna coil inductance for different C_{tun} values vs. tuning frequency . Updated Section 6: Frequency versus application: recommendations . Minor text edits across the whole document.
09-Aug-2021	5	Added ST25TN series. Updated Table 1: Applicable products and Table 2: Antenna coil inductance for different C_{tun} values vs. tuning frequency . Updated Section 6: Frequency versus application: recommendations .
23-Sep-2025	6	Removed former Section 4.1: Inductance of a circular antenna . Updated Section 4.2: Inductance of squared antennas . Updated Figure 2: Tag antenna design example and Figure 15: Synthesis of resonance traces for different voltages . Minor text edits across the whole document.

IMPORTANT NOTICE – READ CAREFULLY

STMicroelectronics NV and its subsidiaries (“ST”) reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST’s terms and conditions of sale in place at the time of order acknowledgment.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of purchasers’ products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, refer to www.st.com/trademarks. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2025 STMicroelectronics – All rights reserved