



Oscillator selection for ST62

Introduction

The purpose of this note is to give indications on how to choose a resonator or a quartz crystal in order to achieve reliable oscillation with the ST62 Microcontroller. This document provides first the major resonator parameters useful for a design. It then proposes measurement methods to ensure a safe oscillation.

Contents

1	Oscillation frequency	3
2	Oscillation conditions	4
2.1	Barkhausen criteria	4
2.2	Start-up	4
2.3	Measurement of the loop gain (open loop)	5
2.4	Frequency stability	5
2.5	Start-up time	6
3	Conclusion	7
Appendix A	Test of a CSA Murata crystal resonator with an ST6210xx	8
A.1	Choice of the network capacitances	8
A.2	Pseudo closed loop measurement	8
A.3	Start-up time	8
A.4	Conclusion.	8
Appendix B	Calculation of the resonant frequency of ceramic resonator	9
B.1	Equivalent circuit at the resonance frequency.	9
B.2	Transformation for simple calculation	9
B.3	Resonant frequency	9
B.4	Note.	10
4	Revision history	11

1 Oscillation frequency

The resonator can be modelised by a serial/parallel oscillator circuit as described in [Figure 1](#).

The additional capacitances C_{ext} are usually connected to the oscillator pins in order to define a stable oscillating frequency. The value of these capacitances is usually given by the manufacturer of the resonator.

The oscillation frequency is the resonant frequency of the equivalent circuit given in [Figure 2](#). The resonator is inductive in the oscillation frequency range.

Figure 1. Resonator model


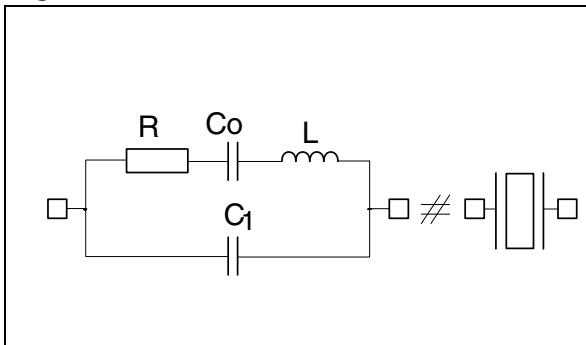


Figure 2. Equivalent circuit

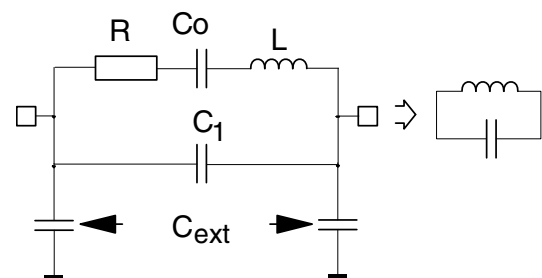

2 Oscillation conditions


The proposed method is based on the Barkhausen criteria. This leads to a safe result providing that the oscillator fulfills these criteria. Three points have to be analysed: oscillator start-up, frequency stability and the start-up time.

2.1 Barkhausen criteria

An oscillator can be modeled as defined in [Figure 3](#). B is the resonator gain and G the amplifier/inverter gain. The value of $B \times G$ defines the oscillator behaviour:

- $B \times G \gg 1$: square waveform, start-up OK
- $B \times G > 1$: waveform with harmonic distortion, start-up OK
- $B \times G = 1$: sine waveform, start-up critical
- $B \times G < 1$: no oscillation

Figure 3. Oscillator model

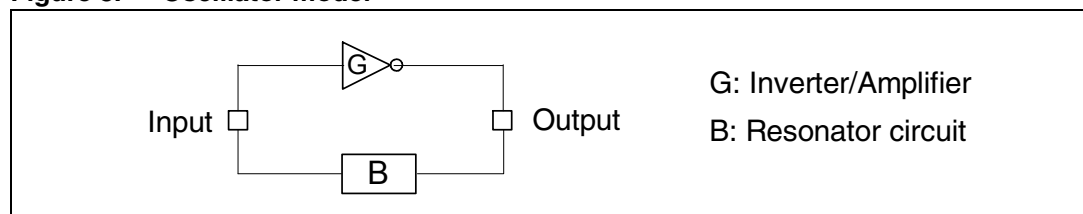

2.2 Start-up

The oscillator can start if the gain $B \times G$ is above 1. The amplifier gain must compensate for the resonator circuit attenuation and provide a sufficient gain margin (>3 dB).

In addition, the resonator circuit B must introduce a 180° phase delay if the G amplifier is an inverter and no rotation if it is a non inverting amplifier.

With classical circuits such as a Pierce type oscillator ([Figure 4](#)), the 180° phase rotation is due to capacitances (C_{out} and C_{in}).

Figure 4. Pierce type oscillator


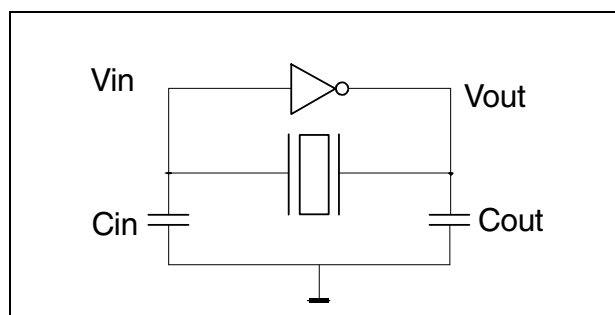


Figure 5. Equivalent schematic at the resonant frequency

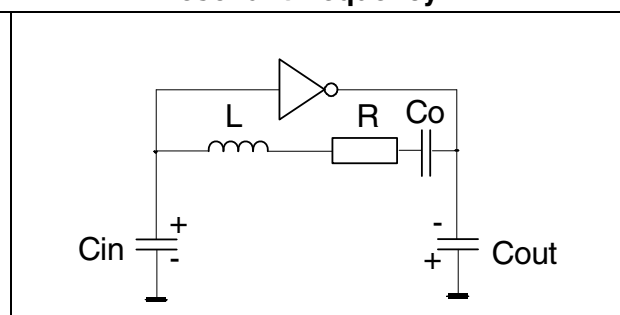

At the resonance frequency (serial mode), the circuit can be modeled as described in [Figure 5](#). The resonator voltage is balanced between the two capacitances. So the phase of the voltages V_{in} and V_{out} is delayed by 180° . Depending on the capacitance values, V_{in} is either higher ($C_{out} > C_{in}$), smaller ($C_{out} < C_{in}$) or equal to V_{out} .

The trade offs in the choice of C_{in} and C_{out} are:

- $C_{out} = C_{in} : V_{in} = V_{out}$
This is the typical case and is to be used as often as possible.
- $C_{out} > C_{in} : V_{in} > V_{out}$
The loop gain is increased but there is a risk that the oscillation occurs at a harmonic of the resonator frequency.
- $C_{out} < C_{in} : V_{in} < V_{out}$
The output voltage is increased. The risk of oscillation at a harmonic of the resonator frequency is low. V_{in} must be high enough to satisfy the condition $B \times G > 1$.


2.3 Measurement of the loop gain (open loop)

The measurement is based on the schematic shown in [Figure 6](#). The method is the following:

1. Open the loop as described in [Figure 6](#).
2. Place an oscillator probe on points 1 and 2. Note that the real C value for the calculation is $C_{probe} + C_{in}$.
3. Inject a voltage S with a signal generator. This signal must be adjusted in frequency to maximize the voltage V_2 .
4. Adjust S to a value small enough to avoid saturation of the amplifier (around 200 mV on V_1).
5. Calculate the ratio V_1/V_2 . This value has to be between +3 and +10 dB (1.5 to 3).

If the ratio is above +3 dB, the oscillator start is safe. If it is below, C_{in} should be decreased.

Figure 6. Gain loop measurement schematic

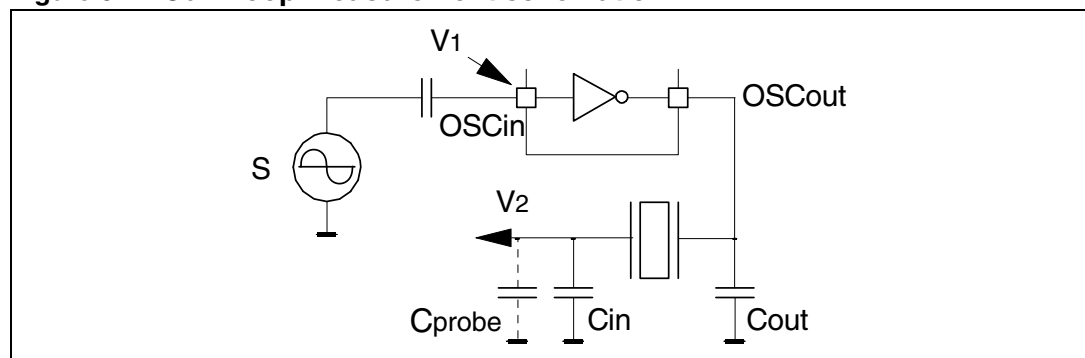


2.4 Frequency stability

The stability is first defined by the resonator characteristics. Nevertheless, if the open loop gain exceeds +10 dB, the oscillation could occur on a harmonic of the resonator frequency. In such cases, the value of C_{in} should be increased to reduce the loop gain or a filter rejecting this harmonic must be added.

2.5 Start-up time

The start-up time depends on the amplifier polarisation time and on the circuit transients. The polarisation of the amplifier can be accelerated by dividing the C_{in} capacitance in two as described in [Figure 7](#).

Figure 7. Amplifier polarisation acceleration

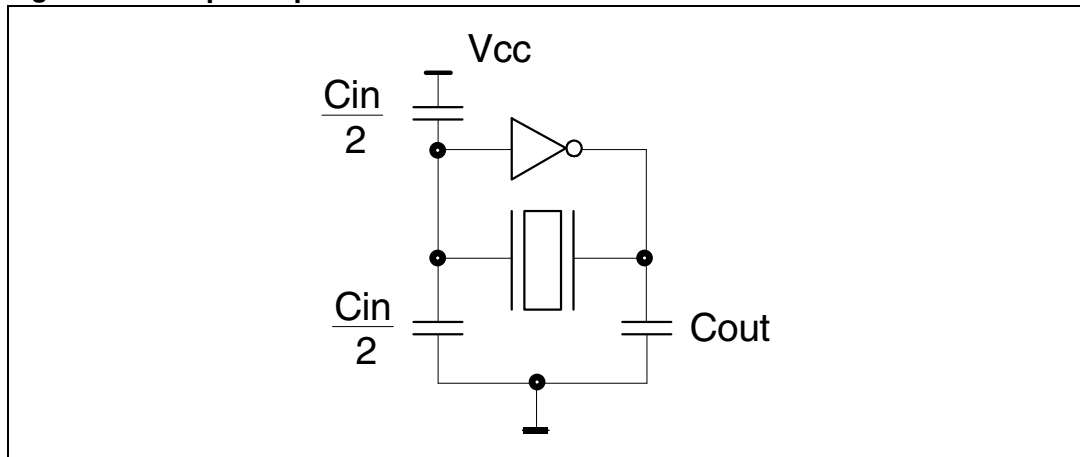

The start-up time is also longer when C_{in} and C_{out} are increased. As a result, for very low start-up time (i.e. low frequency quartz crystal), these capacitances values should be as small as possible. Generally, the higher the crystal Q factor and lower the crystal frequency, the longer the start-up time.

3 Conclusion

This note describes a method to choose oscillator network capacitances adapted to standard resonators and quartz crystals (i.e. $r_s < 60$ ohms and gain > 500). Since several network values can be chosen, the capacitances values should be minimized in order not to affect the resonance frequency and reduce the start-up time.

Appendix A Test of a CSA Murata crystal resonator with an ST6210xx

A.1 Choice of the network capacitances

Resonator equivalent values:

$$L = 385 \mu\text{H}$$

$$C_0 = 4.4 \text{ pF}$$

$$C_1 = 36.3 \text{ pF}$$

$$r_s = 8.7 \text{ ohm}$$

$$Q = 1134$$

The oscillation mode is the fundamental mode.

The recommended load capacitances for 4 MHz oscillation frequency are 2x30 pF.

The corresponding oscillation frequency as calculated from the formula given in [Appendix B](#) is 4.03 MHz.

A.2 Pseudo closed loop measurement

In the worst case (T_{ambient} max, V_{supply} min) the gain $V_{\text{out}}/V_{\text{in}}$ is 4.8. So the safety margin is +13.6 dB.

A.3 Start-up time

The start-up time is measured in closed loop. In the worst conditions (T_{ambient} max, V_{supply} min), it is less than 1 ms.


A.4 Conclusion

The selected ceramic resonator matches with the ST6210 oscillator.

Appendix B Calculation of the resonant frequency of ceramic resonator


B.1 Equivalent circuit at the resonance frequency

Figure 8. Equivalent circuit

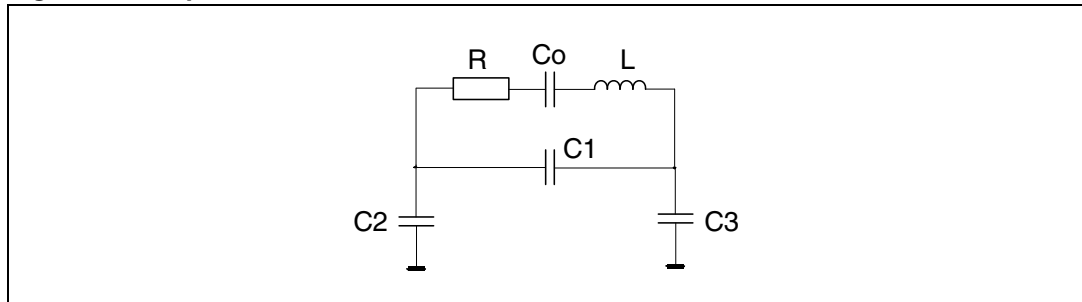

B.2 Transformation for simple calculation

Figure 9. Transformed circuit

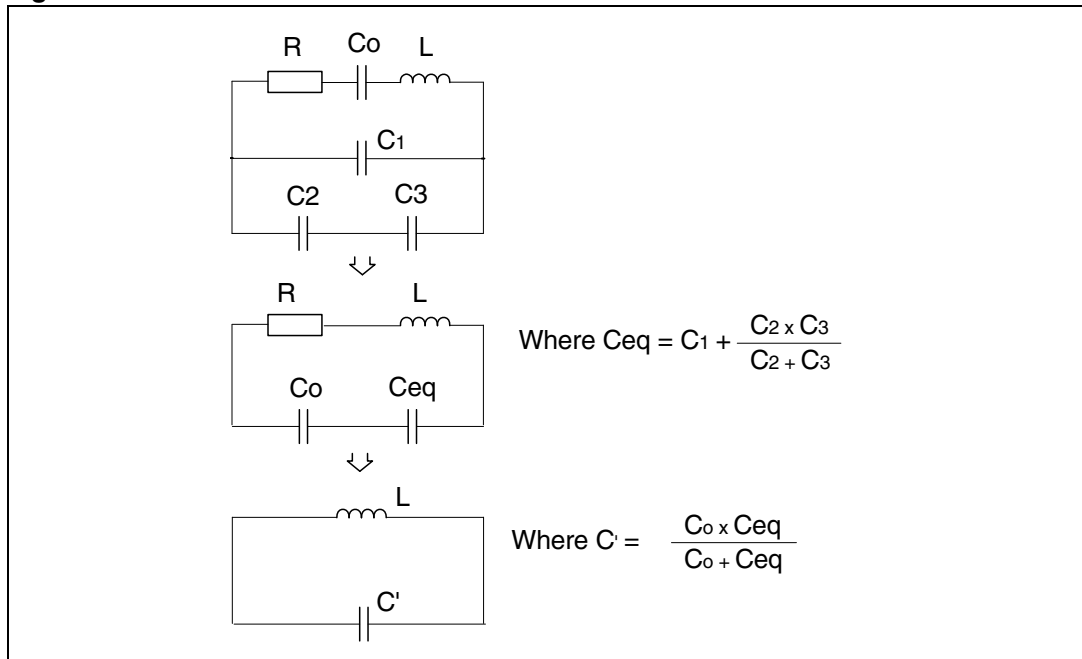

B.3 Resonant frequency

$$f = \frac{1}{2\pi\sqrt{L \times C'}}$$

B.4 Note

When using a ceramic resonator, the oscillation frequency is usually between the parallel and the series resonances. So both C_1 and C_0 have to be included in the calculation.

The resonance frequency of a crystal resonator is very near to the series frequency. So only C_0 has to be used for the frequency calculation.

4 Revision history

Table 1. Document revision history

Date	Revision	Changes
February-1994	1	Initial release.
03-Oct-2008	2	Format changed. Title of Appendix A modified (ST6210xx instead of ST6210). Logo and disclaimer updated.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2008 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com