



AN1495

Application note

Microstepping stepper motor drive using peak detecting current control

By Thomas Hopkins

Introduction

Stepper motors are very well suited for positioning applications since they can achieve very good positional accuracy without complicated feedback loops associated with servo systems. However their resolution, when driven in the conventional full or half step modes of operation, is limited by the configuration of the motor. Many designers today are seeking alternatives to increase the resolution of the stepper motor drives. This application note will discuss implementation of microstepping drives using peak detecting current control where the sense resistor is connected between the bottom of the bridge and ground. Examples show the implementation of microstepping drives with several currently available chips and chip sets.

Contents

1	General description	4
2	Microstepping with the L6208	7
3	Speed limitations	9
4	Slow versus fast decay mode	11
5	Minimum current issues	14
6	L6506 and L6203/L298	17
7	Conclusion	19
8	References	19
	Appendix A Schematic	20
	Appendix B Code	21
9	Revision history	24

Table of figures

Figure 1.	Model of stepper motor	4
Figure 2.	Full step sequence	4
Figure 3.	Example alignment of microstepping	5
Figure 4.	Block diagram of microstepping motor drive.	6
Figure 5.	Circuit connections for the L6208	7
Figure 6.	Microstepping waveforms: typical operation.	8
Figure 7.	Microstepping waveforms: current limited by motor inductance.	9
Figure 8.	Waveforms when motor has stalled	10
Figure 9.	PWM current control decay modes.	12
Figure 10.	Microstepping motor current with slow decay.	13
Figure 11.	Microstepping motor current with fast decay	13
Figure 12.	Waveforms at minimum current operation	14
Figure 13.	Transfer function showing nonlinearity	15
Figure 14.	Microstepping waveforms with improved performance at zero current.	16
Figure 15.	Microstepping using L6506 and L6203 (slow decay)	17
Figure 16.	Microstepping using L6506 and L6203 (fast decay)	18
Figure 17.	Scheme of the EVAL6208N	20

1 General description

Microstepping a stepper motor may be used to achieve one or both of two objectives; 1) increase the position resolution or 2) achieve smoother operation of the motor. In either case the basic theory of operation is the same.

The simplified model of a stepper motor is a permanent magnet rotor and two coils on the stator separated by 90°, as shown in [Figure 1](#). In classical full step operation an equal current is delivered to each of the coils and the rotor will align itself with the resulting magnetic vector along one of the 45° axis. To step the motor, the current in one of the two coils is reversed and the rotor will rotate 90°. The complete full step sequence is shown in [Figure 2](#). Half step drive, where the current in the coil is turned off for one step period before being turned on in the opposite direction, has been used to double the step resolution of a motor. In either full and half step drive, the motor can be positioned only at one of the 4 (8 for half step) defined positions.[\[4\]](#)[\[5\]](#) Therefore, the number of steps per electrical revolution and the number of poles on the motor determine the resolution of the motor. Typical motors are designed for 1.8° steps (200 steps per revolution) or 7.5° steps (48 steps per revolution). The resolution may be doubled to 0.9 or 3.75° by driving the motor in half step. Further increasing the resolution requires positioning the rotor at positions between the full step and half step positions.

Figure 1. Model of stepper motor


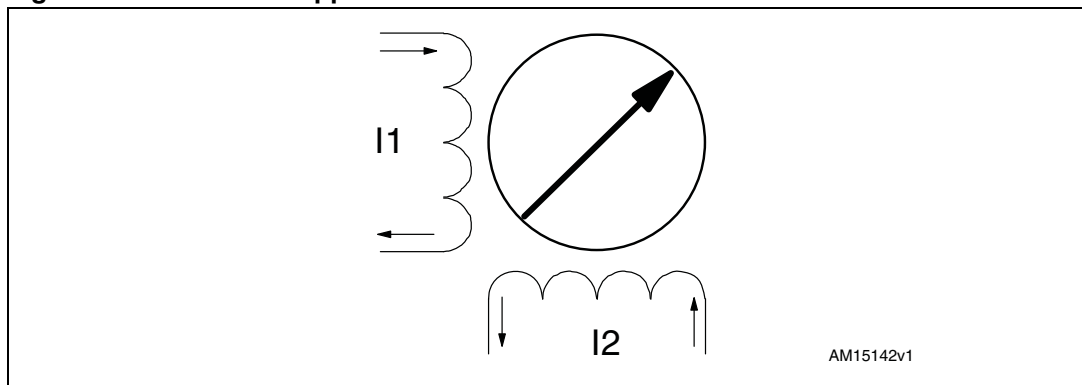


Figure 2. Full step sequence

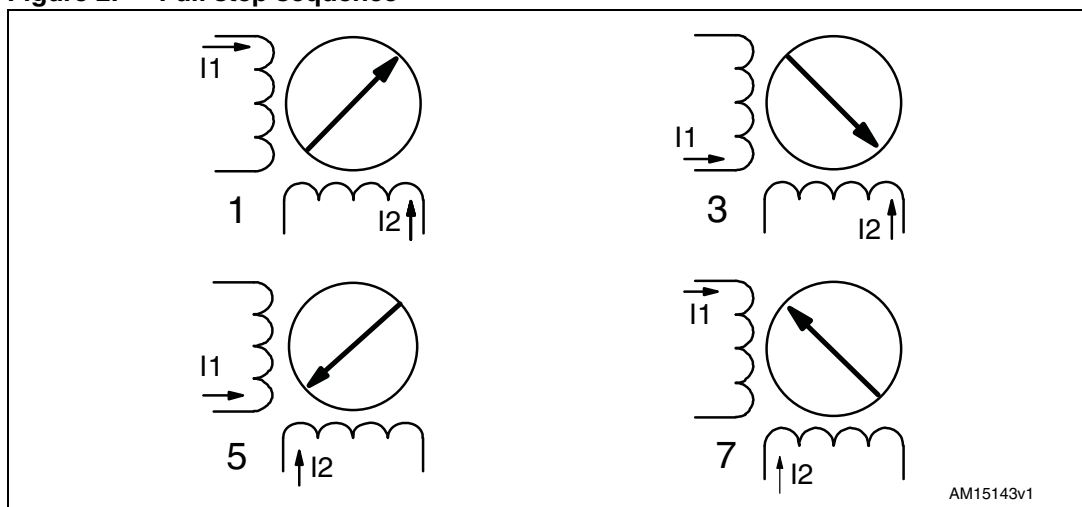


Another issue occurs at low operating speeds. At low speeds, both the full and half step drive tend to make abrupt mechanical steps since the time the rotor takes to move to the next position can be much less than the step period. This stepping action contributes to jerky movement and mechanical noise in the system. Looking at the simplified model of the stepper motor in [Figure 1](#), it can be seen that if the two coils were driven by sine and cosine waveforms the motor would operate as a synchronous machine and run very smoothly. These sinusoidal waveforms may be produced by a microstepping drive.

In current mode drives, the winding current is sensed and controlled to be the appropriate value for the desired position. This application note will consider only current mode drive implemented using peak detecting current controllers.


To understand the microstepping concept, consider the simplified model of the stepper motor as shown in [Figure 1](#). As previously discussed when the two coils are energized with equal currents, the resulting magnetic vector will be at 45° and the permanent magnet of the rotor will align with that vector. However, if the two coils are energized by currents of different magnitude, the resulting magnetic vector will be at an angle other than 45° and the rotor would attempt to align with the new magnetic vector. If one coil were driven with a current that was twice the current in the second coil the magnetic vector would be at 26.56° , as shown in [Figure 3](#). For any given position, the required currents are defined by the sine and cosine of the desired angle.

Figure 3. Example alignment of microstepping

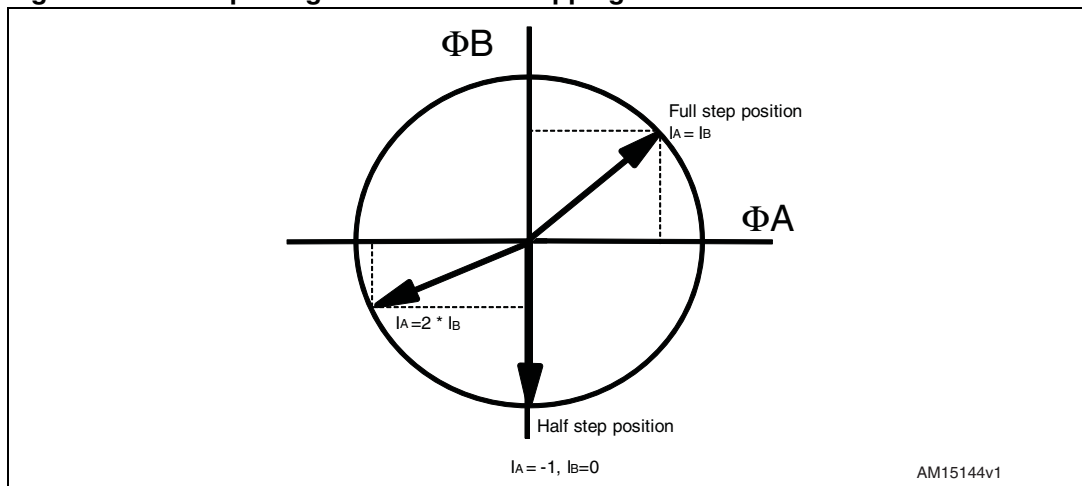

To implement a microstepping drive, two D/A converters are used to set the current level in the coils of the motor, as shown in the block diagram in [Figure 4](#).

Figure 4. Block diagram of microstepping motor drive

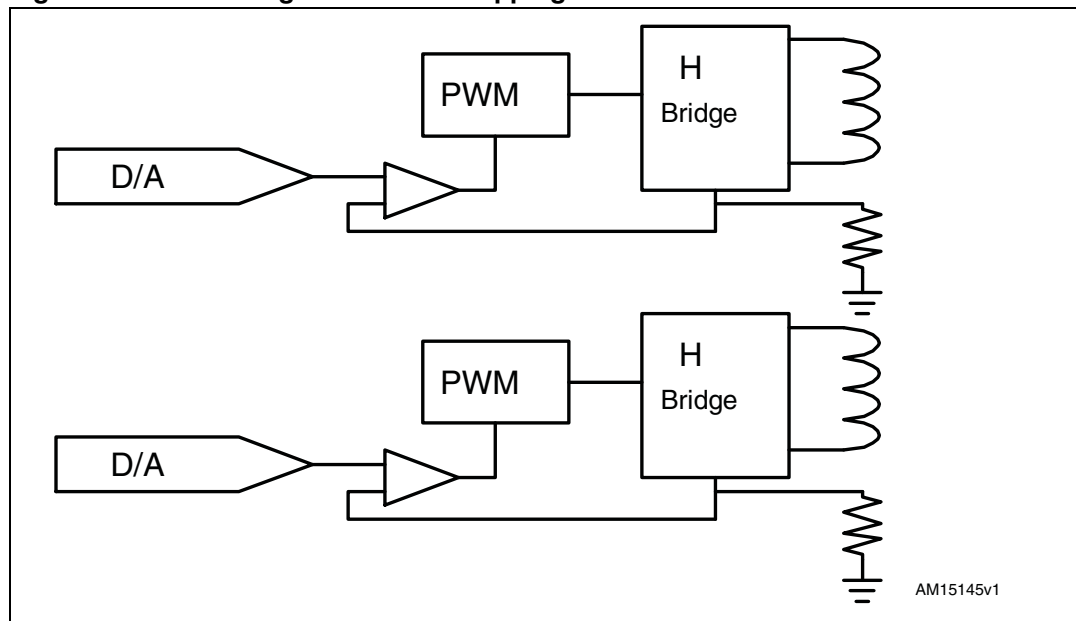

2 Microstepping with the L6208

In a typical application the L6208, which integrates two h-bridges with the current control, drives a bipolar stepper in either full or half step modes. The internal state machine generates the full step or half step sequence from the clock and direction inputs. [1] Although at first glance it is not obvious that the L6208 may be used in a microstepping application, it is possible since the current control circuits have separate reference inputs.

To implement a microstepping application, a variable voltage proportional to the desired output current must be applied to each of the reference pins. In the block diagrams above, the two required D/A converters provide the required voltages. A simple and inexpensive alternative to a D/A converter chip is to use a counter/timer in the microprocessor to generate a PWM output for each phase and pass this through a voltage divider and low pass filter to get the desired voltage. The Vref input voltage is equal to the microprocessor power supply voltage times the divider ratio of the resistor divider times the PWM duty cycle. [Figure 5](#) shows the connection between a microcontroller and the L6208. The complete circuit schematic for the power section is shown in [Appendix A](#).

Since the L6208 includes an internal phase generation circuit, this circuit must be synchronized to the externally provided reference voltages. Again a simple solution is possible. The initial state of the decoding logic after reset is known and may be used as the starting state. After applying a reset to the L6208, either at power up or by forcing a reset from the microprocessor, the full-scale voltage is applied to both Vref pins to align the stepper motor to the known state that corresponds to one of the full step positions. Once the motor is aligned, the references can be reduced to 70.7%, which is the correct value for the currents for the 45° position in the microstepping sequence. After the motor is aligned the microcontroller can move through the sine/cosine table to generate the appropriate reference levels to move in either direction. The software also has to set the appropriate direction on the CW/CCW pin and generate a clock pulse for each phase reversal that is required. This occurs whenever the phase crosses a 90° boundary in the sine table. By operating the L6208 in the full step mode and providing clock signals at the appropriate time, the decoding logic will output the correct phase information for the bridges. Using the L6208 in the half step mode with the appropriate clock signals can improve the performance at the zero crossover of the current, as will be discussed later.

Figure 5. Circuit connections for the L6208


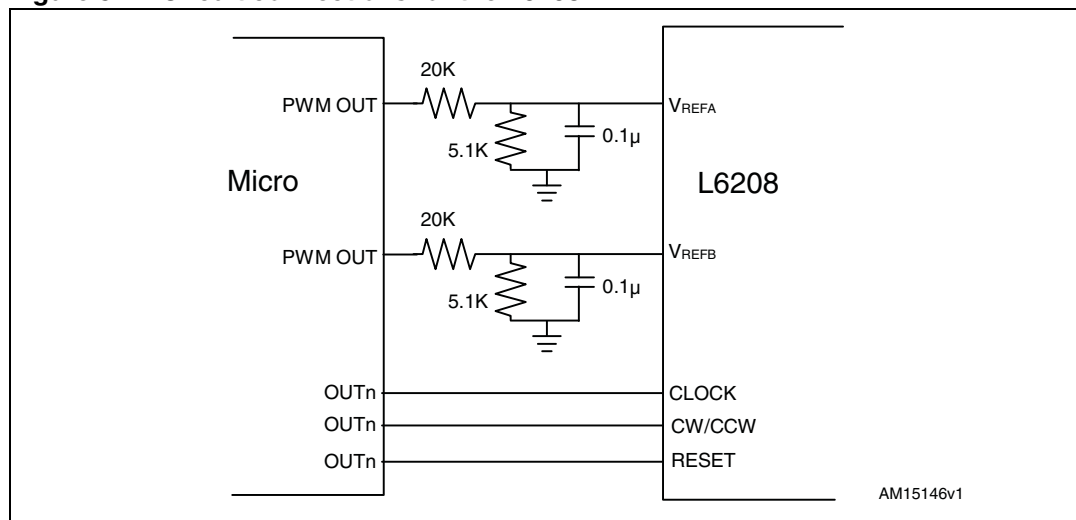


Figure 6 shows the operating waveforms when using the L6208 in full step mode and varying the reference inputs to achieve microstepping. Trace 1 is the clock input to the L6208. Traces 2 and 3 on the plot are the VrefA and VrefB inputs applied to the L6208. Trace 4 is the motor current in channel B. Although the current has the discontinuities near zero that are typical of a peak detection current control method, the resulting output matches the desired sine wave reasonably well.

Figure 6. Microstepping waveforms: typical operation

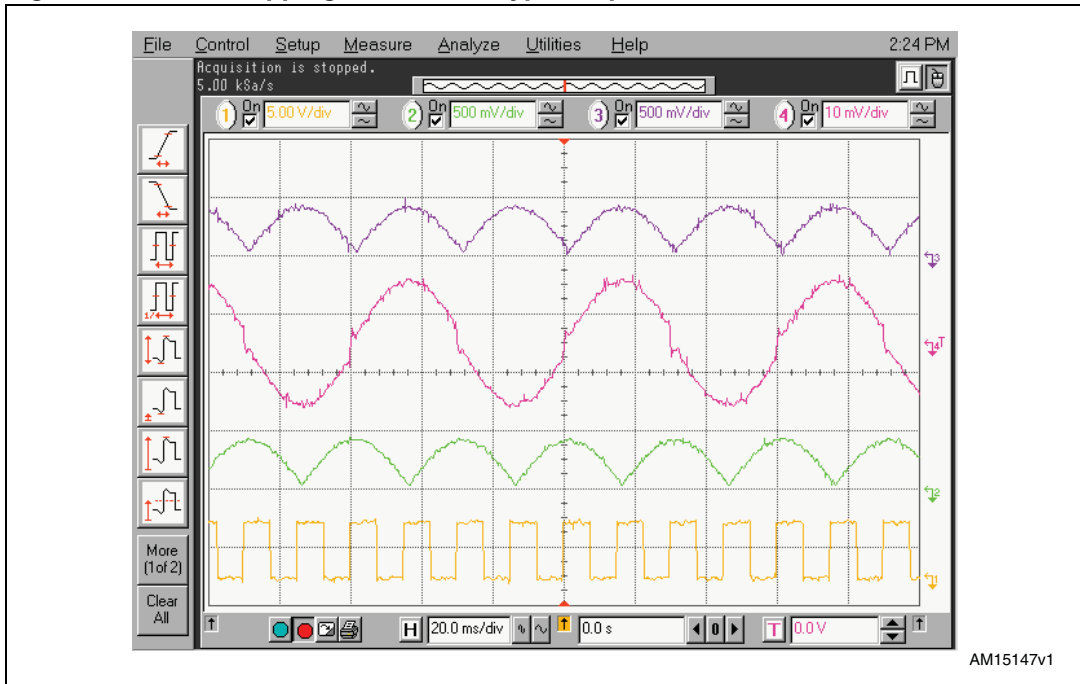

3 Speed limitations

Since the motor coil is primarily an inductance, the rate of current change in the coils is limited by the L/R time constant of the motor. As the motor is operated at higher speeds, the L/R time constant of the motor limits the rate of current change and the current can no longer follow the desired sine wave. *Figure 7* shows the motor current at a higher rotational frequency. On this scope trace, we see two effects. First, the filter on the reference voltage is starting to roll off the reference signal and second, the motor current is limited by the motor time constant and it begins to look more like a triangle waveform than the desired sine wave. Although moving the pole of the filter on the reference voltage will make the reference signal appear more ideal, it will have little effect on the motor current at this point since the motor current is primarily limited by the L/R characteristics of the motor. When approaching this point, the motor will run smoothly in full step mode and the microprocessor could easily change to full step drive.

If the step rate is increased further, the motor will stall when the current can no longer reach a value large enough to produce the required torque. *Figure 8* shows a typical current waveform when the motor has stalled. The almost pure triangular current waveform is similar to the triangular waveform that would result if the motor were being driven in the full step mode at this step rate. At this operating point the current is entirely controlled by the L/R time constant of the motor and no chopping is occurring.

Figure 7. Microstepping waveforms: current limited by motor inductance


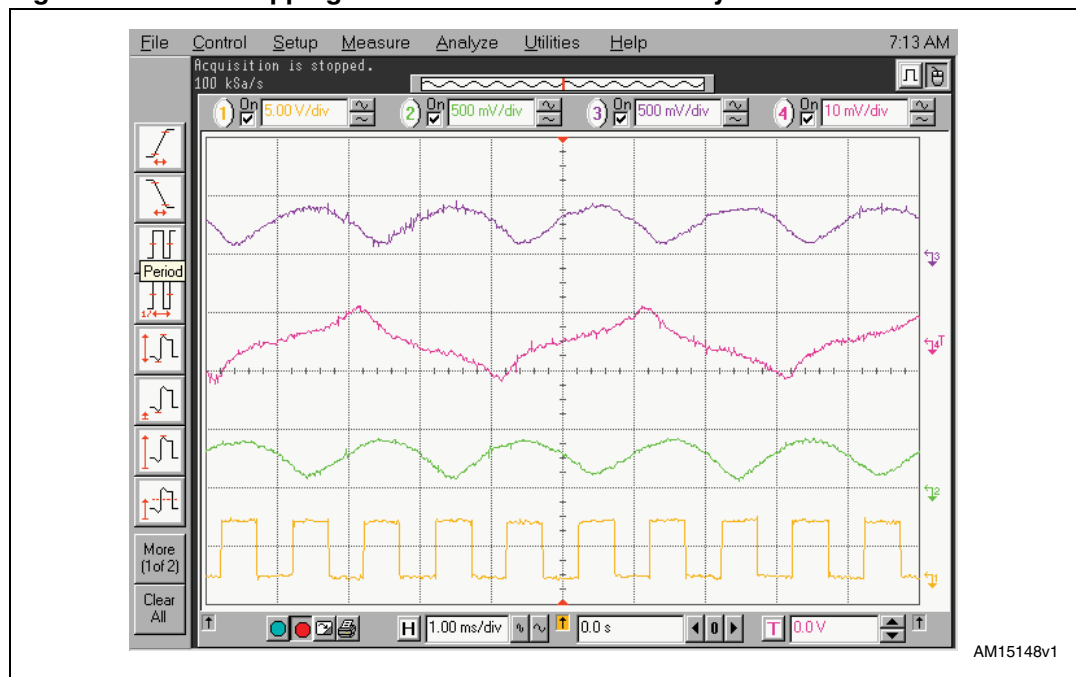


Figure 8. Waveforms when motor has stalled

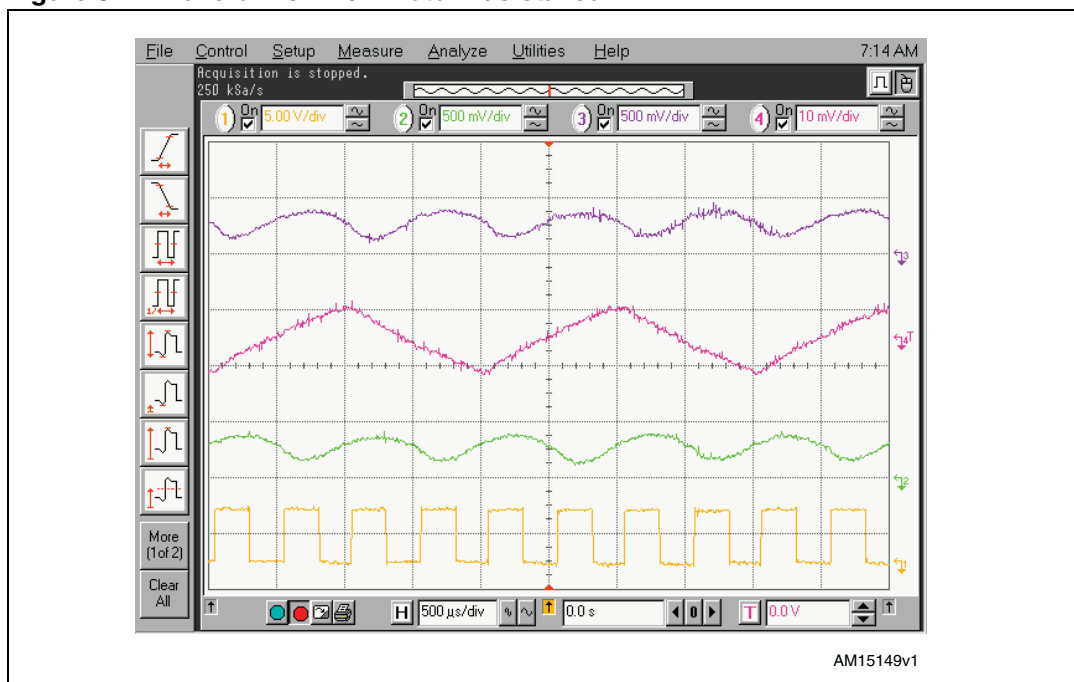

4 Slow versus fast decay mode

When implementing current controlled motor drives, the designer has a choice of the recirculation path the current flows in during the "off" time. [Figure 9](#) shows the two recirculation options implemented in the L6208. Applying the chopping to only one side of the bridge allows the current to recirculate around a low voltage loop, in the upper transistors with the L6208. Since the rate of change of the current is controlled primarily by the L/R time constant of the motor, the current decays relatively slowly, hence the designation of slow decay mode. However, applying the chopping to both sides of the bridge results in the current recirculating back to the power supply and a higher voltage across the coil, hence a fast decay mode. The L6208 also implements a type of synchronous rectification that turns on the MOS transistor in parallel with the conducting diode to reduce the power dissipation. [1]

The selection of the decay mode influences the operation of a microstepping drive in several ways. The most obvious is the magnitude of the ripple current. Drives implemented using the fast decay mode will have, for the same off time or chopping frequency, a higher ripple current than drives implemented using a slow decay mode. This difference in itself is not significant for most stepper motor drives. Issues with the stability of the current control loop are discussed elsewhere [3].

When microstepping at a higher speeds, the selection of the decay mode affects the ability of the drive to follow the desired current level. At any time, the rate of change of current is determined by the inductance of the motor and the voltage across the coil. In the slow decay mode, the voltage across the coil during the off time is only the drop across one transistor and one diode so the current changes very slowly. As the desired current level is lowered, it is the rate of change during the off time that determines how quickly the current transitions to the new level. At low speeds, the effect may not be noticeable. However, at higher speeds, the motor current cannot decay fast enough to follow the desired decreasing slope of the sine wave. During the off time, the current change is limited by the time constant imposed by the motor inductance and the slow decay path and can remain higher than the set value. [Figure 10](#) shows the reference voltage (channel 2) and current output (channel 4) for one phase of the motor. You can see that as the reference decreases, the output current decays slower than the reference input. The current will continue to decay at the slow rate until the desired current crosses zero and a phase reversal occurs, at which point the bridge reverses, applying the full supply voltage across the coil, effectively putting the bridge in a fast decay mode and the current will decay more quickly to zero. This corresponds to the point in [Figure 10](#) where the reference signal reaches zero. The difference in the rate of decay of the current is obvious in [Figure 10](#).

Selecting the fast decay mode can improve the ability of the drive to follow fast decreases in the current. [Figure 11](#) shows the reference voltage and output current under the same operating conditions, except now operating in fast decay. As expected, the ripple current is higher than when using slow decay, but the motor current more closely follows the desired sine wave.

The ability of the drive to increase current on the upper slope of the sine wave is not affected by the choice of the decay mode since the voltage applied to the coil during the on time is the same in either case.

Figure 9. PWM current control decay modes

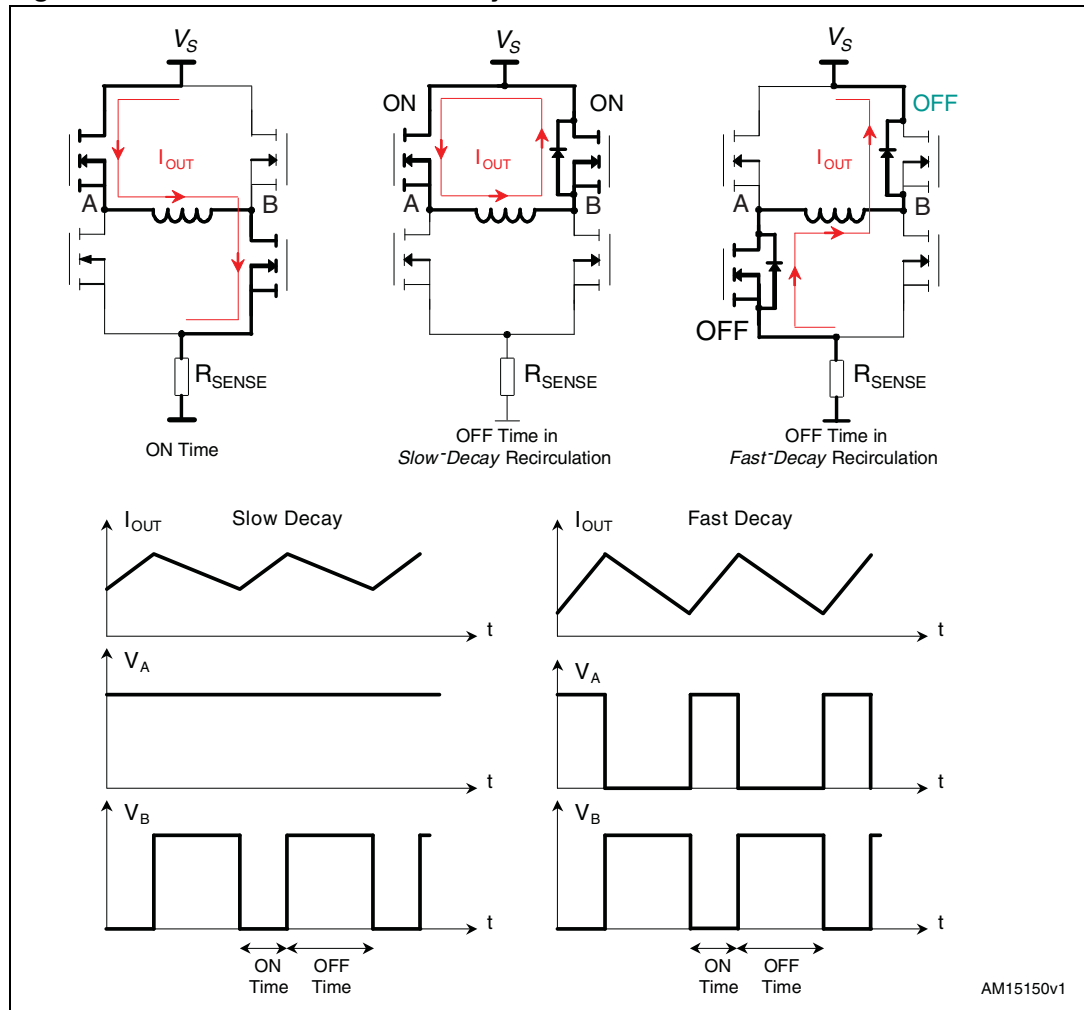


Figure 10. Microstepping motor current with slow decay


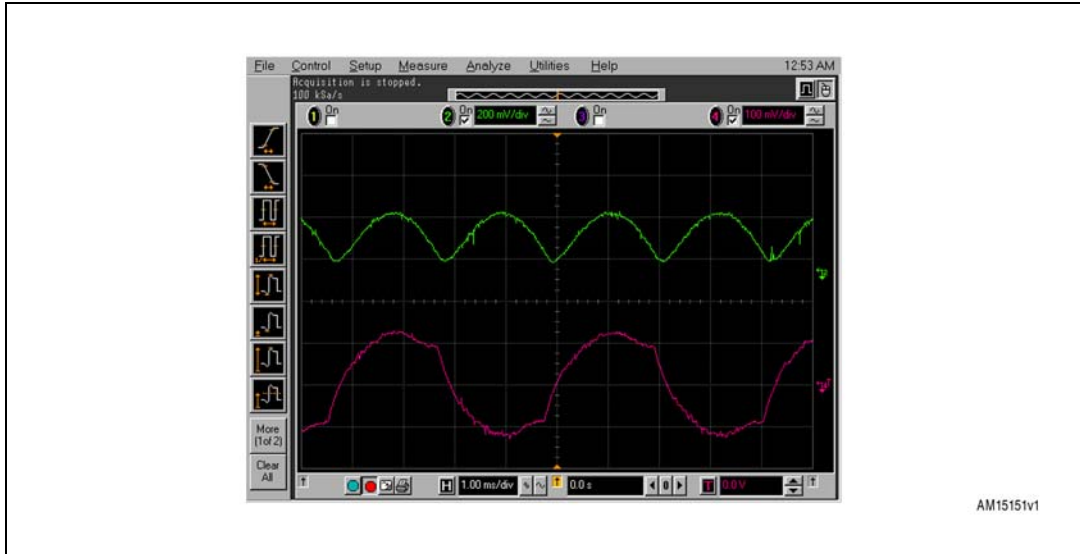


Figure 11. Microstepping motor current with fast decay

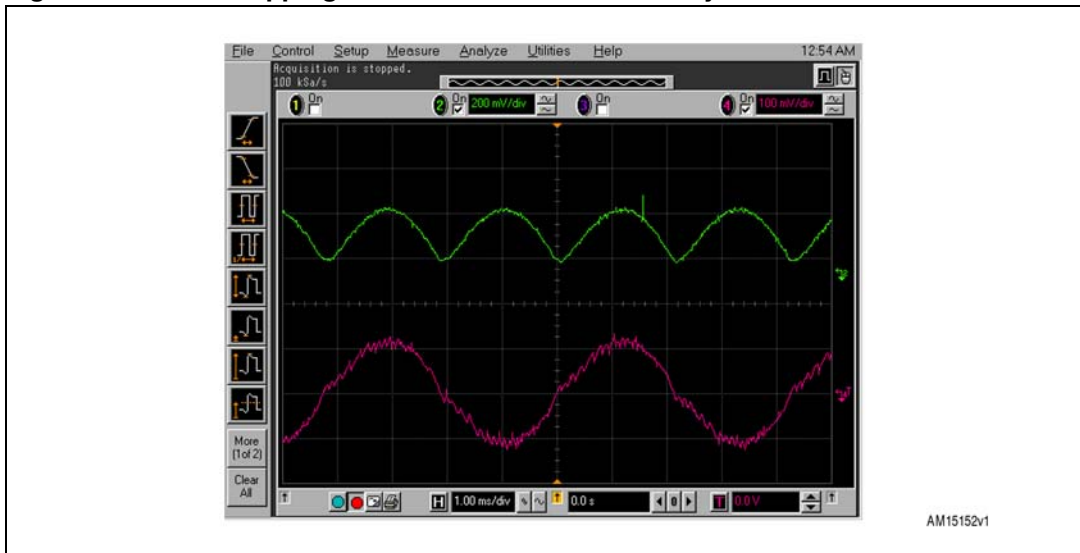

5 Minimum current issues


When operating a chopping current control that has a minimum duty cycle, the current cannot be taken below a level that is effectively set by the motor resistance and the minimum duty cycle. Constant off time controls, like the L6208, have a minimum on time that is set primarily by the propagation delays from the end of the off time until the comparator detects a current above the threshold and retriggers the monostable putting the bridge in the recirculation mode again. This minimum on time and the off time set by the monostable set a minimum working duty cycle for the circuit. When this duty cycle is applied to the motor, a current will be established. If a reference corresponding to a current lower than this minimum is set on the input, the circuit will detect that the motor current is above the reference. However, since the IC is already operating at its minimum duty cycle, the current cannot go any lower and thus will not reach the current level desired by the reference level. The minimum duty cycle in other controllers can sometimes be adjusted. The minimum on time in the L6506, for example, is set by the width of the sync pulse. By varying the duty cycle of the oscillator, the minimum duty cycle of the output can also be changed. Since the sync pulse is also used to mask the switching noise in the system, reducing the minimum duty cycle is not always possible. [3.]

Figure 12 shows the operating waveforms at the minimum current level.

The traces in *Figure 12* are:

- Ch 1: voltage on output pin
- Ch 2: V_{ref}
- Ch 3: V_{sense}
- Ch 4: load current (20 mA/div)

Figure 12. Waveforms at minimum current operation

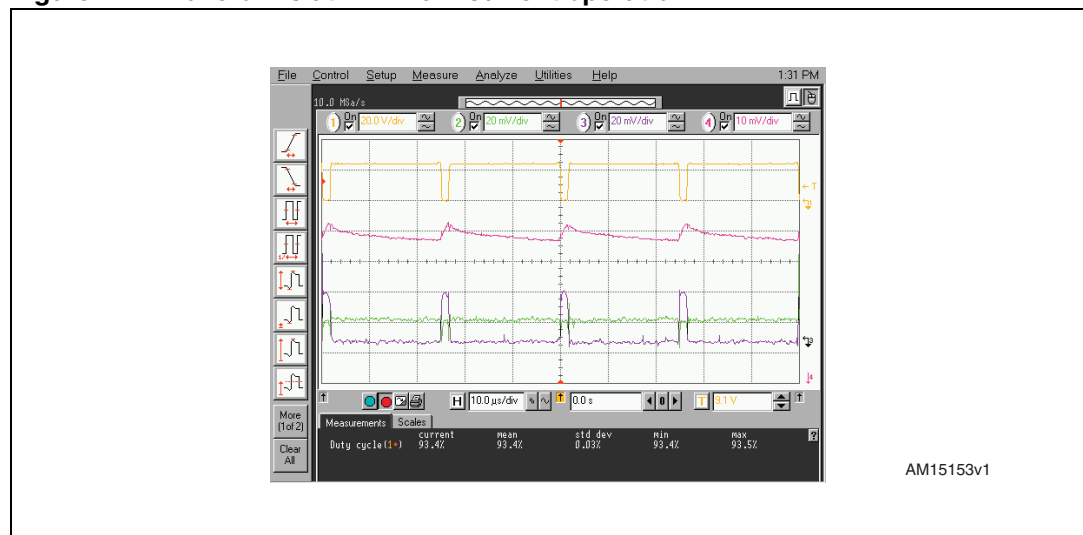


At the start of each cycle the bridge is turned on and the motor current flows through the sense resistor to produce the voltage V_{sense} . However at this operating point the sense voltage is already greater than the V_{ref} input voltage, as can be seen in *Figure 12*. The comparator will detect that V_{sense} is greater than V_{ref} and cause the circuit switch the bridge into the recirculation mode and the output is switched off after a delay that is determined by the response time of the circuit. The output pulse width, and hence the

operating current, are set by the response of the circuit to a condition where the current sense comparator detects a current above the set value as soon as the drive is turned on. Since this pulse width cannot be reduced further, the current that flows is the minimum that the device can regulate. In *Figure 12*, the minimum current is approximately 100 mA.

The minimum current level means a nonlinear transfer function exists between reference in (usually a voltage) to current out. *Figure 13* shows the resulting transfer function between reference and output current.

Figure 13. Transfer function showing nonlinearity

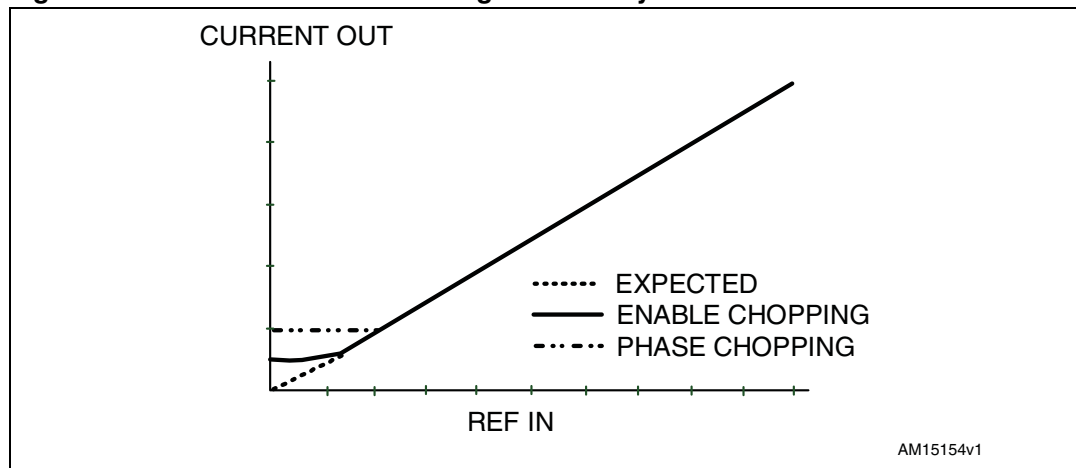


The transfer function also depends on the chopping mode, fast decay (enable chopping) or slow decay (phase chopping) as shown in *Figure 13*. In slow decay mode the current changes very slowly during recirculation and has a small ripple value. When operating in fast decay the transfer function also has a discontinuity in the slope at low levels. At the minimum current level, the duty cycle is small and when operating at this point the current typically is discontinuous, that is the current rises to a peak value and decays back to zero during each cycle. The flat section of the current transfer function corresponds to this minimum current. When the reference is increased, the device begins to regulate current however the device will still operate in the discontinuous mode. Continuing to increase the reference, the device will begin to operate in the continuous current mode, where the current does not decay to zero in each cycle. When the current changes from discontinuous to continuous, the slope of the transfer function changes. The result is that there are two discontinuities in the transfer function, one set by the minimum current and one set by the change in slope. In theory the slow decay mode could also have two discontinuities, however in practical examples the minimum current is reached before the current goes discontinuous.

The minimum achievable current effectively sets a limit on the number of microsteps per step by setting minimum current for the first microstep. Since the fast decay mode has a lower minimum current, fast decay can be used to minimize the effect of the minimum current, but will introduce another error due to the change of the slope. The latter can be compensated for by adjusting the DAC value.

It is, however, possible to get zero current in a phase by disabling the bridge when zero current is desired in that phase. When using drivers that have an enable input for each bridge simply disabling the bridge will force the current to zero. The L6208, however, does not have a separate enable input for each bridge so we need to use another trick of the logic to disable the bridge at the appropriate time. When driven in the half step mode, one bridge is disabled in each of the even states [2]. This operating sequence can be used to disable

the bridge at the appropriate times. To achieve this, operate the L6208 in half step mode and apply a pulse to the clock input at the same time that the desired current is set to zero. At the next change of current apply a second pulse to the clock input and set the current value for the first microstep. The step sequence generator in the L6208 will cause the change from current in one direction in the bridge, to the bridge being disabled, to current in the reverse direction as shown in [Figure 14](#).

Figure 14. Microstepping waveforms with improved performance at zero current

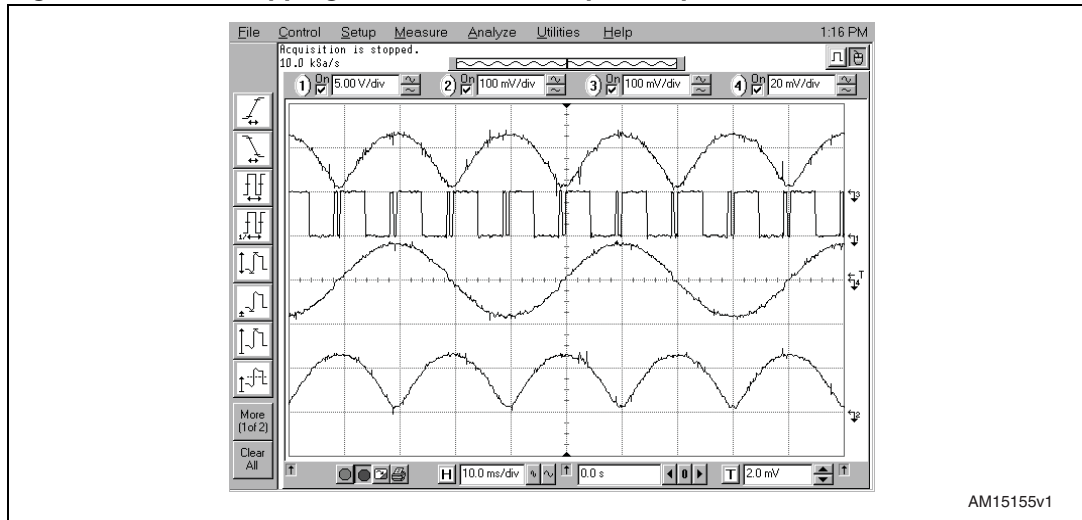

The effects of the minimum current can be seen in the motor movement as errors in the motor position or as a jerky movement in a constant speed movement. How much the minimum current affects the drive depends primarily on the number of microsteps implemented per step. Since zero current can be achieved as described above, the positions at the 90° intervals where one coil is driven by zero current and the other is driven by the full scale current can easily be implemented. However, the next microstep where the current in one coil is small is most affected. If the desired current for any position is less than the minimum current, an error occurs. If the current required for the first microstep after the zero current position is greater than the minimum current, no error is contributed. Fortunately, since the desired current profile is a sine wave, the first step after the zero crossing has the largest relative increase in current of any microstep. If the required current for this first microstep is greater than the minimum current the device can regulate, there will be no error in the current to the motor due to the minimum current.

If the design required that one step (90°) be divided into 16 microsteps, the angle for the first step would be 5.625°. The sine of 5.625° is 0.098. When using an 8-bit D/A, the closest available value would correspond to an input of 25 out of 255. No other microstep needs a current less than this (except the 0 as discussed above). As long as the minimum current is less than the value corresponding 25/255 of the peak current, there will be no noticeable error contributed by the minimum current. Another way to express this that no error will be noticeable if the output current can be regulated to plus or minus 1 LSB over the range 24 to 255. There is no system level requirement to maintain the accuracy for inputs less than 24.

6 L6506 and L6203/L298

Microstepping drives can be implemented using the L6506 controller and bridge IC's like the L6201, L6202, L6203 and L298. The main difference between the standard half step application and a microstepping application is that the two references of the L6506 are set by D/A converter outputs. *Figure 15* and *Figure 16* show microstepping applications using the L6506 and the L6203. Outputs Px1 through Px4 from the microprocessor set the phase for the L6506/L6203 combination and output Px5 and Px6 are used to enable the bridges. Again, the D/A function could be implemented using the PWM outputs of the microprocessor as was done in the example above or it could be implemented using an integrated D/A. The same logic configuration can be used with the L6201, L6202 or L298. When using the typical connection between the L6506 and the L6203 (as shown in *Figure 15*), the PWM signal is applied to one of the phase inputs (the phase that is normally high) and you get the slow decay mode of operation.

To implement the fast decay mode of operation, the PWM signal needs to be applied to the ENABLE inputs of the L6203s. This can be accomplished by rearranging the connections from the microprocessor. Inputs IN 1 and IN 2 of the L6203s are disconnected from the L6506 and connected directly to the Px1 through Px4 outputs of the microprocessor, which will continue to provide the phase information as before. The two PWM current control loops in the L6506 are then used to control the ENABLE inputs of the two L6203, as shown in *Figure 16*. Px5 and Px6 are now connected to the inputs of the L6506 so that each bridge can be disabled to get zero current. Finally the power on reset (POR) is connected to the RESET input of the L6506 to disable the bridge during power up.

Figure 15. Microstepping using L6506 and L6203 (slow decay)


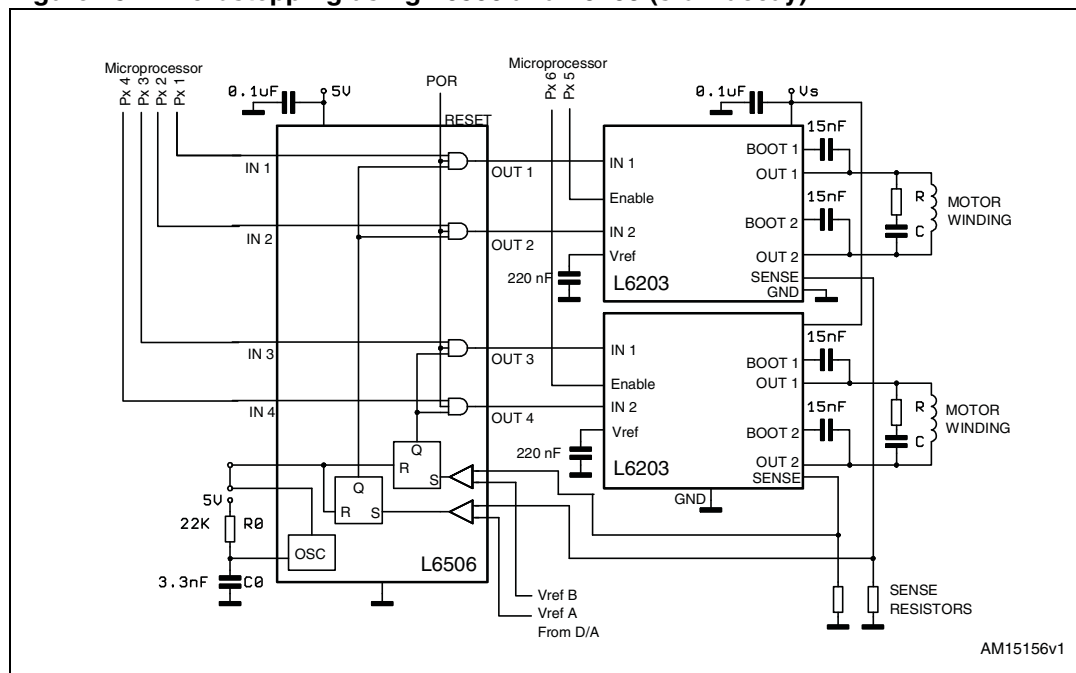


Figure 16. Microstepping using L6506 and L6203 (fast decay)

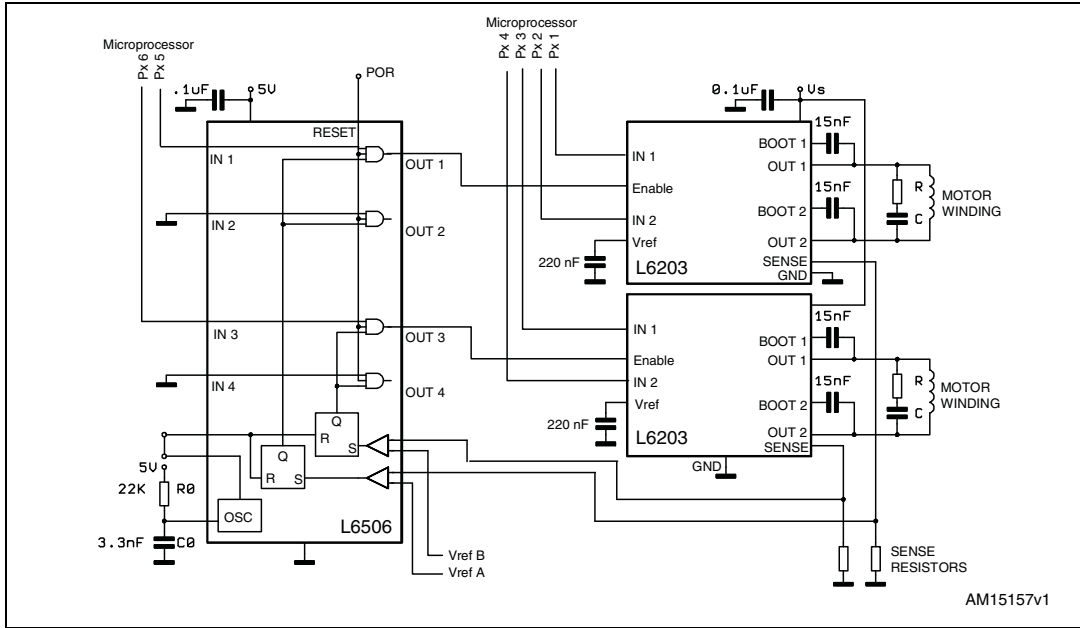

7 Conclusion


Although they were not designed specifically to implement microstepping, many of the integrated motor control/drive circuits can be used to implement microstepping stepper motor drives. The limits imposed by a peak detecting current control technique and the selected decay mode will directly affect the performance of the motor drive, specifically its ability to follow the desired current waveform. So long as these limits allow the designer to achieve the desired resolution in the microstepping application the devices provide a cost effective implementation.

8 References

1. A new fully integrated stepper motor driver IC, Domenico Arrigo, Thomas L. Hopkins, Angelo Genova, Vincenzo Marano, and Aldo Novelli, Proceedings of PCIM 2001, September 2001, Intertech Communication
2. L6208 datasheet
3. Stepper motor drives, common problems and solutions, AN460, T. Hopkins, STMicroelectronics
4. L297 data sheet
5. The L297 Stepper motor controller, AN470, STMicroelectronics
6. Stepper motor driving, AN235, H. Sax, T. Hopkins, STMicroelectronics

Appendix A Schematic

Figure 17. Scheme of the EVAL6208N

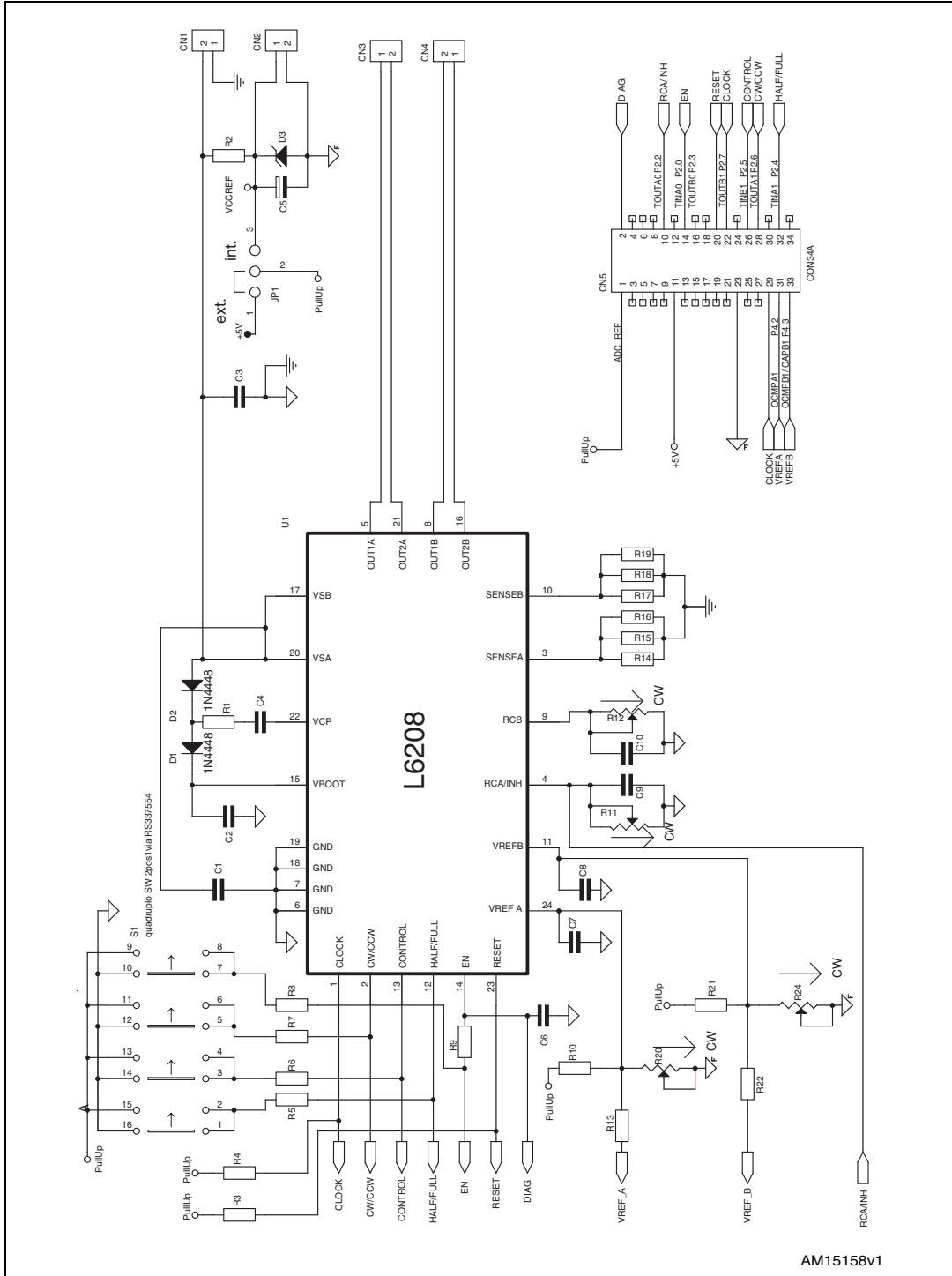

Appendix B Code

The following is an excerpt from the firmware which executes on the ST7264 based control which is part of the PractiSPIN™ evaluation system. This code segment is executed when the decision has been made that it is time for the L6208 to take the next microstep (either forward or reverse).

```

; PB.4 is the L6208 clock pin
; PB.5 is the L6208 reset pin
; stepstate is a byte variable which controls the motor stepping.
; torquescaler is a byte used to modulate the normalized sine wave values
read from the table to set the current level
; TAOC1LR is a register that controls Vrefa (via the duty cycle into the low
pass filter)
; TBOC1LR is a register that controls Vrefb (via the duty cycle into the low
pass filter)

    bres PBDR,#4      ;take clock back low ready to generate rising edge later
    bset PBDR,#5      ;normal state for reset jumpifflagclear forward,
doclockrev; jump if direction is reverse

;direction is forward
    inc stepstate
    jrne for002      ; skip if stepstate has not rolled over to zero
    bres PBDR,#5      ; activate reset to maintain sync (just for added noise
immunity insurance)

for002:
    ld a,stepstate
    and a, #00011111 ; use only lower five bits as index for table lookup
    ld x,a           ; save index

; on indexes 8 and 9, clock L6208 to sequence through zero and then polarity
reversal and a, #00001110
    cp a, #8         ; 8 or 9
    jrne for001
    bset PBDR,#4     ; rising edge for clock

for001:
    ld a, (microtable1,x); get normalized value from table
    ld y, torquescaler
    mul y,a          ; y:a = (table value) * torquescaler
    ld TAOC1LR,y     ; duty cycle = (table value) * torquescaler/256

; repeat for phase B

```

```
    ld a, (microtable2, x)
    ld y, torquescaler
    mul y, a
    ld TBOC1LR, y
    jp pwmend      ; end of routine for forward step

doclockrev:
;direction is reverse
    dec stepstate
    jrne rev002
    bres PBDR, #5  ; activate reset to maintain sync

rev002:
    ld a, stepstate
    and a, #%00011111
    ld x,a
    inc a          ; 7 or 8 ==> 8 or 9
    and a, #%00001110
    cp a, #8      ; 8 or 9
    jrne rev001
    bset PBDR,#4  ; rising edge for clock

rev001:
    ld a,(microtable1,x)
    ld y,torquescaler
    mul y,a
    ld TAOC1LR, y
    ld a, (microtable2,x)
    ld y, torquescaler
    mul y, a
    ld TBOC1LR, y
    jp pwmend
; The lookup table holds the magnitude of a sine wave normalized to a peak
value of 256.
; Each line of 16 entries represents 90 degrees or one full step (thus 16
microsteps per
step).
; Table reference labels at 45 degrees (microtable1) and 135 degrees
(microtable2) are
provided for convenience
; to allow easy lookup of two waveforms with 90 degree phase relationship.
; Since only five bits (0 to 31) of the stepstate table index are used,
references using
microtable1 roll over through
; just the first two lines of the table while references using microtable2
stay within
```

```
the second and third lines
; of the overall table.
microtable1:
; degrees 45 90
dc.b 180,197,212,224,235,244,250,253,254,253,250,244,235,224,212,197
microtable2:
; degrees 135 0
    dc.b 180,161,141,120,097,074,049,024,000,024,049,074,097,120,141,161
; degrees 45 + 90
    dc.b 180,197,212,224,235,244,250,253,254,253,250,244,235,224,212,197
```

9 Revision history

Table 1. Document revision history

Date	Revision	Changes
18-Apr-2002	1	Initial release.
08-Jun-2004	2	Replaced the Appendix B that contains assembler code for an ST7264. Changed the style-sheet following the new "Corporate technical publications design guide".
26-Sep-2012	3	Removed section 7 related to the previous version of the document, titled "PBL3717, TEA3717, TEA3718 and L6219". Revised Figure 3 , Figure 10 and Figure 11 . Minor text changes.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2012 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

