

## THD improvement at light-load in applications using STCMB1

A **design tip** is a description of an application oriented, technical implementation that leads to a specific benefit. For more information or support, visit [www.st.com](http://www.st.com)

By Giovanni Gritti

Main components	
STCMB1	TM PFC with X-cap discharge and LLC resonant combo controller

### Purpose and benefits

This design tip provides a simple modification with respect to the standard reference schematic based on the STCMB1 device, aimed to minimize the input current Total Harmonic Distortion (THD) down to 25% of full load.

The main purpose is to maximize the load range with low input current THD, making the AC/DC converters based on the STCMB1 capable of covering the latest LED lighting market requirements.

### Description

The main change is an optimization of the control method of the PFC section (constant on-time control) adding a simple circuit composed by one Resistor and one Diode (RD circuit), which allows to reduce the burst-mode threshold intervention while keeping the best performance in terms of THD.

The suggested circuit can be also easily applied to the existing STCMB1 development kits (the formula is provided to design the suggested RD circuit).

Figure 1 shows the suggested RD circuit: an  $R_G$  resistor is connected between the current sense pin of the PFC section (ISEN\_PFC pin) and the auxiliary winding of the PFC choke through a  $D_G$  diode. As a consequence, a current proportional to the instantaneous input voltage  $V_{IN}$  during the power switch on-time is sunk from the current sense ISEN\_PFC pin, modulating the THD optimizer threshold (see STCMB1 datasheet, Section 7.6, where the THD optimizer threshold -preset  $I_{Lth}$  value- is constant).

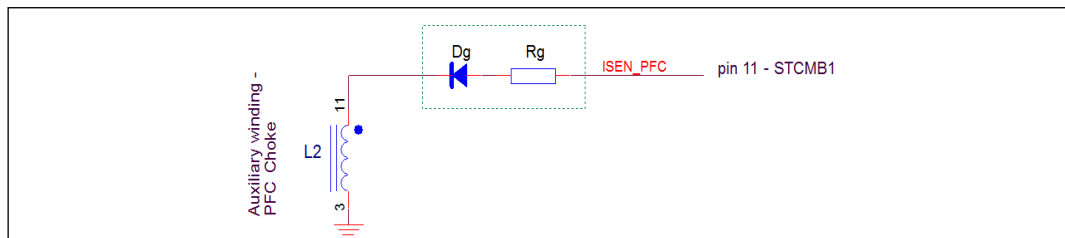


Figure 1. Suggested circuit diagram inside the green dotted line box.

As demonstrated in the following mathematical steps, this modulation improves the constant on-time control of the PFC converter, reducing the burst-mode threshold intervention but keeping the best performance in terms of THD.

Referring to the STCMB1 datasheet, equation 3 in Section 7.6 provides the analytic expression of the input current for a standard constant on-time control (COT), which is equal to the average value of the inductor current in a switching cycle:

$$I_{IN}(\theta) = \langle I_L \rangle = \frac{1}{2}(I_{Lvy} + I_{Lpk}) = \frac{V_{in,pk} \sin \theta}{2L} T_{ON} + \sqrt{\frac{C_{drain}}{L}} V_{in,pk} \sin \theta - \sqrt{\frac{C_{drain}}{L}} V_{out} . \quad (1)$$

where L is the PFC choke and  $Y_L = \sqrt{C_{drain}/L}$  is the admittance of the parasitic resonant tank.

The STCMB1 embeds a proprietary ECOT control, which activates the timer that sets the power switch on-time ( $T_{ON\_C}$ ) once the inductor current reaches a preset  $I_{Lth}$ , comparing the ISEN\_PFC pin voltage with an internal  $V_{ISEN\_PFC\_Z}$  fixed threshold.

Designing the  $I_{Lth}$  inductor preset value equal to the terms  $\sqrt{\frac{C_{drain}}{L}} V_{out}$ , the input current results:

$$I_{IN}(\theta) = \langle I_L \rangle = \frac{1}{2}(I_{Lvy} + I_{Lpk}) = \frac{1}{2} \left( T_{ON\_C} + \sqrt{\frac{C_{drain}}{L}} \right) V_{in,pk} \sin \theta . \quad (2)$$

Assuming a narrow control loop bandwidth, like in any high-PF converter, the  $T_{ON\_C}$  is constant along a line half-cycle. Therefore, the previous equation shows that the control on-time method (ECOT) achieves sinusoidal input current.

By averaging the product of  $I_{IN}(\theta)$  given by (2), by the instantaneous line voltage  $V_{IN}(\theta) = V_{in,pk} \sin \theta$  over a line half-cycle, it is possible to find the DC input power  $P_{IN}$  to the converter:

$$P_{IN} = \frac{V_{in,pk}^2}{4} \left( \frac{T_{ON\_C}}{L} + Y_L \right) . \quad (3)$$

Now considering the efficiency  $\eta$  of the PFC converter, the output power  $P_{OUT}$  results:

$$P_{OUT} = \eta P_{IN} = \eta \frac{V_{in,pk}^2}{4} \left( \frac{T_{ON\_C}}{L} + Y_L \right) . \quad (4)$$

The previous equation shows that the PFC converter gives a minimum output power, even in the ideal case where the on-time control loop  $T_{ON\_C}=0$ :

$$P_{OUT\_MIN\_IDEAL} = \eta \frac{V_{in,pk}^2}{4} Y_L . \quad (5)$$

Considering a minimum on-time  $T_{ON\_MIN}$  (sum of the STCMB1 delay to output  $t_{d(H-L)}$  and the power switch off-time  $t_{d(OFF)}$ ), the minimum output power results:

$$P_{OUT\_MIN} = \eta \frac{V_{in,pk}^2}{4} \left( \frac{T_{ON\_MIN}}{L} + Y_L \right) . \quad (6)$$

If the power requested by the PFC load is lower than (6) the PFC converter enters into burst-mode, to keep the output voltage regulation, much increasing the THD.

Considering the suggested RD circuit, the current sunk from the ISEN\_PFC pin is:

$$I_G(\theta) = \frac{V_{IN}(\theta)}{m R_G} , \quad (7)$$

where m is the primary-to-auxiliary turns ratio ( $m = N_P / N_{AUX}$ ) of the PFC choke.

As a consequence, the  $I_{ROS}$  current flowing in the  $R_{OS}$  resistor results:

$$I_{ROS}(\theta) = I_{OS} - I_G(\theta) = I_{OS} - \frac{V_{IN}(\theta)}{m R_G}, \quad (8)$$

where  $I_{OS}$  is the constant current sourced from the ISEN\_PFC pin ( $I_{OS}=50 \mu\text{A}$  typ., see STCMB1 datasheet). The resulting ISEN\_PFC pin voltage is:

$$V_{ISEN\_PFC}(\theta) = -R_S I_L(\theta) + R_{OS} I_{ROS}, \quad (9)$$

where  $R_S$  is the PFC current sense resistor.

Replacing (8) in (9) and considering that the device activates the timer that sets the power switch on-time ( $T_{ON\_C}$ ) once the ISEN\_PFC pin voltage reaches the  $V_{ISEN\_PFC\_Z}$  internal fixed threshold ( $V_{ISEN\_PFC\_Z} = -25 \text{ mV}$  typ., see datasheet), the  $I_{Lth}$  preset inductor value results:

$$I_{Lth}(\theta) = \left( \frac{|V_{ISEN\_PFC\_Z}| + R_{OS} I_{OS}}{R_S} \right) - \left( \frac{V_{IN}(\theta) R_{OS}}{m R_G R_S} \right). \quad (10)$$

It is worth noting that the  $I_{Lth}$  inductor preset value is not constant and is composed by two terms: the first term is constant, and the second term depends on the input voltage.

Selecting the  $I_{Lth}$  preset value equal to  $\sqrt{\frac{C_{drain}}{L}} V_{out} - \sqrt{\frac{C_{drain}}{L}} V_{in\_pk} \sin \theta$ , after some simple calculations the (1) results:

$$I_{IN}(\theta) = \langle I_L \rangle = \frac{1}{2} \left( \frac{T_{ON\_C}}{L} \right) V_{in\_pk} \sin \theta \quad (11)$$

which is still sinusoidal as in (1).

Considering (11), as done in (3), the output power  $P_{OUT}$  results:

$$P_{OUT} = \eta \frac{V_{IN\_pk}^2}{4} \left( \frac{T_{ON\_C}}{L} \right). \quad (12)$$

The previous equations show that with the suggested RD circuit that the input current is sinusoidal, but the minimum output power can be zero in the ideal case ( $T_{ON\_C}=0$ ). This permits to maximize the load range with low input current THD (no burst-mode intervention).

Considering (10) and the desired inductor preset value  $\sqrt{\frac{C_{drain}}{L}} V_{out} - \sqrt{\frac{C_{drain}}{L}} V_{in\_pk} \sin \theta$ , after some simple mathematical steps, results:

$$R_{OS} = \frac{R_S V_{out} \sqrt{C_{drain}/L} - |V_{ISEN\_PFC\_Z}|}{I_{OS}} \quad (13)$$

which is the same formula reported in the STCMB1 datasheet (the suggested RD circuit does not influence the design of the  $R_{OS}$ ) and:

$$R_G = \frac{R_{OS}}{m R_S \sqrt{C_{drain}/L}} \quad (14)$$

It is worth noting that the suggested  $R_G$  resistor depends on the equivalent capacitance afferent to the switching node, which is mainly composed by the sum of the parasitic capacitance associated to the MOSFET and the added capacitor between drain to ground, so some fine-tuning on the real application could be needed.

## Test results


The effectiveness of the proposed RD circuitry has been validated on a 150 W dimmable LED driver, where the main characteristics of the whole AC/DC converter and the PFC power section are reported in table 1. Applying the formula (14), the suggested  $R_G$  resistor results:

$$R_G = \frac{R_{OS}}{m R_S \sqrt{C_{DRAIN}/L}} = \frac{470}{10 \cdot 0.082 \sqrt{720 \cdot 10^{-12}/310 \cdot 10^{-6}}} = 376 k\Omega$$

AC/DC LED driver - parameter	Symbol	Value	Unit
Line voltage range	$V_{IN}$	90 - 265	Vac
Line frequency range	$f_{line}$	47 - 63	Hz
Regulated output current	$I_{LED}$	0.05 to 1	A
Rated output voltage	$V_{LED}$	150	V
PFC section - parameter			
Regulated output voltage	$V_{OUT\_PFC}$	400	V
Inductance	$L$	310	$\mu$ H
Inductor turns-ratio	$m = N_P / N_{AUX}$	10	-
Current sense resistor	$R_S$	0.082	$\Omega$
Current sense offset resistor	$R_{OS}$	470	$\Omega$
Equivalent drain capacitor (parasitic + external)	$C_{DRAIN}$	250+470	pF

**Table 1. Main characteristic of the 150 W LED driver converter.**

Figure 2 shows the THD comparison between the original board (dark) and the modified board (green) adding the optimized RD circuit ( $R_G = 300 k\Omega$ ,  $D_G = 1N4148$ ), versus output power.

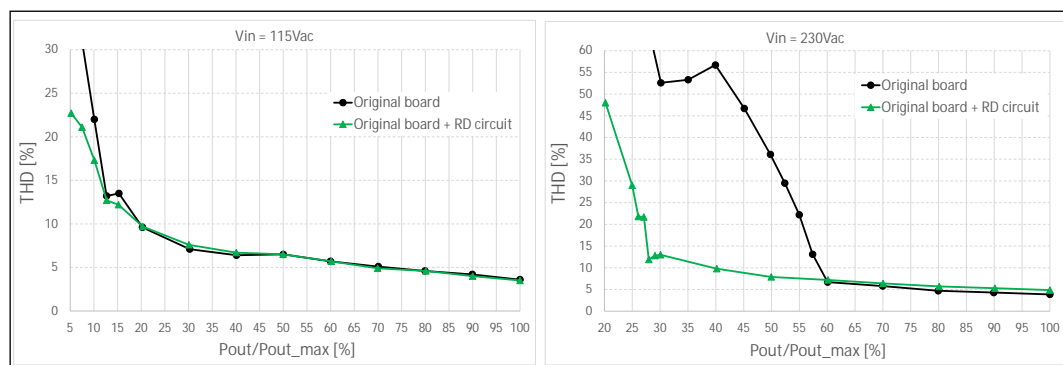

**Figure 2. THD comparison adding the optimized RD circuit.**

It is evident the huge improvement of the THD at high line. Basically, the burst-mode intervention is reduced from around 60% to around 25% of the load.

The following images show the Power Factor (PF) comparison results.

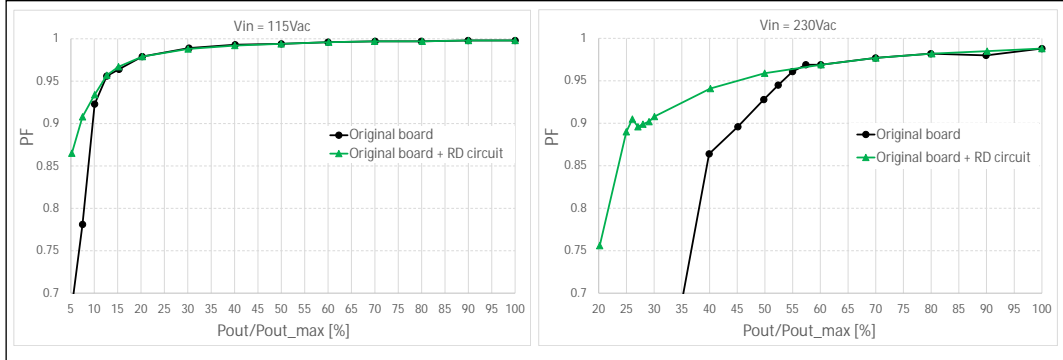


Figure 3. PF comparison adding the optimized RD circuit.


### Note: PFC choke value impacts and suggestion

Equations (6) and (12) show that the minimum output power of the PFC converter depends also on the PFC choke value L: the higher the inductor value, the lower the minimum output power.

Considering (12) and indicating the desired burst-mode threshold intervention as a percentage of the maximum output power, results:

$$BM[\%] = \frac{P_{OUT\_MIN}}{P_{OUT\_MAX}} 100 = \eta \frac{V_{IN,pk}^2}{4} \left( \frac{T_{ON\_MIN}}{L} \right) \frac{1}{P_{OUT\_MAX}} 100 \quad (15)$$

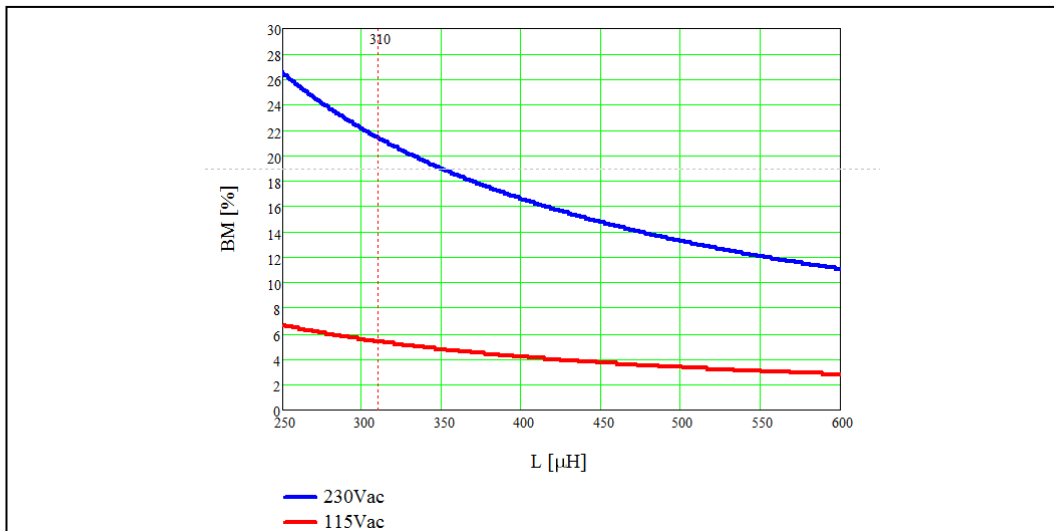For example, considering a minimum on-time of 420 ns ( $t_{d(H-L)}=220$  ns,  $t_{dOFF}=200$  ns), figure 4 shows the burst-mode threshold versus the PFC choke value.



---

#### Figure 4. Burst-mode threshold (BM) versus PFC choke value (L).

Finally, solving (15) for the PFC choke value, it is possible to find an estimate of the required inductor value to obtain the desired burst-mode threshold:

$$L_{BM} = \left( \eta \frac{V_{IN,pk}^2 T_{ON\_MIN}}{4} \right) \frac{1}{P_{OUT\_MAX}^{BM}[\%]} 100 \quad (16)$$

### Support material

Documentation
Datasheet, STCMB1 - TM PFC with X-cap discharge and LLC resonant combo controller

### Revision history

Date	Version	Changes
01-Dec-2021	1	Initial release.

---

### **Please Read Carefully**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at anytime, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2021 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)