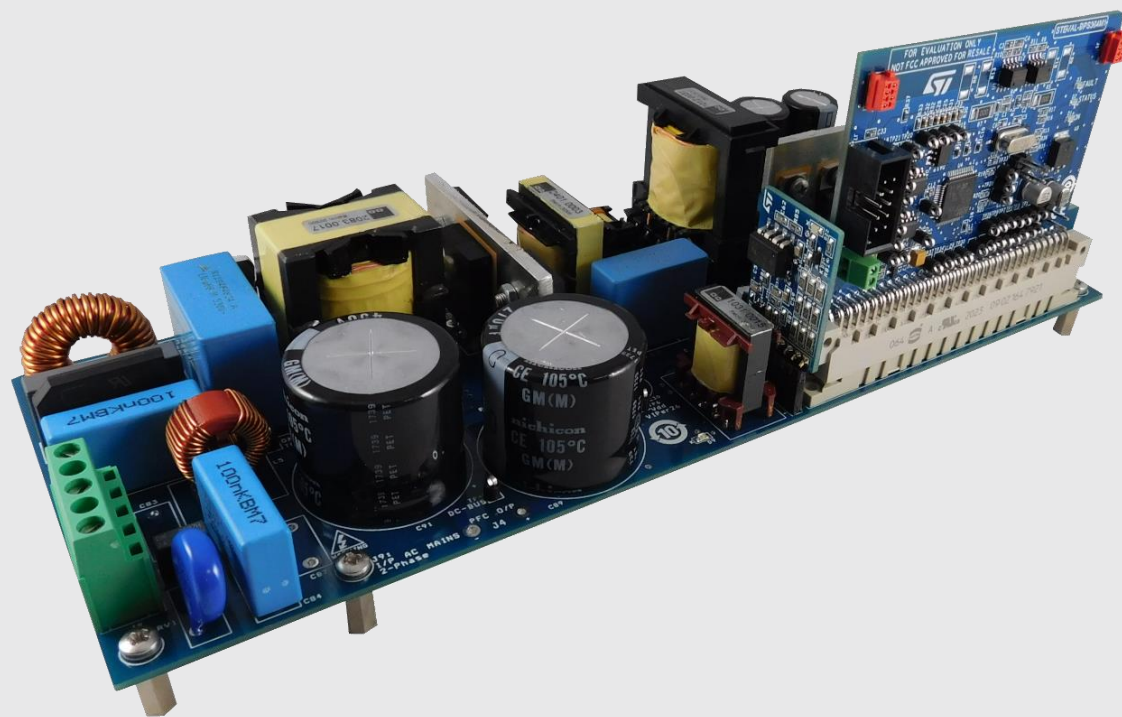




life.augmented



STEVAL-LLL009V1

300 W very high AC input voltage
LED driver with digital power
control

System Research and Application

Agenda

1

Introduction

2

Specification and outline

3

Architecture & key products

4

Key products overview

5

LCC topology fundamentals and synchronous rectification

6

Efficiency, operative performance

7

FW architecture

8

Schematics & layout



Introduction

A digitally-controlled 300 W power supply

Configuration: PFC + DC-DC conversion + synchronous rectification

- PFC working in Transition Mode
- DC-DC conversion based on Half Bridge LCC resonant converter, controlled by MCU
- Synchronous rectification based on Full Bridge topology, controlled by MCU

The evaluation board can either work in **Constant Voltage (CV)** mode or **Constant Current (CC)** mode

Design challenges

- Very high input voltage range: 270 V – 480 V AC
- THD @ Full load (270 V – 480 V AC): <10%
- Peak efficiency @ maximum load: >93.5%

Specification and outline

STEVAL-LLL009V1 evaluation kit

Specification and features

- **Configuration:** PFC + HB-LCC + FB-Sync. Rectification
- **Input voltage range:** 270 V – 480 V AC
- **PFC output voltage:** $725 \pm 2.5\%$
- **PFC operating mode:** Transition Mode
- **Power factor @ Full load (270 V–480 V AC):** > 0.95
- **Power factor over input voltage span 270 V–480 V AC:** > 0.9 for Load $> 33\%$ of Maximum Load
- **THD @ Full load (270 V – 480 V AC):** $< 10\%$
- **THD over input voltage span 270 V – 480 V AC:** $< 20\%$ for Load $> 25\%$ of maximum load
- **Peak efficiency @ maximum load:** $> 93.5\%$
- **Maximum output power:** 300 W
- **Output configuration:** Constant Voltage (CV) or Constant Current (CC)
- **Output:** Constant Voltage (CV) Mode: $48.5 \text{ V} \pm 1\%$ with maximum of 6.25 A
- **Output:** Constant Current (CC) Mode: $6.25 \text{ A} \pm 2.5\%$ with output voltage ranging from 36 V to 48 V

- **DC-DC converter topology:** Half bridge LCC resonant converter
- **Half bridge LCC resonant converter:** Closed loop switching frequency: 90 kHz to 275 kHz
- **Half bridge LCC resonant converter:** Start-up switching frequency: 280 kHz
- **Synchronous rectification topology:** Full bridge
- **HF transformer isolation:** 3 kV
- **Cooling:** Natural air
- **Dimming approach:** Analog dimming
- **Dimming control:** 0 - 10 V
- **Default brightness level:** 100%
- **Dimming resolution:** 1%




Architecture & key products



life.augmented

Architecture

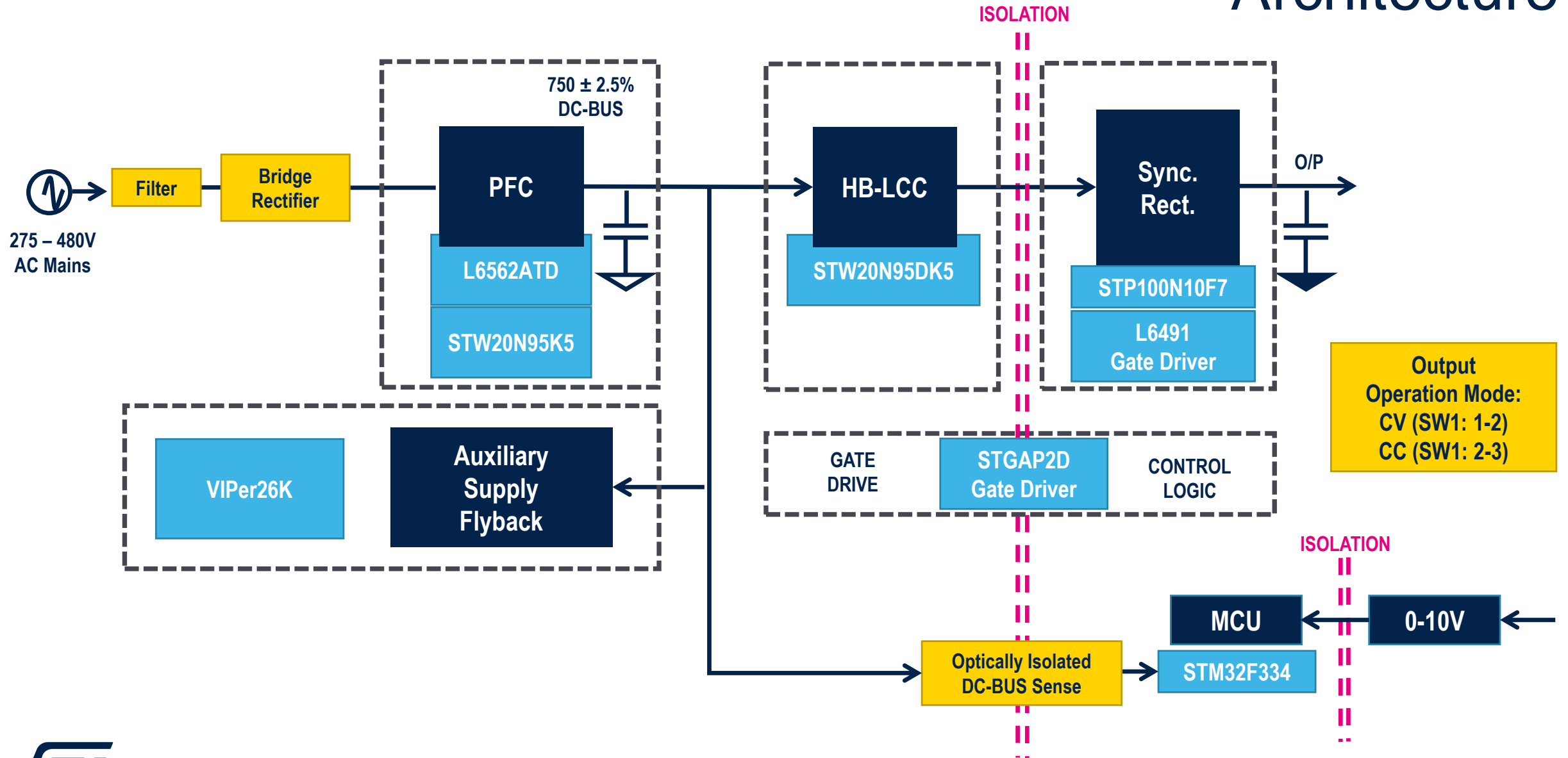

STEVAL-LLL009V1 evaluation kit

Key products



STW20N95DK5 (MDmesh™ DK5 N-channel Power MOSFET)
STW20N95K5 (MDmesh™ K5 N-channel Power MOSFET)
STP100N10F7 (STripFET™ F7 N-channel Power MOSFET)



STM32F334R8 (Cortex-M4 32-bit CPU with FPU core)



STGAP2D (Isolated Half-Bridge Gate Driver)
L6491 (High Voltage High and Low-Side Gate Driver)
PM8841 (Low-Side Gate Driver)



VIPER267K (Auxiliary Supply: High Voltage Converter)



KF50BD-TR (Low Drop Voltage Regulators)



TSZ121 (Operational Amplifier)



STTH512 (Ultrafast Diode)
STTH112 (Ultrafast Diode)
STTH1L06 (Low Drop Ultrafast Diode)
STPS3L60 (Power Schottky Diode)

Key products overview

Control unit & gate driving

STM32F334

32-bit Microcontroller

- Cortex-M4 at 72MHz (90DMIPS)
- HRTIMER 10ch - 217ps (4.6GHz eq)
- High-speed ADCs and Built-in analog
- T° -40/105°C



STGAP2D

Isolated half-bridge gate driver

- Functional Isolation 1700V
- 4 A Sink/Source current capability
- 3V3 / 5 V logic inputs
- Up to 26 V supply voltage



L6491

4 A half-bridge gate driver

- 600V Half Bridge
- Up to 4A gate driving current capability
- On Chip OpAmp
- Integrated Bootstrap Diode





F3 series STM32F334 – 64kB

Cortex-M4 at 72MHz (90DMIPS)

LQFP 32/48/64, T° -40..105°C

HRTIM timer is made of Hi-Resolution + Waveform Builder & Event Handler


- 217ps (4.6GHz eq.) high resolution guaranteed on all channels vs voltage, temperature or manufacturing deviation. 10-channels timer made of 6 timings units that can be cross-coupled or work independently
- Advanced PWM waveforms generation with SW minimized
 - Smart functions, such as a HW burst mode controller
 - One DMA channel per timer
 - One parameter modification can change multiple events (timer chaining)
- Complex event management: 10 external events inputs and 5 Fault inputs
- Numerous interconnect

High-speed ADCs for precise and accurate control

- 12-bit SAR – 5MSps, single-ended and diff. inputs
- Down to 21ns sampling time
- Multiple triggers for PWM

Built-in analog for protection and signal conditioning

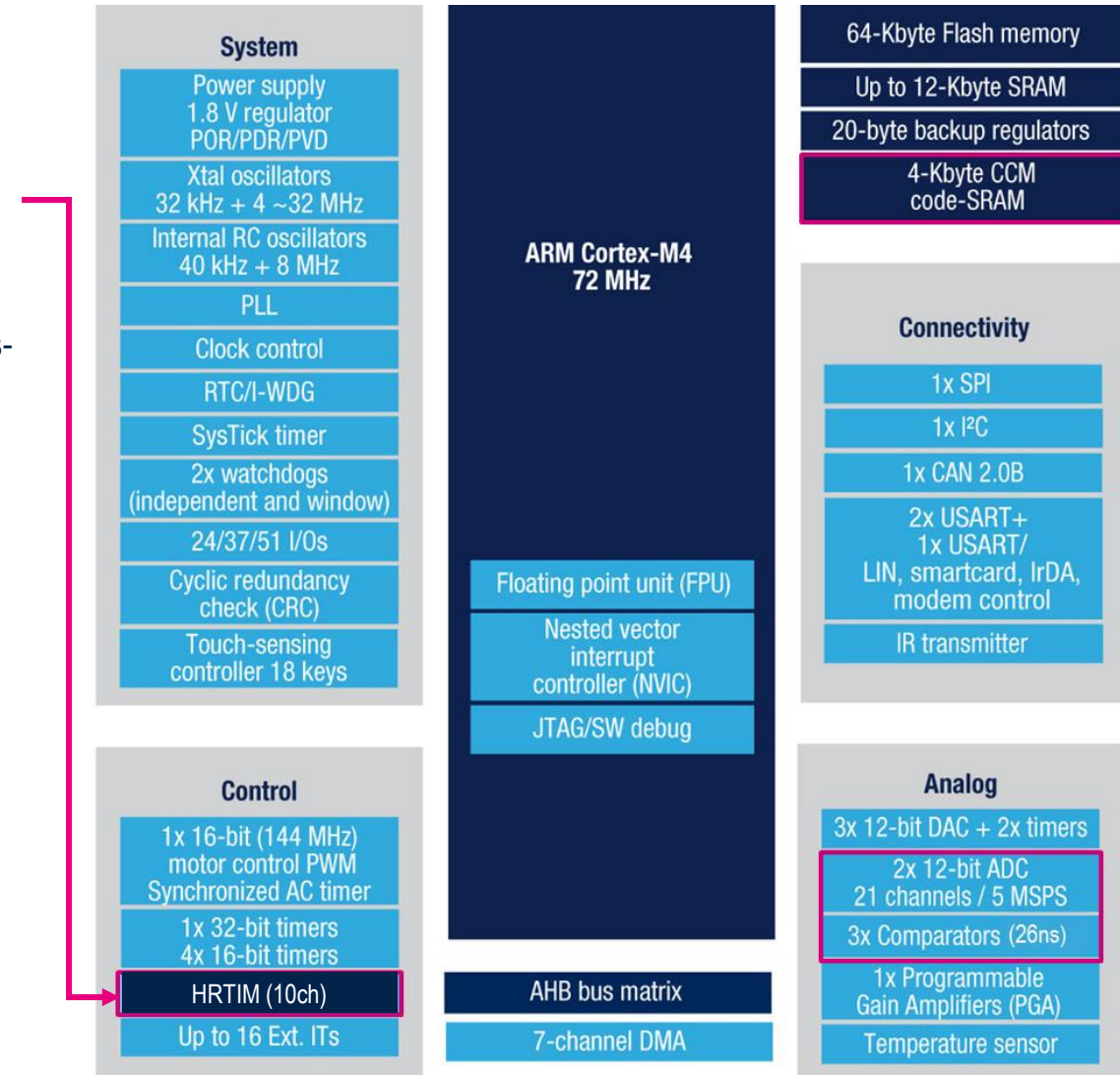
- Ultra Fast comparators (26ns)
- Op-Amp with built in Gain (PGA)





STGAP2D isolated half-bridge gate driver

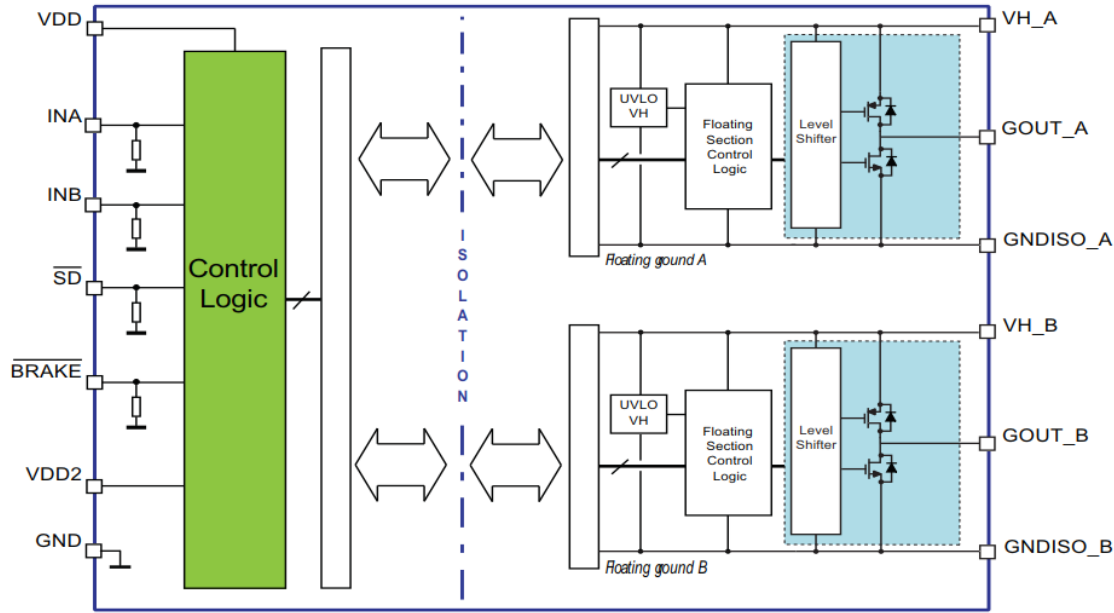Functional Isolation 1700 V, 4 A half-bridge gate




- 3V3 / 5 V logic inputs (logic thresholds 1/3, 2/3 of VDD)
- **Up to 26 V supply voltage**
- **4 A Sink/Source current capability**
- Short propagation delay: 80 ns
- UVLO Function
- Stand-by function
- 100 V/ns CMTI
- Functional Isolation up to 1700 V
- Temperature shut-down protection

Key applications

- Motor control
- Factory automation
- Industrial drives and fans
- DC-DC converters
- Induction heating
- Welding

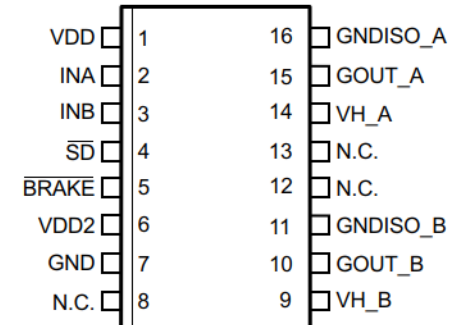- Single input pin, in phase with output
- Shut-Down SD pin, with integrated pull-down
- BRAKE pin
- Interlocking
- Negative gate drive ability
- SO16 Package





L6491 half-bridge gate driver

4 A half-bridge gate drivers




Embedded diode reduces BOM

Embedded features optimized for Field Oriented Control (F.O.C.) applications

Shutdown input or OCP indicator

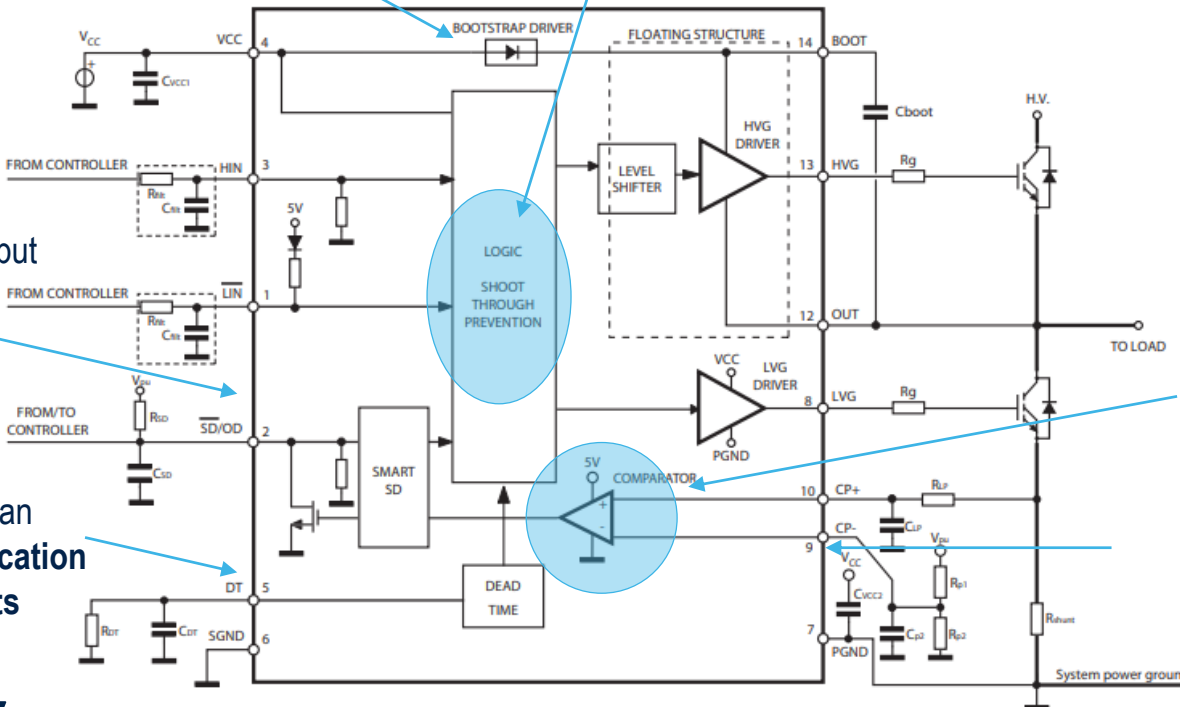Dead Time can match application requirements



Overcurrent Protection has a fast response and information is transferred to controller

OCP Threshold is externally settable

- 600 V Half Bridge
- Up to 4A gate driving current capability
- On-chip OpAmp
- Embedded Comparator
- Integrated Bootstrap Diode
- Adjustable Dead Time
- Interlocking function
- SO-14 Package

- Key applications**
- Home appliances
 - Factory automation
 - HID ballast
 - DC-DC converters
 - Induction heating
 - UPS

LCC power MOSFETs & auxiliary power supply

STW20N95DK5 N-channel power MOSFET

- Fast-recovery body diode
- $V_{(BR)DSS} = 950\text{ V}$
- $R_{DS(on)} \text{ max.} = 0.330\text{ Ohm}$
- $I_D = 18\text{ A}$



Viper267K High voltage converter


- 1050 V Avalanche Rugged Primary MOSFET
- Embedded HV Start Up (800 V)
- PWM Current Mode Controller
- $IDLIM = 700\text{ mA}$





MDMesh DK5 STW20N95DK5 950 V, 330 mΩ, 18 A

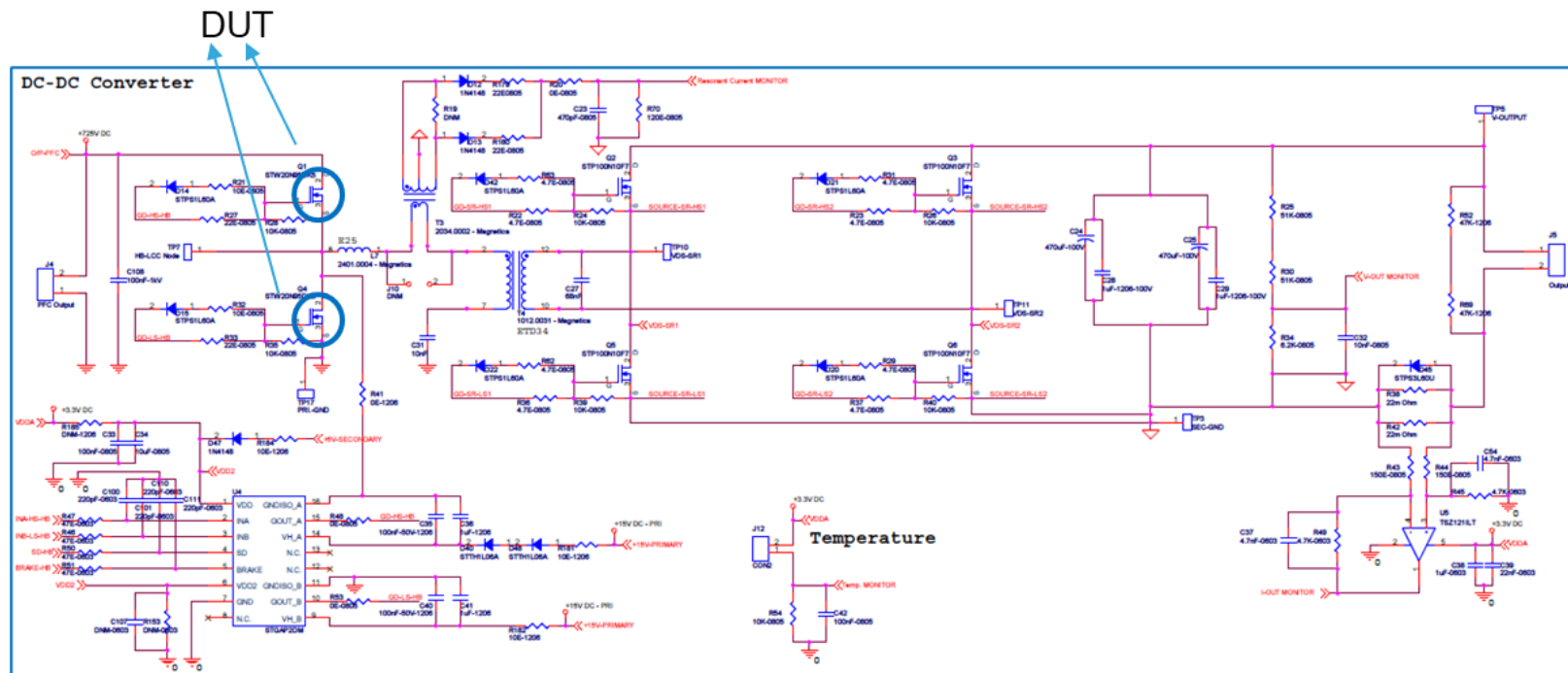STEVAL-LLL009V1: LCC Stage Electrical Schematic



- BVDSS 950V VHV Blocking Voltage
- Fast Recovery Body Diode
- Ideal for Bridge-based topology
- Extremely good Coss / Ciss profiles



Key applications

- Atmosphere Lighting
- Industrial Lighting
- Green House Lighting
- Hi-Bay Lighting
- Welding





NEW

VIPer26k

Make a robust SMPS for super wide range input



Key features

- 1050 V Avalanche Rugged integrated primary MOSFET
- Embedded HV start up (800V)
- PWM current mode controller
- Fixed frequency 60 with jittering
- Embedded E/A (3.3V reference voltage) for direct feedback using a resistor divider

	BV	Max R _{DS(on)}	ILIM	Fly Back
VIPER26K	1050V	8 W	500-700 mA	10W

Versatile for key SMPS topologies

- Buck converter / inductor-based topology
- Fly-back in **primary side** w/o opto-coupler
- Fly-back isolated with opto-coupler

Benefits in applications

- **Easy compliance with IEC 61000-4-2/4/5 immunity test** (8kV Burst/ 2kV Surge, 20kV Air Elect. discharge, 10kV Contact discharge) Low Stand-by : 30mW @ 230VAC
- **Low Stand-by** : 30mW @ 230VAC
- **High efficiency at light load**
- **Reduced EMI filter** thanks to the jittering
- **Protections** : Short circuit, Open loop, Thermal shutdown
- **Current Limit options (500 and 700mA)** to limit the max power and optimize the inductor/transformer size.

Isolated and non-isolated auxiliary power supply




Ecosystem

- eDesignSuite (Design, BoM , transformer design, Simulation)
- Spice Models
- Evaluation boards: Buck converter boards, Fly-back PSR isolated, Fly-back SSR Isolated



VIPer26k parameter table

Pin	Short description
GND	Controller ground and MOSFET source
N.C.	Not internally connected
N.A.	Not available for user (recommended to connect to GND)
VCC	Controller supply
FB	3.3V reference voltage / EA input for direct voltage feedback
COMP	EA output for compensation network in non isolated flyback Optocoupler connection in isolated flyback
DRAIN	1050 V FET drain

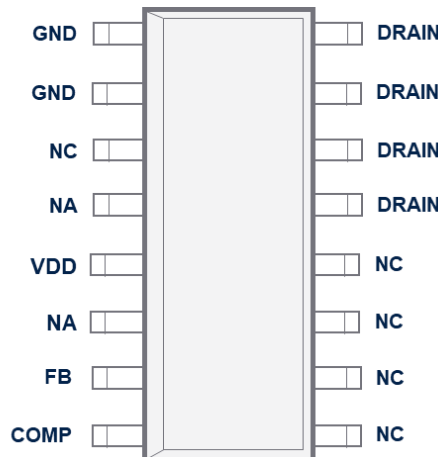


VIPer26xK

P_{OUT} @85-265V _{AC} Flyback converter 50C amb temp	10W
I_{OUT} Buck converter	250 mA (VIPER265K) 350 mA (VIPER267K)
BV_{DSS}	1050 V
R_{DSon}	8 Ω max
I_{DLIM} [mA]	500 mA (VIPER265K) 700 mA (VIPER267K)
F_{OSC} [kHz] \pm Jittering	60 kHz \pm 7%
V_{CC}	11.5V to 23.5V
$V_{DRAIN START}$	60V DC max
Package	SO16N

LCC topology fundamentals and synchronous rectification



LCC resonant converter block diagram

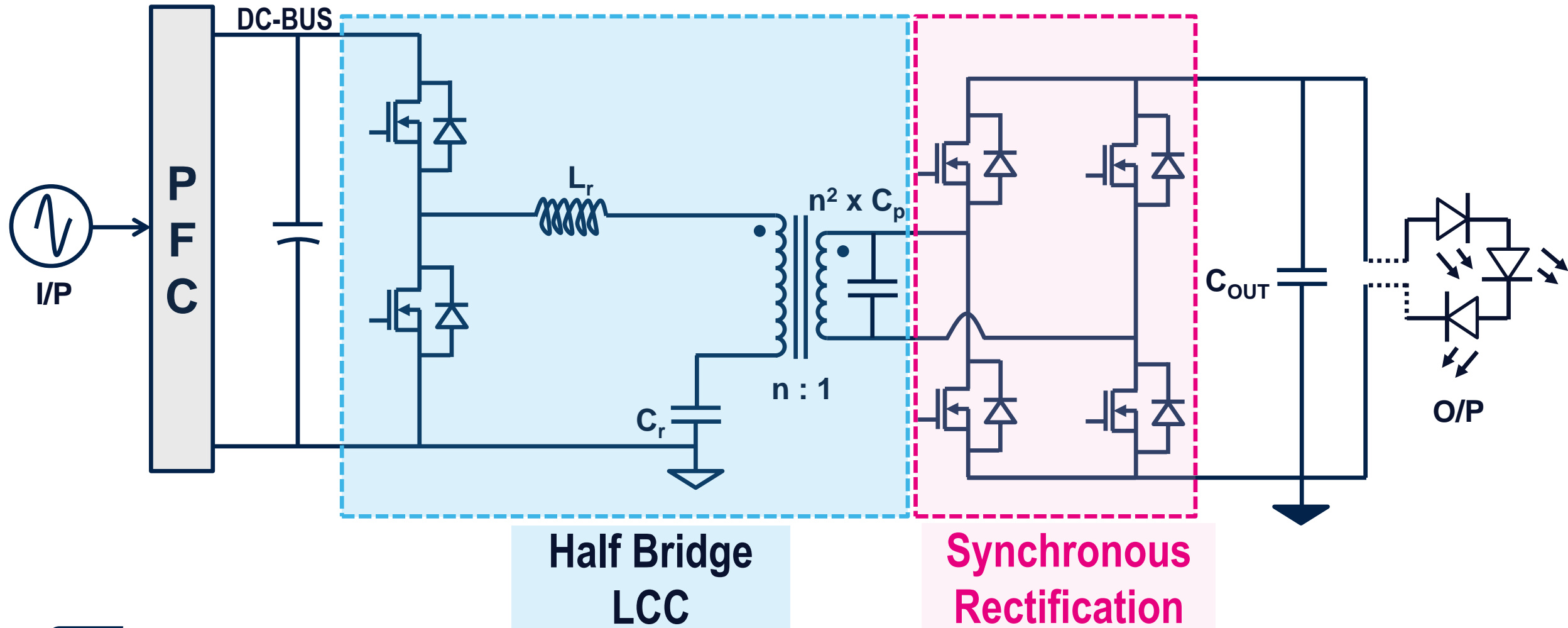

LCC resonant converter gain vs normalized frequency

$$\text{Resonant Frequency } f_r = \frac{1}{2\pi\sqrt{L_r C_r}}$$


$$\lambda = \frac{L_m}{L_r}$$

$$A = \frac{C_r}{C_p}$$

$$\text{Characteristic Impedance } Z_0 = \sqrt{\frac{L_r}{C_r}}$$

$$\text{Quality Factor } Q = \frac{1}{R_{ac}} \sqrt{\frac{L_r}{C_r}}$$


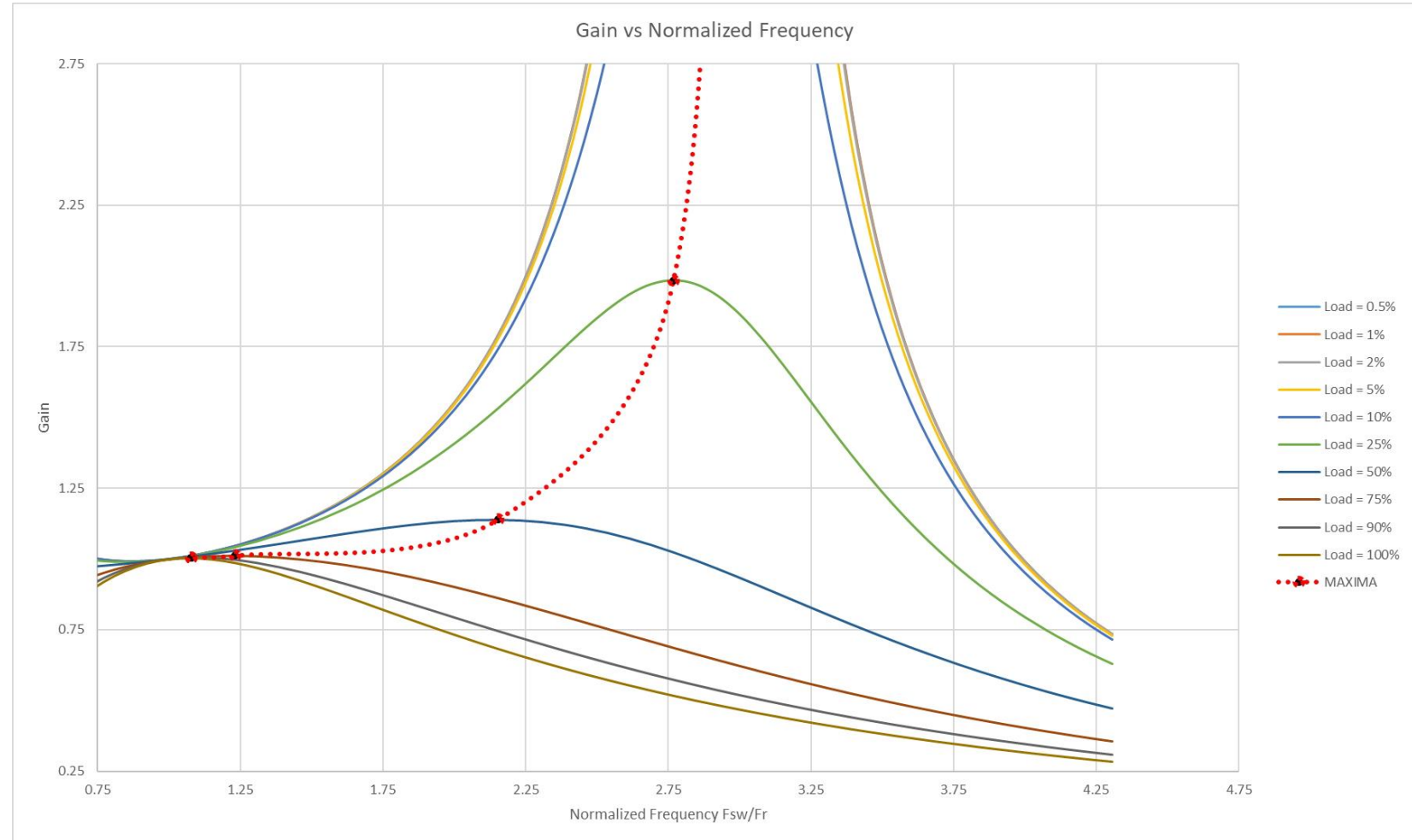
$$\text{Normalized Frequency } f_n = \frac{f_{sw}}{f_r}$$



$$\text{Mg}(f_n, Q, \lambda, A) = \left| \frac{V_o'}{V_{in}'} \right| = \frac{1}{\sqrt{\left[1 + \frac{1}{\lambda} \left(1 - \frac{1}{f_n^2} \right) + \frac{1}{A} (1 - f_n^2) \right]^2 + Q^2 \left(f_n - \frac{1}{f_n} \right)^2}}$$

LCC vs LLC resonant converter operating frequency



Frequency	LCC Converter	LLC Converter
f_{r1}	$\frac{1}{2\pi\sqrt{L_r\left(\frac{C_r C_p}{C_r + C_p}\right)}}$	$\frac{1}{2\pi\sqrt{(L_r + L_m)C_r}}$
f_{r2}	$\frac{1}{2\pi\sqrt{L_r C_r}}$	$\frac{1}{2\pi\sqrt{L_r C_r}}$
Desired Operating Region $f_{\text{operation}}$	$f_{\text{operation}} > f_{r2}$	$f_{r1} < f_{\text{operation}} < f_{r2}$

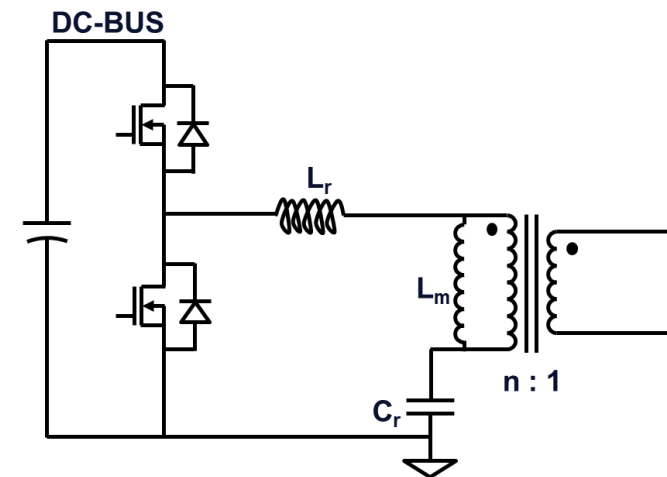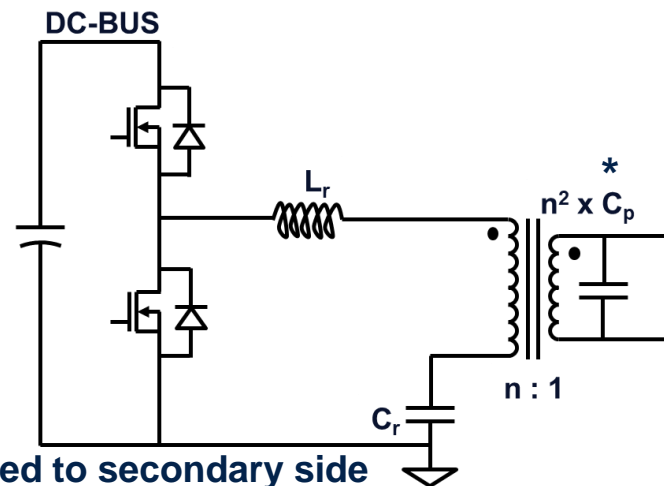


Synchronous rectification VDS sensing technique

Synchronous rectification (SR) stage node voltages (V_{DS_SR1} and V_{DS_SR2}) are sensed to drive SR stage MOSFETs.

- The sensing network is composed of a fast diode and a pull-up resistor connected to the microcontroller (MCU) supply voltage.
- When the SR MOSFET drain voltage is above the MCU V_{cc} , the diode is reverse biased and the sensed voltage is pulled up to V_{cc} .
- When drain voltage is below V_{cc} , the diode is forward biased and the sensed voltage is equal to this voltage plus the voltage drop of the diode that gives a positive shift.
- The current during positive biasing is limited by the pull-up resistor.

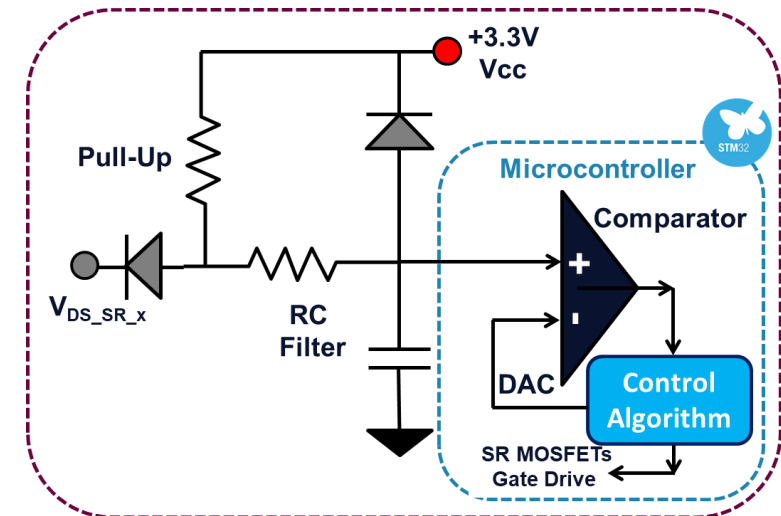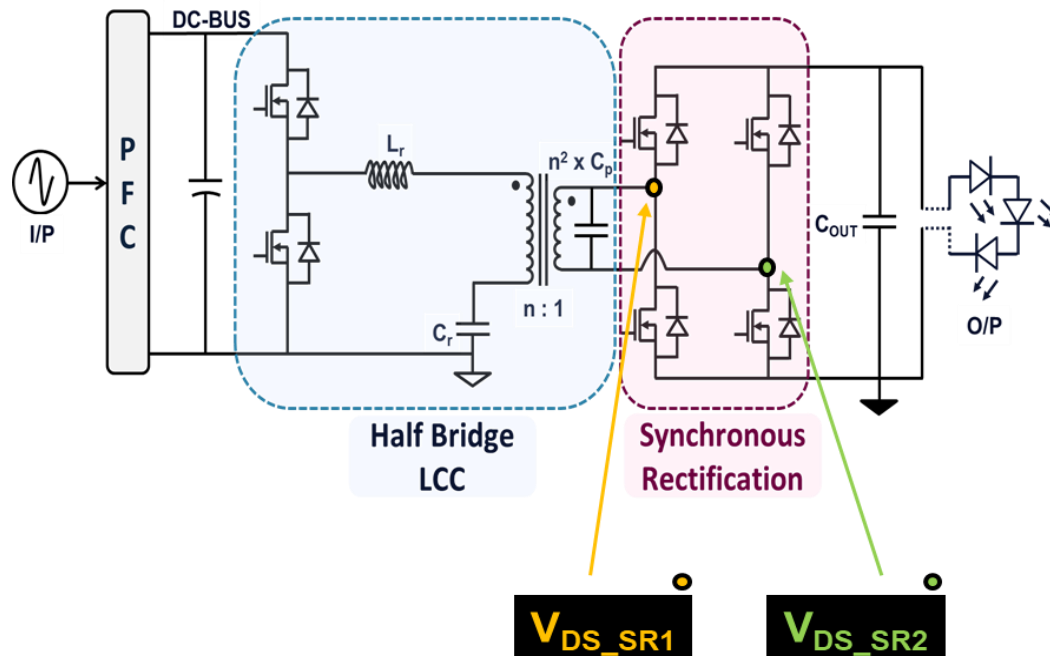

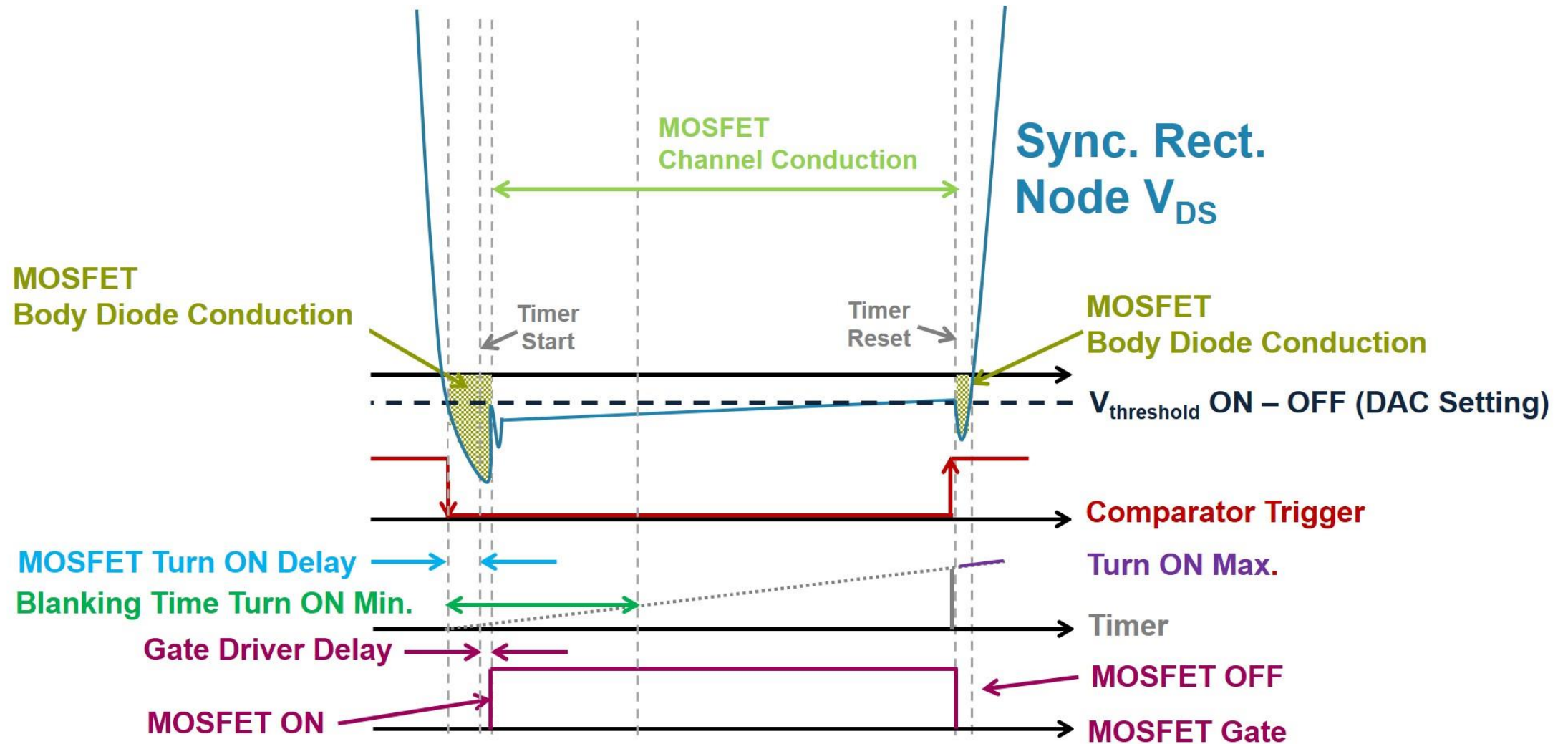Synchronous rectification digital control scheme




Efficiency, operative performance




Input voltage vs efficiency w.r.t. Load CV configuration

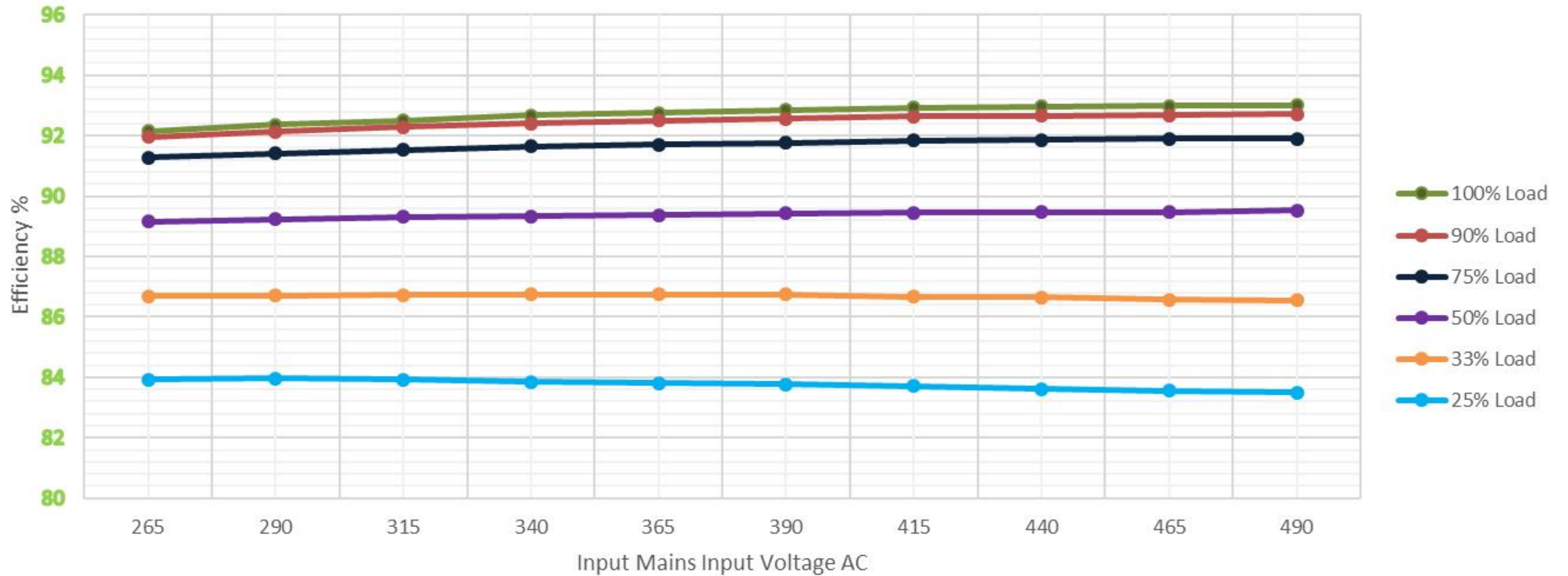Input Voltage vs Efficiency (%) w.r.t. Load




Input voltage vs power factor w.r.t. Load CV configuration

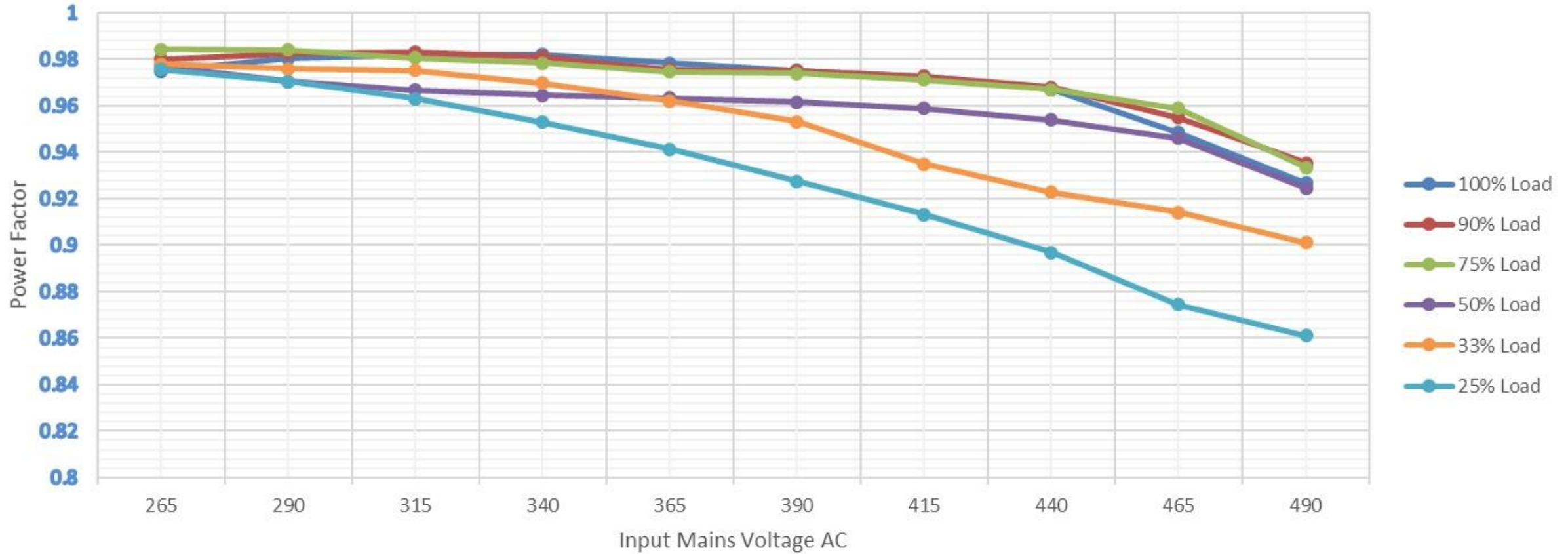
Input Voltage vs Power Factor w.r.t. Load



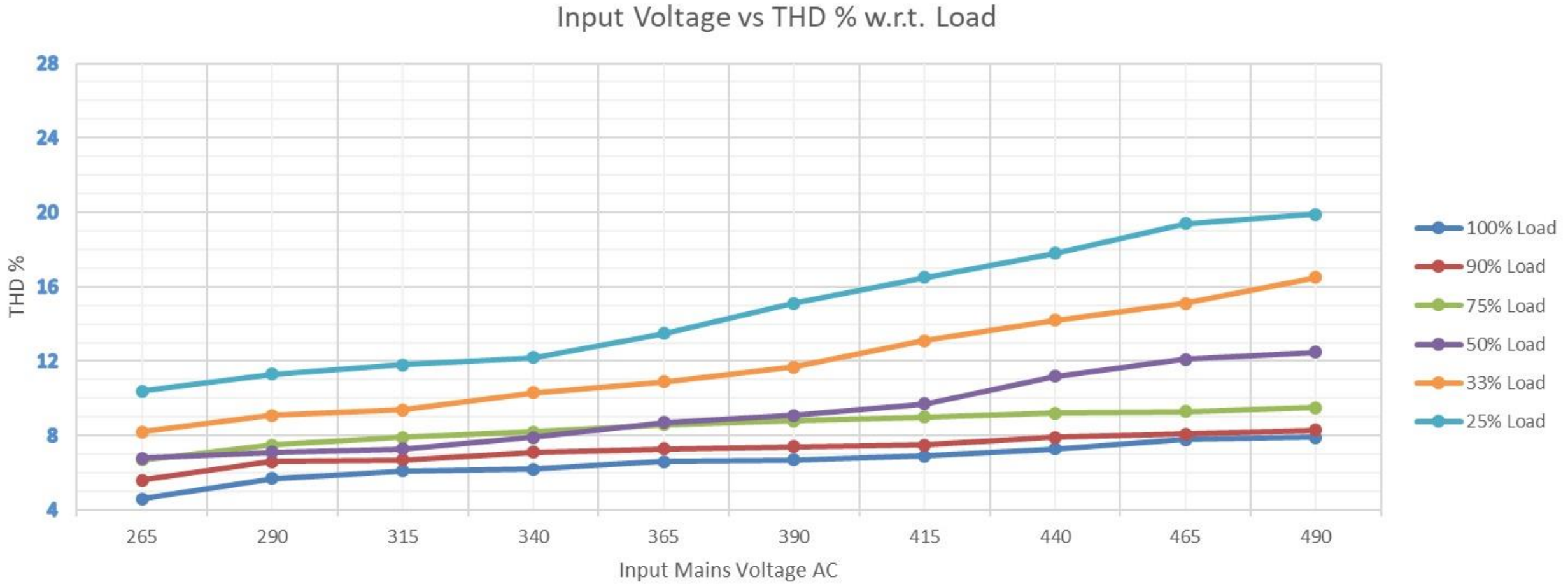
Input voltage vs THD w.r.t. Load CV configuration



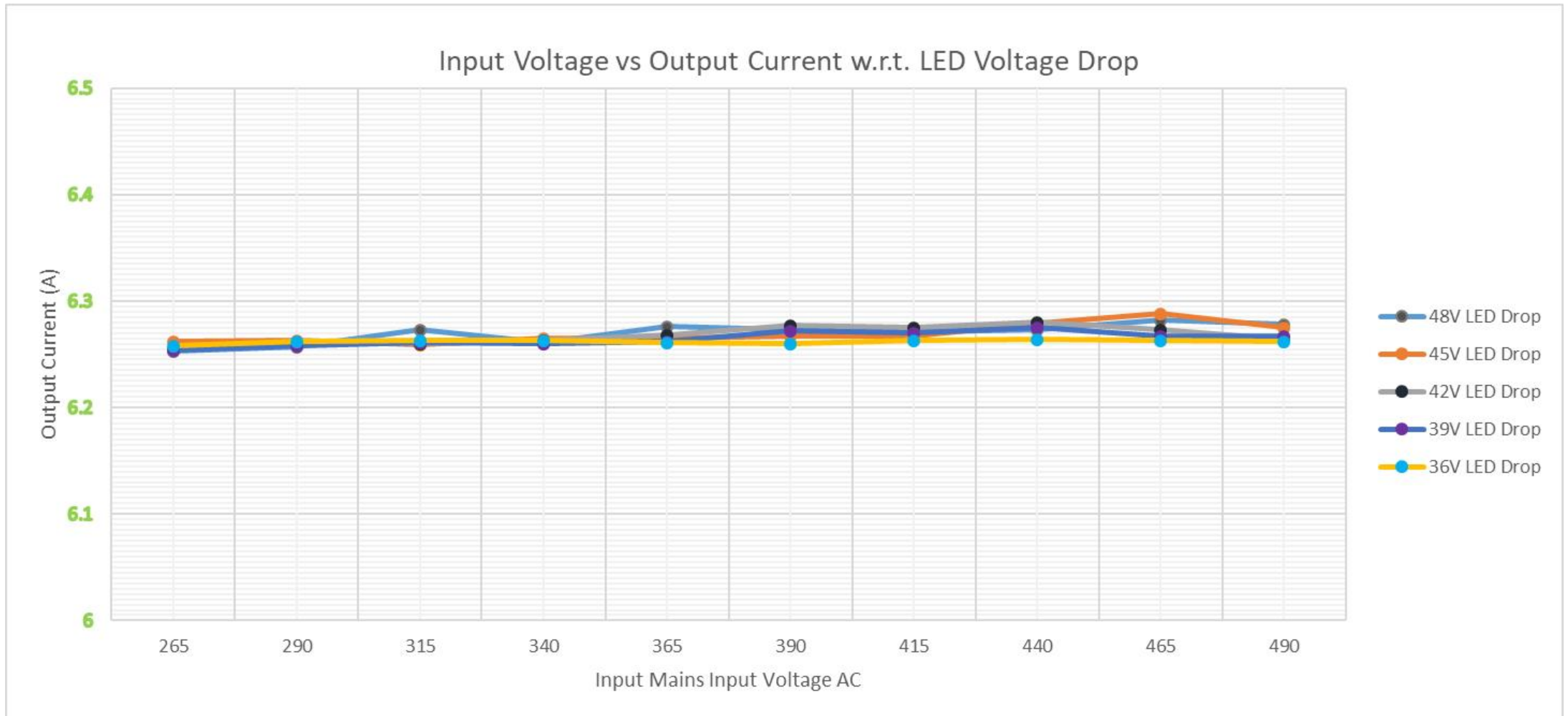Input voltage vs output current w.r.t LED drop CC configuration



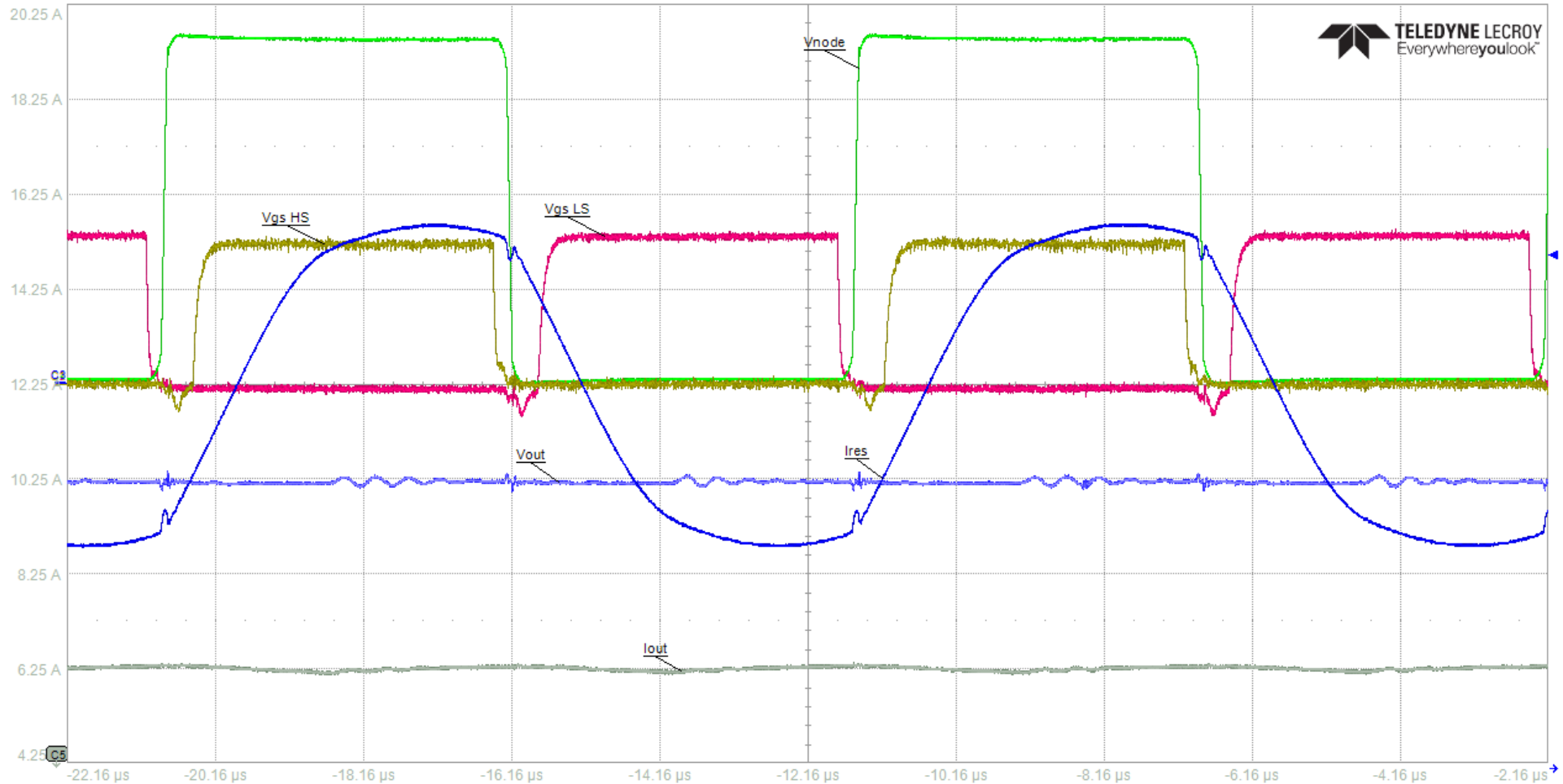
HB-LCC stage - 100% load CV configuration



Measure	P1:rms(C3)	P2:freq(C1)	P3:max(C4)	P4:rms(C5)	P5:rms(C6)	P6:mean(C7)	P7:freq(C2)	P8:dutv(C8)	P9:freq(C8)	P10:mean(C7)	P11:---	P12:---
value	1.3535 A	107.13344 kHz	737 V	6.248 A	49.130 V							
status												
C1	E B D	C2	E B D	C3	E B D	C4	E B D	C5	E B D	C6	ESR/DC1M	
	10.0 V/div		10.0 V/div		1.00 A/div		200 V/div		2.00 A/div		10.0 V/div	
	0 mV offset		0 mV offset		0.0 mA ofst		0.00 V ofst		-12.2500 A		-59.500 V	

HD	Tbase	12.16 μs	Trigger	C3 UC
12 Bits		2.00 μs/div	Stop	1.35 A
		200 kS	Edge	Positive

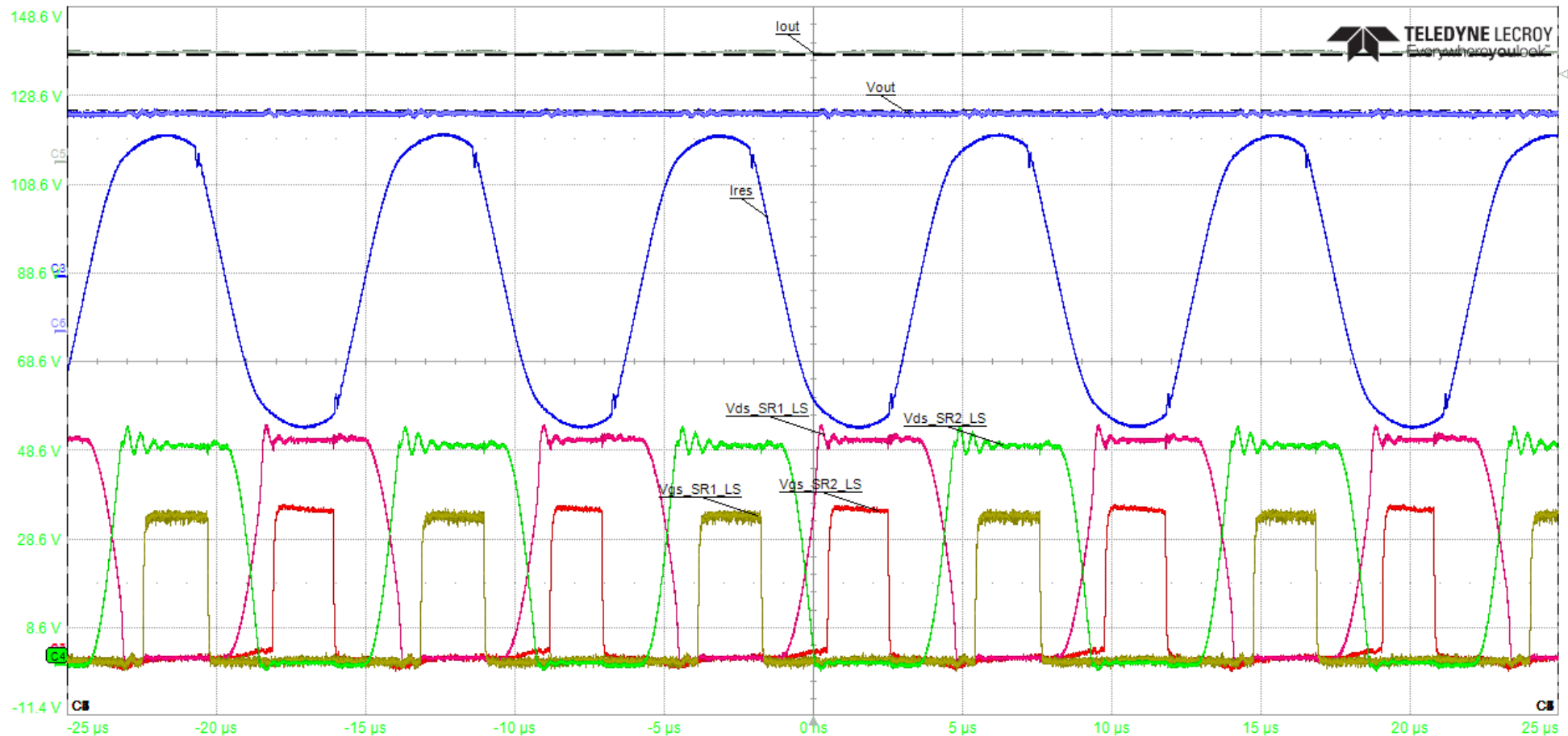Synchronous rectification with 48V output CC configuration




Measure	P1:rms(C3)	P2:freq(C1)	P3:max(C4)	P4:rms(C5)	P5:rms(C6)	P6:mean(C7)	P7:freq(C2)	P8:duty(C8)	P9:freq(C8)	P10:mean(C7)	P11:---	P12:---
value	1.2914 A	107.75701 kHz	54.0 V	6.154 A	48.97 V							
status	✓	⚠	✓	✓	✓							
C1	C2	C3	C4	C5	C6	C7						
10.0 V/div	20.0 V/div	1.00 A/div	20.0 V/div	5.00 A/div	20.0 V/div	10.0 V/div						
-33.920 V	-66.728 V	950.0 mA	-68.588 V	11.250 A	6.800 V	-33.200 V						
62.2 V	123.3 V	1.88 A	125.2 V	2.90 A	49.8 V	61.5 V						
68.4 V	135.7 V	2.50 A	137.6 V	6.00 A	62.2 V	67.7 V						
Δy 6.2 V	Δy 12.4 V	Δy 620 mA	Δy 12.4 V	Δy 3.10 A	Δy 12.4 V	Δy 6.2 V						

HD	Timebase	0.0 μs	Trigger	C5	DC
12 Bits	5.00 μs/div	Stop	5.00 A		
	500 kS	10 GS/s	Edge	Positive	
	X1= 24.9999 μs	ΔX=	-49.9999 μs		
	X2= -25.0000 μs	1/ΔX=	-20.00004 kHz		

FW architecture

Control Features

- 50 kHz PI voltage control loop.
- PWMs generation with 217 ps resolution (HRTIM).
- Startup with linear frequency decreasing to avoid current spikes.
- Start-up protection on mismatch of output voltage.
- SR based on embedded comparators and voltage sensing.
- Automatic SR activation depending on output load.
- Fast overcurrent protection with internal comparator.
- Analog watchdog on output voltage for overvoltage protection.

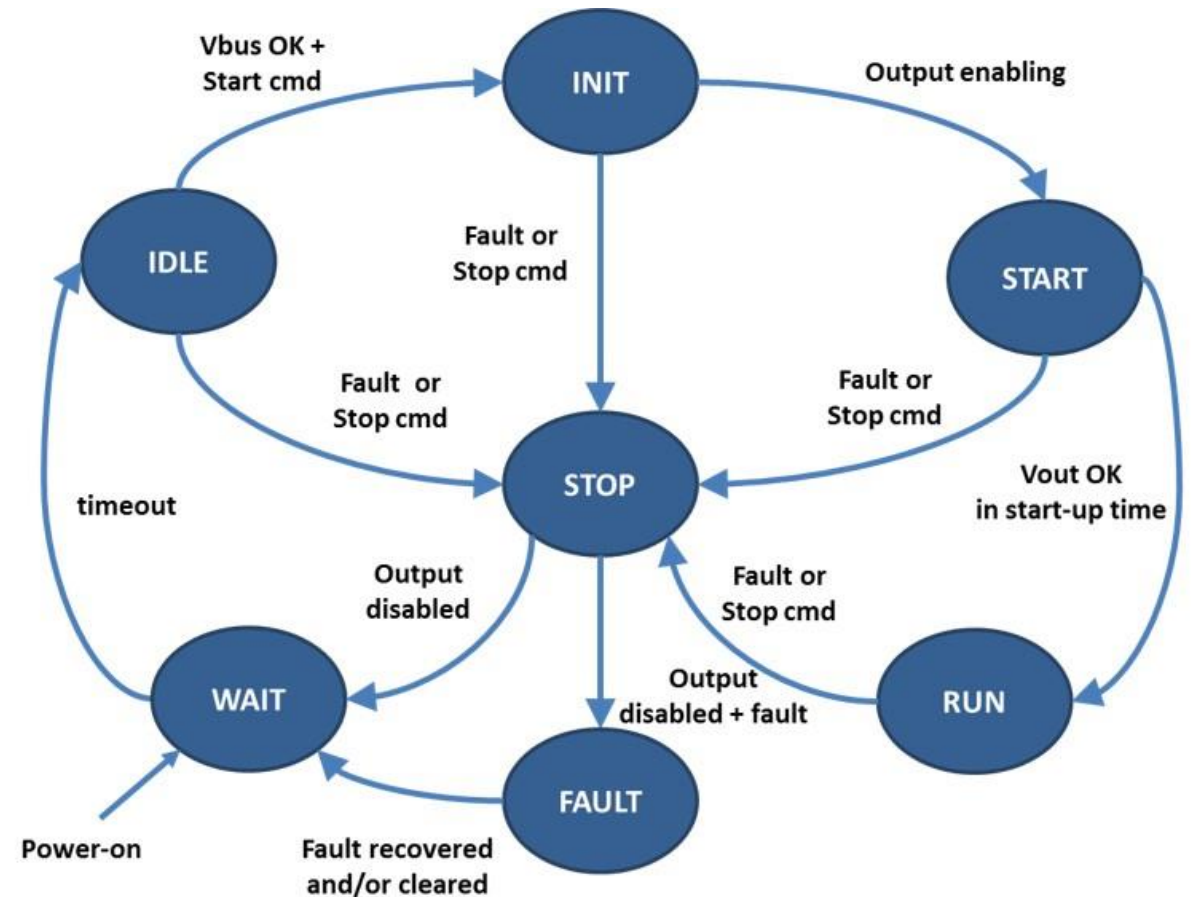

STEVAL-DPS334C1 MCU control board and adapter board

**Digital Power Supply Control
Board based on STM32F334**



STEVAL-DPS334M1

Features

- STM32F334R8 microcontroller
- 64 pin connector for control signals
- Opto-coupled serial communication (board-to-board communication)
- RC filters for analog inputs
- Diode arrays for analog signal protection (DA108S1)
- CAN, RS232, and SMBus communication channels
- External power Supply voltage: 5V
- Embedded 5V/3.3V voltage regulator
- Dedicated test points for debugging
- LEDs for power-on, faults and general purpose

Adapter board




STEVAL-DPSADP01

Features


- Enabling Debug (SWD connection)

Schematics & layout

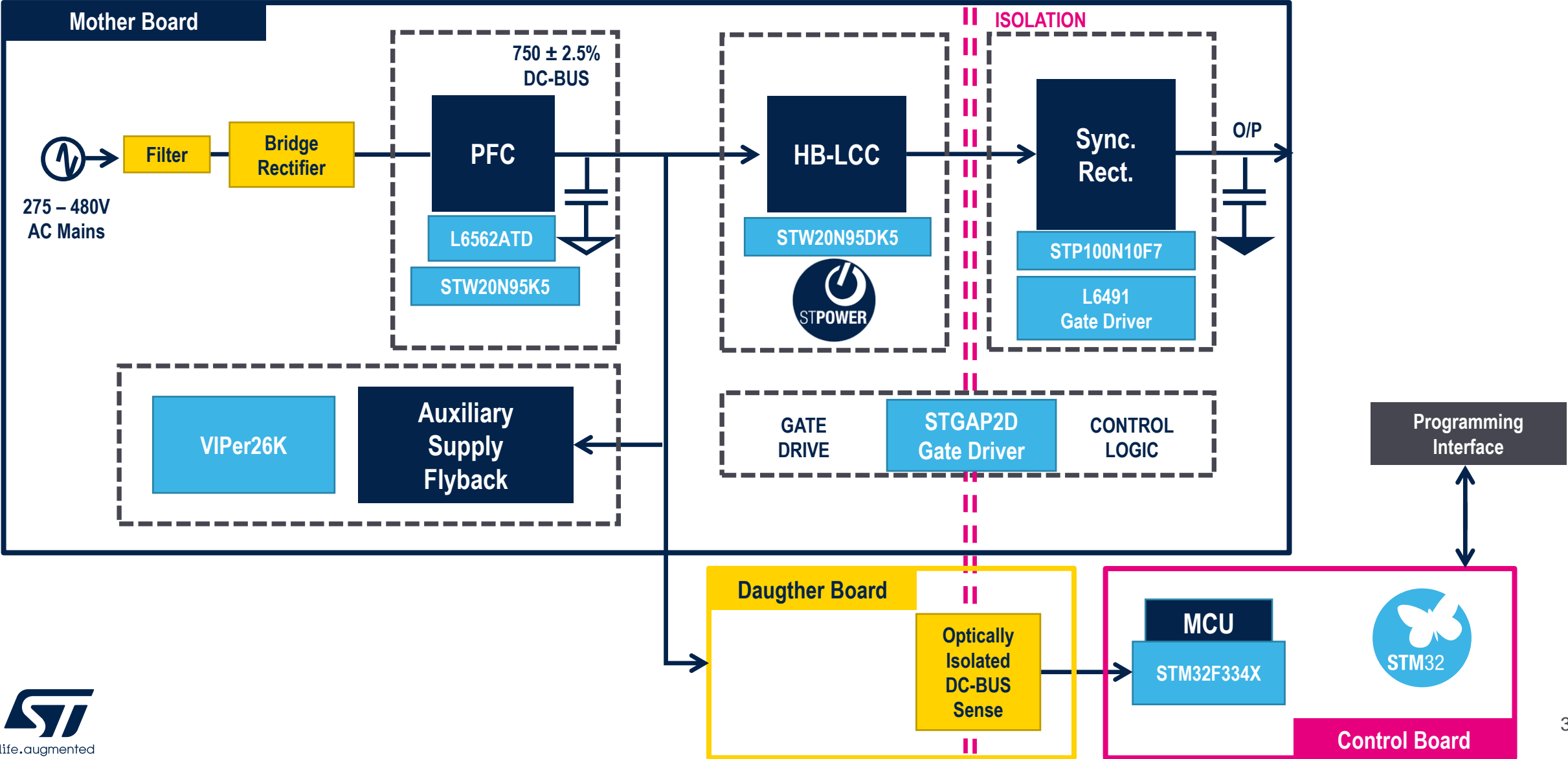
STEVAL-LLL009V1 - Evaluation boards involved




Mother board schematic: PFC section

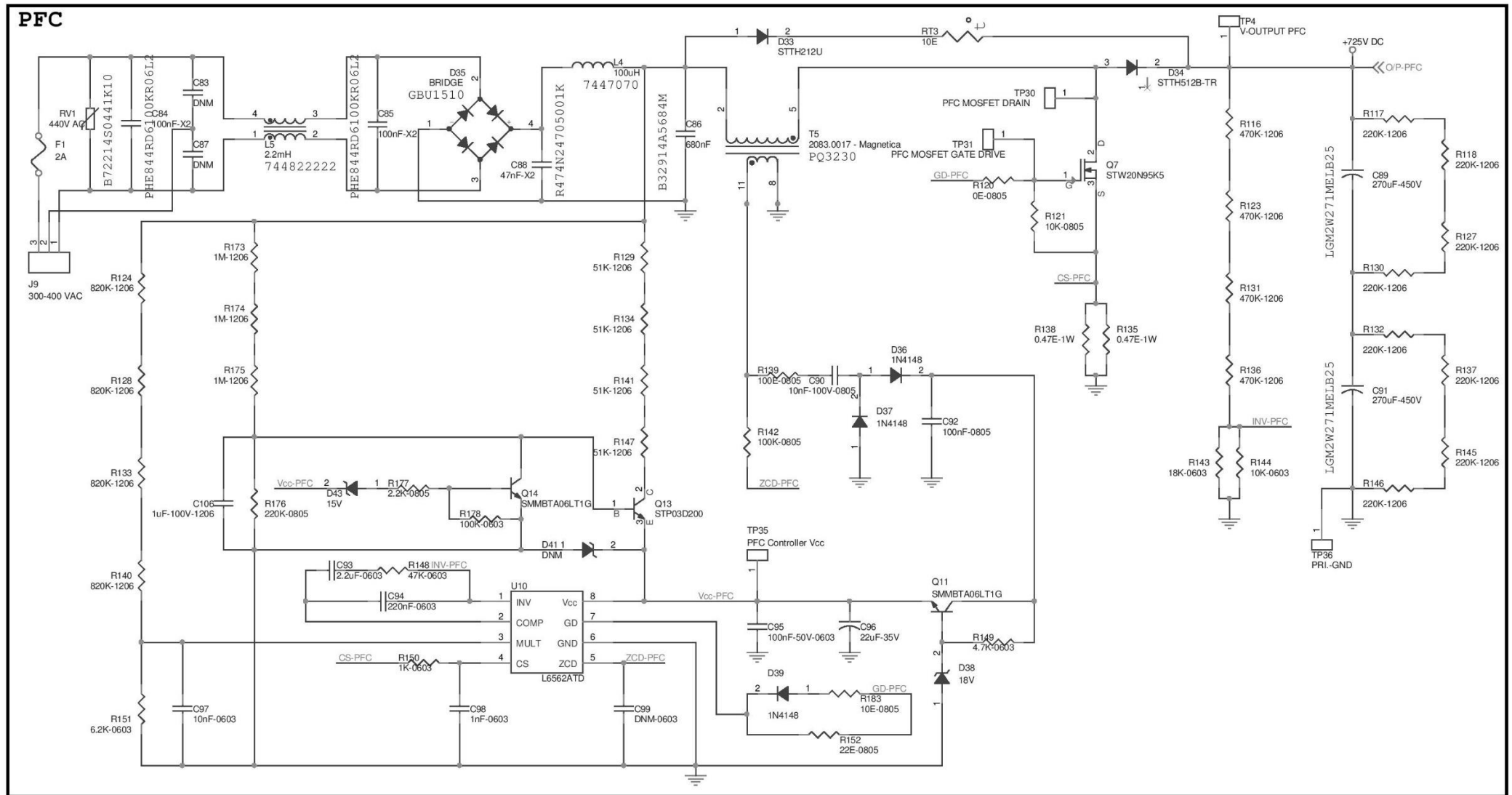


Mother board schematic: DC-DC section

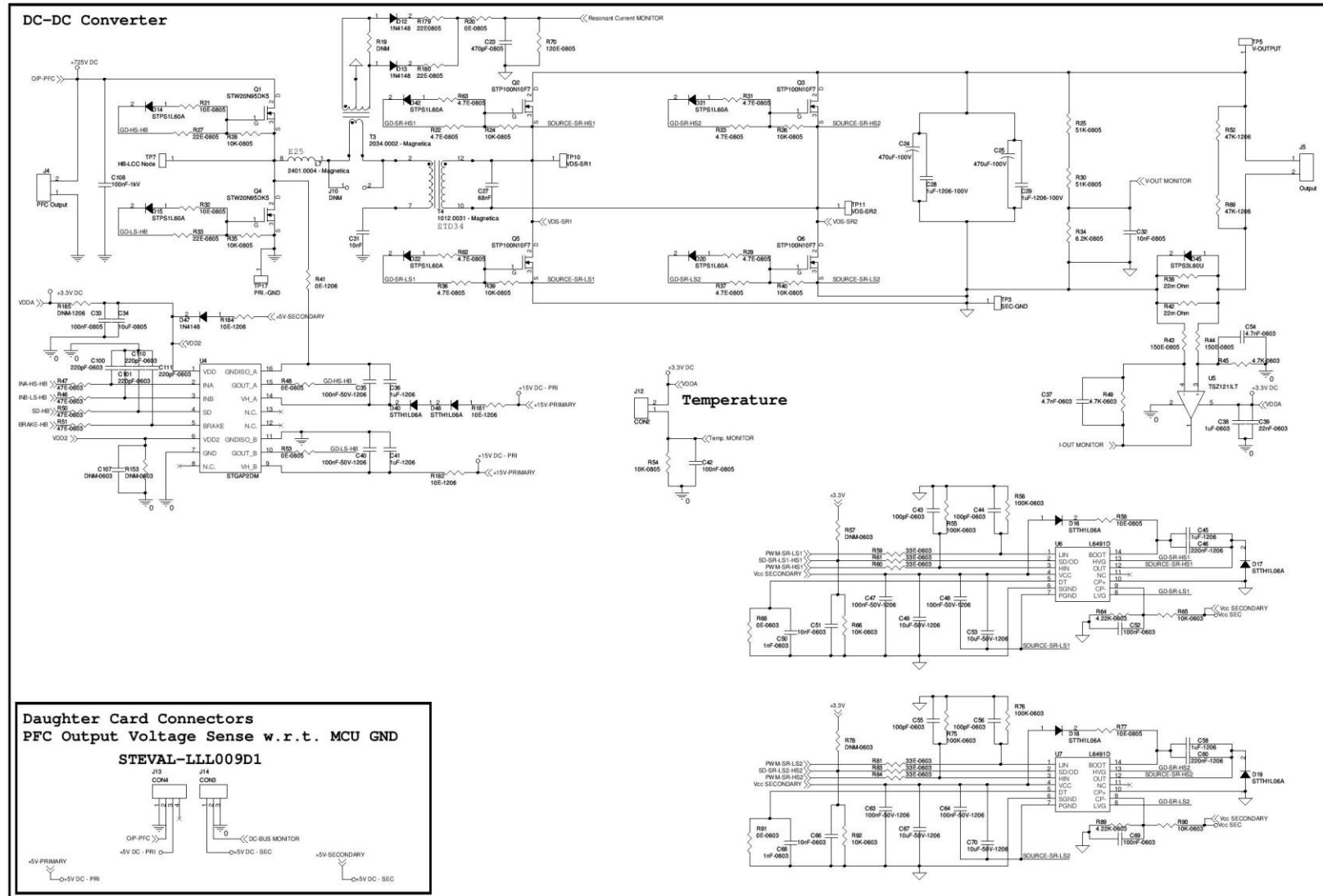


Control board schematic: MCU section

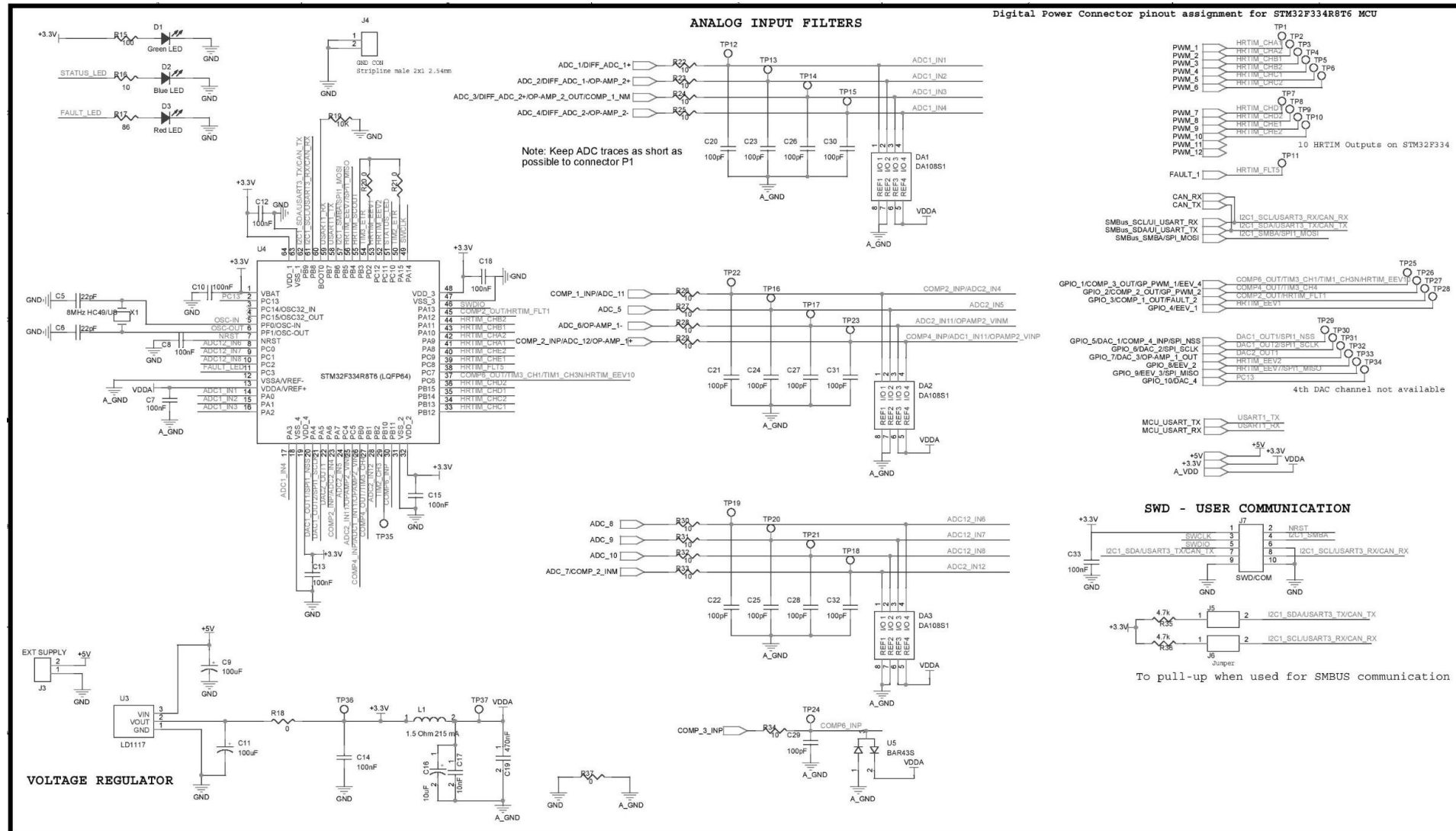

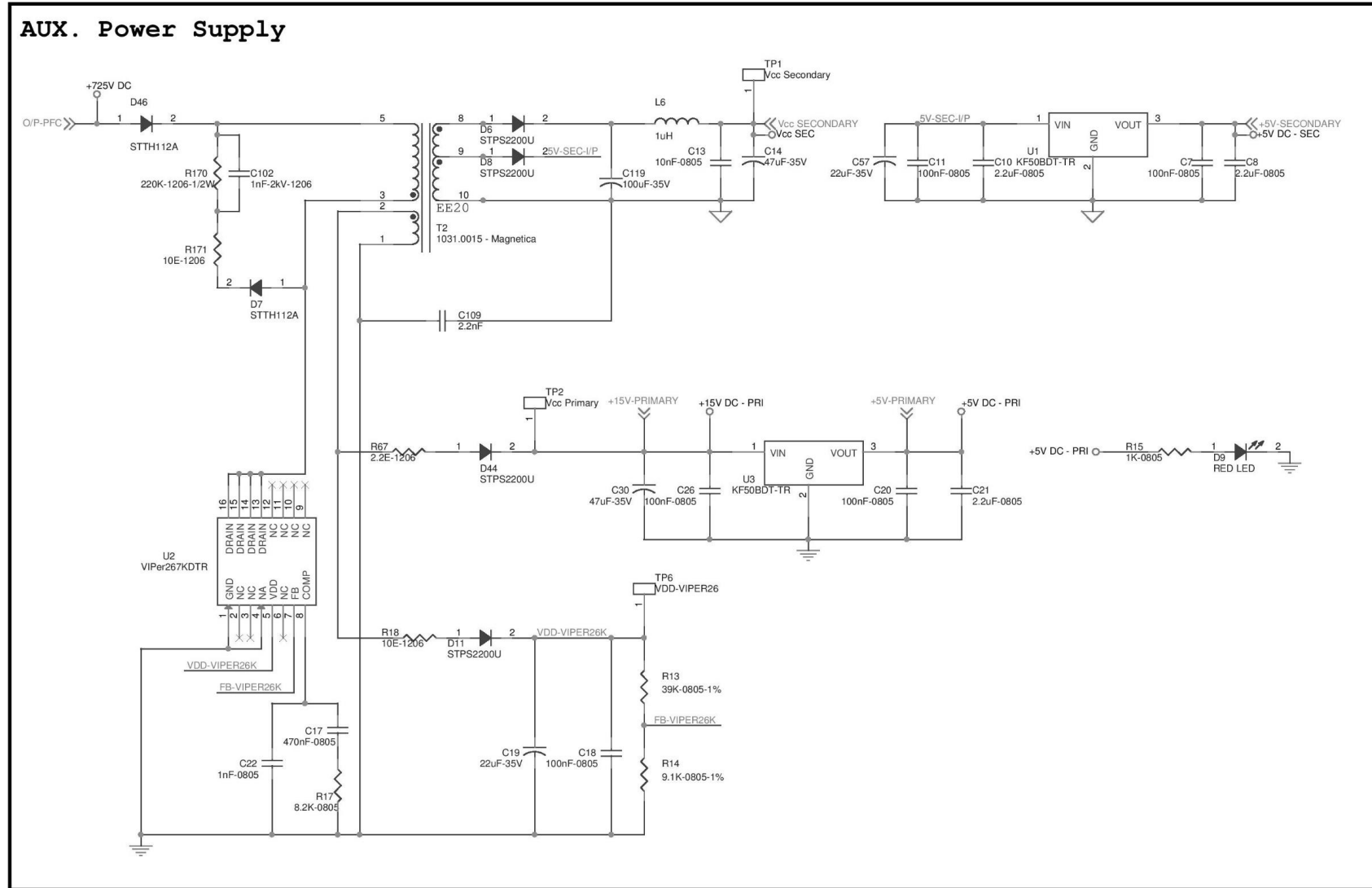
Mother board schematic: Aux. supply section



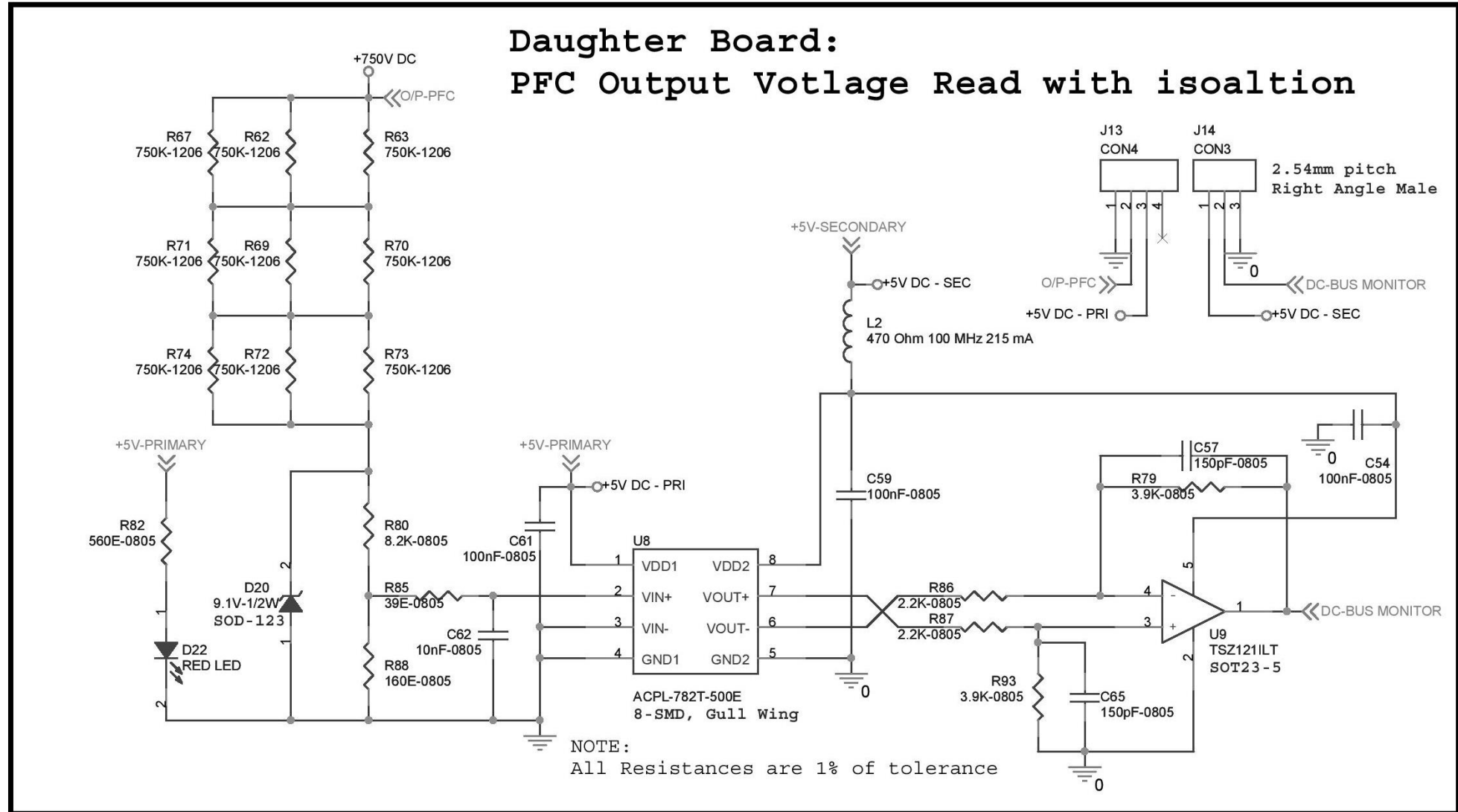
Daughter board schematic: PFC output sensing




Mother board schematic: 0 – 10 V input

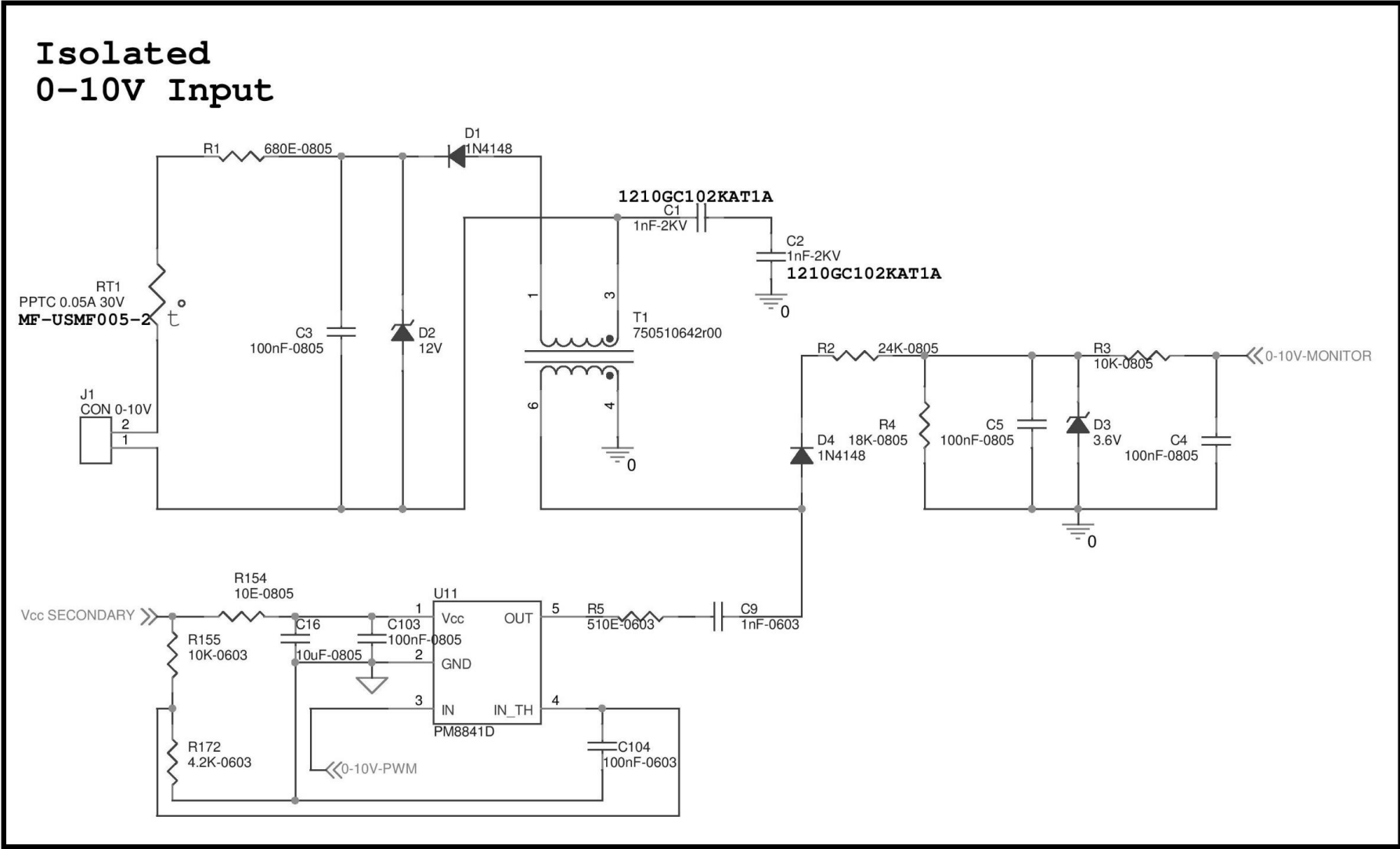

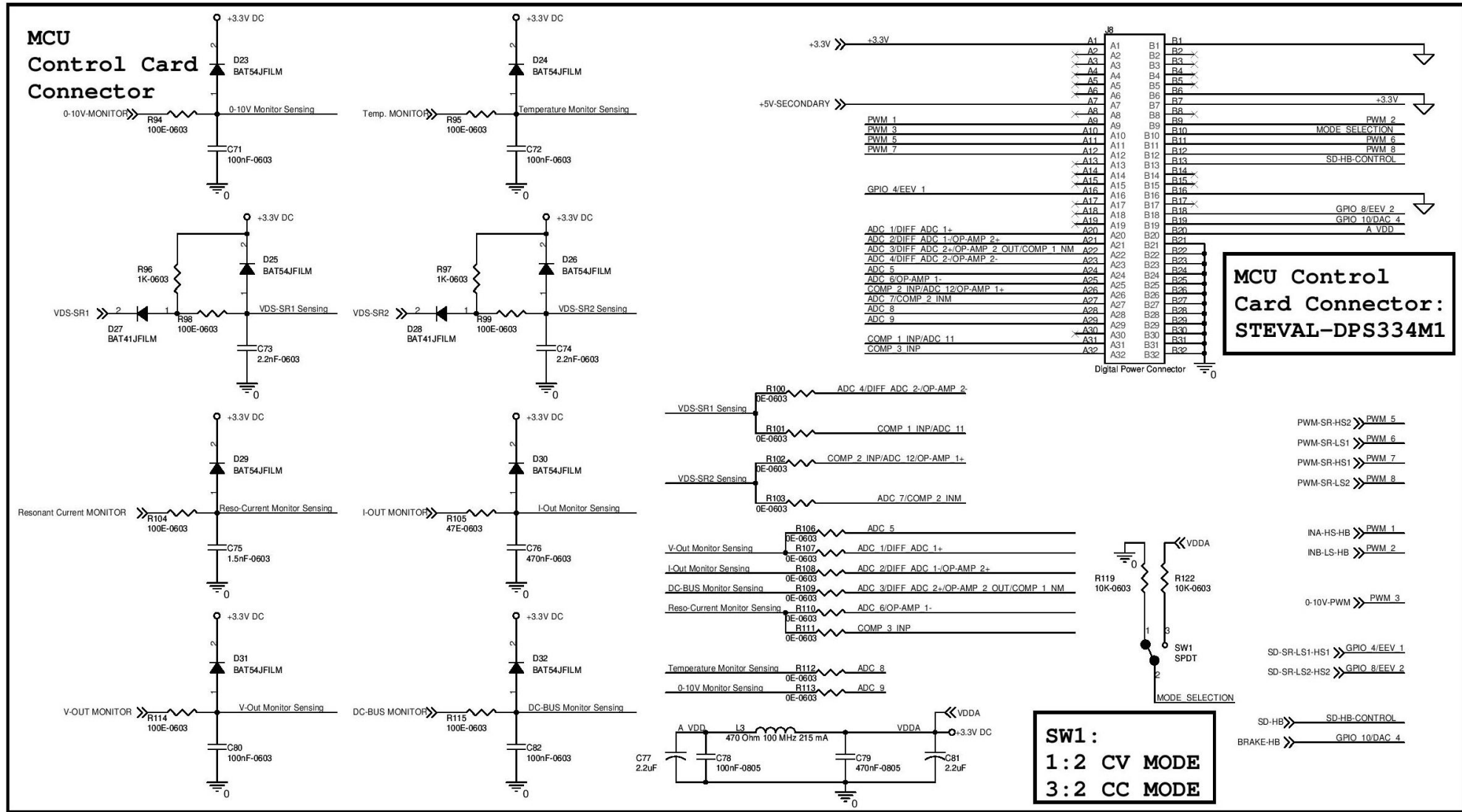
Mother board schematic: MCU card connector



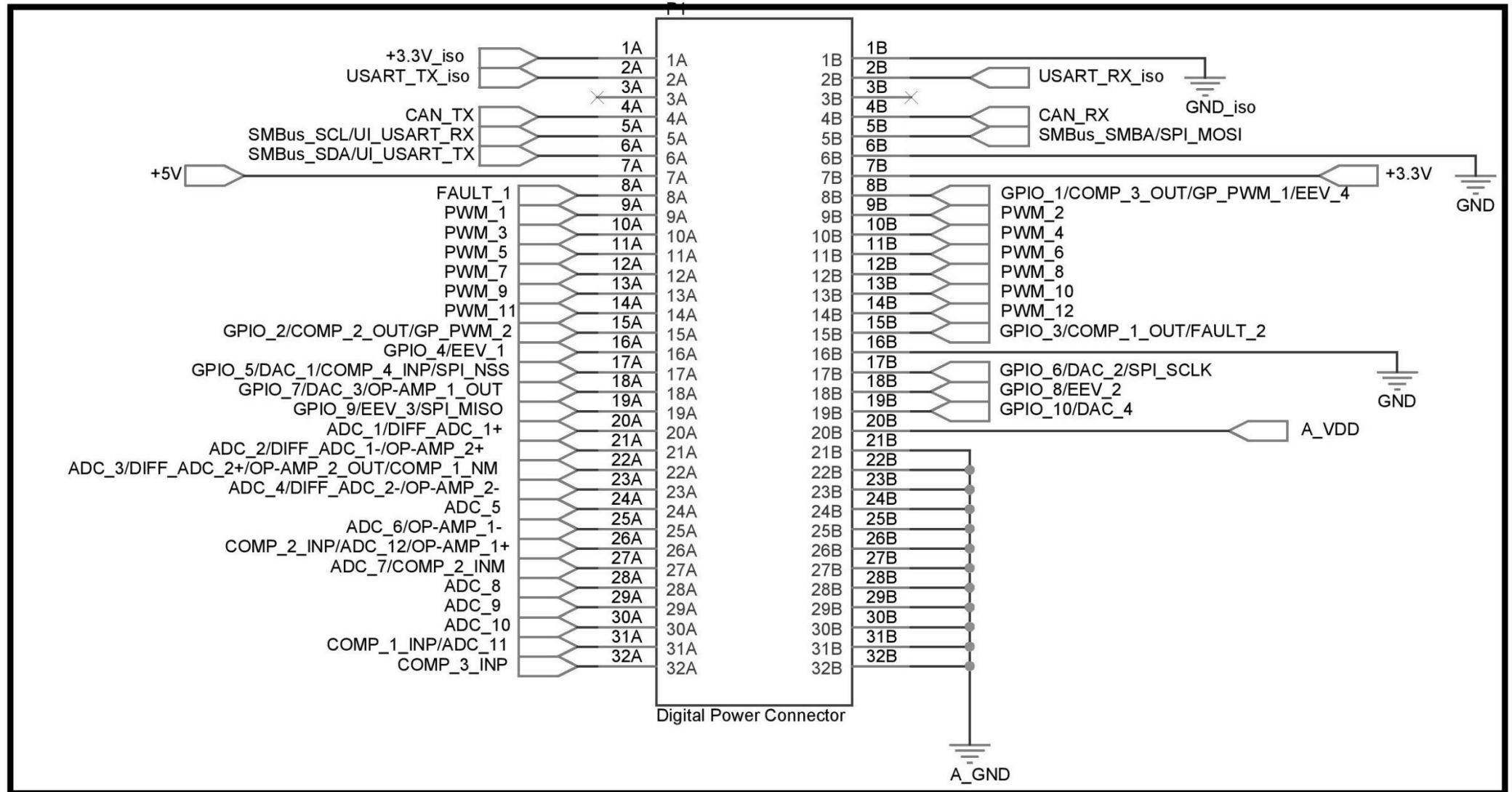
Control board schematic: MCU card connector



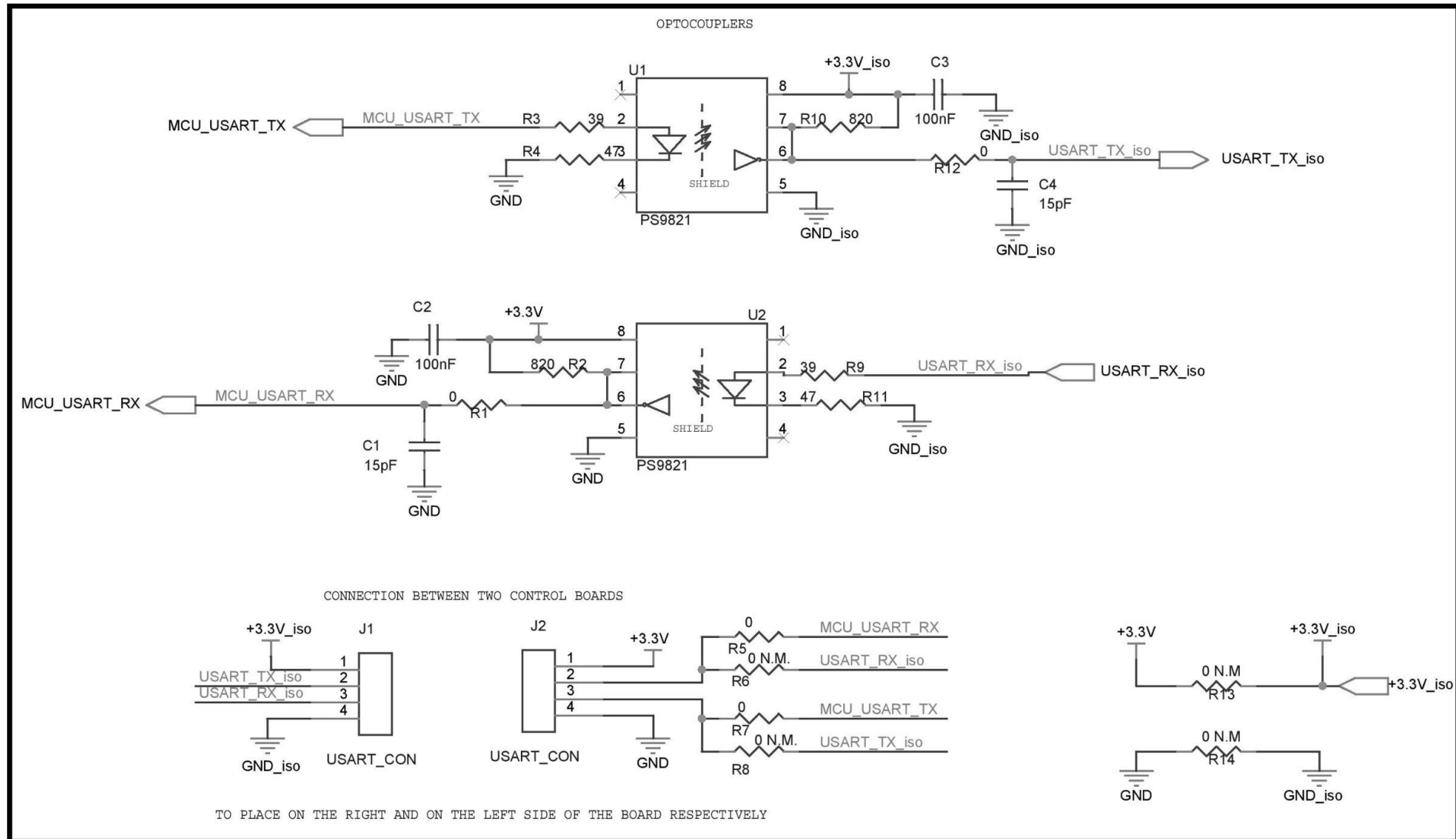Mother board schematic: USART connections



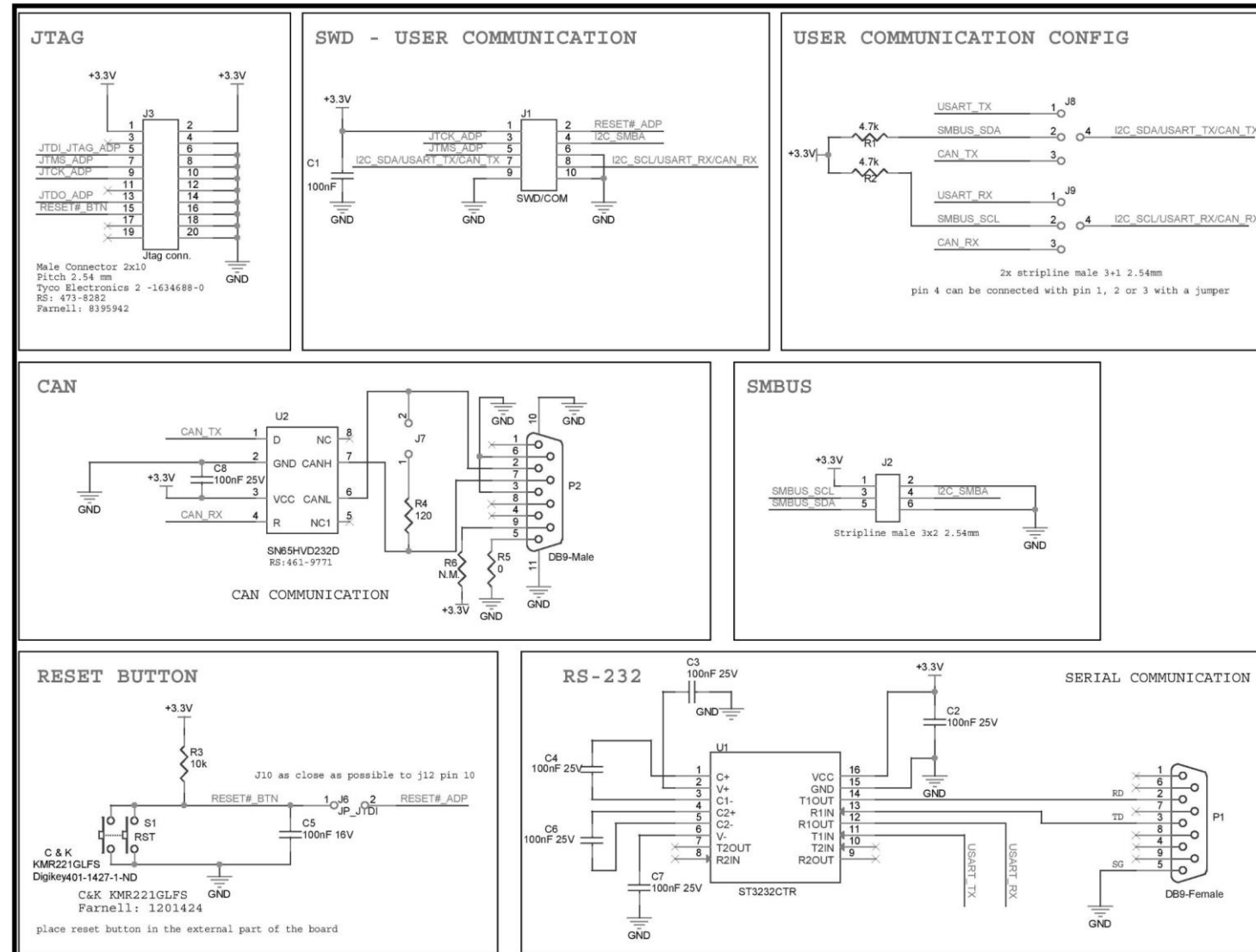Adapter board schematic: Programming connector



STEVAL-LLL009V1

300 W very high AC input voltage LED driver
with digital power control



Thank you

© STMicroelectronics - All rights reserved.

ST logo is a trademark or a registered trademark of STMicroelectronics International NV or its affiliates in the EU and/or other countries.

For additional information about ST trademarks, please refer to www.st.com/trademarks.

All other product or service names are the property of their respective owners.



life.augmented