

How to use the product evaluation board STEVAL-ISQ014V1 for low-side current sensing with the TSZ121 operational amplifier

Introduction


This document describes how to use the product evaluation board STEVAL-ISQ014V1 for low-side current sensing with the TSZ121 operational amplifier (op amp).

Power management mechanisms are found in most electronic systems and power protection is of vital importance for them. One useful method of protecting an application is by sensing the current. The low-side current sensing method consists of placing a sense resistor between the load and the ground of the circuit. The resulting voltage drop is amplified using the TSZ121.

This user manual describes how to accurately measure the current in your application and describes the advantages of the low-side current sensing method. In addition, it provides:

- the schematics of the STEVAL-ISQ014V1 evaluation board
- a method for selecting the most appropriate components for your application
- theoretical and practical results

Figure 1. STEVAL-ISQ014V1 product evaluation board

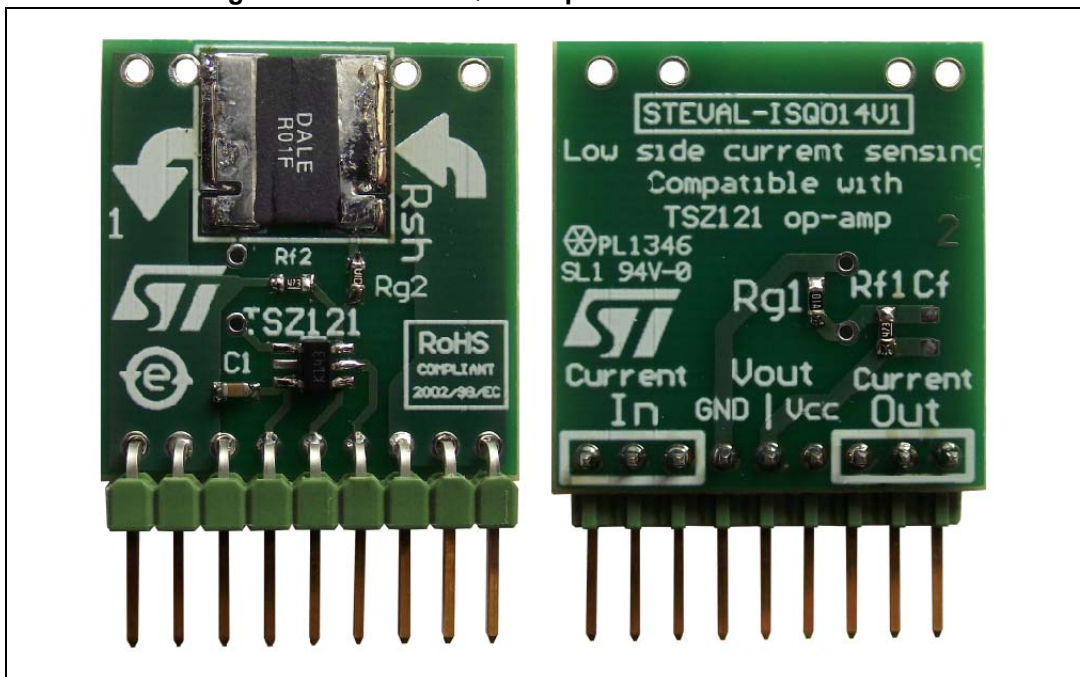

Contents

1	Advantages of the low-side current sensing method	3
2	STEVAL-ISQ014V1 product evaluation board schematic	3
3	How to choose the right components for your application	4
4	Theoretical and practical measurements	5
4.1	Theoretical measurements	5
4.2	Practical measurements	8
5	Frequency behavior	11
6	Bill of materials	12
7	Conclusion	12
8	Revision history	13

1 Advantages of the low-side current sensing method

With the low-side current sensing method, the common mode voltage of the op amp is close to ground, regardless of the voltage of the power source. Therefore, the current voltage that is sensed can be amplified by a low input rail operational amplifier (there is no need for a rail-to-rail input op amp).


The TSZ121 is a very accurate op amp, which allows you to measure the current through your application precisely with a smaller shunt value. Thus, the dissipated power is also reduced.

If you need to sense the current with the high-side sensing method, STMicroelectronics also provides the appropriate products with the TSC series.

2 STEVAL-ISQ014V1 product evaluation board schematic

Figure 2 shows the STEVAL-ISQ014V1 schematic. The voltage drop through the shunt resistor R_s , created by the current I_{meas} , is amplified by the TSZ121.

Figure 2. STEVAL-ISQ014V1 schematic

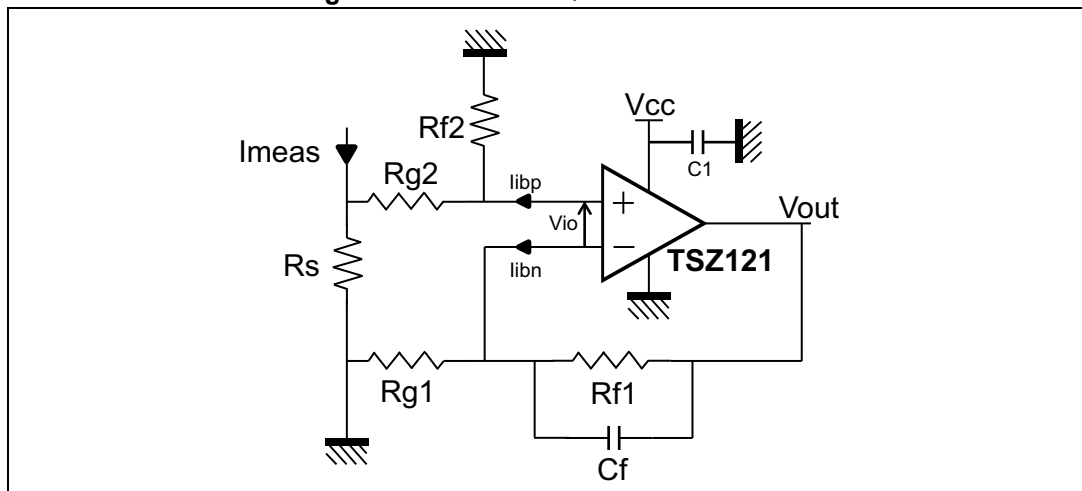

1. I_{meas} = current, R_s = shunt resistor, R_g , R_f = resistors, lib_p , lib_n = input currents, C = capacitor

The TSZ121 is a very accurate op amp which operates from 1.8 V to 5.5 V. It has a rail-to-rail configuration on both its input and output. At 25 °C, it demonstrates the following features:

- V_{io} = 5 μ V (max)
- AVD = 135 dB
- GBP = 400 kHz
- V_{ol} = 30 mV (max) with R_I = 10 k Ω

Further details on this op amp can be found at www.st.com.

3 How to choose the right components for your application

Various component values can be selected for your application. They include:

- Rshunt
- resistors for the amplifier gain

The four steps below describe how to select the correct component values.

1. Find the maximum current

This is the maximum current that goes through the sensing resistor (the maximum current to sense in your system).

Example

$$I_{max} = \text{Power}_{max} / \text{Voltage} = 5 \text{ W} / 5 \text{ V} = 1 \text{ A}$$

2. Find the correct shunt resistor

This value has to be limited to avoid a significant voltage drop (for example, 1 % of the application voltage) and to limit the power dissipation. It must, however, be high enough to obtain good accuracy.

Example

$$V_{sense_max} = 1 \% \text{ voltage, with voltage} = 5 \text{ V and } I_{max} = 1 \text{ A}$$

$$R_{shunt} \times I_{max} \leq V_{sense_max}$$

$$\Rightarrow R_{shunt} \leq (1 \% \times 5 \text{ V}) / 1 \text{ A}$$

So, Rshunt must be lower than or equal to 50 mΩ. In the current application example, Rshunt has been set to 10 mΩ.

3. Calculate the maximum power dissipation in the shunt resistor

To avoid damaging the shunt resistor itself, the shunt resistor has to sustain a suitable wattage.

Example:

$$P_{max} = R_{shunt} \times I^2 = 0.01 \times 1^2 = 0.01 \text{ W}$$

Another advantage of using the high accuracy TSZ121 op amp is that it allows you to amplify small signals while maintaining a good signal-to-noise ratio. Thus, the power dissipation is limited and the shunt resistor price is reduced.

4. Choose the appropriate configuration gain

$$V_{out} = (R_f/R_g) \times R_{shunt} \times I$$

To avoid saturation: $V_{out} \leq V_{oh} \Rightarrow R_f < (V_{oh} \times R_g)/(R_{shunt} \times I_{max})$

In the current application configuration, $R_g = 100 \Omega$ and $V_{oh} = 4.970 \text{ V}$ (TSZ121 at $25 \text{ }^\circ\text{C}$, $V_{cc} = 5 \text{ V}$).

$$\text{Therefore, } R_f \text{ max} = (4.970 \times 100)/(0.01 \times 1) = 49.7 \text{ k}\Omega$$

Consequently, R_f must be lower than $49.7 \text{ k}\Omega$ to avoid saturation of the TSZ121 at maximum currents. It is recommended to choose the highest possible R_f to benefit from the output voltage capability of the amplifier. Selecting R_f in the E24 series leads to an R_f of $47 \text{ k}\Omega$.

To minimize the offset caused by the input currents, the feedback resistors must be minimized. The higher the R_f , the higher the error due to I_{io} (see [Section 4.1: Theoretical measurements](#)). An R_g of 100Ω must be considered (the lower R_g , the lower R_f) but, R_f should not be so low that the output saturation voltages cannot be increased.

Note: If the accuracy obtained is not sufficient, go back to step 2 and increase the R_{shunt} value.

4 Theoretical and practical measurements

4.1 Theoretical measurements

C_f can be ignored for the DC analysis.

[Equation 1](#) can be calculated using [Figure 2](#) as a reference for the components.

Equation 1

$$V_{out} = R_s \times I \times \left(1 - \frac{R_{g2}}{R_{g2} + R_{f2}}\right) \times \left(1 + \frac{R_{f1}}{R_{g1}}\right) + I_{ibp} \times \left(\frac{R_{g2} \times R_{f2}}{R_{g2} + R_{f2}}\right) \times \left(1 + \frac{R_{f1}}{R_{g1}}\right) - I_{ibn} \times R_{f1} - V_{io} \times \left(1 + \frac{R_{f1}}{R_{g1}}\right)$$

[Equation 1](#) can be simplified as [Equation 2](#) assuming that $R_{f2} = R_{f1} = R_f$ and $R_{g2} = R_{g1} = R_g$.

Equation 2

$$V_{out} = R_s \times I \times \frac{R_f}{R_g} - V_{io} \times \left(1 + \frac{R_f}{R_g}\right) + R_f \times I_{io}$$

Thanks to the good matching of resistors R_f and R_g on the inputs, I_{ib} has no affect on V_{out} .

In [Equation 2](#), the only error remaining is due to V_{io} and I_{io} . The I_{io} represents the input offset current ($I_{io} = I_{ibp} - I_{ibn}$) and the V_{io} represents the input offset voltage. To obtain a precision current sensing solution, the V_{io} should be as low as possible. For the TSZ121, V_{io} is equal to $5 \mu\text{V}$ max which corresponds to a very high accuracy.

Considering the errors due to resistor inaccuracy, [Equation 3](#) is obtained.

Equation 3

$$V_{out} = V_{th} \times \left(1 + \frac{\Delta R_s}{R_s} + \frac{R_f}{R_f + R_g} \left(\frac{\Delta R_{f1}}{R_{f1}} - \frac{\Delta R_{g1}}{R_{g1}} \right) + \frac{R_g}{R_f + R_g} \left(\frac{\Delta R_{f2}}{R_{f2}} - \frac{\Delta R_{g2}}{R_{g2}} \right) \right) + R_f \times I_{io} - V_{io} \left(1 + \frac{R_f}{R_g} \right)$$

Where:

$$V_{th} = R_s \times I_x \times (R_f/R_g)$$

$\Delta R/R$ is the resistance tolerance. In the current application example, the tolerance of R_g and R_f is 0.1 % and that of R_{shunt} is 1 %.

If the accuracy of the resistors R_{f1} , R_{f2} , R_{g1} , and $R_{g2} = \epsilon_1$ and the accuracy of $R_{shunt} = \epsilon_2$, there is a maximum deviation of $(2.\epsilon_1 + \epsilon_2) \times V_{th}$ as shown in [Equation 4](#).

Equation 4

$$V_{th} \left(\frac{\Delta R_s}{R_s} + \frac{R_f}{R_f + R_g} \left(\frac{\Delta R_{f1}}{R_{f1}} + \frac{\Delta R_{g1}}{R_{g1}} \right) + \frac{R_g}{R_f + R_g} \left(\frac{\Delta R_{f2}}{R_{f2}} + \frac{\Delta R_{g2}}{R_{g2}} \right) \right) = V_{th}(2\epsilon_1 + \epsilon_2)$$

[Equation 3](#) can be simplified as [Equation 5](#)

Equation 5


$$V_{out} = V_{th}(1 + 2\epsilon_1 + \epsilon_2) + R_f \times I_{io} - V_{io} \left(1 + \frac{R_f}{R_g} \right)$$

[Figure 3](#) shows the theoretical behavior of the above defined application.

V_{out_th} , V_{out_min} , and V_{out_max} are referred to the left Y-axis.

V_{out_min} and V_{out_max} take into consideration the V_{oh} and V_{ol} errors due to input currents, V_{io} , and resistor inaccuracy. In practice, the measured values should be between the V_{out_min} and V_{out_max} curves.

Figure 3. Theoretical output voltage and error vs. I_s/I_{max}

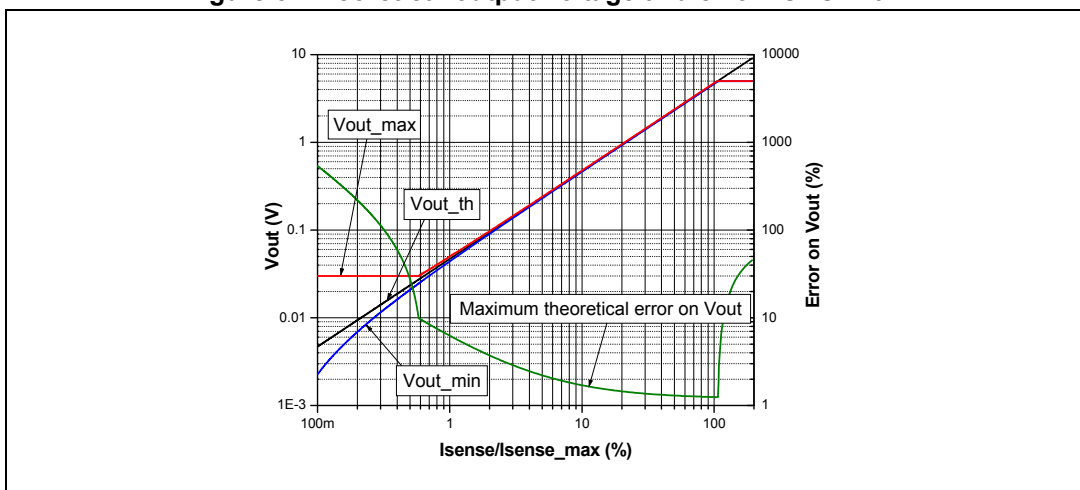

The maximum theoretical error on the output voltage (shown in green) is referred to the right Y-axis and is defined in [Equation 6](#).

Equation 6

$$\text{Error}(\%) = \frac{\text{Max}(|V_{\text{out_max}} - V_{\text{out_th}}|, |V_{\text{out_min}} - V_{\text{out_th}}|)}{V_{\text{out_th}}} \times 100$$

Example:

If $I_{\text{max}} = 1\text{A}$ with the same conditions on the resistors as shown in [Figure 3](#), the following applies:

- For $I_{\text{sense}} = 10\text{ mA}$, $I_{\text{sense}}/I_{\text{max}} = 1\%$, the maximum error on the measured voltage is lower than 7 %.
- For $I_{\text{sense}} = 70\text{ mA}$ to 1 A (7 % to 100 % of I_{max}), the maximum error on the measured voltage is lower than 2 %.

Note: When I_{sense} is used at its full scale, the offset caused by V_{io} and the input bias current is limited and the errors on the output voltage converge towards the predicted value $2 \times 0.1\% + 1\% = 1.2\%$

The accuracy of the measured value depends on the accuracy of the resistors R_f , R_g , and R_{shunt} but, also on $V_{\text{sense_max}}$ and of course the amplifier. [Table 1](#) shows the maximum error for various configurations of the TSZ121 while applying the methods described in this user manual.

Table 1. Maximum error on the measured value (depending on I_{max}) for the TSZ121

I_{max} (A)	R_s (Ω) $\epsilon = 1\%$	R_g (Ω) $\epsilon = 0.1\%$	R_f (k Ω) $\epsilon = 0.1\%$	Maximum absolute error (%)				
				$I_{\text{sense}}/I_{\text{max}}$ 1 %	$I_{\text{sense}}/I_{\text{max}}$ 3 %	$I_{\text{sense}}/I_{\text{max}}$ 10 %	$I_{\text{sense}}/I_{\text{max}}$ 30 %	$I_{\text{sense}}/I_{\text{max}}$ 100 %
1	0.05	100	9.76	2.2	1.5	1.3	1.2	1.2
2	0.02	100	12.1	2.5	1.6	1.3	1.2	1.2
3	0.01	100	16.2	2.9	1.8	1.4	1.3	1.2
4	0.01	100	12.1	2.5	1.6	1.3	1.2	1.2
5	0.01	100	9.76	2.2	1.5	1.3	1.2	1.2
7	0.005	100	14	2.7	1.7	1.3	1.2	1.2
10	0.005	100	9.76	2.2	1.5	1.3	1.2	1.2
12	0.003	100	13.3	2.6	1.7	1.3	1.2	1.2
15	0.003	100	10.7	2.3	1.6	1.3	1.2	1.2
20	0.002	100	12.1	2.5	1.6	1.3	1.2	1.2

R_s is calculated for a maximum sense voltage of 50 mV. It represents 1 % of the voltage drop for a 5 V voltage source.

4.2 Practical measurements

This section summarizes the results of several practical measurements:

- Case 1, use of the TSZ121 op amp which has a maximum V_{io} of 5 μV for $V_{cc} = 5\text{ V}$ and $V_{icm} = 2.5\text{ V}$ (see [Figure 4](#) and [Figure 5](#)).
- Case 2, use of another op amp which has a maximum V_{io} of 1 mV (see [Figure 6](#) and [Figure 7](#))

In both cases, five devices were measured on different boards using the following component values:

- $R_{shunt} = 10\text{ m}\Omega$
- $R_g = 100\ \Omega$
- $R_f = 47\text{ k}\Omega$
- $I_{max} = 1\text{ A}$

All resistors had an accuracy of 0.1 % except for the shunt resistors which had an accuracy of 1 %.

[Figure 4](#) and [Figure 6](#) show the output voltage versus I_{sense}/I_{max} (100 % means that $I_{sense} = I_{max} = 1\text{ A}$). The maximum and minimum theoretical output voltage trends are shown in red and blue respectively. These have been calculated using [Equation 3](#). The output voltage of the op amps is, as predicted, between these two trends.

[Figure 5](#) and [Figure 7](#) show the absolute error on the output voltage versus I_{sense}/I_{max} . The red trend shows the maximum theoretical error that can occur. As expected, all ST measurements are below this trend. The main error contribution is due to the V_{io} i.e. the lower V_{io} is, the more accurate the results are. This is why it is important to use a very accurate op amp such as the TSZ121.

[Figure 4](#) and [Figure 5](#) show that thanks to the TSZ121, it is possible to highly reduce the inaccuracy on the current measurement. This is especially true when there is a small signal that has to be amplified (because with the signal amplification, an error due to the amplification of the V_{io} is added).

Figure 4. Output voltage vs. I_{sense}/I_{max} using the TSZ121

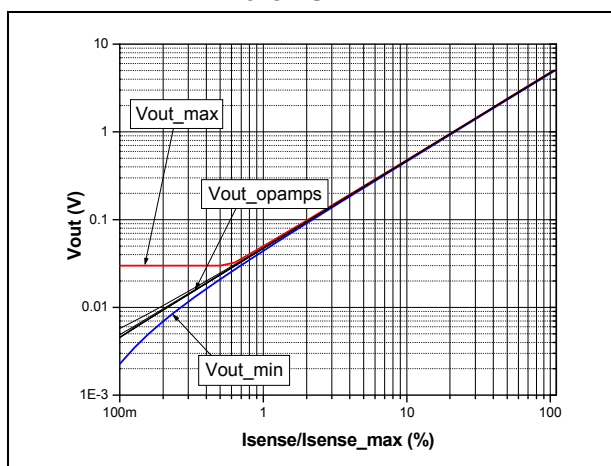


Figure 5. Absolute error on the output voltage vs. I_{sense}/I_{max} using the TSZ121

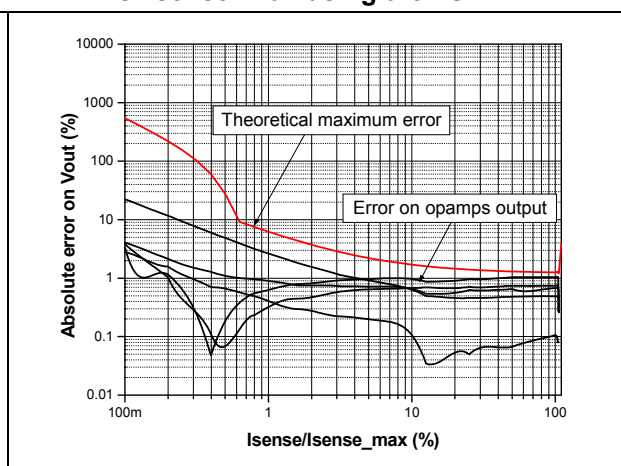


Figure 6. Output voltage vs. I_{sense}/I_{max} using an alternative op amp

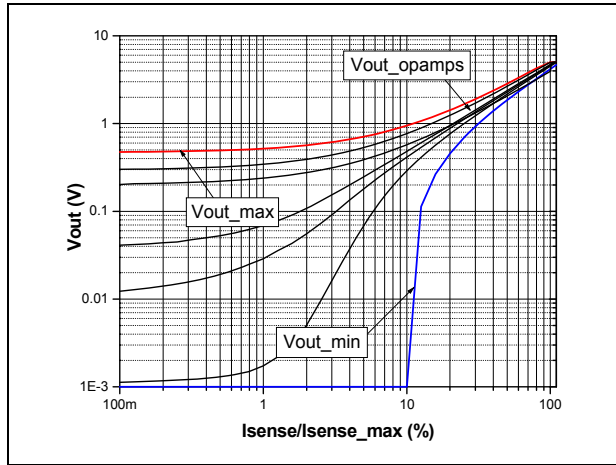


Figure 7. Absolute error on the output voltage vs. I_{sense}/I_{max} using an alternative op amp

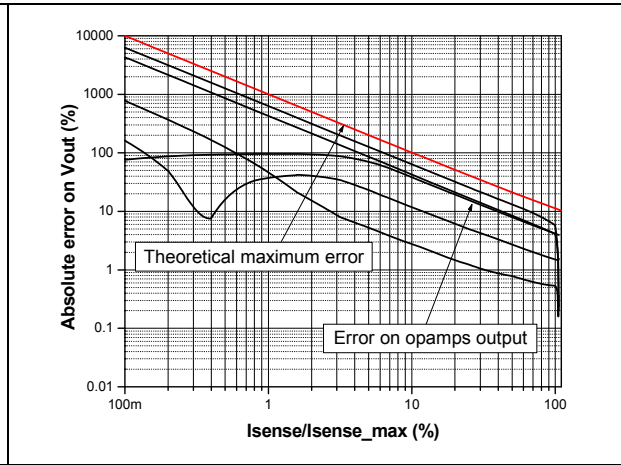


Figure 8 and Figure 9 show the error contribution of each parameter to overall error for case 1 and case 2.

For a low I_{sense}/I_{sense_max} the error is mainly due to the saturation. When I_{sense}/I_{sense_max} increases, the error is mainly caused by the V_{io} . After this, the most significant error contribution is caused by the inaccuracy of the shunt resistor. Finally, when I_{sense}/I_{sense_max} is high, close to or above the upper rail of the amplifier, the maximum error contribution is the saturation.

Figure 8. Contribution of each parameter to overall error for the TSZ121


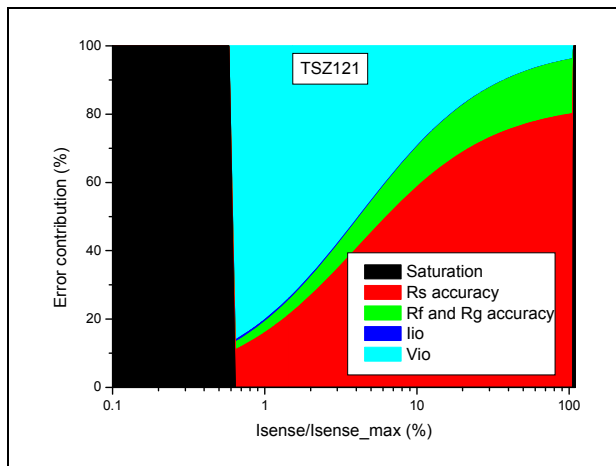


Figure 9. Contribution of each parameter to overall error for a 1 mV V_{io} op amp

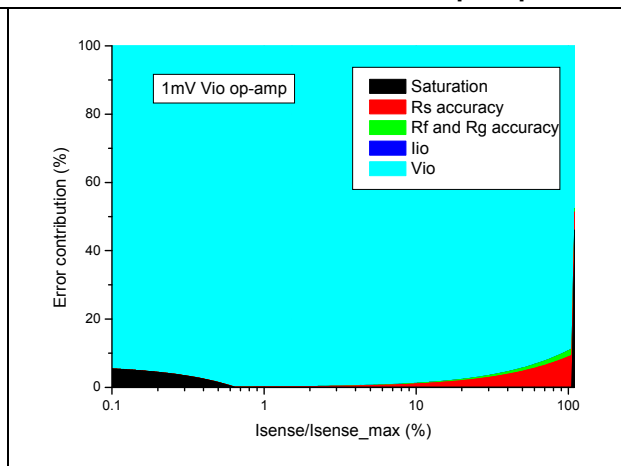

The error due to the AVD parameter has not been taken into consideration in this document, because it is negligible. If the schematic gain equals 470 (gain used for the measurements) and the AVD equals 120 dB, there is an inaccuracy of 0.047%.

Equation 7 demonstrates this.

Equation 7

$$\frac{V_{out}}{R_s \times I} = \frac{\frac{R_f}{R_g}}{1 + \frac{R_f}{R_g} \frac{1}{AVD}}$$

When:

$$R_f/R_g \ll AVD$$

$$\frac{V_{out}}{R_s \times I} = \frac{\frac{R_f}{R_g}}{1 + \varepsilon} \approx \frac{R_f}{R_g} (1 - \varepsilon)$$

$$\text{Error}(\%) = -\frac{1 + \frac{R_f}{R_g}}{AVD} \times 100$$

Example:

$$R_f/R_g = 470$$

AVD = 120 dB (the minimum value for the TSZ121)

$$\text{Error} = -\frac{1 + \frac{R_f}{R_g}}{AVD} \times 100 = -0.047\%$$

Clearly, the higher the gain of the schematics, the higher the inaccuracy, but in this case the error is negligible.

5 Frequency behavior

This section describes how the measurements are filtered.

To sense in a large bandwidth, the gain of the application must not exceed the capability of the amplifier. If the gain is too big, the application is limited by the gain-bandwidth product or by the slew rate of the amplifier. For test purposes, the same conditions as for DC measurements are selected:

Rshunt = 10 mΩ, Rg = 100 Ω, and Rf = 47 kΩ.

This example deals with filtering the measurement of an AC current source which has overlapping oscillations. The easiest way to achieve overlapping oscillations is to add a capacitor e.g. see the Cf capacitor in [Figure 2](#).

[Figure 10](#) and [Figure 11](#) show that the period of oscillations is T = 300 μs. In order to efficiently filter 3.3 kHz, we can cut by a factor of ten earlier, and thus choose fc = 330 Hz.

Thus, choose:

$$C_f = \frac{1}{2\pi \times f_c \times R_f} = \frac{1}{2\pi \times 330 \times 47000} = 10\text{nF}$$

In [Figure 10](#), the measurement was performed without the capacitor.

In [Figure 11](#) a capacitor of 10 nF was added. An AC current from 0.4 A to 1 A was then applied. The signal is correctly filtered by the capacitor and the overlapping oscillations on the current source are no longer visible on the op amp output voltage.

Figure 10. Filtering without the Cf capacitor


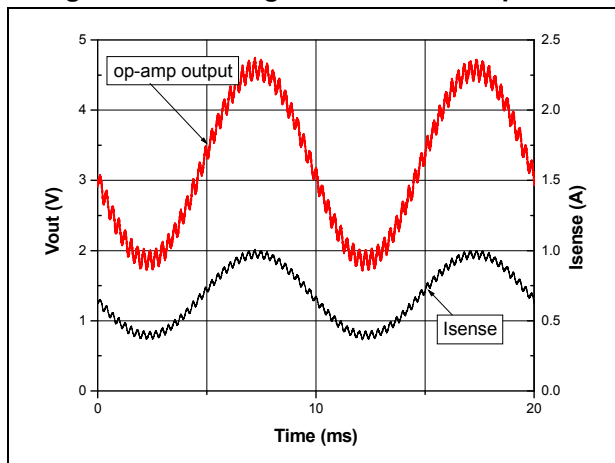


Figure 11. Filtering with Cf capacitor = 10 nF

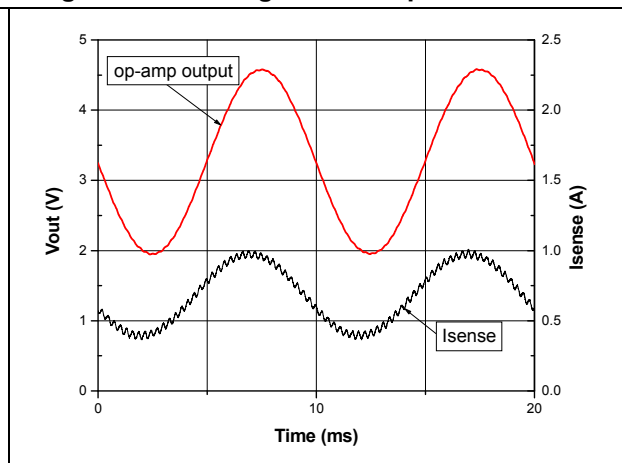

Note: Verification of this behavior with the spice model and, above all, checking the results on the bench is recommended.

6 Bill of materials

Table 2. Bill of materials

Part	Footprint	Description	Value	Qty
TSZ121	SOT23-5	Very high accurate amplifier	TSZ121ILT	1
Rf	0603	0.1 % resistor	47 k Ω ⁽¹⁾	2
Rg	0603	0.1 % resistor	100 Ω	2
Rs	9.4 x 9.1 mm	1 % 4-terminal shunt resistor	10 m Ω ⁽¹⁾	1
Cf	0603	Capacitor	33 nF	1
C1	0603	Decoupling capacitor	22 nF	1

1. To choose the correct component values, refer to [Section 3](#). The default value has been chosen for a power source of 5 V, sourcing a maximum current of 1 A

7 Conclusion

This document provides the information necessary to develop a low-side current sensing application using the TSZ121. You can accurately measure current with a limited number of components even if the sense current is noisy. Moreover, using the TSZ121 high precision op amp allows you to reduce the shunt resistor value and to increase the schematic gain without losing accuracy. Thanks to a lower shunt value, there is a lower dissipated power within the shunt resistor. Consequently, the shunt resistor's size can be reduced and the customer can save money.

With the theoretical equations provided, you can easily predict the maximum error on the output voltage. To minimize errors, you must select the components correctly according to the parameters described in [Section 3](#).

8 Revision history

Table 3. Document revision history

Date	Revision	Changes
23-May-2014	1	Initial release

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2014 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com